

# **Basic Electronic Circuits**

## **(IEC-103)**



### **Lecture-03**

# **Operational Amplifiers**


# Operational Amplifier

- ☐ Typically called 'Op Amp' for short.
- ☐ Used in large variety of electronic circuits.
- ☐ It acts like a voltage controlled voltage source.
- ☐ In combination with other elements it can be made into other dependent sources
- ☐ It performs mathematical operations on analog signals


# 741 Op Amp IC

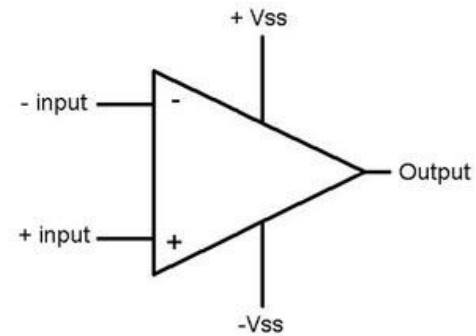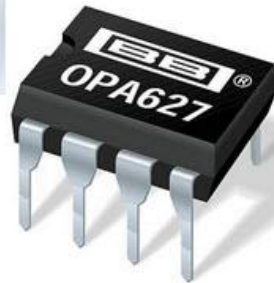

## OP-AMP

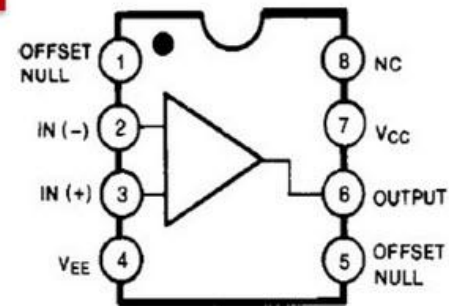


# 741 Op Amp IC (Pin Diagram)

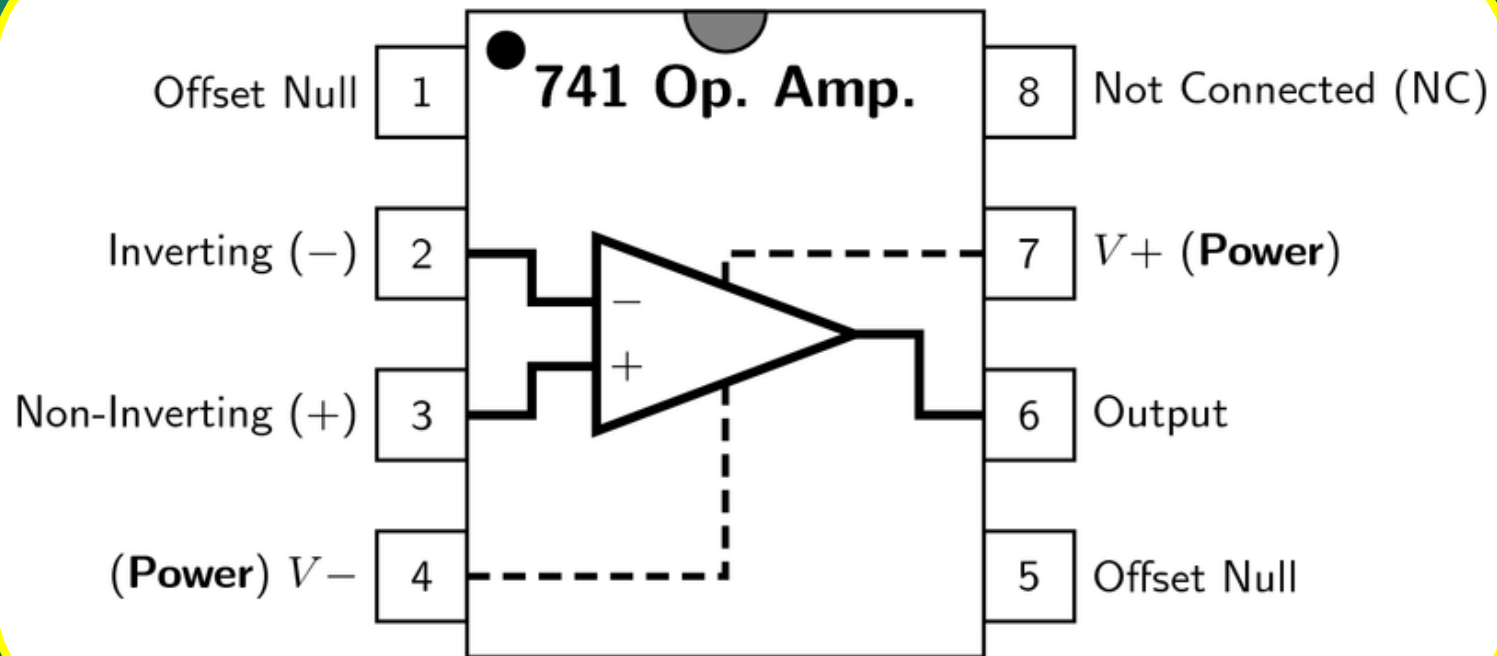




# 741 Op Amp IC (Circuit Diagram)

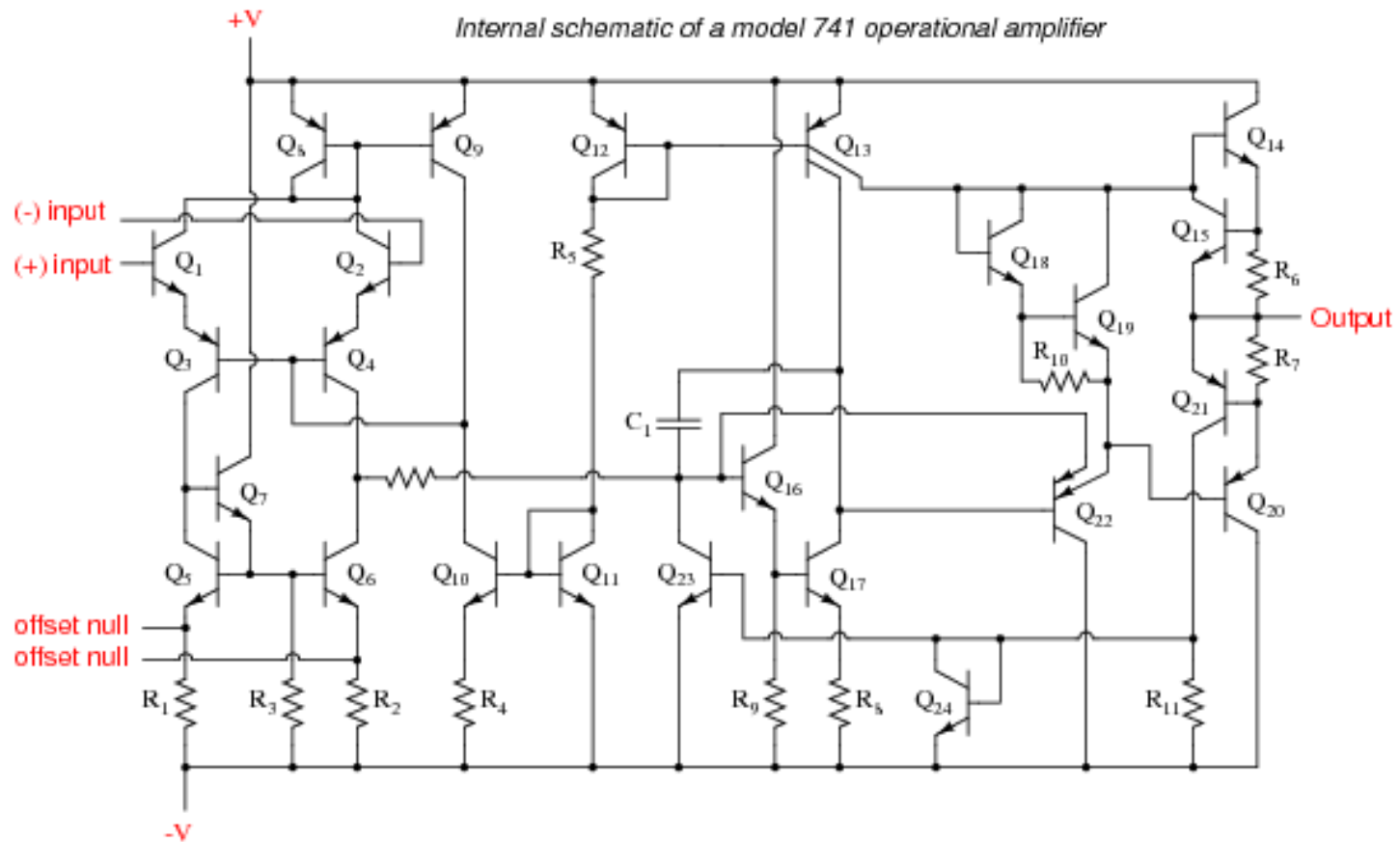


# 741 Op Amp IC

- ❑ It is most versatile IC available.
- ❑ It is a linear amplifier.
- ❑ It is an 8 Pin Chip.
- ❑ **Applications** – Filters, ECG amplification, strain gauges, signal conditioning in transducers, control systems.
- ❑ Available in 2 configurations – 8 Pin and 14 Pin.

# 14 Pin Op-amp Chip

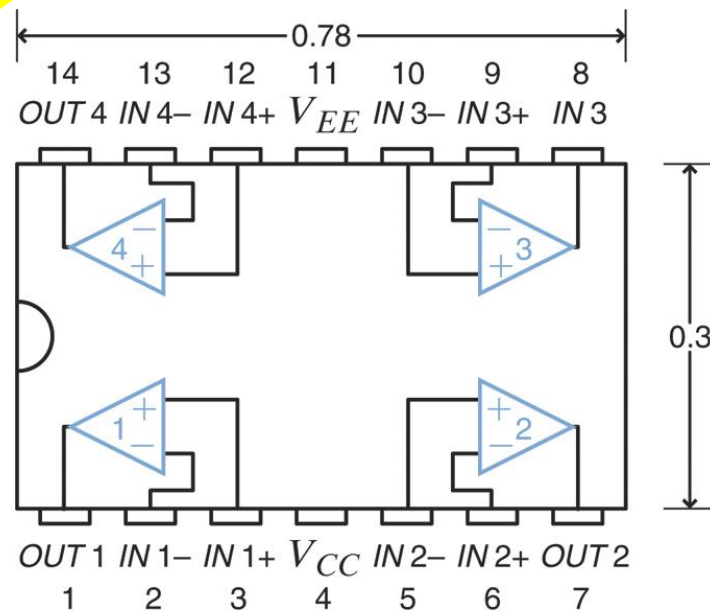

(a)

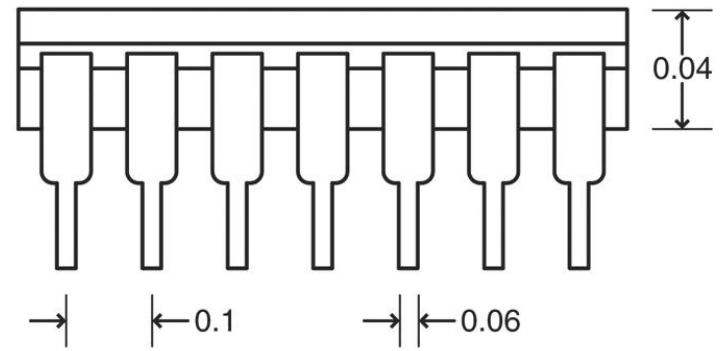

(b)




# **Operational Amplifiers**

**The op amp is capable of many math operations, such as addition, subtraction, multiplication, differentiation, and integration.**


**There are five terminals found on all op-amps**

- The inverting input**
- The noninverting input**
- The output**
- The positive and negative power supplies.**

# Operational Amplifier

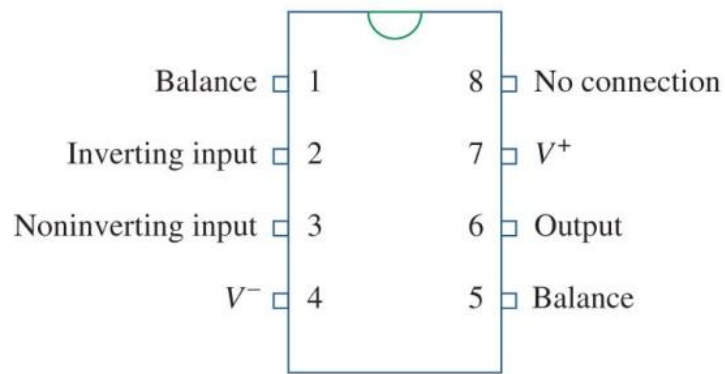

(a)

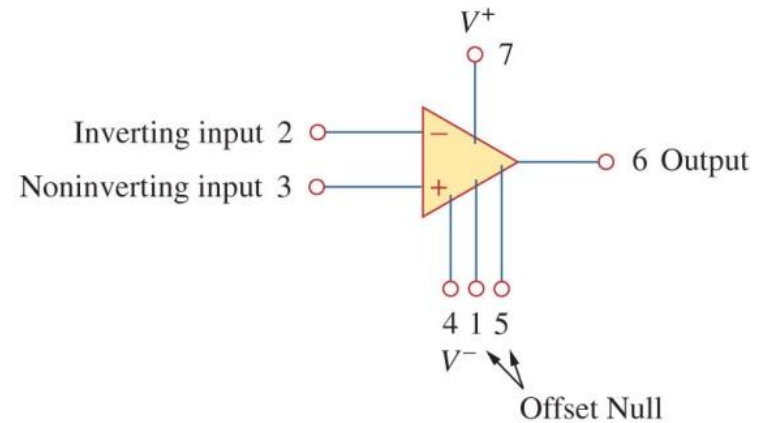

(b)

# Powering an Op-amp

- ☐ As an active element, the op-amp requires a power source.
- ☐ Often in circuit diagrams the power supply terminals are obscured.
- ☐ It is taken for granted that they must be connected.
- ☐ Most op-amps use two voltage sources, with a ground reference between them.
- ☐ This gives a positive and negative supply voltage.

# Output Voltage of an Op-amp


- The voltage output of an op-amp is proportional to the difference between the noninverting and inverting inputs

$$v_o = A v_d = A(v_+ - v_-)$$

- A is called the open loop gain
- Ideally it is infinite
- In real devices, it is still high:  $10^5$  to  $10^8$  volts/volt



# Equivalent Circuit of an Op-amp

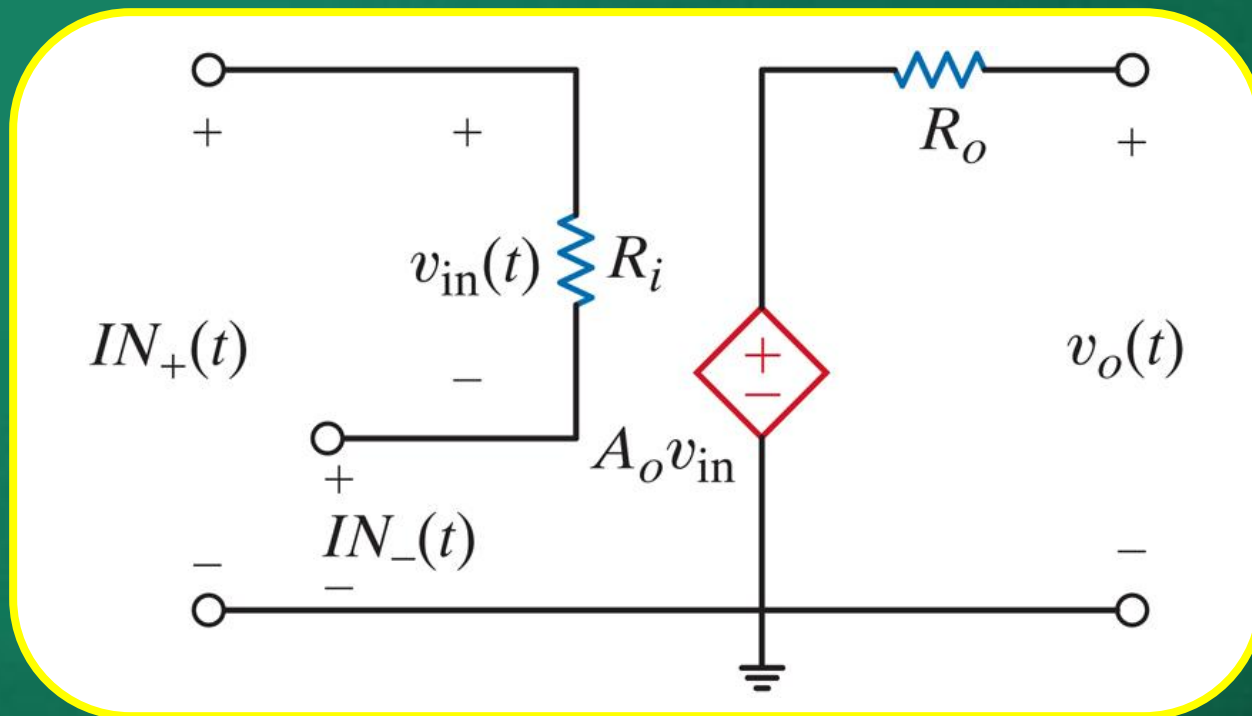




# Typical Ranges of Op-amp Parameters

**TABLE 5.1**


Typical ranges for op amp parameters.

Parameter	Typical range	Ideal values
Open-loop gain, $A$	$10^5$ to $10^8$	$\infty$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output resistance, $R_o$	10 to $100 \Omega$	$0 \Omega$
Supply voltage, $V_{CC}$	5 to 24 V	


# Transfer Characteristics of an Op-amp

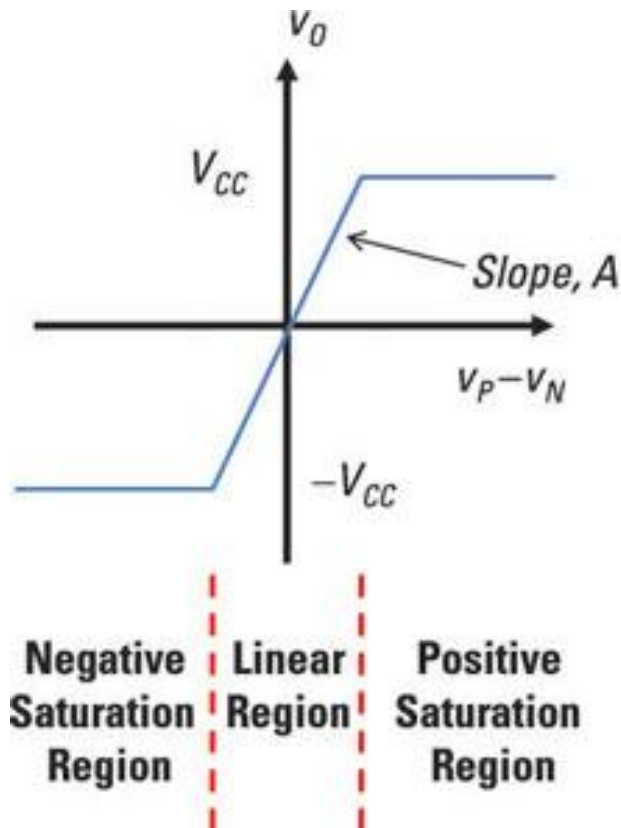

# Transfer Characteristics of an Op-amp

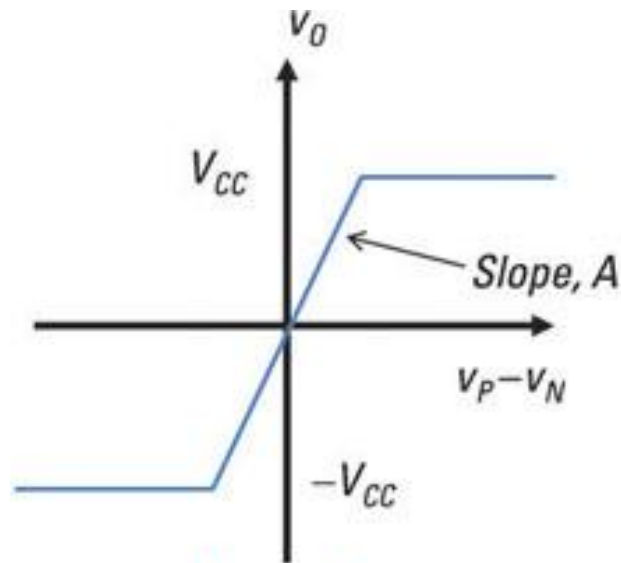

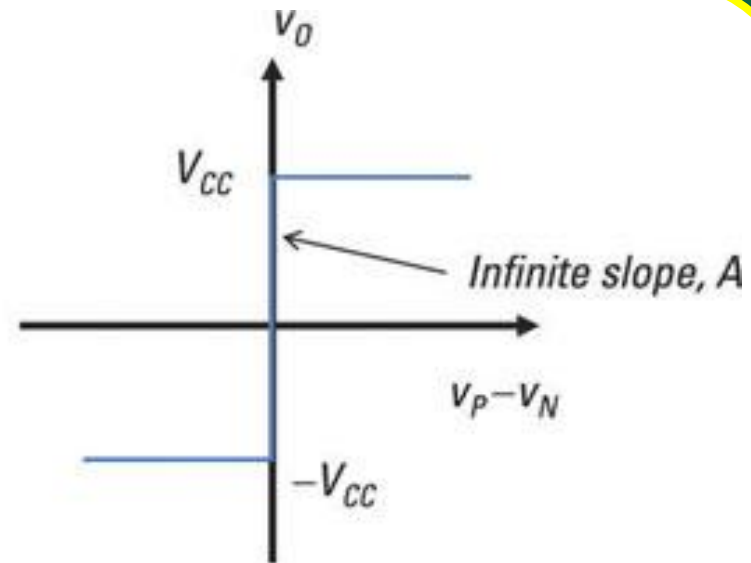Negative Saturation Region    Linear Region    Positive Saturation Region



Transfer Characteristic of an Ideal Op Amp


# Feedback

- ❑ **Op-amps take on an expanded functional ability with the use of feedback.**
- ❑ **The idea is that the output of the op-amp is fed back into the inverting terminal.**
- ❑ **Depending on what elements this signal passes through the gain and behavior of the op-amp changes.**
- ❑ **Feedback to the inverting terminal is called negative feedback.**
- ❑ **Positive feedback would lead to oscillations.**


# Op-amp Analysis




# Unity Gain Buffer

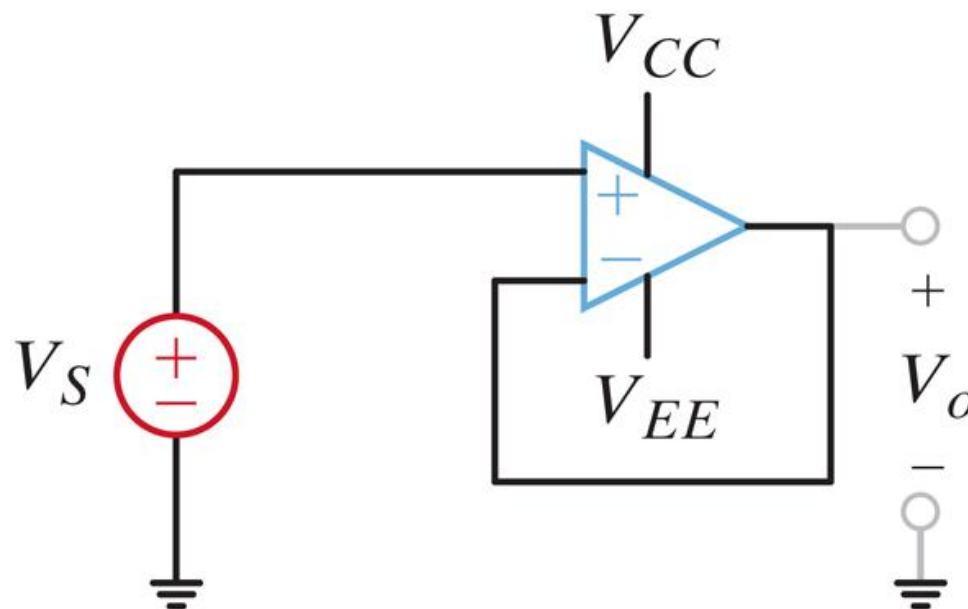

# Analysis using Circuit Model

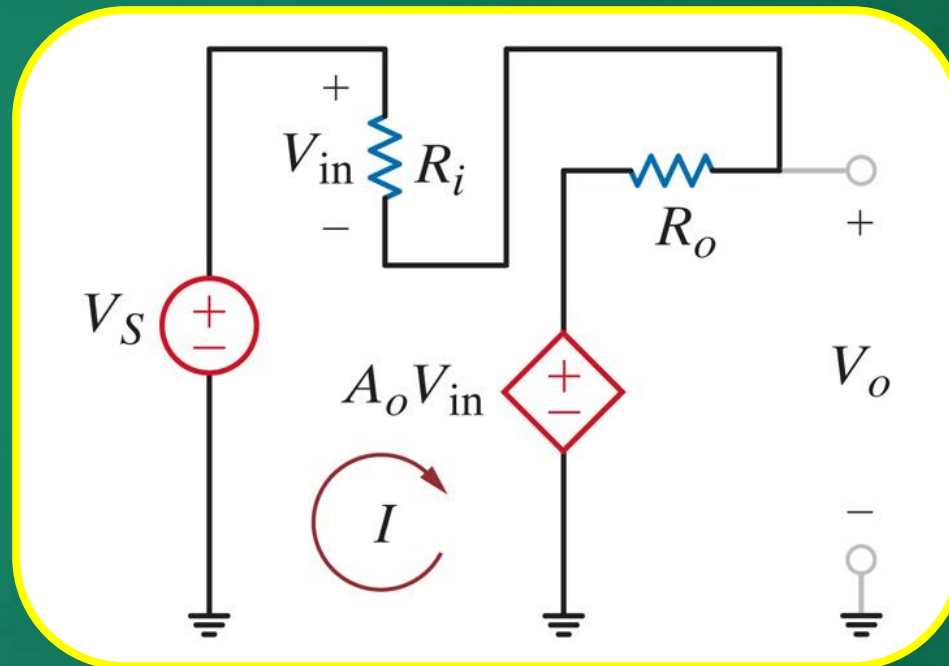

# Analysis using Circuit Model

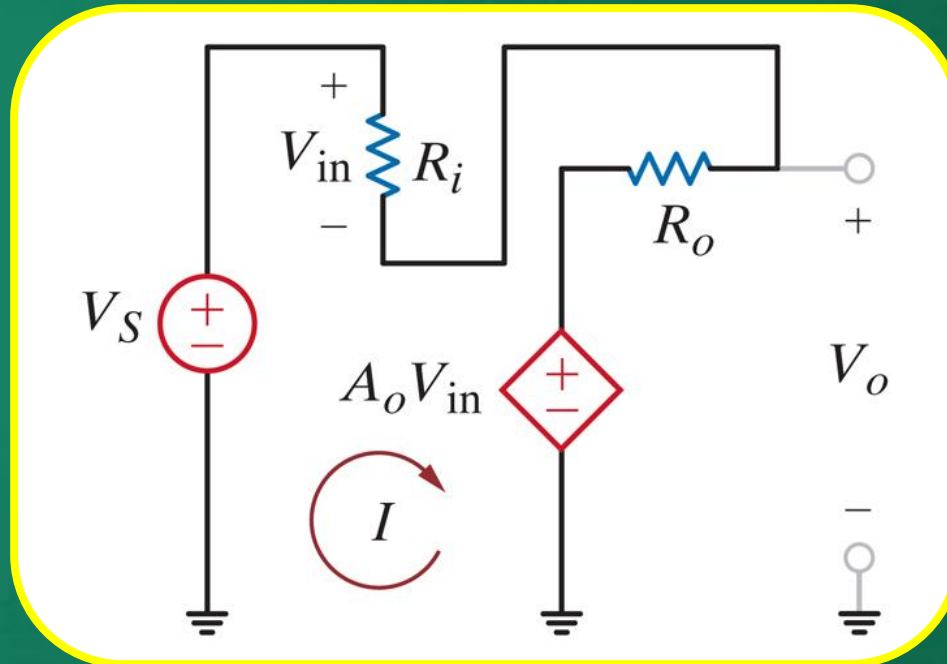

$$\frac{V_o}{V_s} = \frac{1}{1 + \frac{R_i}{R_o + A_o R_i}}$$

# Ideal Op-amp Rules


- **No current ever flows into either of the input terminals.**

# **Ideal Op-amp Rules**


- ☐ **No current ever flows into either of the input terminals.**
- ☐ **There is no voltage difference between the two input terminals.**



# Analysis using Ideal Op-amp

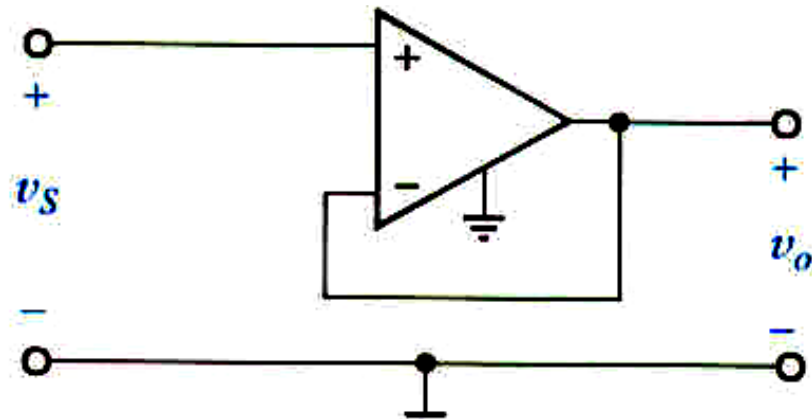


# Analysis using Ideal Op-amp

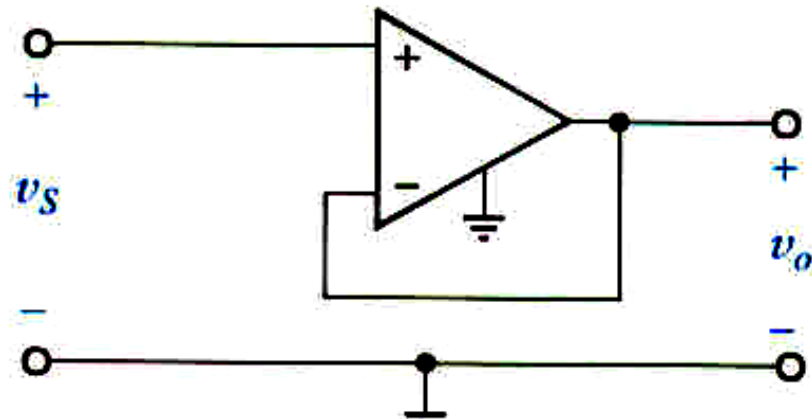


$$\frac{V_o}{V_s} = 1$$

# Advantages of Buffer

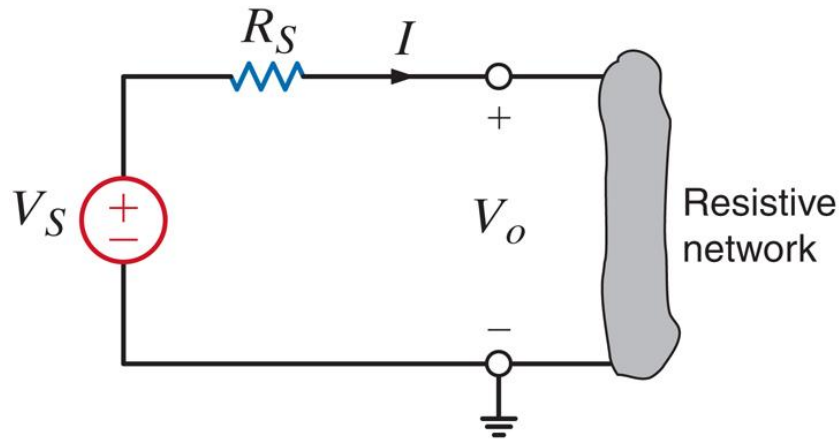


# Advantages of Buffer

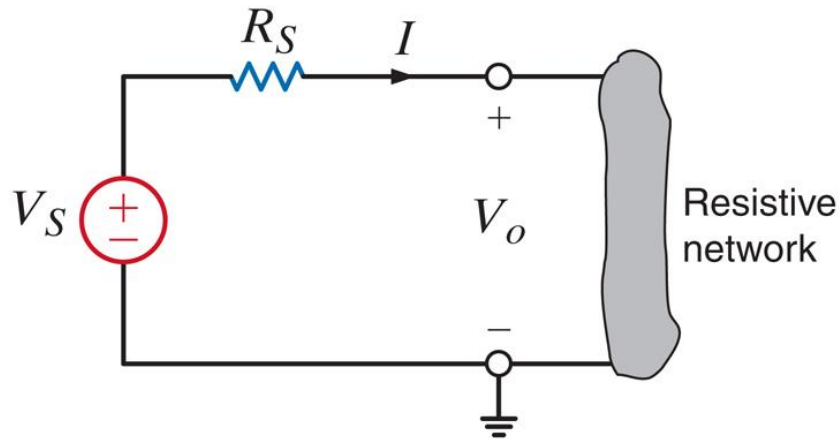


$$V_o = V_s - R_s I$$

# Advantages of Buffer

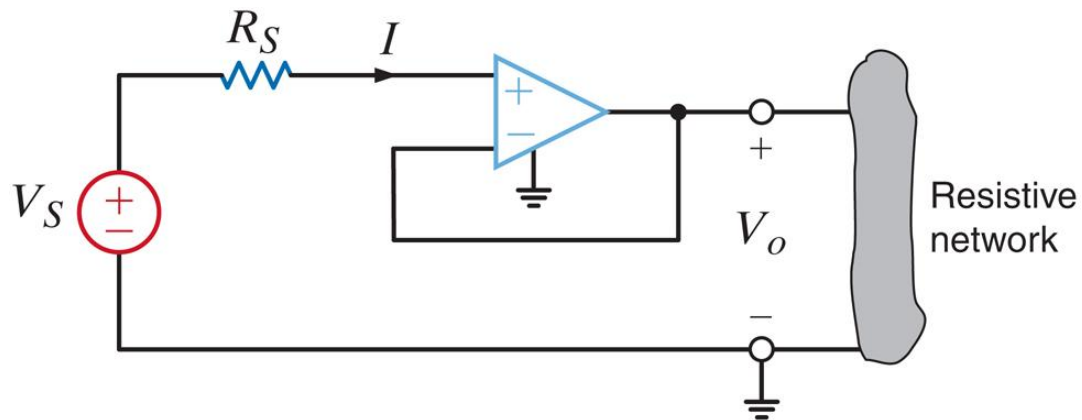




# Advantages of Buffer

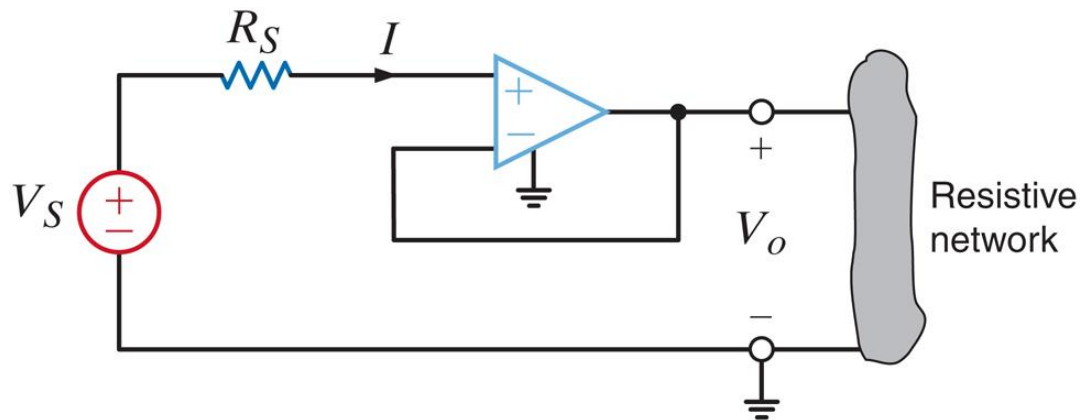


$$V_o = V_s$$

# Inverting Amplifier

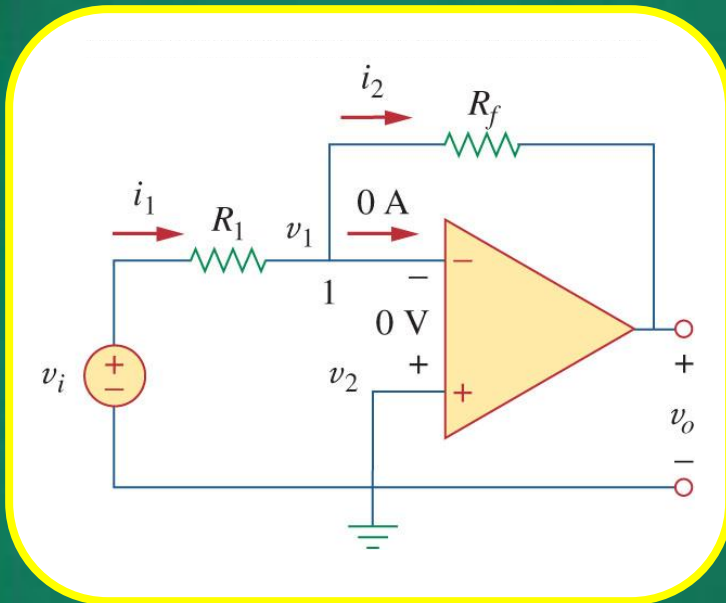

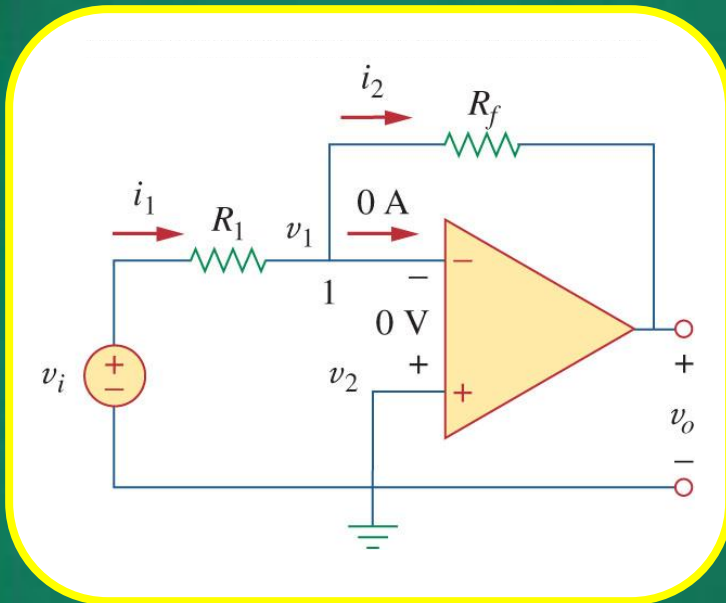
# Inverting Amplifier

- This is called the inverting amplifier.




# Inverting Amplifier

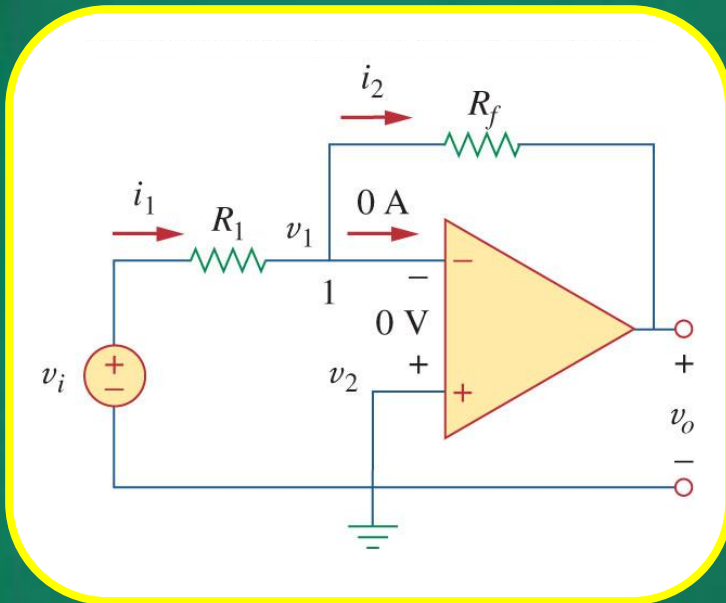

- This is called the inverting amplifier.
- Here the noninverting input is grounded.


# Inverting Amplifier

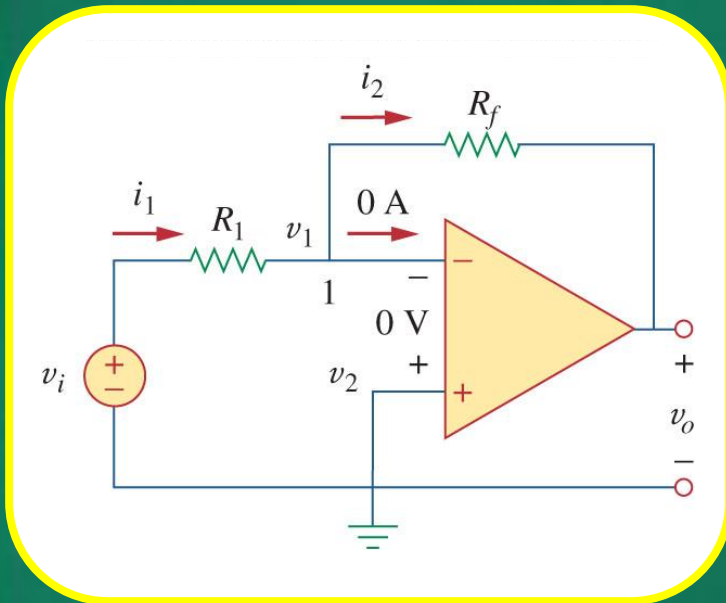

- This is called the inverting amplifier.
- Here the noninverting input is grounded.
- The inverting terminal is connected to the output via a feedback resistor,  $R_f$ .




# Inverting Amplifier

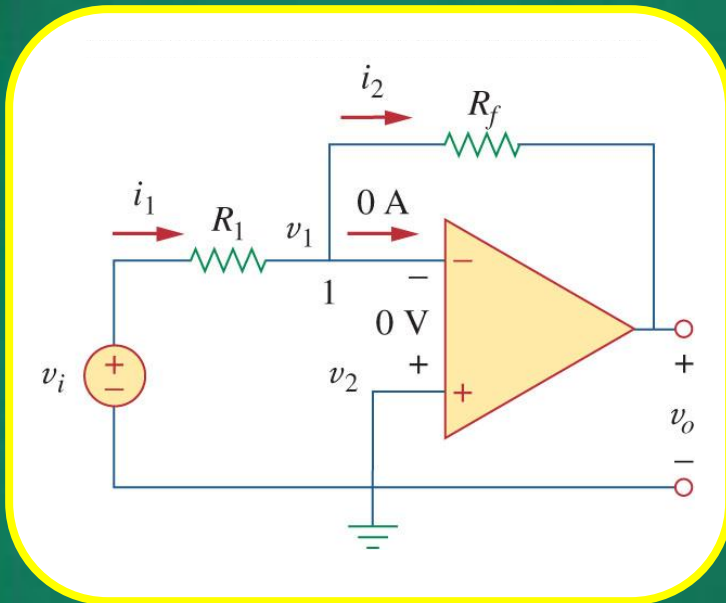

- This is called the inverting amplifier.
- Here the noninverting input is grounded.
- The inverting terminal is connected to the output via a feedback resistor,  $R_f$ .
- The input is connected to the inverting terminal via another resistor,  $R_1$ .


# Inverting Amplifier

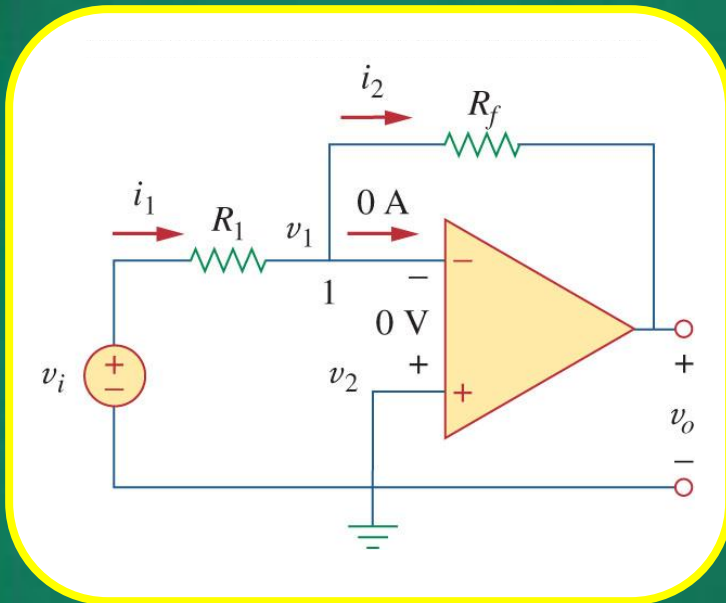

$$v_o = -\frac{R_f}{R_1} v_i$$


- This is called the inverting amplifier.
- Here the noninverting input is grounded.
- The inverting terminal is connected to the output via a feedback resistor,  $R_f$ .
- The input is connected to the inverting terminal via another resistor,  $R_1$ .

# Inverting Amplifier

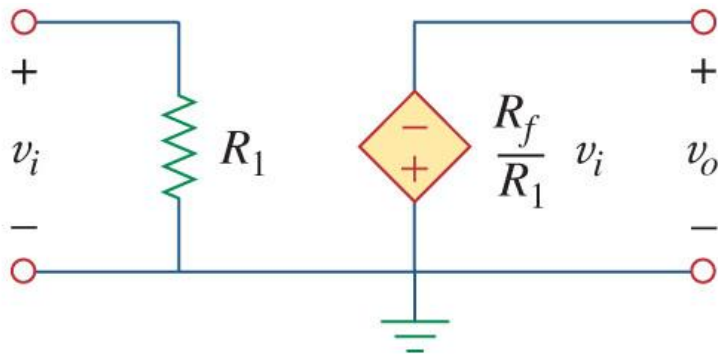

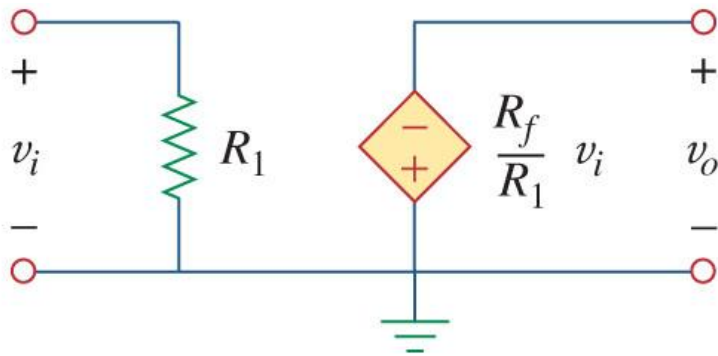
# Inverting Amplifier

- The inverting amplifier's equivalent circuit is shown here.



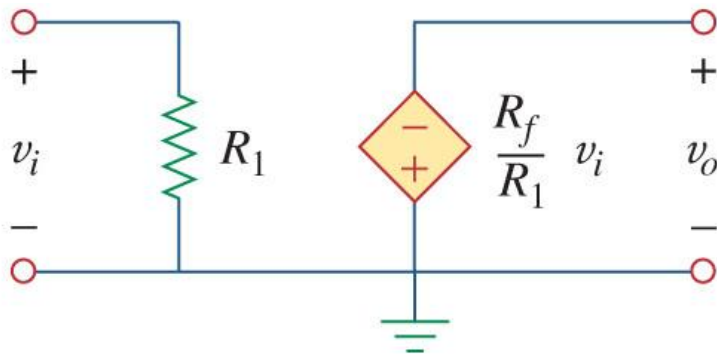
# Inverting Amplifier

- The inverting amplifier's equivalent circuit is shown here.
- Note that it has a finite input resistance.






# Inverting Amplifier

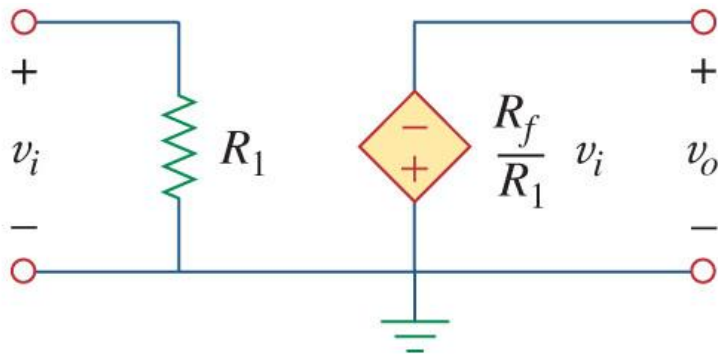


- The inverting amplifier's equivalent circuit is shown here.
- Note that it has a finite input resistance.
- It is also a good candidate for making a current-to-voltage converter

# Non-Inverting Amplifier

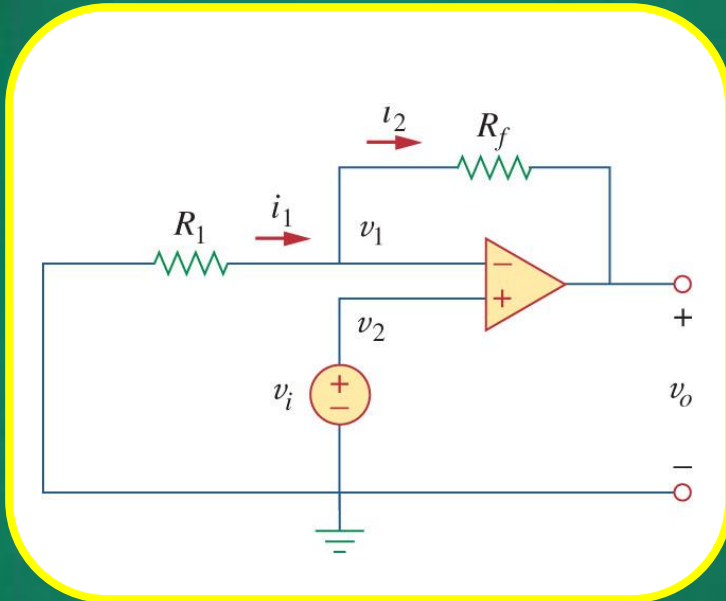


# Non-Inverting Amplifier

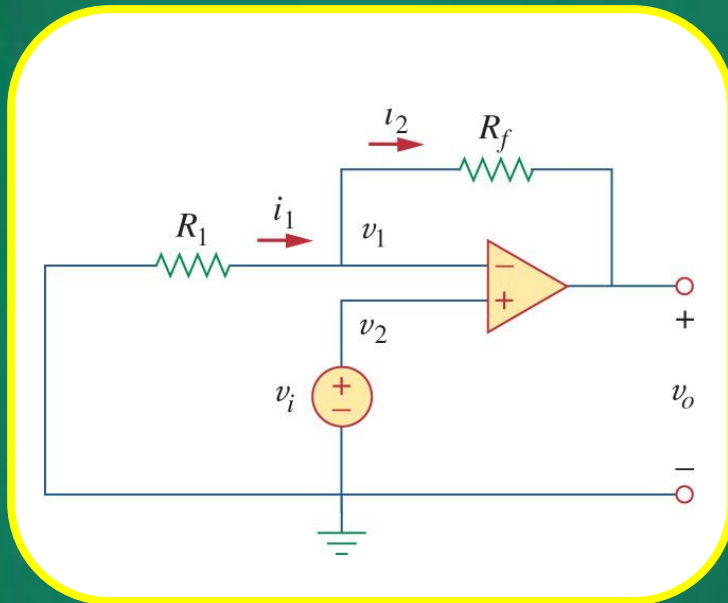


- Another important op-amp circuit is the noninverting amplifier.

# Non-Inverting Amplifier

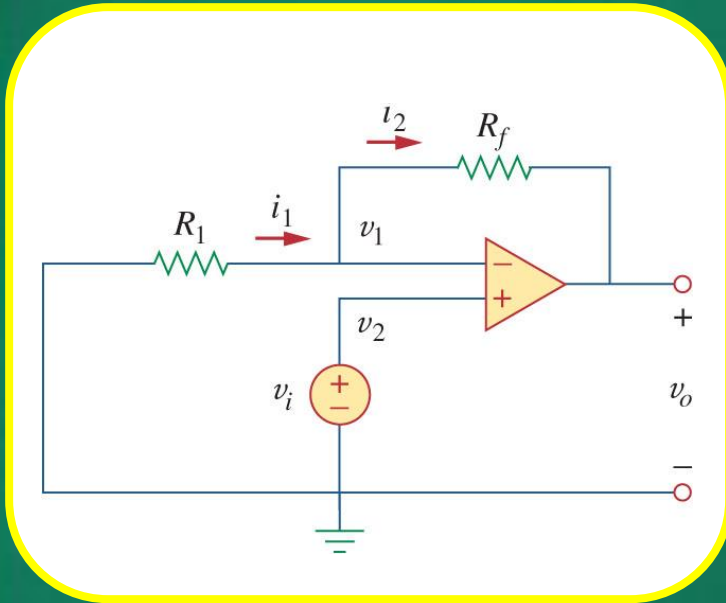

- Another important op-amp circuit is the noninverting amplifier.
- The basic configuration of the amplifier is the same as the inverting amplifier


# Non-Inverting Amplifier

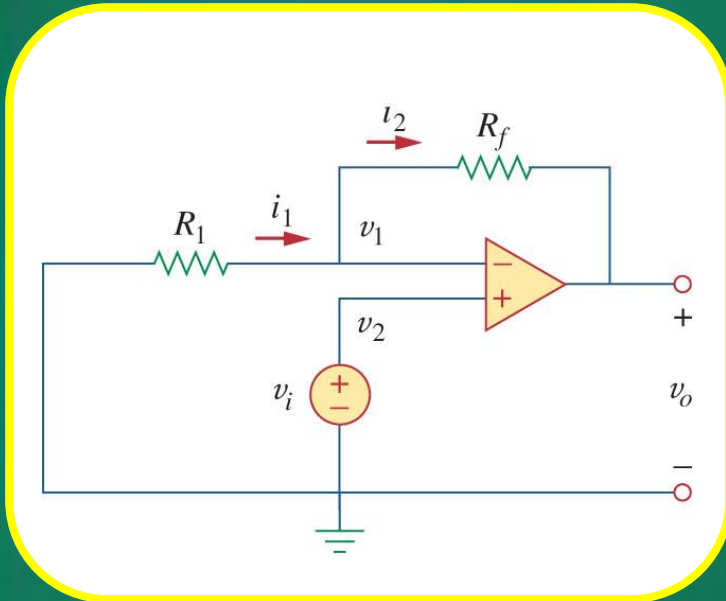

- Another important op-amp circuit is the noninverting amplifier.
- The basic configuration of the amplifier is the same as the inverting amplifier
- Except that the input and the ground are switched



# Non-Inverting Amplifier

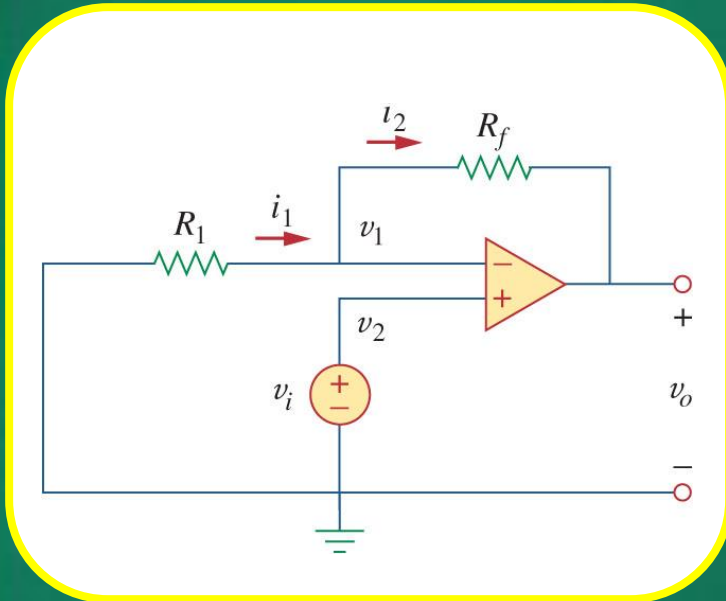

$$v_o = \left( 1 + \frac{R_f}{R_1} \right) v_i$$

- Another important op-amp circuit is the noninverting amplifier.
- The basic configuration of the amplifier is the same as the inverting amplifier
- Except that the input and the ground are switched

# Non-Inverting Amplifier

- **Gain here is positive, thus the amplifier is noninverting.**

# **Non-Inverting Amplifier**

- **Gain here is positive, thus the amplifier is noninverting.**
- **This amplifier retains the infinite input impedance of the op-amp.**

# Non-Inverting Amplifier

- **Gain here is positive, thus the amplifier is noninverting.**
- **This amplifier retains the infinite input impedance of the op-amp.**
- **One aspect of this amplifier's gain is that it can never go below 1.**

# Non-Inverting Amplifier

- **Gain here is positive, thus the amplifier is noninverting.**
- **This amplifier retains the infinite input impedance of the op-amp.**
- **One aspect of this amplifier's gain is that it can never go below 1.**
- **One could replace the feedback resistor with a wire and disconnect the ground and the gain would still be 1 (voltage follower).**