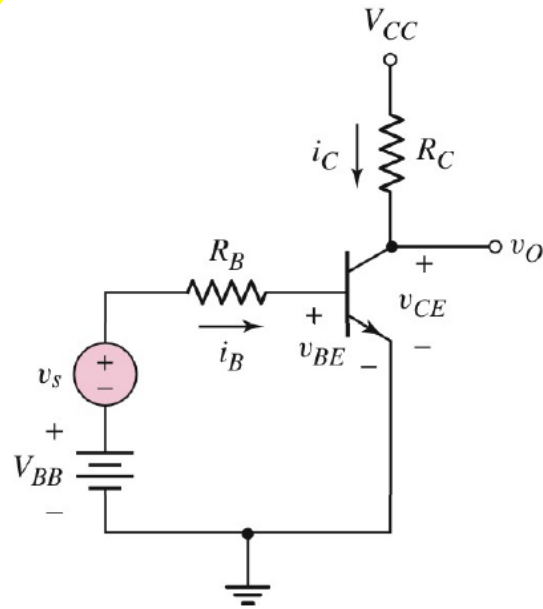


Basic Electronic Circuits (IEC-103)


Lecture-18

Small Signal Analysis


Small Signal Voltage Gain



Small Signal Voltage Gain

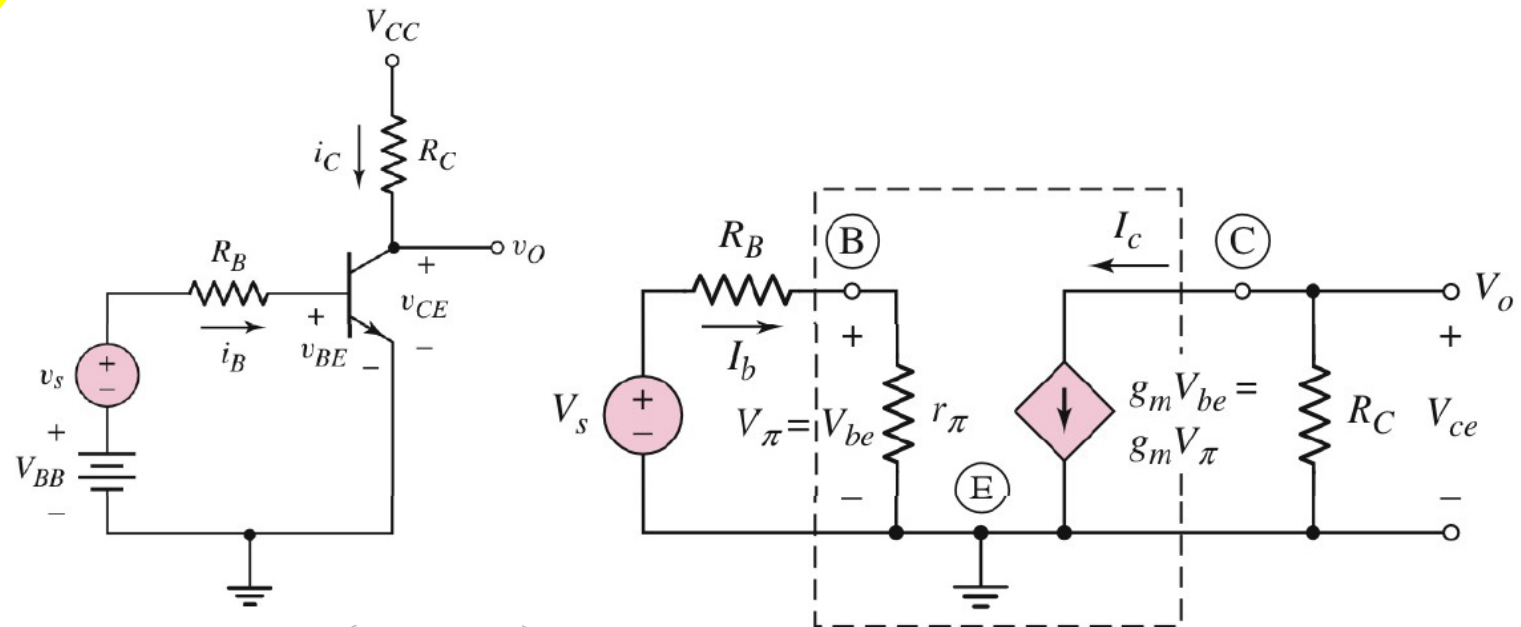


Small Signal Voltage Gain

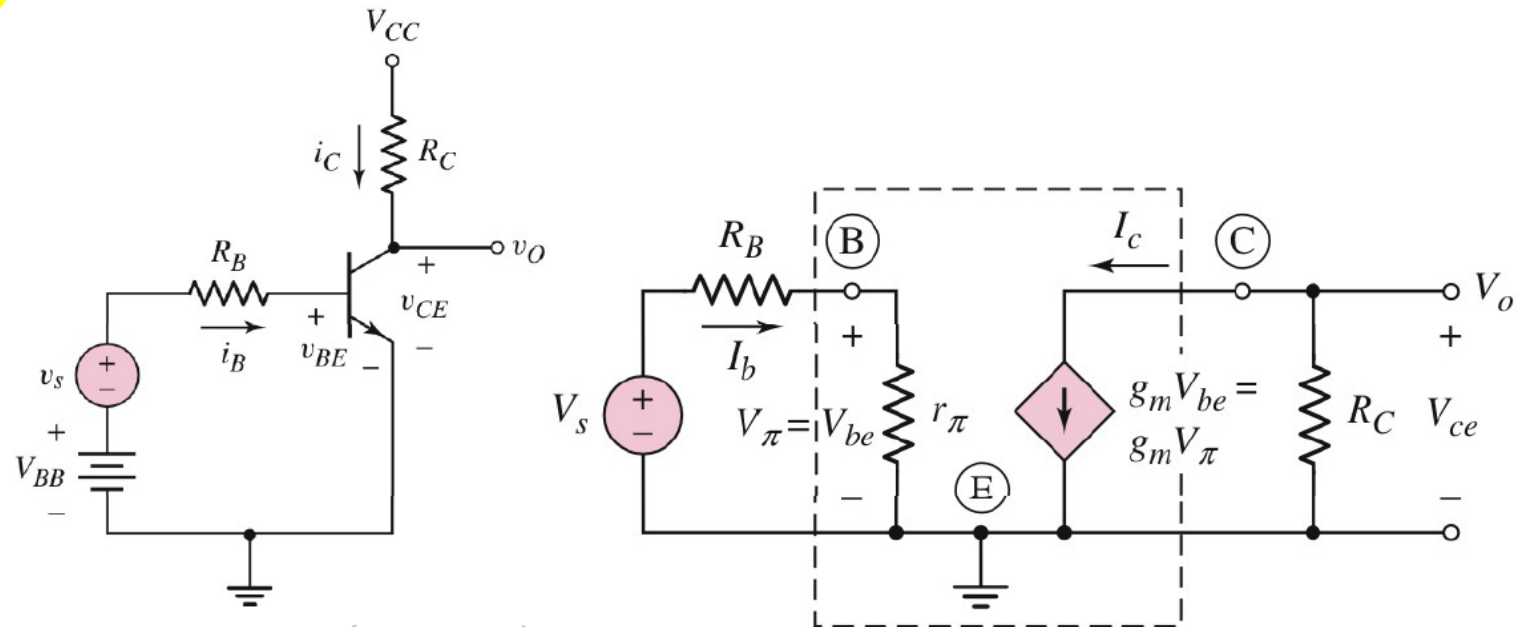

$$V_\pi = V_{be} = V_s \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_\pi) R_C = -(g_m V_{be}) R_C$$

Small Signal Voltage Gain

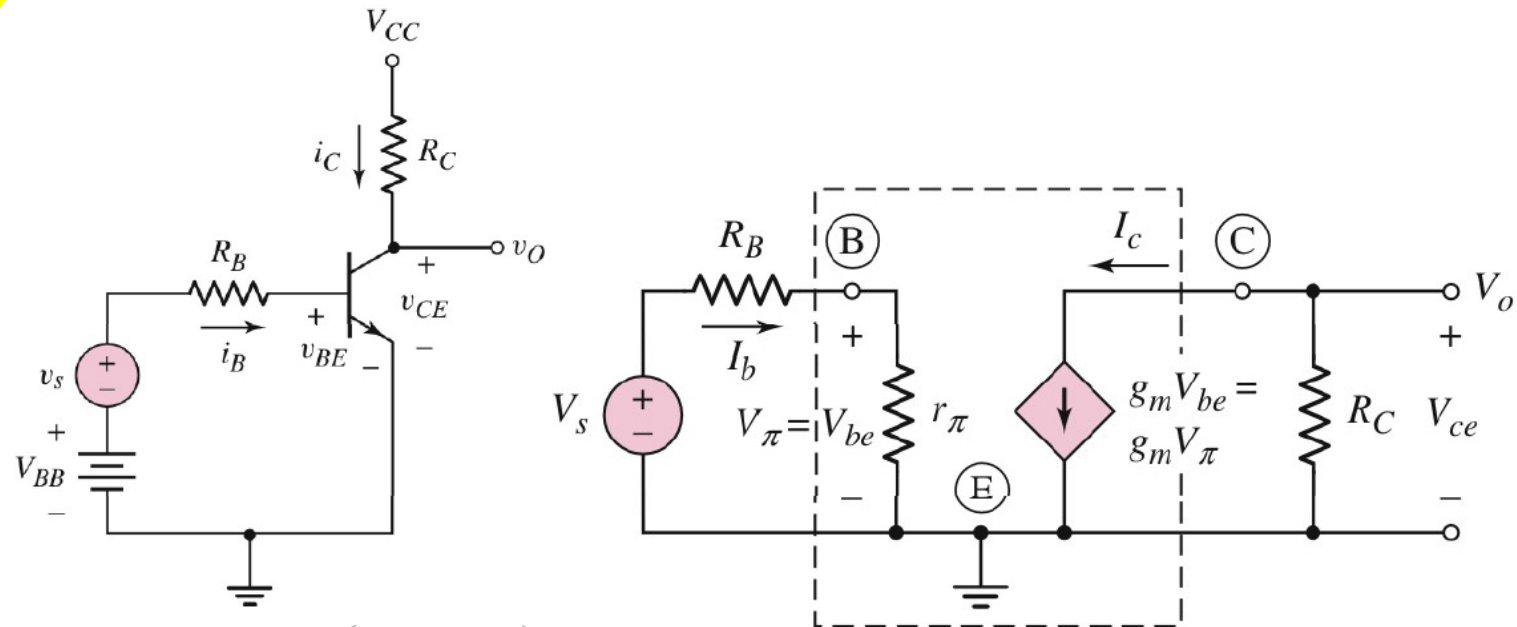


$$V_\pi = V_{be} = V_s \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_\pi) R_C = -(g_m V_{be}) R_C$$


Small-signal voltage gain:

$$A_v = \frac{V_o}{V_s} = -(g_m R_C) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

Input and Output Resistances

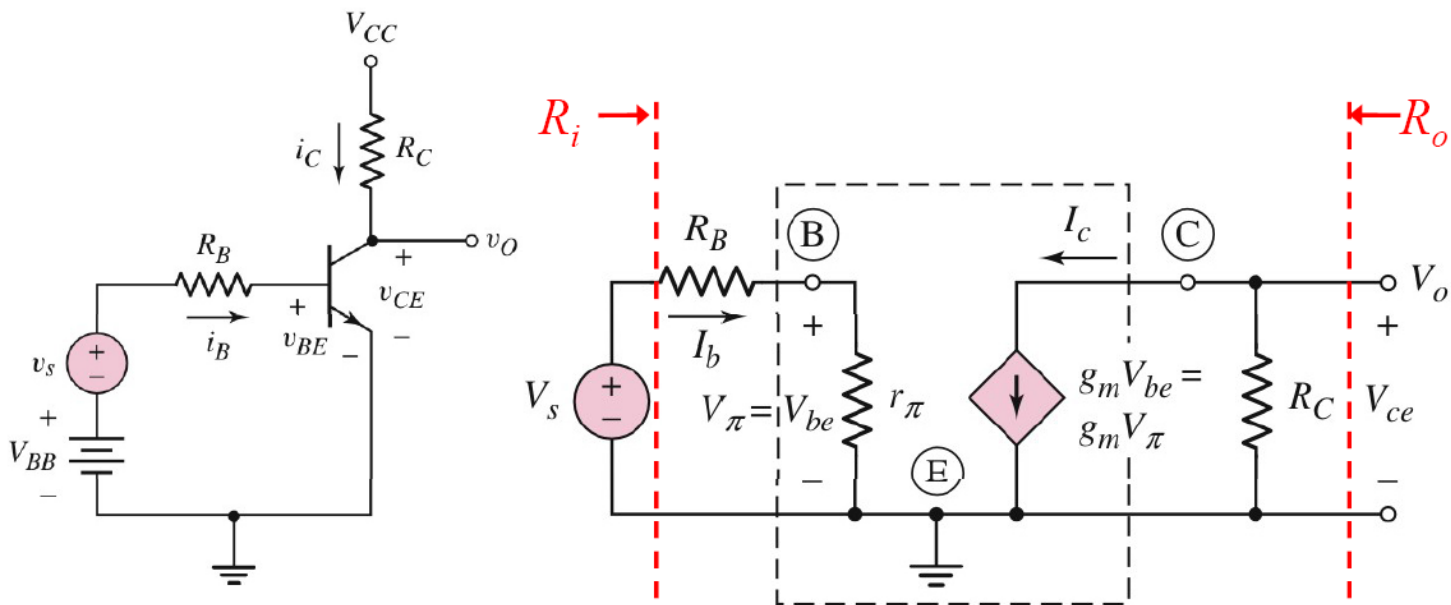

Input and Output Resistances

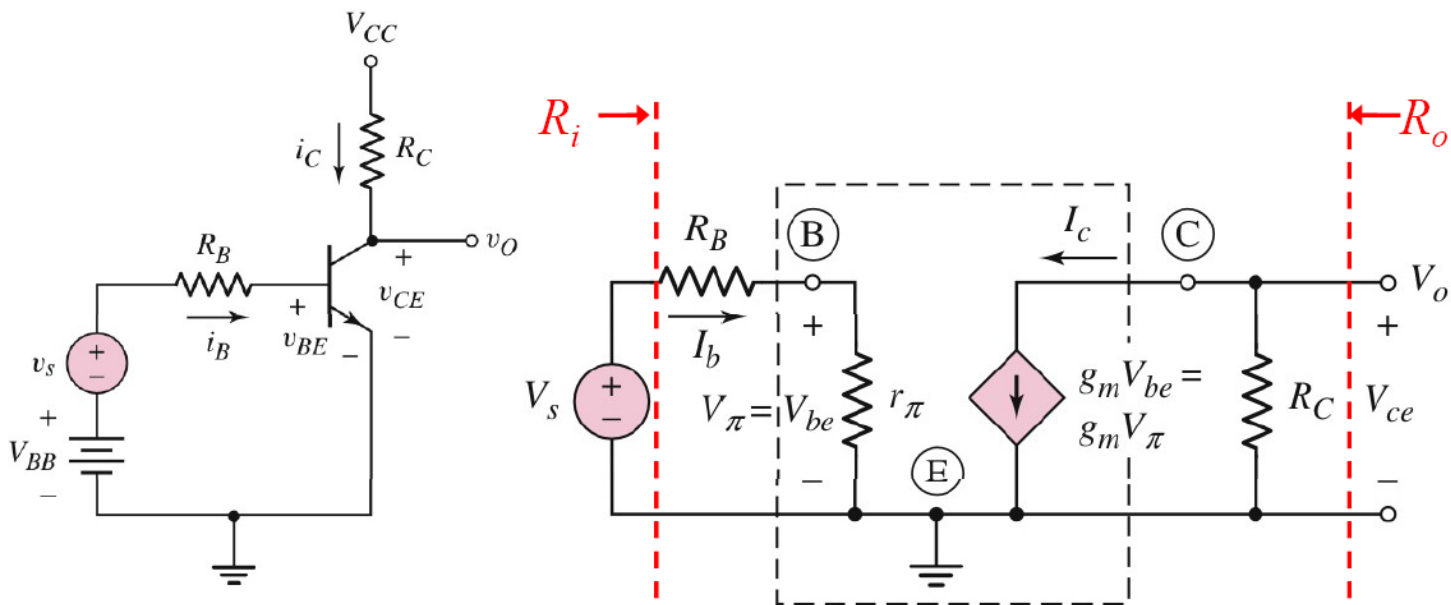


Input resistance: $R_i = R_B + r_\pi$

Output resistance: $R_o = R_C$

[Setting $V_s = 0$ (short), then $V_\pi = 0$ & $g_m V_\pi = 0$ (open)]

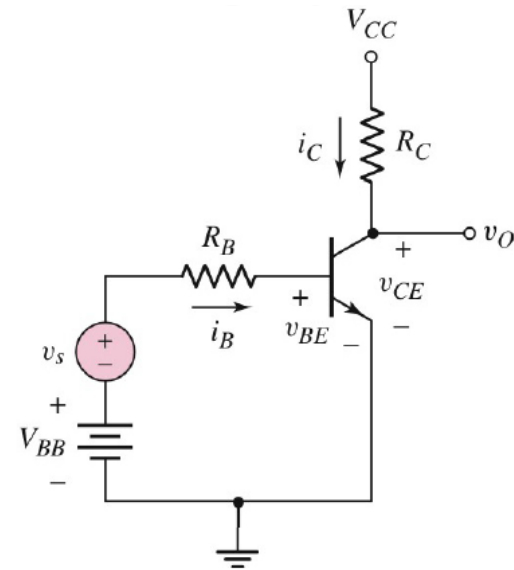Example


- Calculate the small-signal voltage gain, input resistance & output resistance of the BJT amplifier circuit at 300 K. Assume that the BJT & circuit parameters are: $\beta = 100$, $V_{CC} = 12$ V, $V_{BE} = 0.7$ V, $R_C = 6$ k Ω , $R_B = 50$ k Ω & $V_{BB} = 1.2$ V.



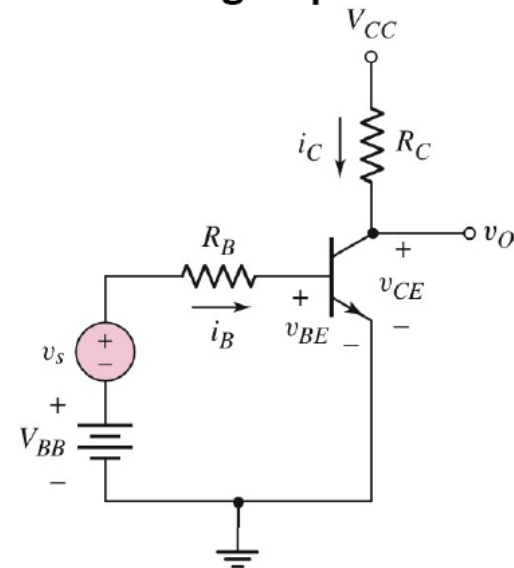Example

- Calculate the small-signal voltage gain, input resistance & output resistance of the BJT amplifier circuit at 300 K. Assume that the BJT & circuit parameters are: $\beta = 100$, $V_{CC} = 12$ V, $V_{BE} = 0.7$ V, $R_C = 6$ k Ω , $R_B = 50$ k Ω & $V_{BB} = 1.2$ V.

Step 1: Perform dc analysis to determine the dc biasing Q-point:



Example

- Calculate the small-signal voltage gain, input resistance & output resistance of the BJT amplifier circuit at 300 K. Assume that the BJT & circuit parameters are: $\beta = 100$, $V_{CC} = 12$ V, $V_{BE} = 0.7$ V, $R_C = 6$ k Ω , $R_B = 50$ k Ω & $V_{BB} = 1.2$ V.


Step 1: Perform dc analysis to determine the dc biasing Q-point:

$$I_{BQ} = \frac{V_{BB} - V_{BE}(\text{on})}{R_B} = \frac{1.2 - 0.7}{50\text{k}} = 10\mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (100)(10\mu) = 1\text{mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C = 12 - (1\text{m})(6\text{k}) = 6\text{V}$$

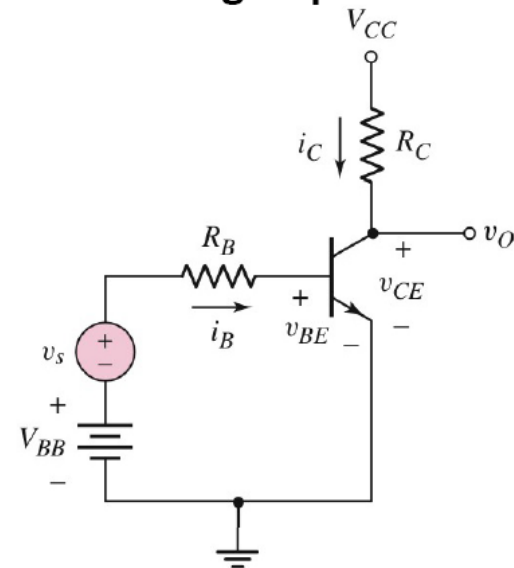Since $I_{BQ} > 0$ A, $V_{BB} > V_{BE}(\text{on})$ & $V_{CEQ} > V_{BE}(\text{on})$, the BJT amplifier is biased in forward-active mode about the Q-point ($V_{CEQ} = 6$ V, $I_{CQ} = 1$ mA, $I_{BQ} = 10$ μ A).



Example (continued)

Step 2: Perform ac analysis using small-signal hybrid- π equiv. cct:

Example (continued)


Step 2: Perform ac analysis using small-signal hybrid- π equiv. cct:

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{\beta(kT/e)}{I_{CQ}} = \frac{(100) \left[(86 \times 10^{-6} e)(300) / e \right]}{1\text{m}} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{2.6\text{k}} = 38.5 \text{ mA/V}$$

$$A_v = \frac{V_o}{V_s} = -(g_m R_C) \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right)$$
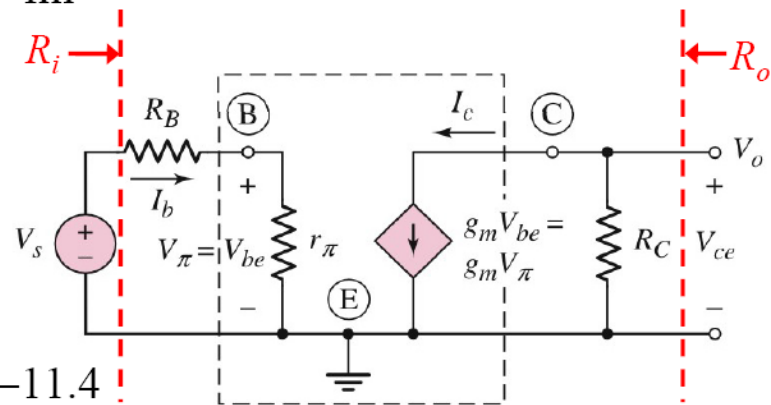
$$= -(38.5\text{m})(6\text{k}) \left(\frac{2.6\text{k}}{2.6\text{k} + 50\text{k}} \right) = -11.4$$



The BJT amplifier is capable of amplifying the input signal amplitude by 11.4 times. The -ve sign indicates a phase reversal of 180°.

$$R_i = R_B + r_{\pi} = 50\text{k} + 2.6\text{k} = 52.6 \text{ k}\Omega$$

$$R_o = R_C = 6 \text{ k}\Omega$$

Example (continued)

Further Discussion:


Let $v_s = 0.25 \sin \omega t$ V

$$i_b = \frac{v_s}{R_B + r_\pi} = \frac{0.25 \sin \omega t}{50\text{k} + 2.6\text{k}} = 4.75 \sin \omega t \mu\text{A} \Rightarrow i_B = I_{BQ} + i_b = 10 + 4.75 \sin \omega t \mu\text{A}$$


$$i_c = \beta i_b = (100)(4.75 \mu \sin \omega t) = 0.475 \sin \omega t \text{ mA} \Rightarrow i_C = I_{CQ} + i_c = 1 + 0.475 \sin \omega t \text{ mA}$$

$$v_{ce} = -i_c R_C = -(0.475\text{m})(6\text{k}) \sin \omega t = -2.85 \sin \omega t \text{ V} \Rightarrow v_{CE} = V_{CEQ} + v_{ce} = 6 - 2.85 \sin \omega t \text{ V}$$
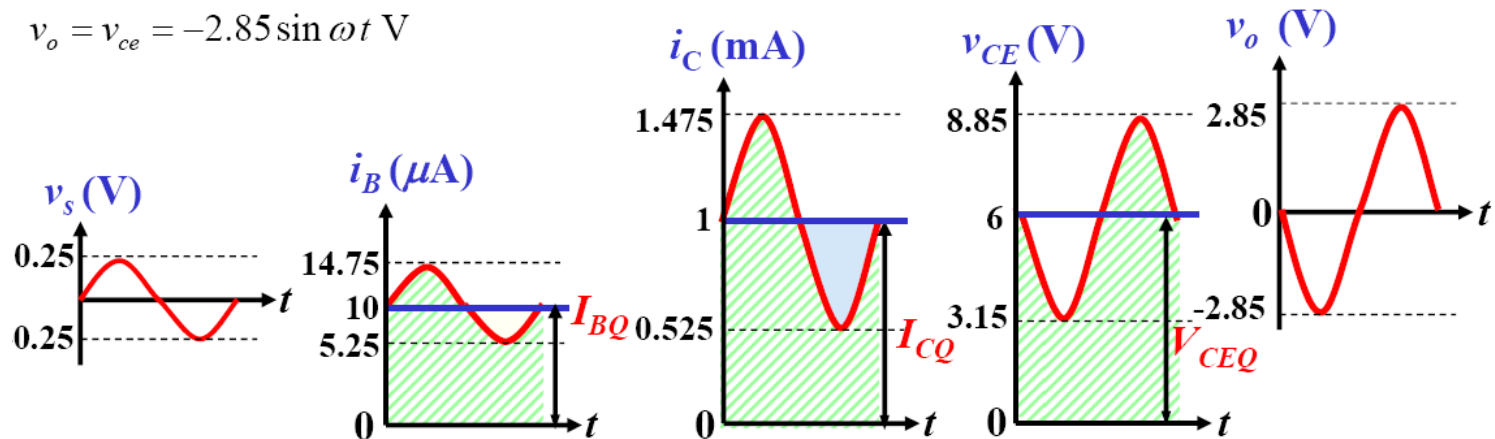
$$v_o = v_{ce} = -2.85 \sin \omega t \text{ V}$$




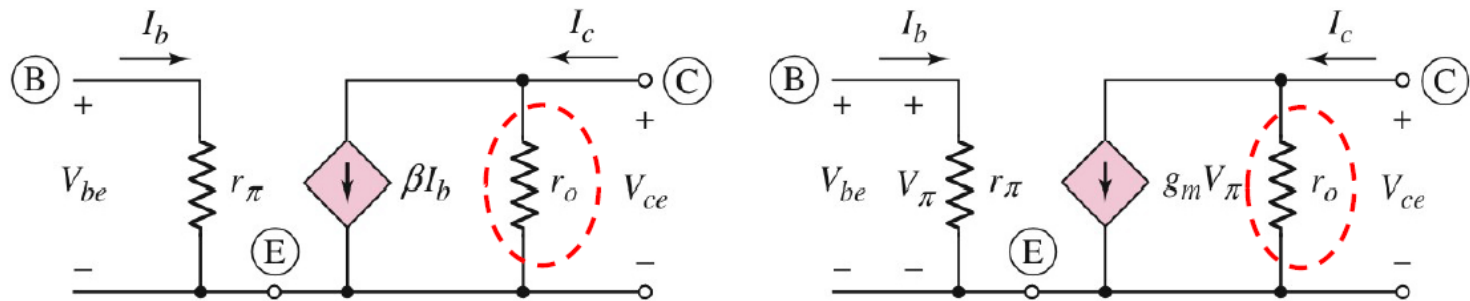Small Signal Hybrid- π Equivalent with Early Effect



$$r_o = \left. \frac{\partial v_{CE}}{\partial i_C} \right|_{Q\text{-point}} \cong \frac{V_A}{I_{CQ}}$$

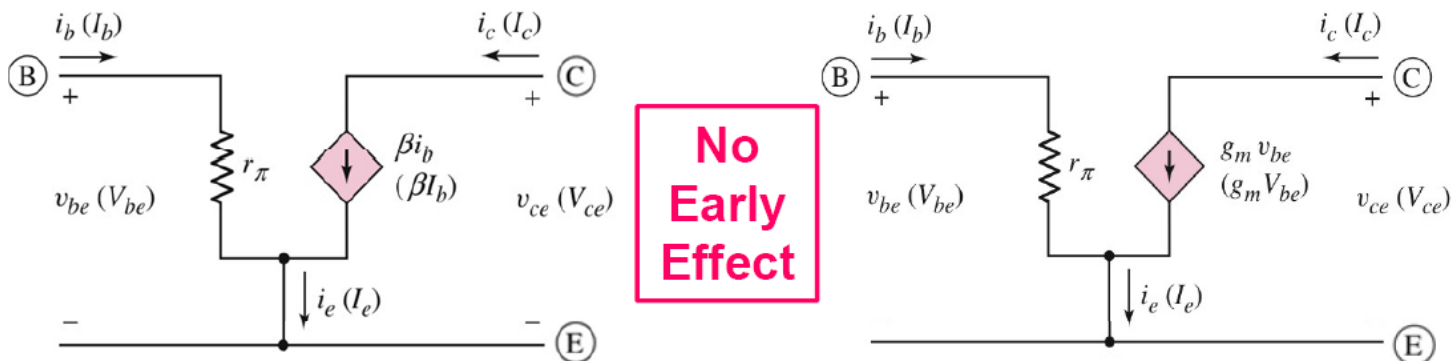r_o = small-signal transistor output resistance
 V_A = early voltage ($50 < V_A < 300$)



Example

Determine the small-signal voltage gain, input resistance, and output resistance of the BJT amplifier circuit in previous example with the early effect. Assume that the early voltage is 50 V.

Example

Determine the small-signal voltage gain, input resistance, and output resistance of the BJT amplifier circuit in previous example with the early effect. Assume that the early voltage is 50 V.

$$r_o = \frac{V_A}{I_{CQ}} = \frac{50}{1\text{m}} = 50\text{ k}\Omega$$


$$A_v = \frac{V_o}{V_s} = -g_m (r_o \parallel R_C) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$= -(38.5\text{m})(50\text{k} \parallel 6\text{k}) \left(\frac{2.6\text{k}}{2.6\text{k} + 50\text{k}} \right) = -10.2$$


$$R_i = R_B + r_\pi = 50\text{ k} + 2.6\text{ k} = 52.6\text{ k}\Omega$$

$$R_o = r_o \parallel R_C = 50\text{ k} \parallel 6\text{ k} = 5.4\text{ k}\Omega$$


r_o reduces both $|A_v|$ from 11.4 to 10.2 & R_o from 6 to 5.4 k Ω .

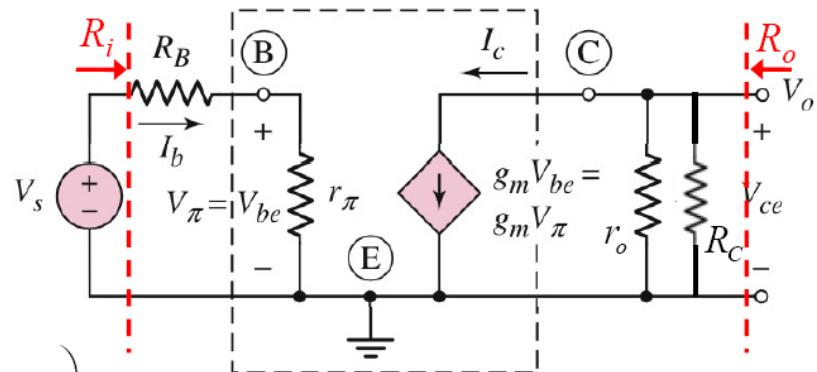

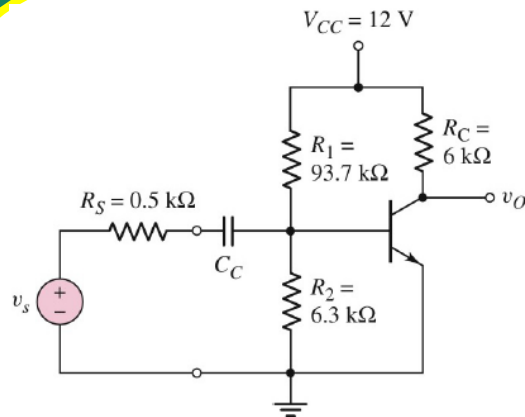
CE amplifier (with voltage-divider biasing & coupling capacitor)



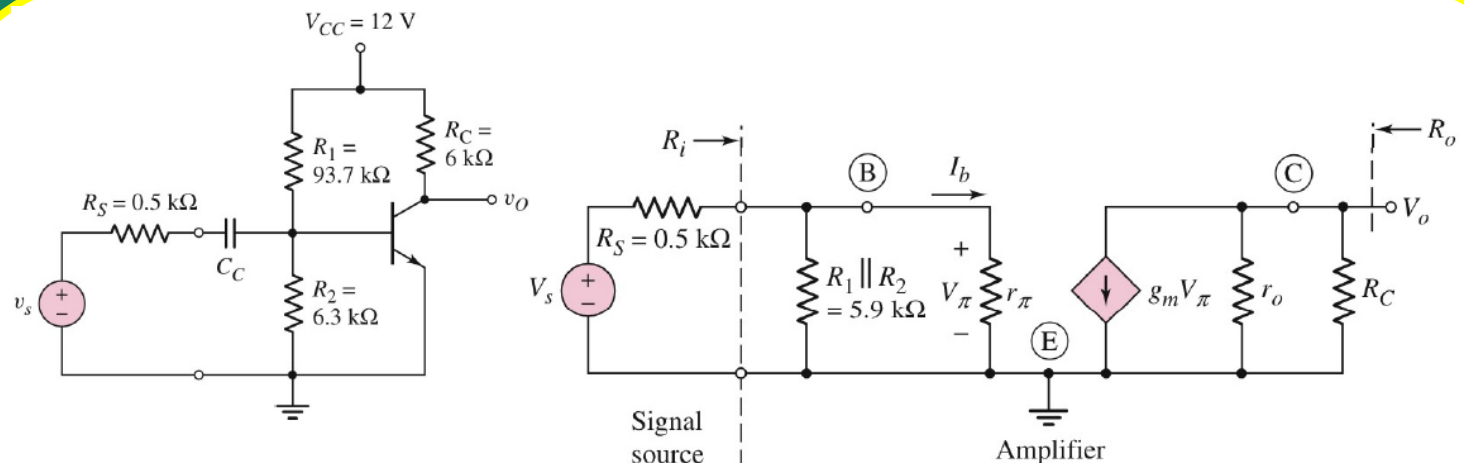CE amplifier (with voltage-divider biasing & coupling capacitor)



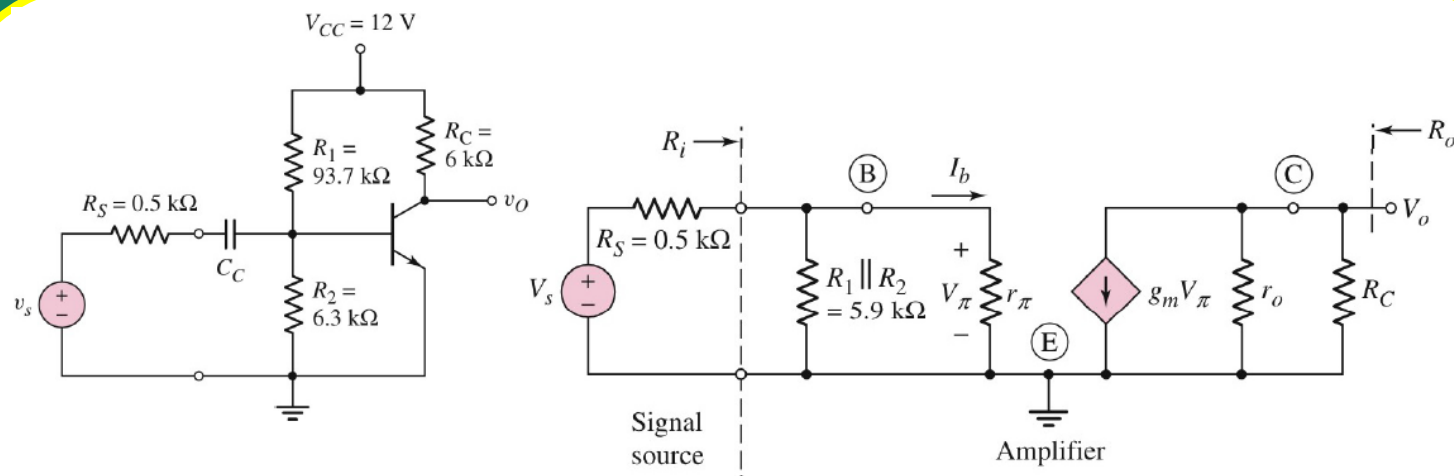
CE amplifier (with voltage-divider biasing & coupling capacitor)



$$V_\pi = V_{be} = V_s \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right)$$

$$V_o = -g_m V_\pi (r_o \parallel R_C) = -g_m V_s \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) (r_o \parallel R_C)$$

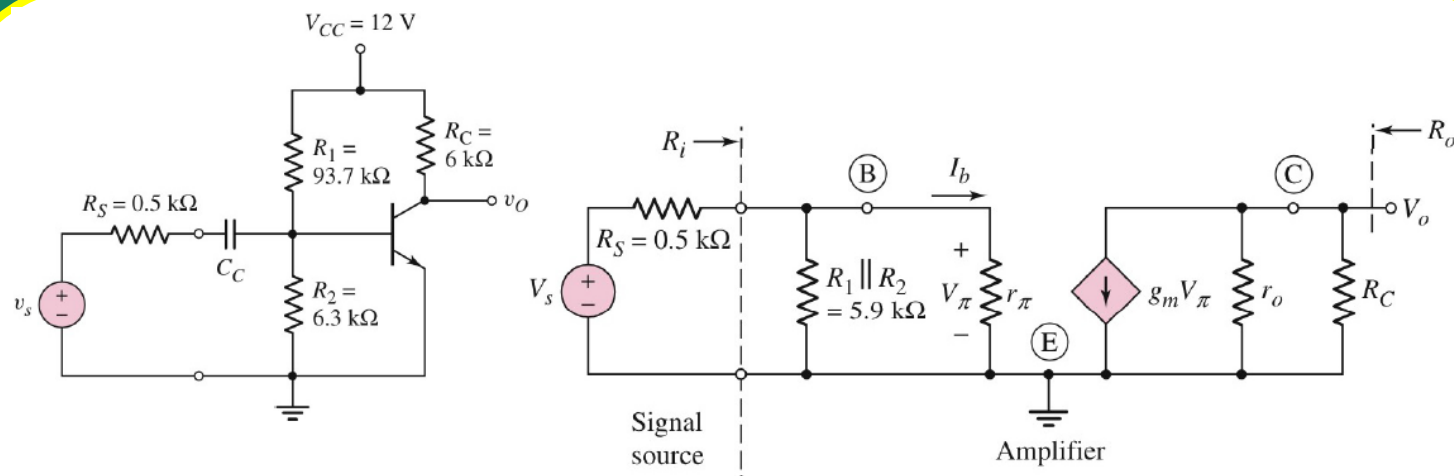CE amplifier (with voltage-divider biasing & coupling capacitor)




$$V_\pi = V_{be} = V_s \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right)$$

$$V_o = -g_m V_\pi (r_o \parallel R_C) = -g_m V_s \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) (r_o \parallel R_C)$$


Small-signal voltage gain: $A_V = \frac{V_o}{V_s} = -g_m \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) (r_o \parallel R_C)$

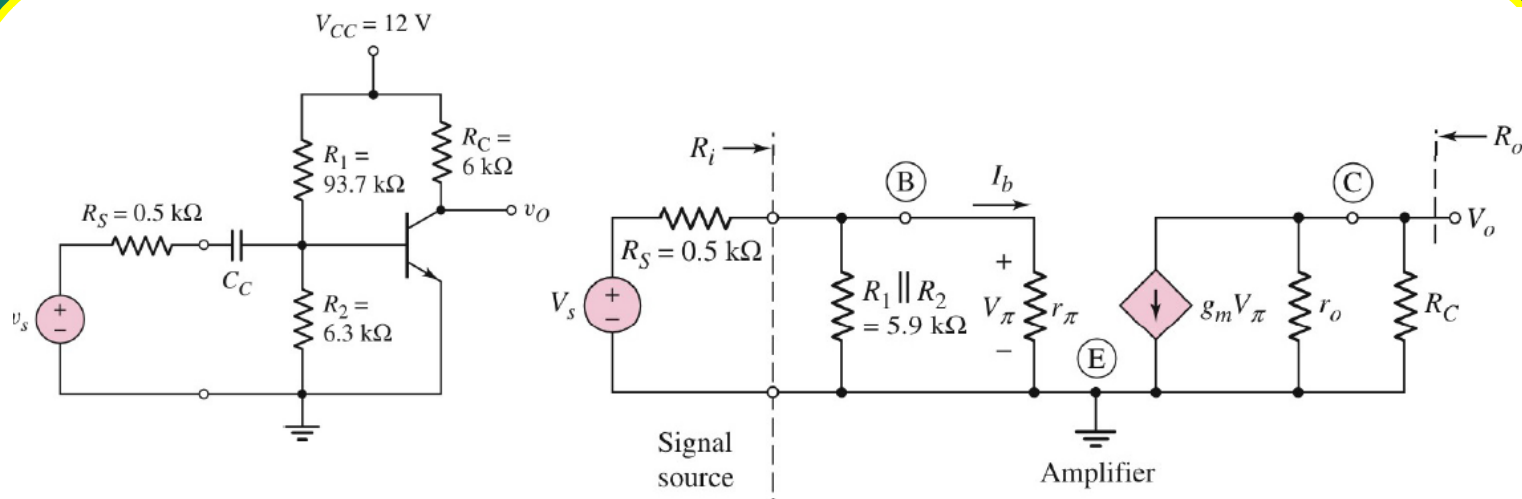CE amplifier (with voltage-divider biasing & coupling capacitor)



Input resistance: $R_i = R_1 \parallel R_2 \parallel r_\pi$

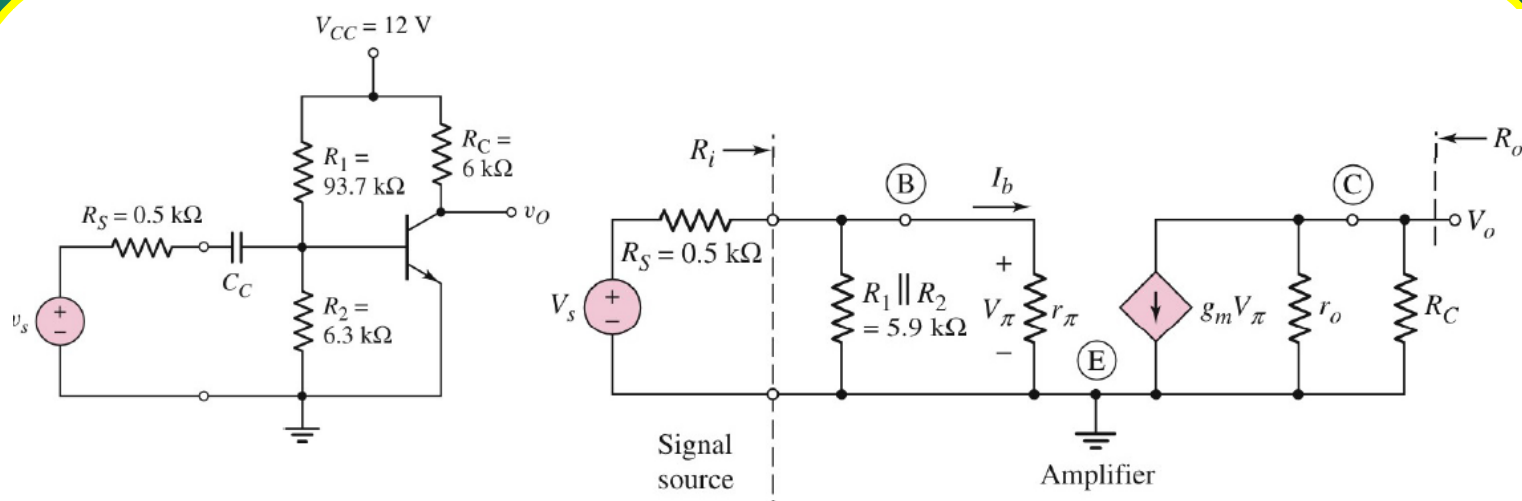CE amplifier (with voltage-divider biasing & coupling capacitor)




Input resistance: $R_i = R_1 \parallel R_2 \parallel r_\pi$

Output resistance: $R_o = r_o \parallel R_C$

[Setting $V_s = 0$ (short), then $V_\pi = 0$ & $g_m V_\pi = 0$ (open)]

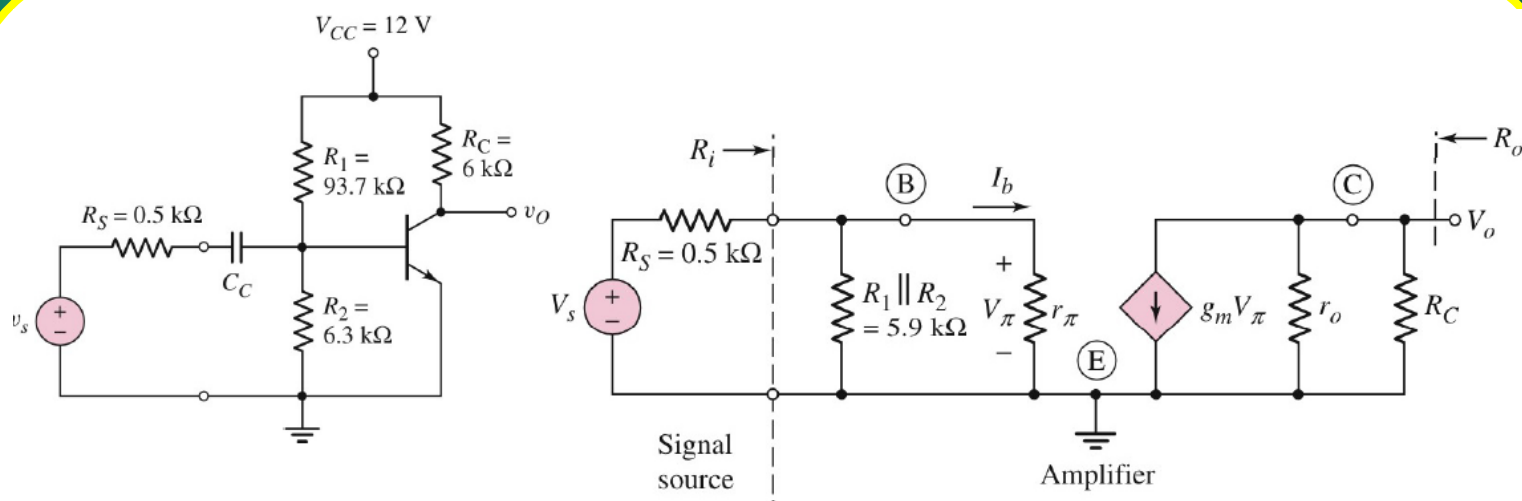CE amplifier (with voltage-divider biasing & coupling capacitor)




Input resistance: $R_i = R_1 \parallel R_2 \parallel r_\pi$


Output resistance: $R_o = r_o \parallel R_C$

[Setting $V_s = 0$ (short), then $V_\pi = 0$ & $g_m V_\pi = 0$ (open)]

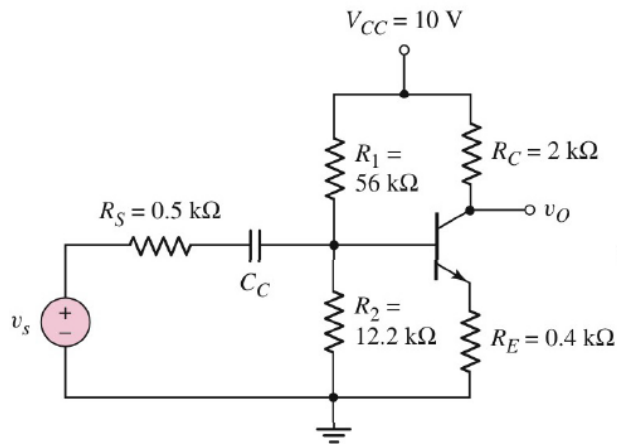
CE amplifier (with voltage-divider biasing, coupling capacitor & R_E)



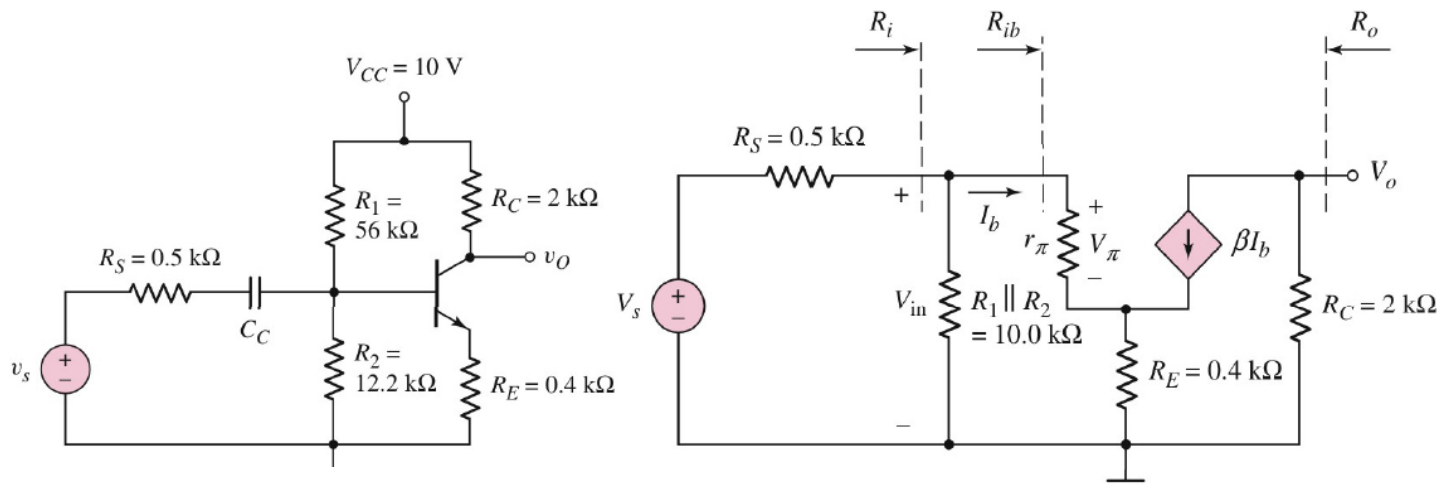CE amplifier (with voltage-divider biasing, coupling capacitor & R_E)



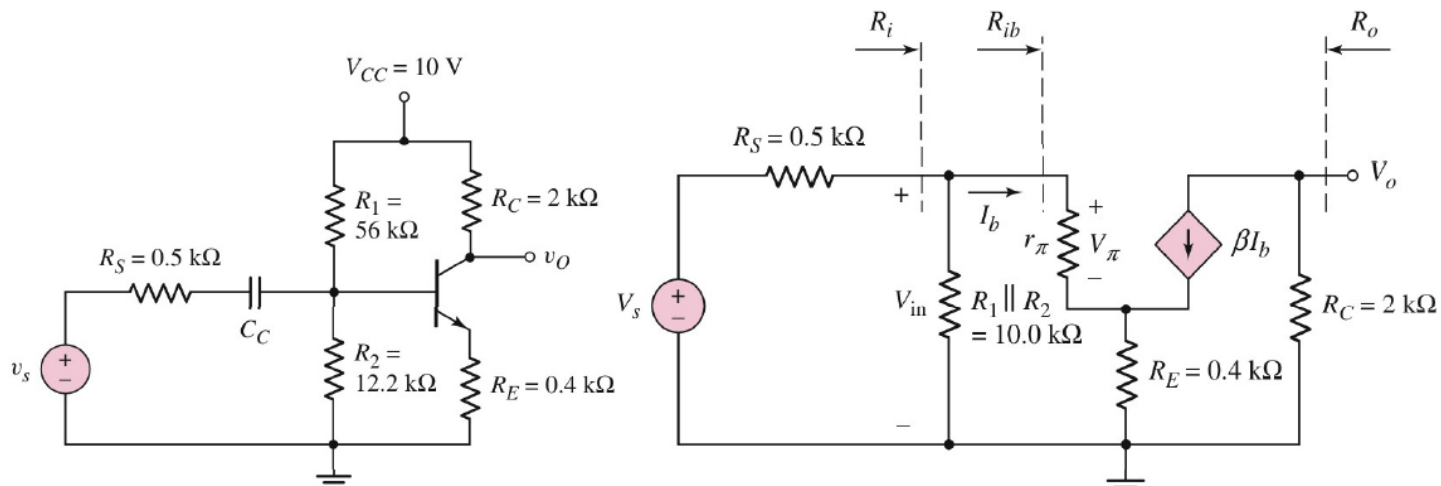CE amplifier (with voltage-divider biasing, coupling capacitor & R_E)




$$V_o = -(\beta I_b) R_C$$

$$V_{in} = I_b r_\pi + (I_b + \beta I_b) R_E$$

$$R_{ib} = \frac{V_{in}}{I_b} = r_\pi + (1 + \beta) R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

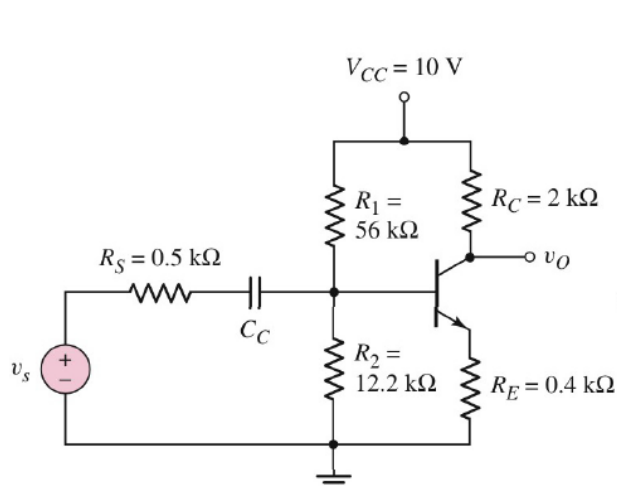CE amplifier (with voltage-divider biasing, coupling capacitor & R_E)




$$V_o = -(\beta I_b) R_C$$

$$V_{in} = I_b r_\pi + (I_b + \beta I_b) R_E$$

$$R_{ib} = \frac{V_{in}}{I_b} = r_\pi + (1 + \beta) R_E$$
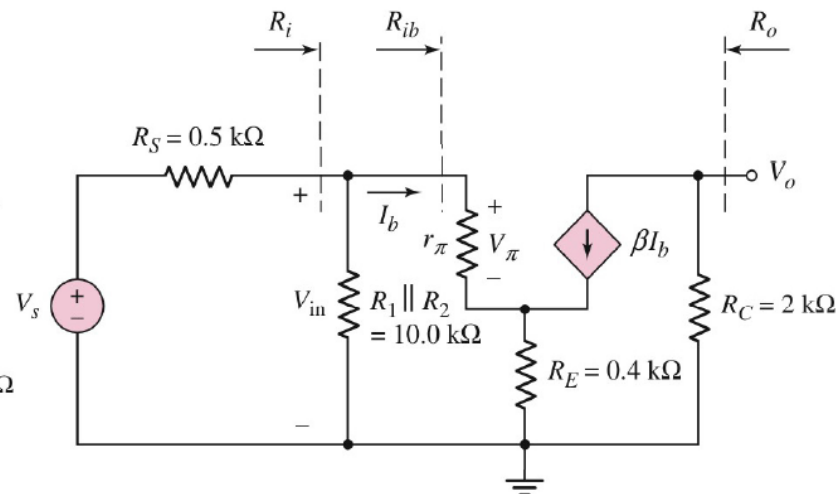
$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$



$$V_{in} = V_s \left(\frac{R_i}{R_S + R_i} \right)$$

$$A_v = \frac{V_o}{V_s} = \frac{-\beta R_C}{r_\pi + (1 + \beta) R_E} \left(\frac{R_i}{R_i + R_S} \right)$$

DC and AC Load Lines

- ❑ **DC load line is used to find Q-point**
- ❑ **AC load line is used to determine graphically the operation of a BJT amplifier**
- ❑ **DC and AC load lines are essentially different since capacitors appear as an open circuit for a DC operation but a short circuit for an AC operation**

DC Load Line

- The DC load line is found by writing a dc KVL equation for the C-E loop as follows:


$$V^+ = I_C R_C + V_{CE} + I_E (R_{E1} + R_{E2}) + V^-$$

- Noting that $I_E = [(1 + \beta) / \beta] I_C$, v_s

$$V_{CE} = (V^+ - V^-)$$

$$-I_C \left[R_C + \left(\frac{1 + \beta}{\beta} \right) (R_{E1} + R_{E2}) \right]$$

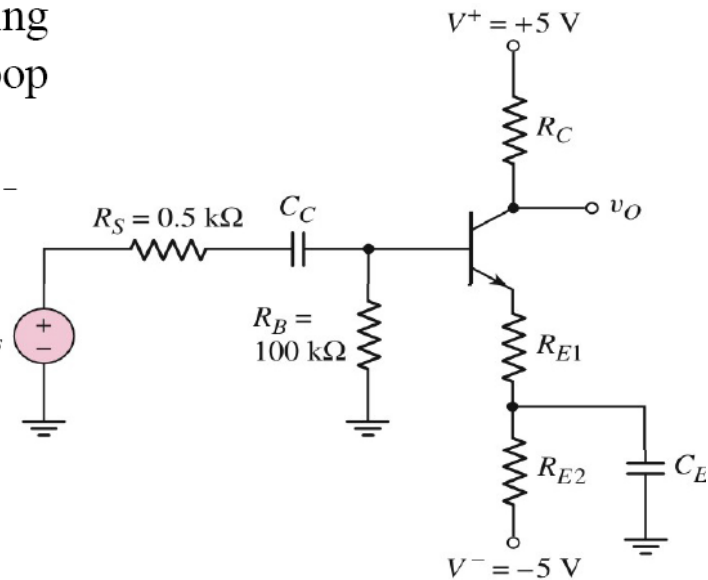- If $\beta \gg 1$, the $(1 + \beta) / \beta \approx 1$. The slope of the dc load line is $\frac{-1}{R_C + R_{E1} + R_{E2}}$



AC Load Line

- The ac load line is found by writing an ac KVL equation for the C-E loop as follows:


$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

- Assuming $(i_c \cong i_e)$


$$v_{ce} = -i_c (R_C + R_{E1})$$

- The slope of the ac load line is

$$\frac{-1}{R_C + R_{E1}}$$

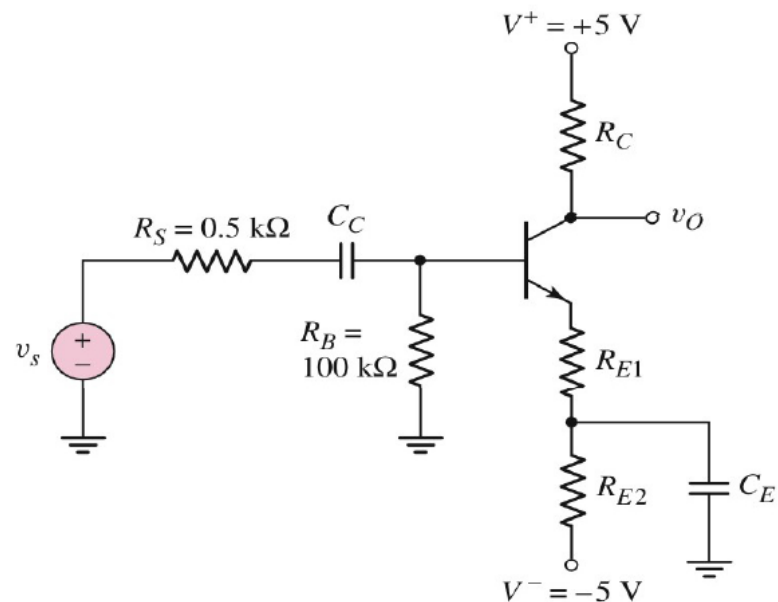


Maximum Output Symmetrical Swing

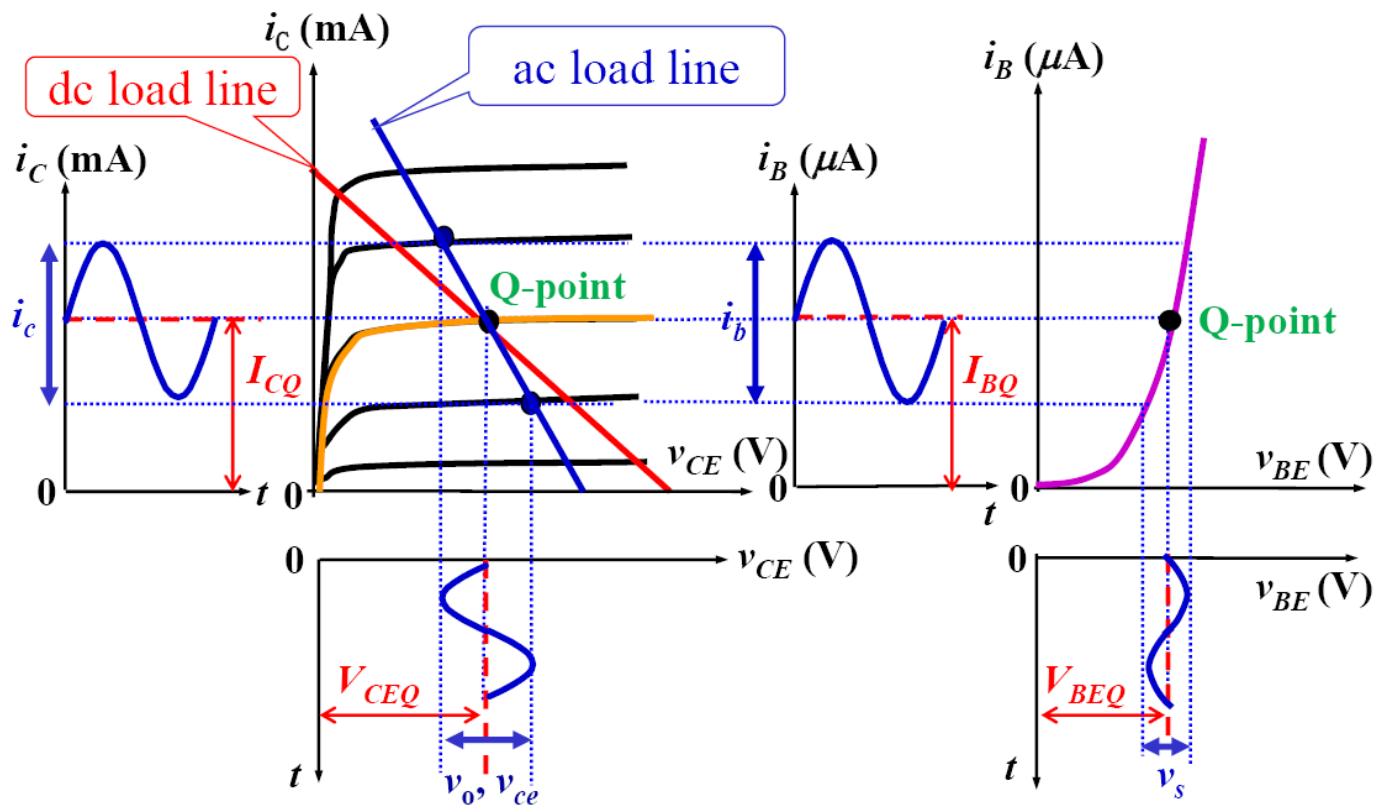


Saturation

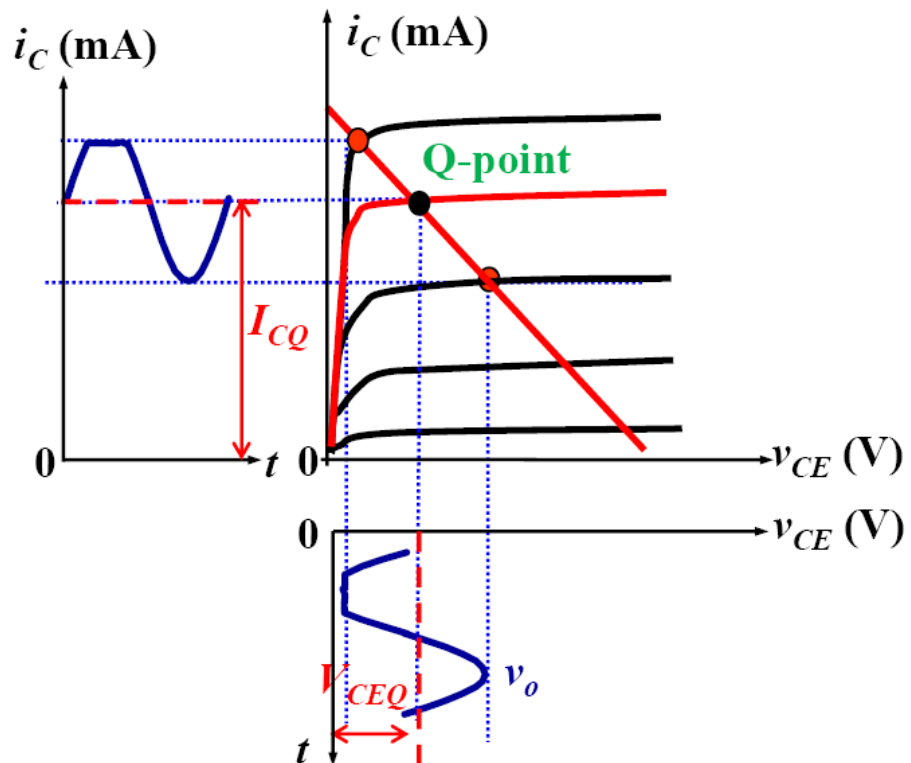- ❑ If the Q-point is not set properly, the BJT may get into saturation or cutoff, resulting in nonlinear distortion.
- ❑ If the Q-point is set too high, the BJT gets into saturation, & a reduction in I_{BQ} is required.
- ❑ Even with a proper Q-point setting, if the signal amplitude is too large, distortion will also result, & a reduction of signal amplitude is required.



Cutoff

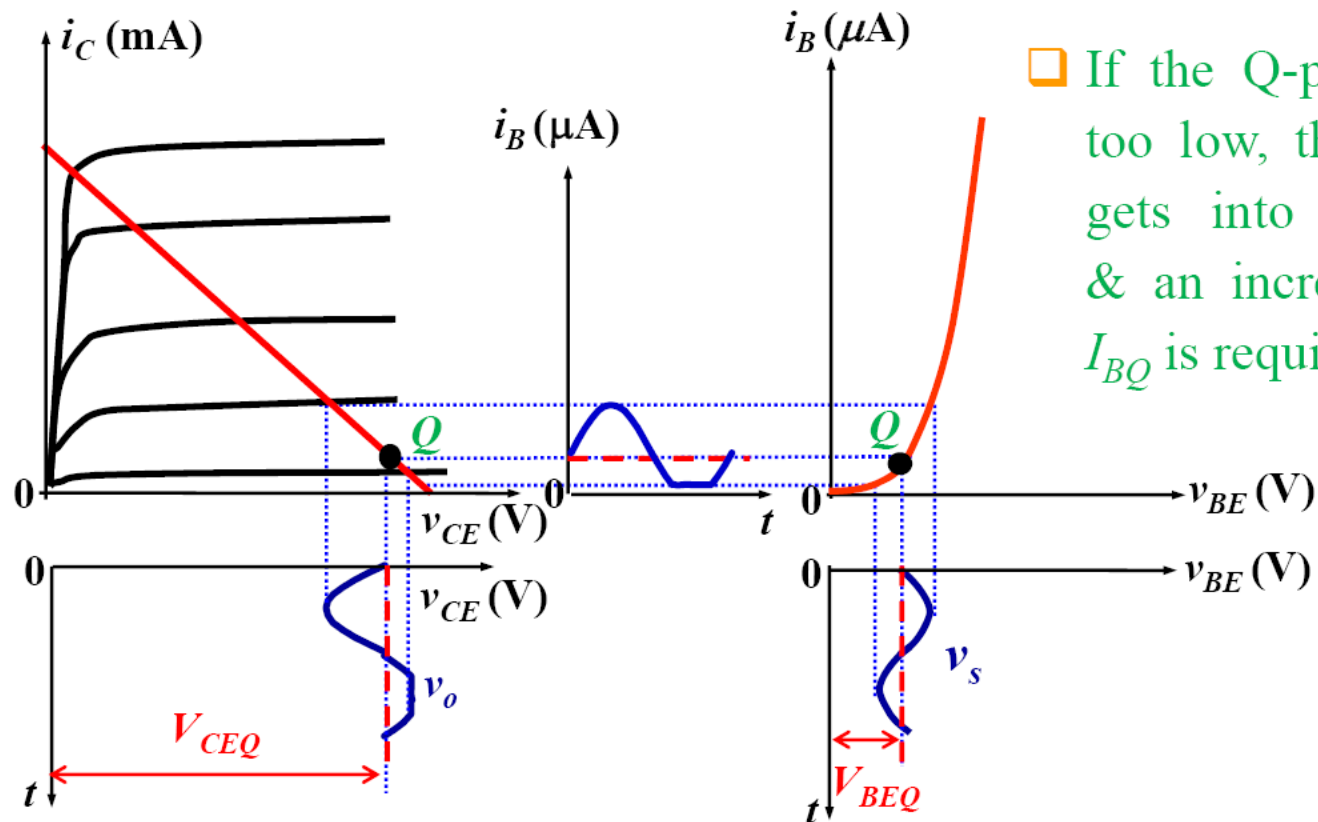

□ If the Q-point is too low, the BJT gets into cutoff, & an increase in I_{BQ} is required.