

Basic Electronic Circuits (IEC-103)


Lecture-16

Transistor Biasing Circuits


BJT 'Q' Point (Bias Point)

- ❑ Q point means Quiescent or Operating point.
- ❑ Very important for amplifiers because wrong 'Q' point selection increases amplifier distortion.
- ❑ Need to have a stable 'Q' point, meaning the operating point should not be sensitive to variation to temperature or BJT β (h_{FE}), which can vary widely.


Typical Amplifier Operation

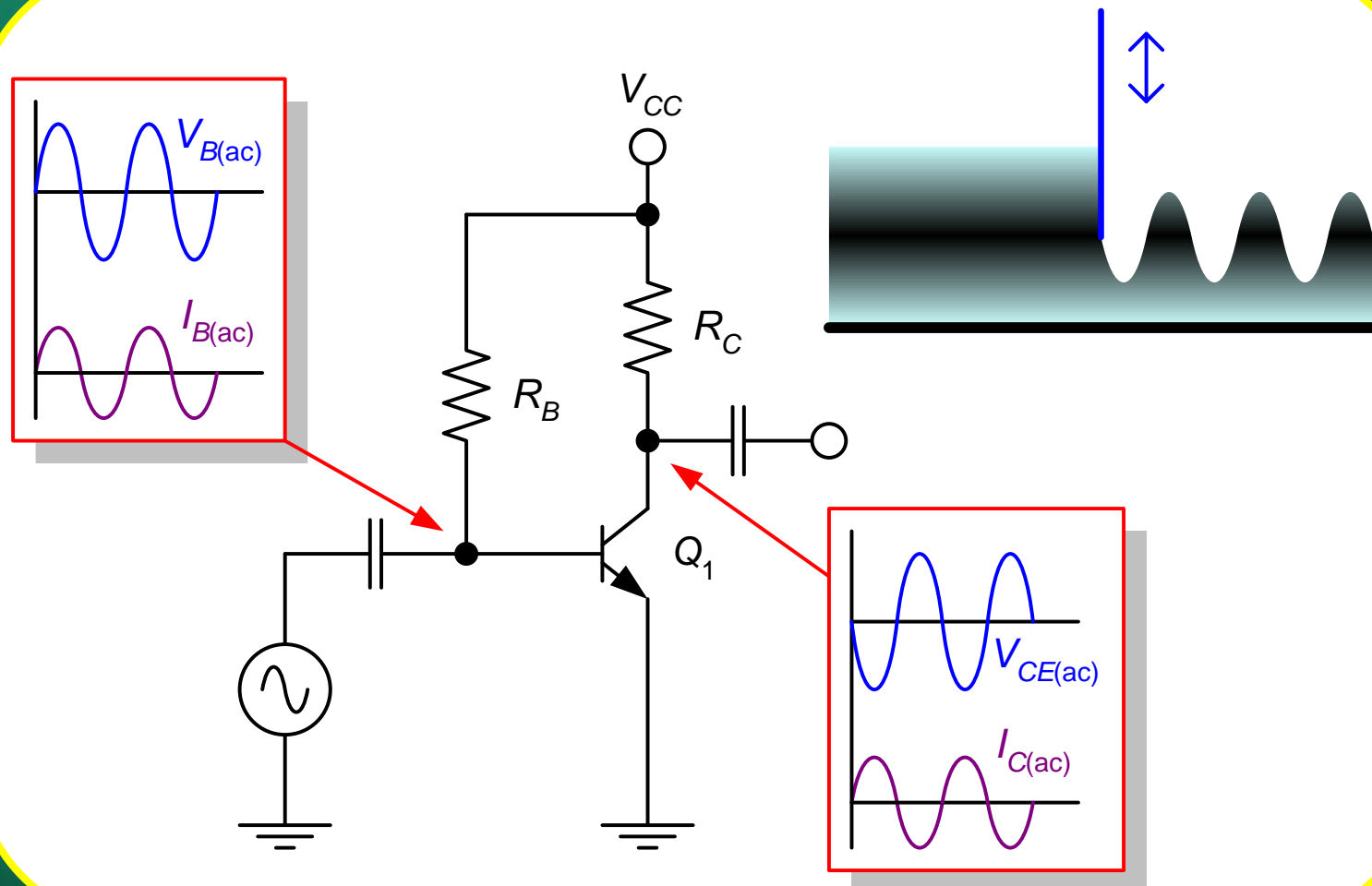

A Generic DC Load Line

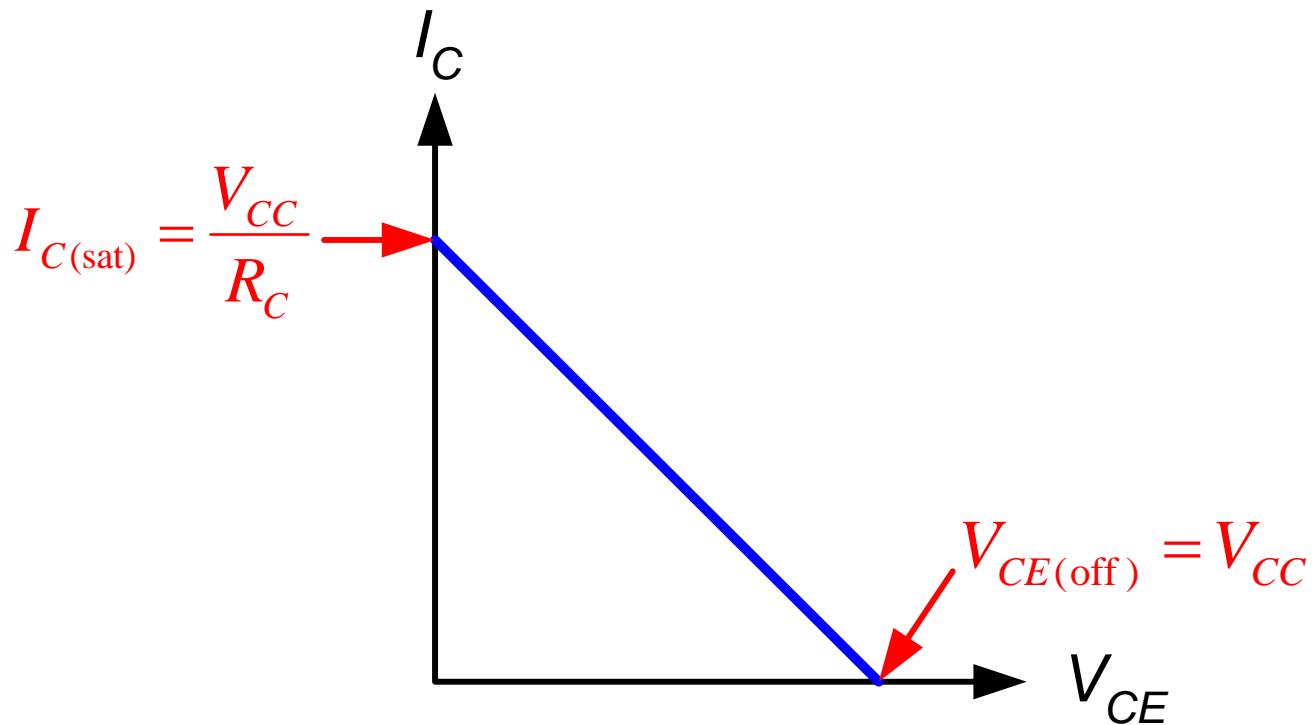


A Generic DC Load Line

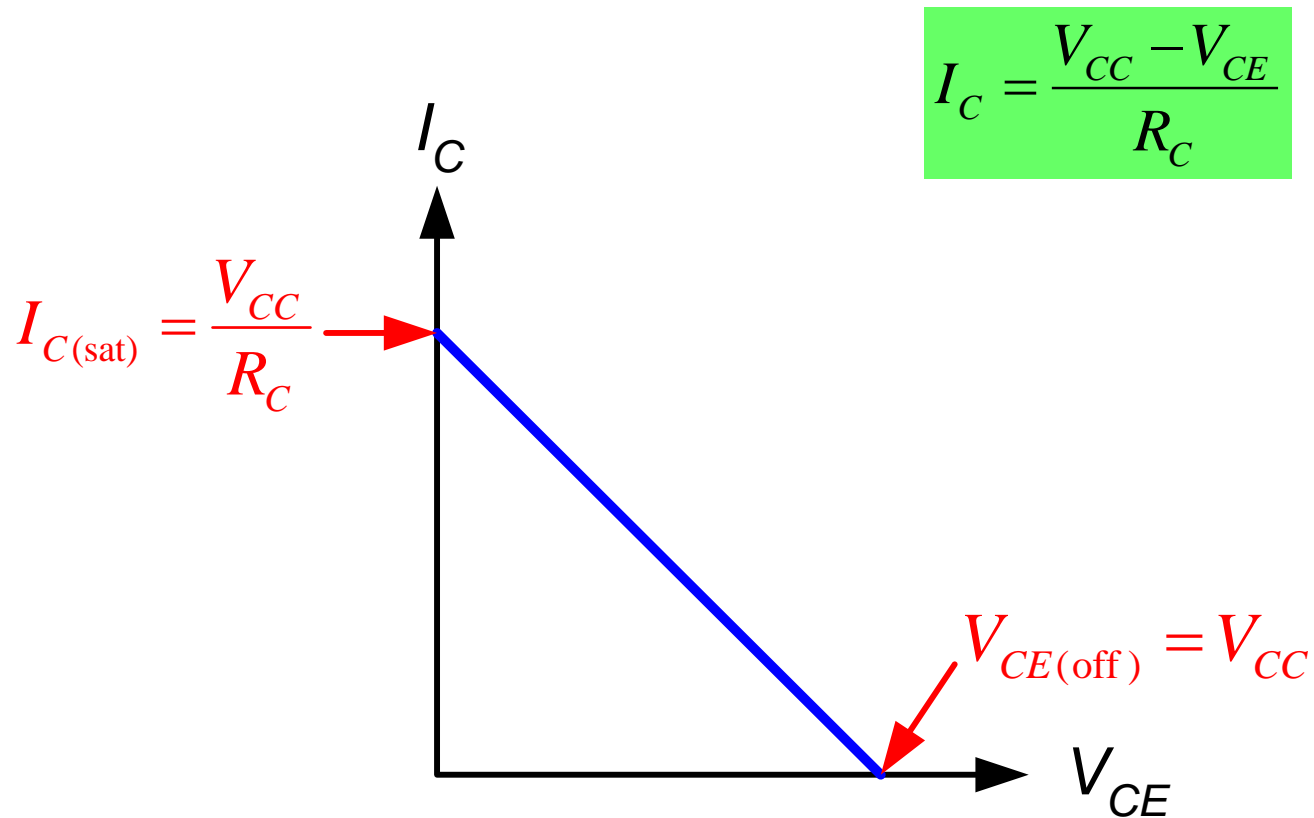


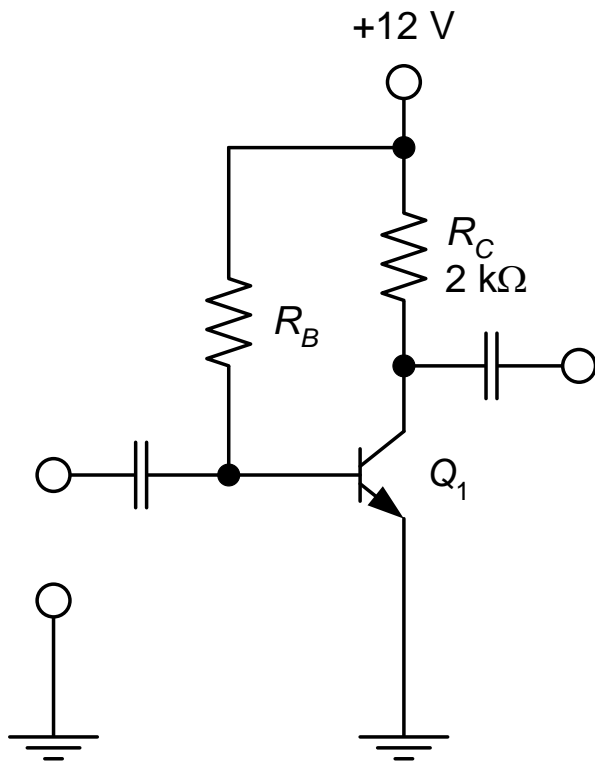
Example

Plot the dc load line for the circuit shown below.




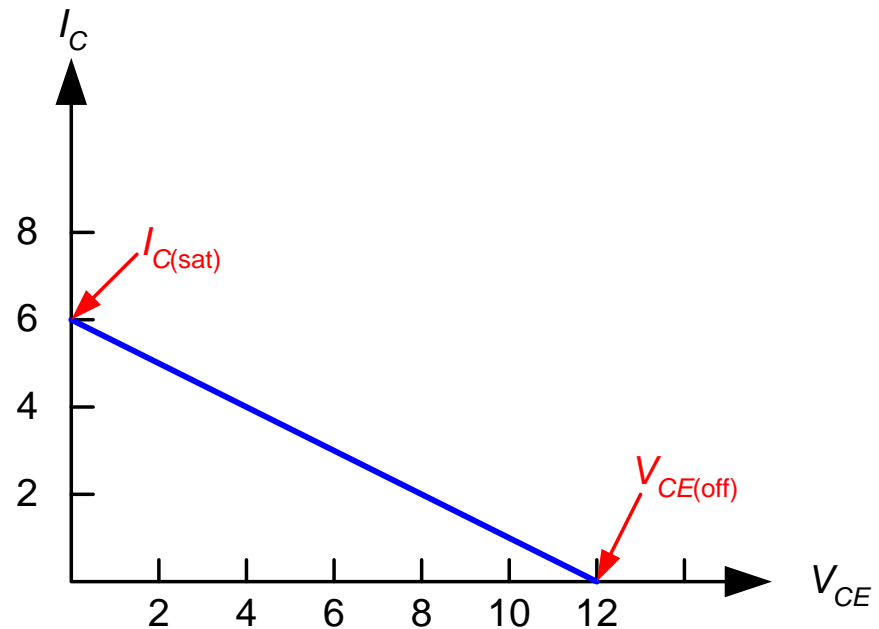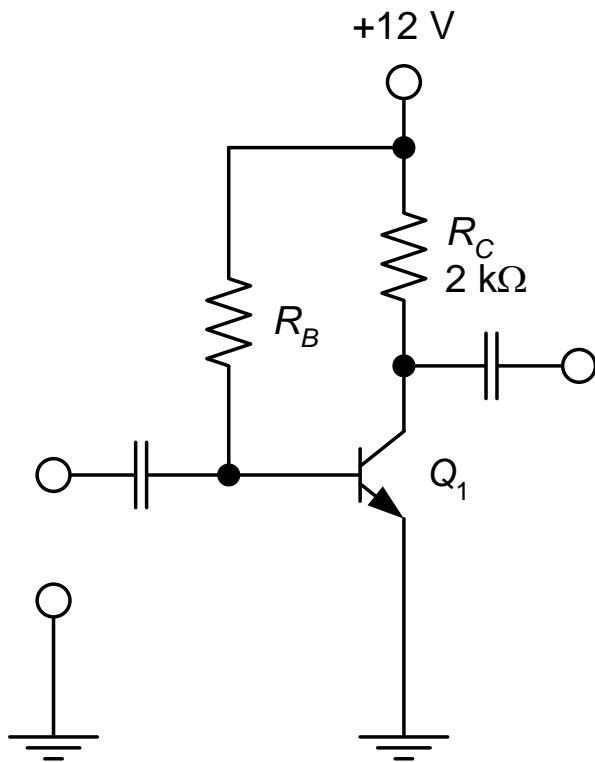Example

Plot the dc load line for the circuit shown below.




Optimum Q-point

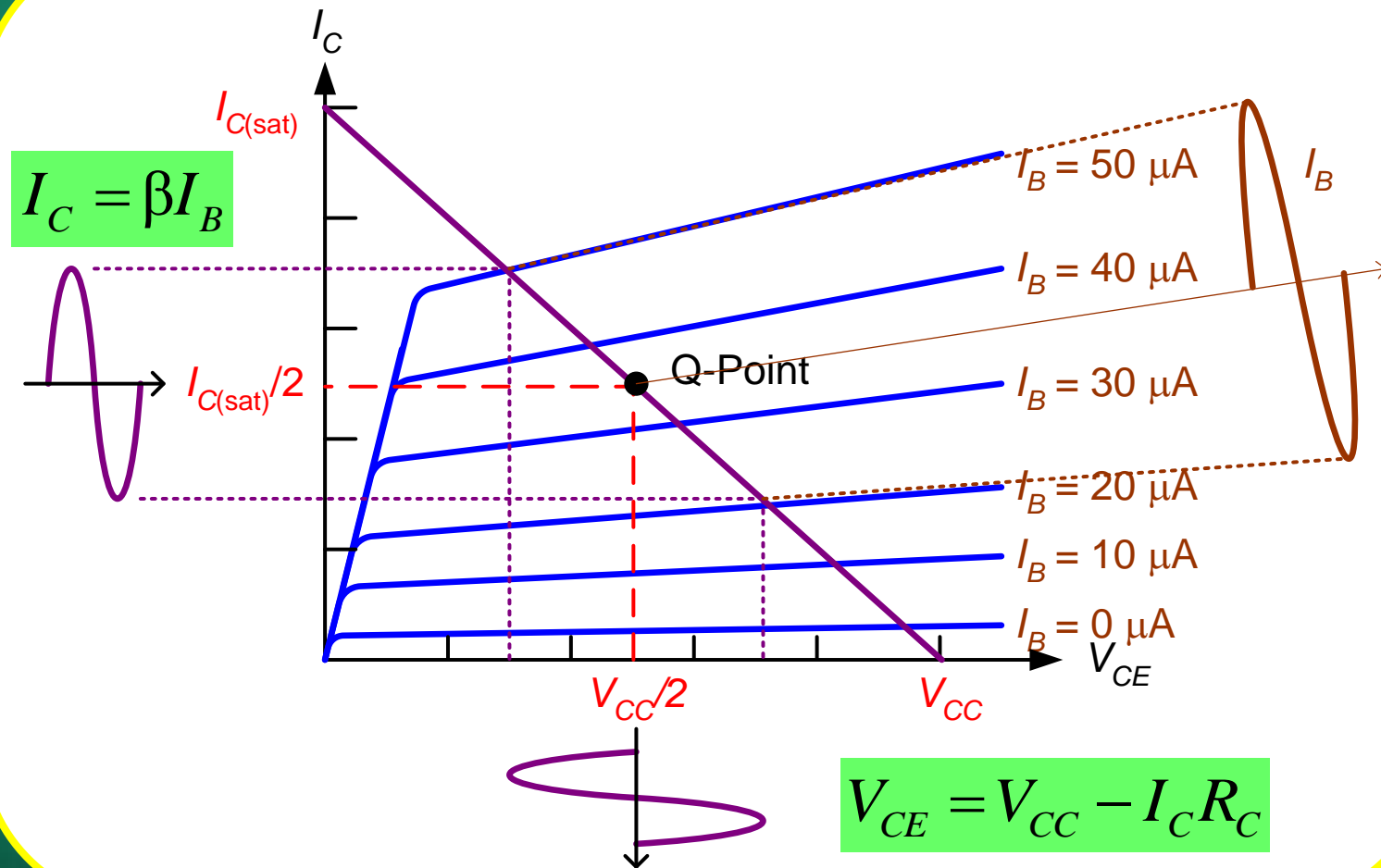


Bias Circuits

- **Different types bias circuits**
 - **Base Bias**
 - **Voltage Divider Bias**
 - **Emitter Bias**
 - **Collector Feedback Bias**
 - **Emitter Feedback Bias**

Base Bias (Fixed Bias)

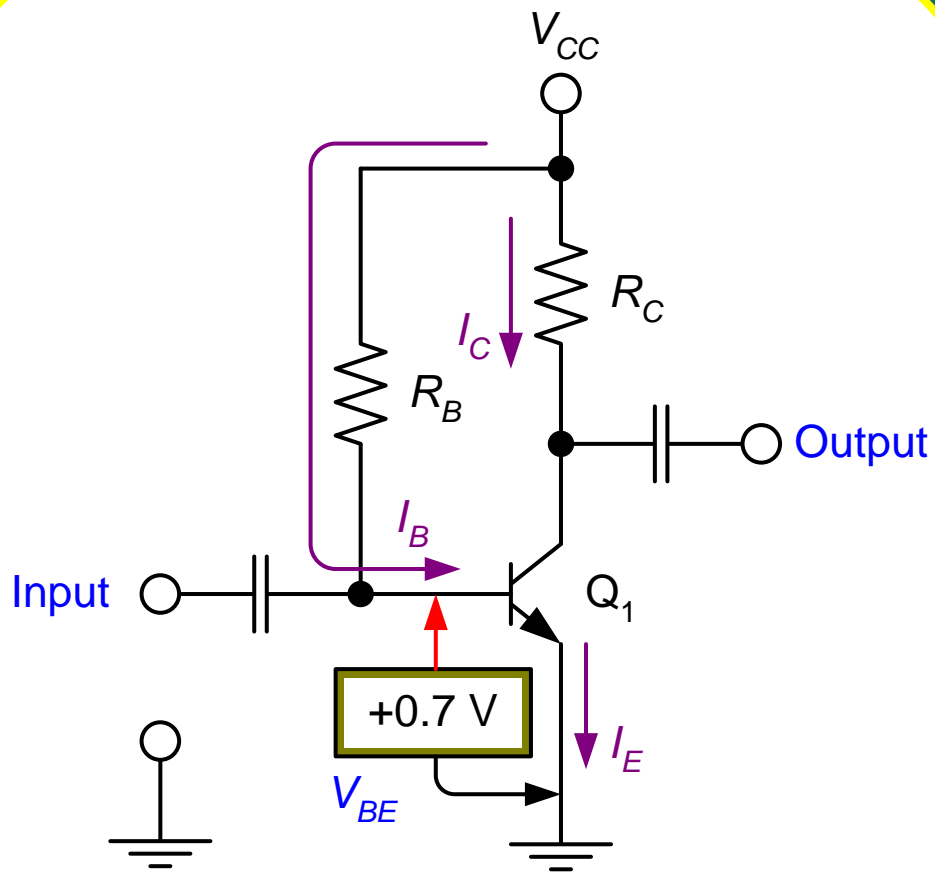


Base Bias (Fixed Bias)

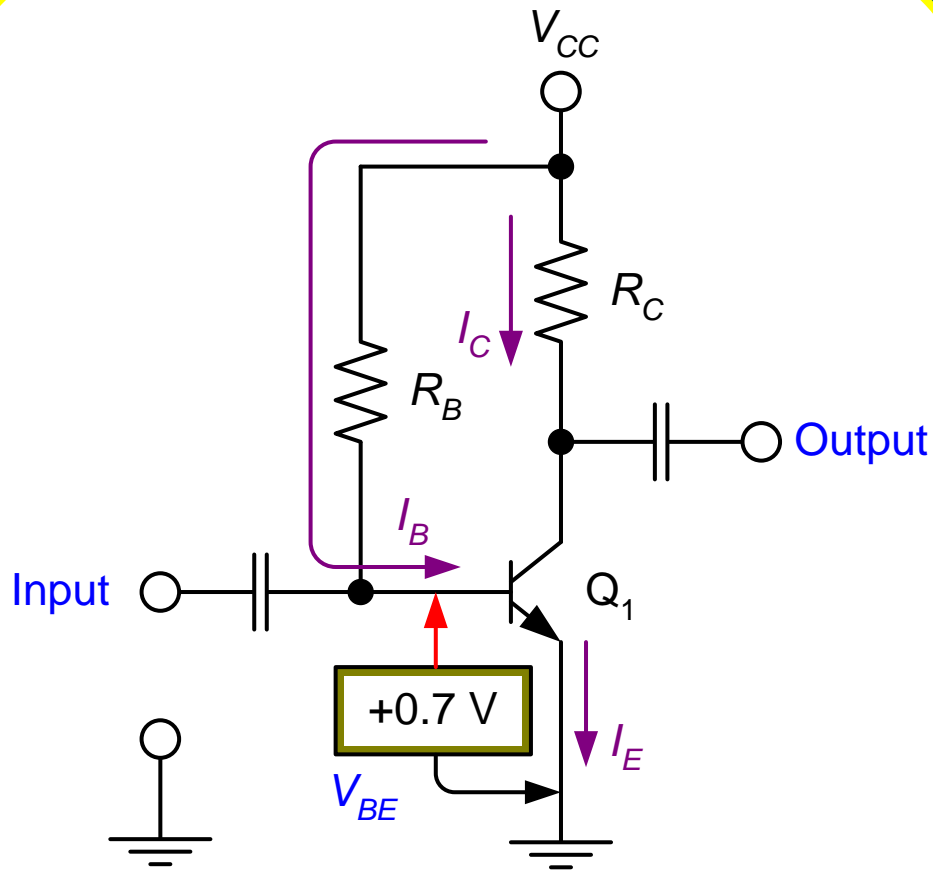

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


Base Bias (Fixed Bias)

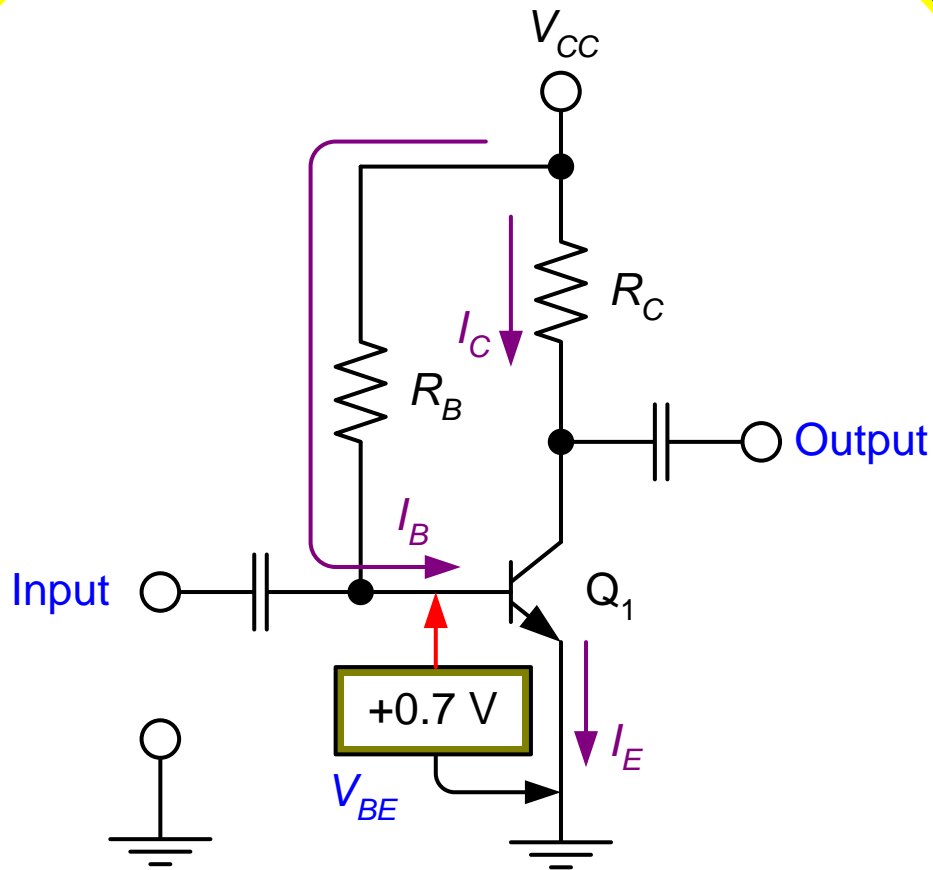

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

Base Bias (Fixed Bias)

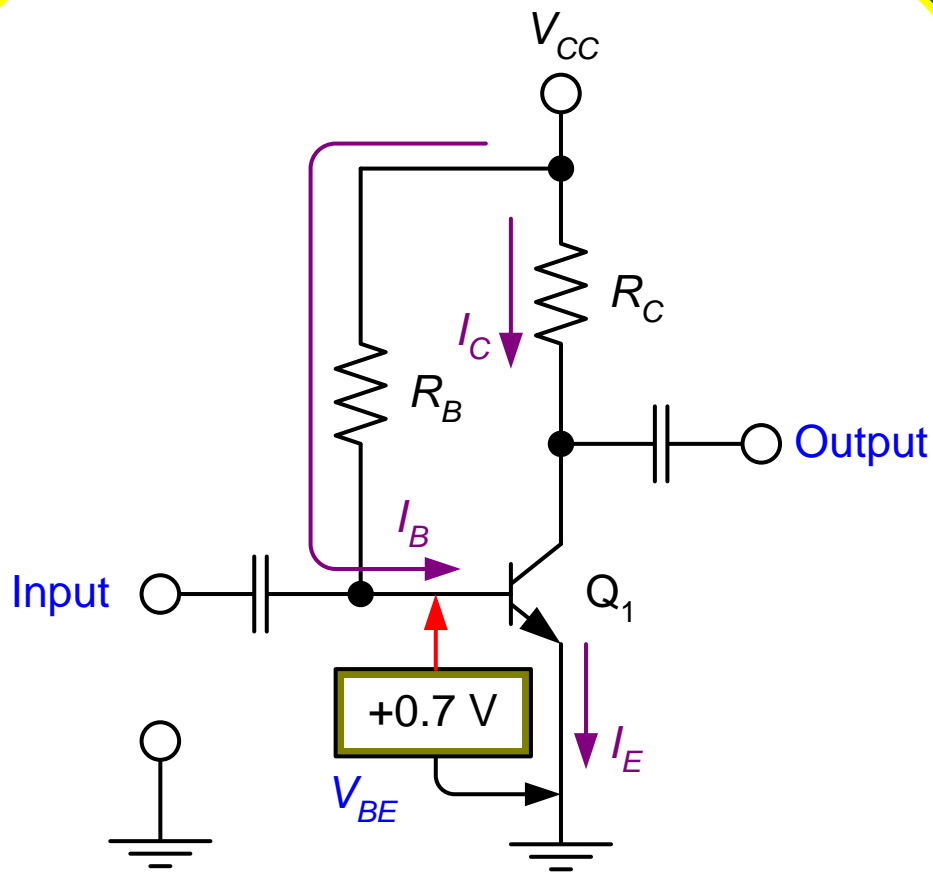


$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

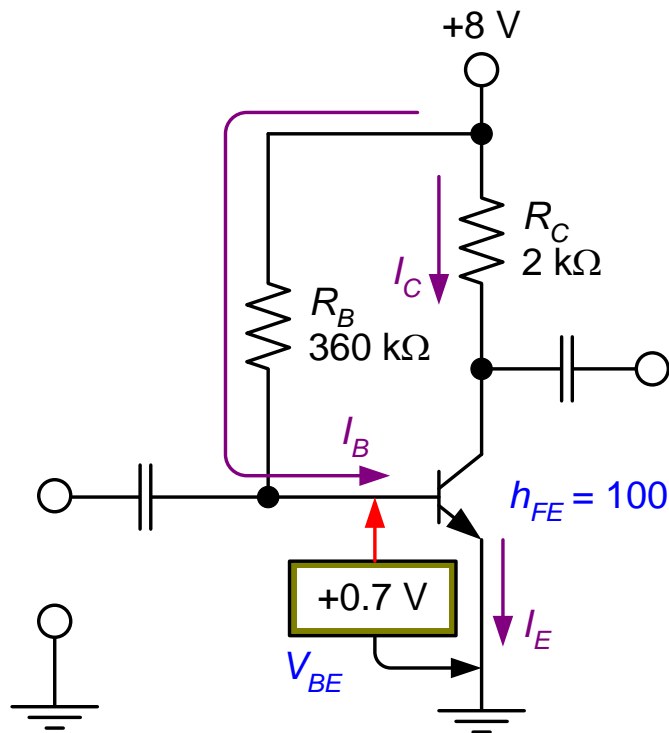
Example

Find the Q-point of the transistor given in the circuit.



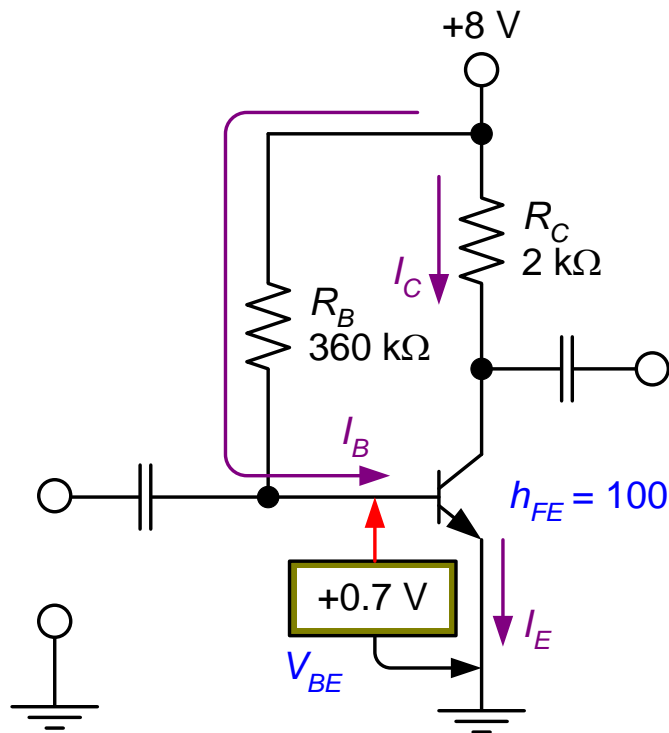Example


Find the Q-point of the transistor given in the circuit.



$$I_B = \frac{V_{CC} - 0.7 \text{ V}}{R_B} = \frac{8 \text{ V} - 0.7 \text{ V}}{360 \text{ k}\Omega} = 20.28 \mu\text{A}$$

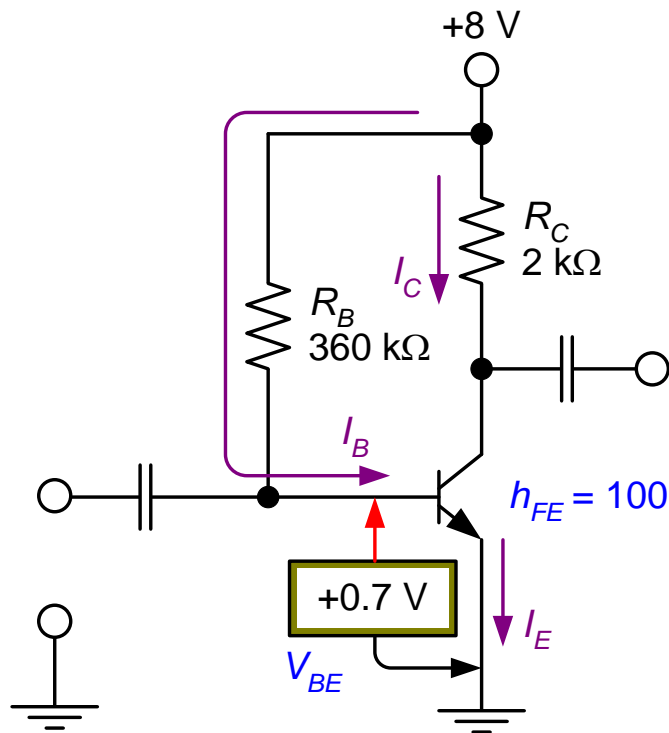Example

Find the Q-point of the transistor given in the circuit.




$$I_B = \frac{V_{CC} - 0.7 \text{ V}}{R_B} = \frac{8 \text{ V} - 0.7 \text{ V}}{360 \text{ k}\Omega} = 20.28 \mu\text{A}$$

$$I_C = h_{FE} I_B = (100)(20.28 \mu\text{A}) = 2.028 \text{ mA}$$

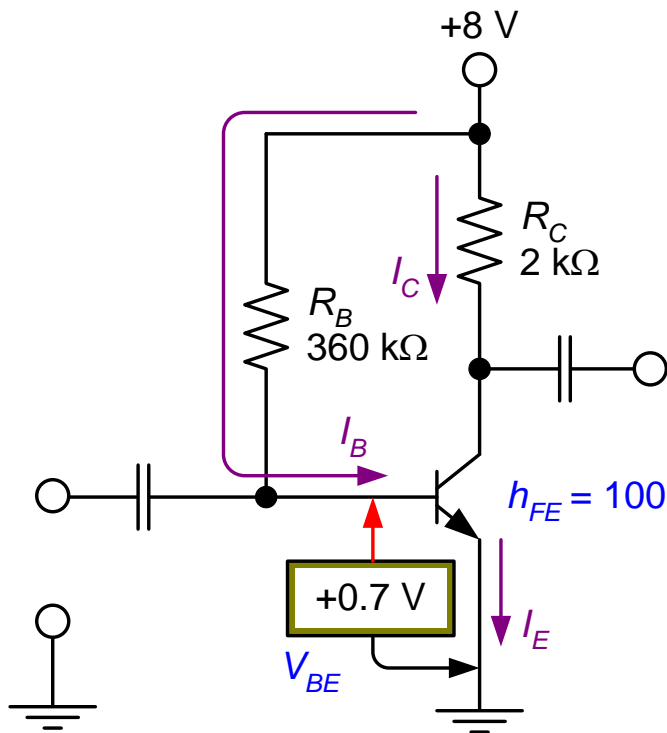Example

Find the Q-point of the transistor given in the circuit.



$$I_B = \frac{V_{CC} - 0.7\text{V}}{R_B} = \frac{8\text{V} - 0.7\text{V}}{360\text{k}\Omega} = 20.28\mu\text{A}$$

$$I_C = h_{FE} I_B = (100)(20.28\mu\text{A}) = 2.028\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 8\text{V} - (2.028\text{mA})(2\text{k}\Omega) = 3.94\text{V}$$

Example

Construct the dc load line for the circuit shown in previous example and plot the Q-point from the values obtained. Determine whether the circuit is midpoint biased.

Example

Construct the dc load line for the circuit shown in previous example and plot the Q-point from the values obtained. Determine whether the circuit is midpoint biased.

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{8\text{V}}{2\text{k}\Omega} = 4\text{mA}$$

Example


Construct the dc load line for the circuit shown in previous example and plot the Q-point from the values obtained. Determine whether the circuit is midpoint biased.

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{8\text{V}}{2\text{k}\Omega} = 4\text{mA}$$

$$V_{CE(\text{off})} = V_{CC} = 8\text{V}$$

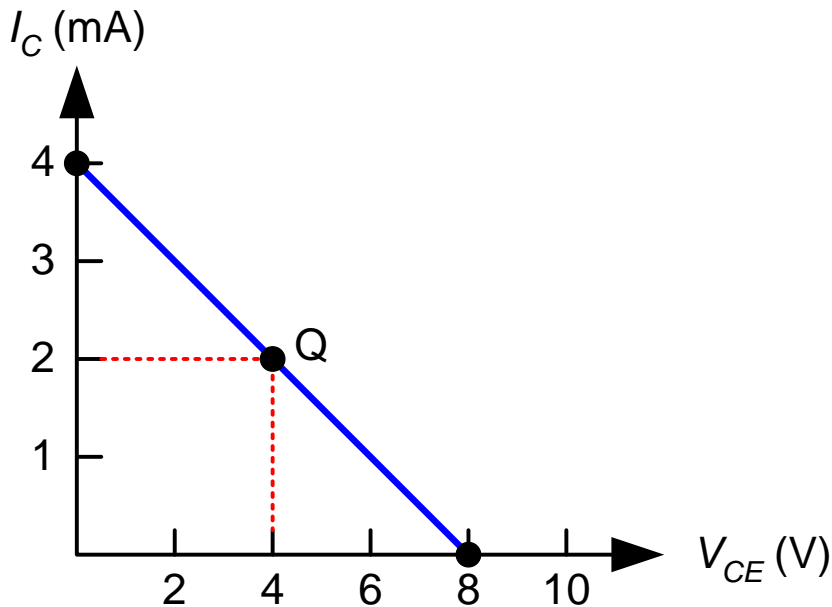Example

Construct the dc load line for the circuit shown in previous example and plot the Q-point from the values obtained. Determine whether the circuit is midpoint biased.




$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{8\text{V}}{2\text{k}\Omega} = 4\text{mA}$$

$$V_{CE(\text{off})} = V_{CC} = 8\text{V}$$

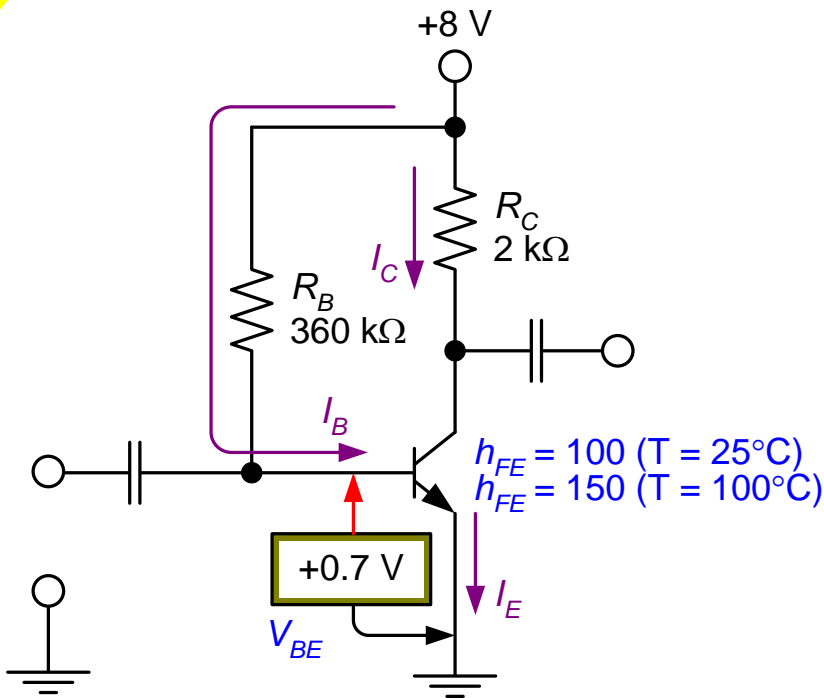
Example (Q-point Shift)

The transistor in the circuit has values of $h_{FE}=100$ when $T=25\text{ }^{\circ}\text{C}$ and $h_{FE}=150$ when $T=100\text{ }^{\circ}\text{C}$. Determine the Q-point values of I_C and V_{CE} at both of these temperatures.



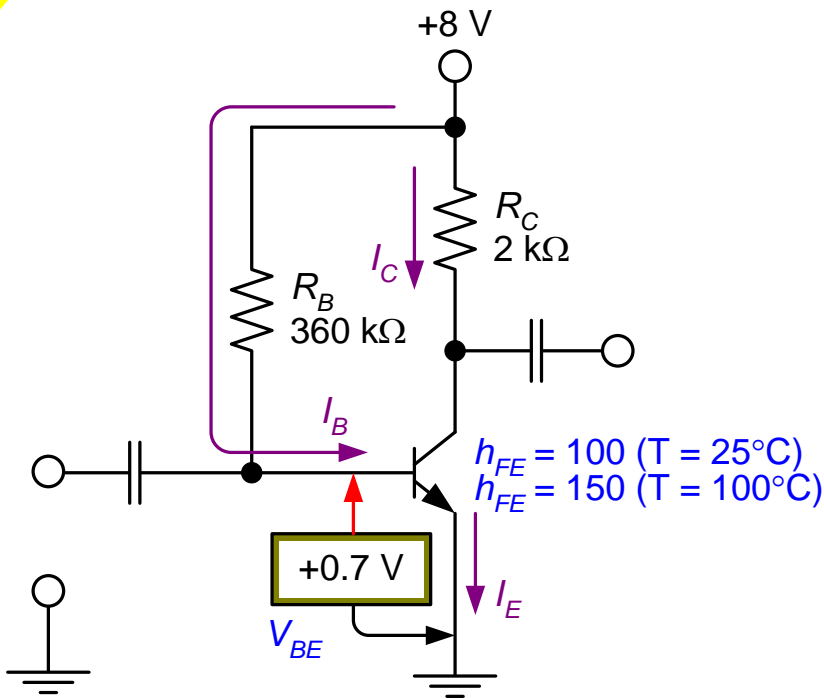
Example (Q-point Shift)

The transistor in the circuit has values of $h_{FE}=100$ when $T=25\text{ }^{\circ}\text{C}$ and $h_{FE}=150$ when $T=100\text{ }^{\circ}\text{C}$. Determine the Q-point values of I_C and V_{CE} at both of these temperatures.




Temp($^{\circ}\text{C}$)	I_B (μA)	I_C (mA)	V_{CE} (V)
25	20.28	2.028	3.94
100	20.28	3.04	1.92

Base Bias Characteristics

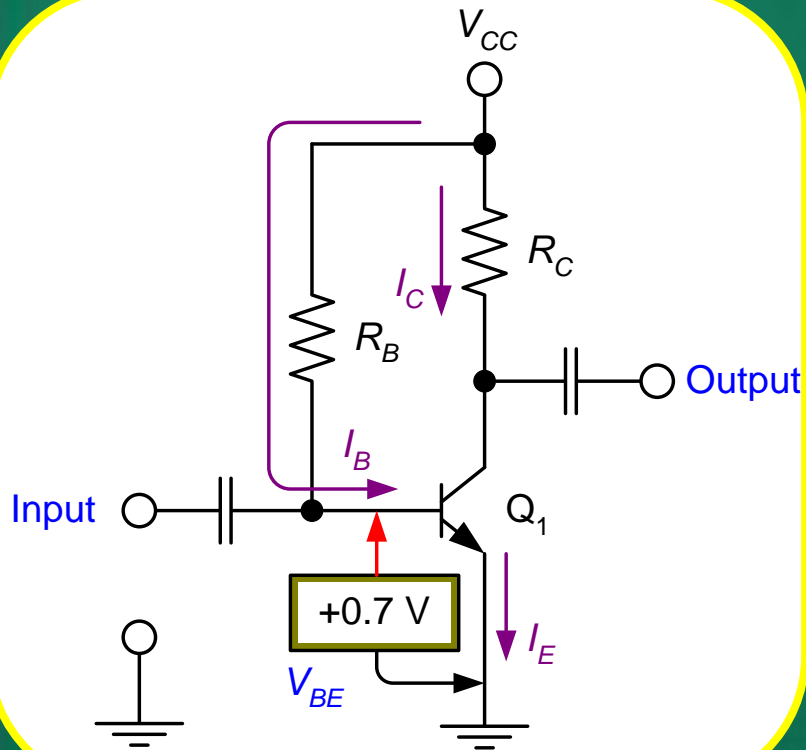


Base Bias Characteristics

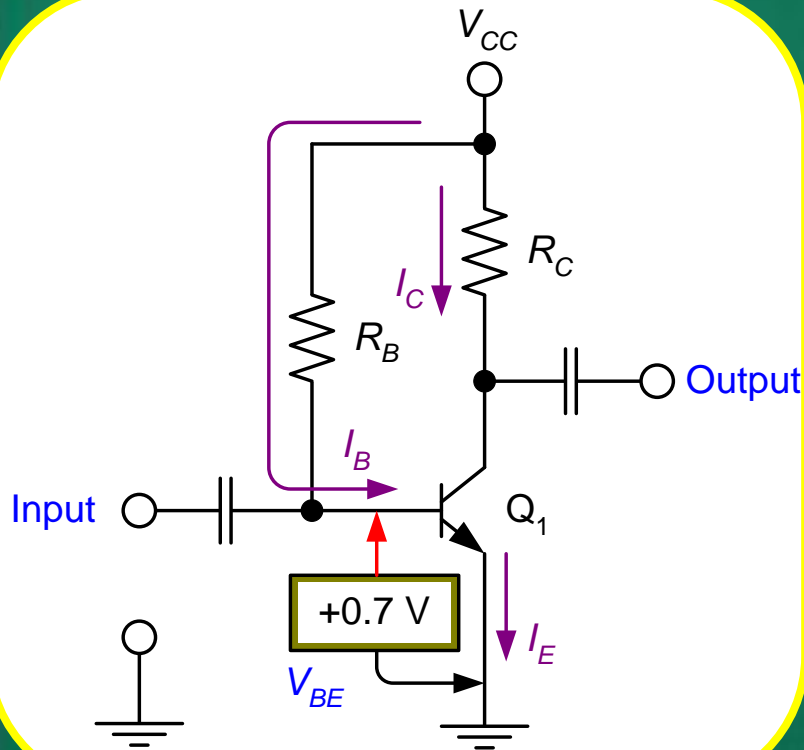

Circuit recognition: A single resistor (R_B) between the base terminal and V_{CC} . No emitter resistor.

Base Bias Characteristics

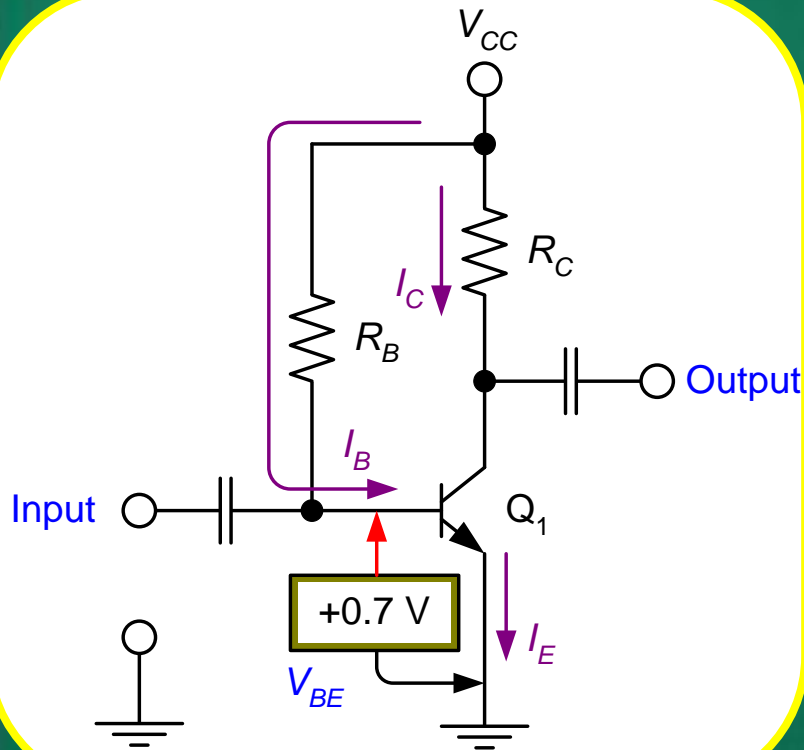

Circuit recognition: A single resistor (R_B) between the base terminal and V_{CC} . No emitter resistor.


Advantage: Circuit simplicity.

Disadvantage: Q-point shift with temp.

Applications: Switching circuits only.

Base Bias Characteristics

Load line equations:

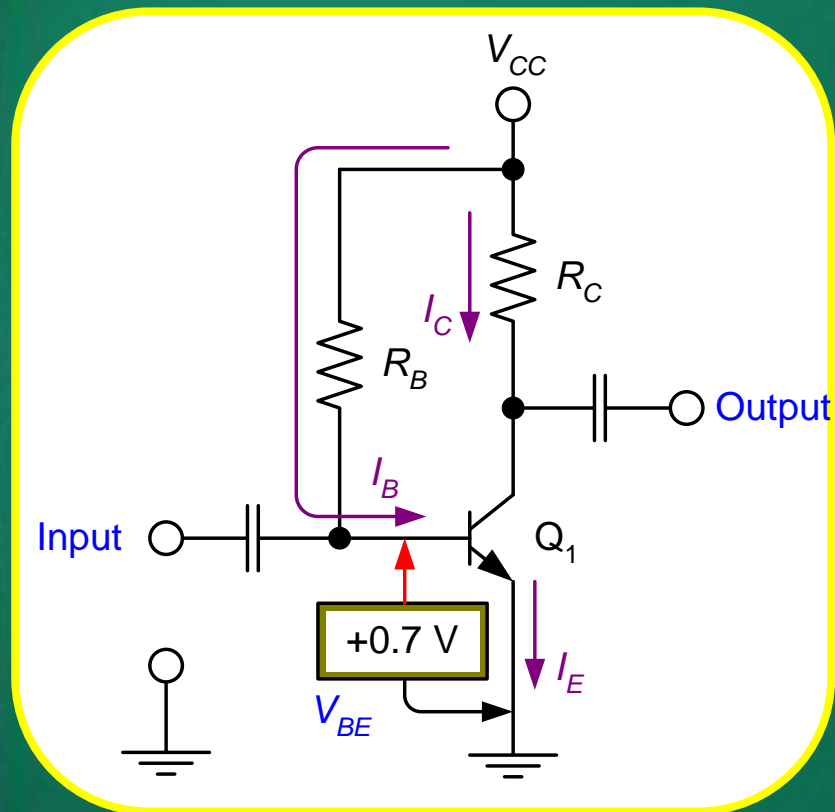


Base Bias Characteristics


Load line equations:

$$I_{C(\text{sat})} \cong \frac{V_{CC}}{R_C}$$

$$V_{CE(\text{off})} = V_{CC}$$

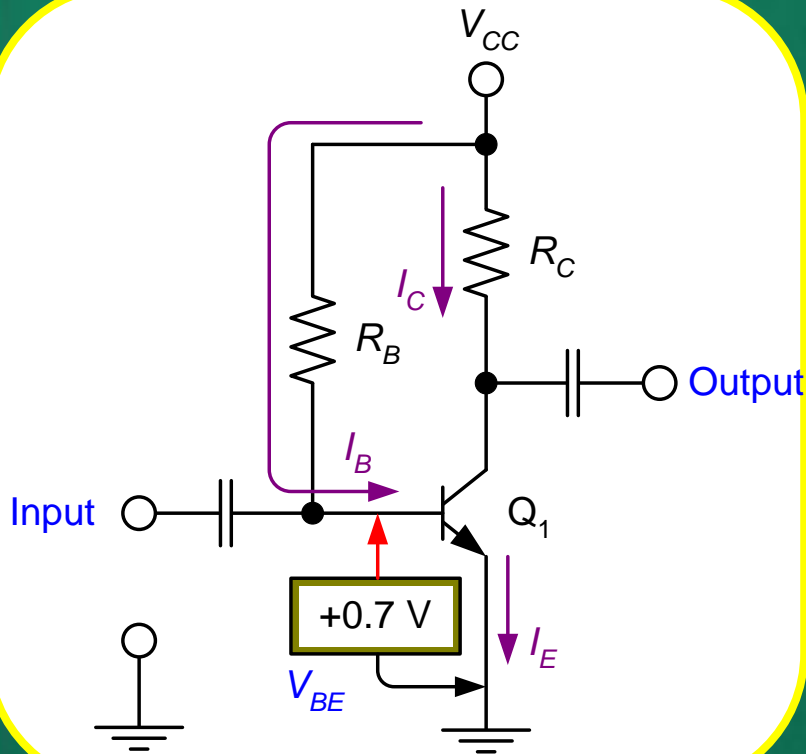

Base Bias Characteristics

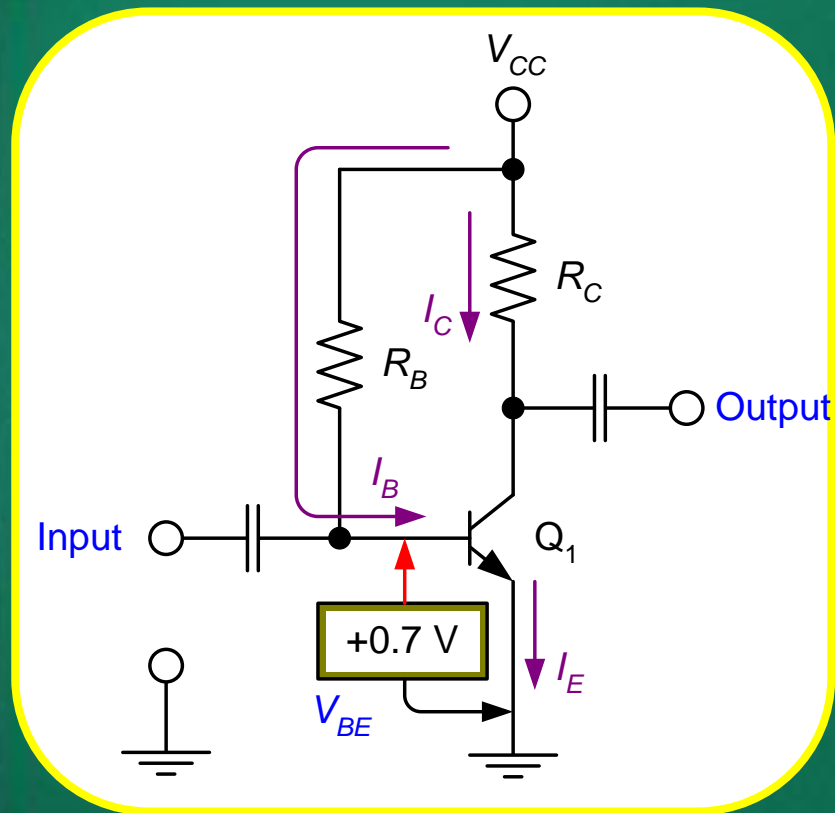


Load line equations:

$$I_{C(\text{sat})} \cong \frac{V_{CC}}{R_C}$$

$$V_{CE(\text{off})} = V_{CC}$$

Q-point equations:

Base Bias Characteristics

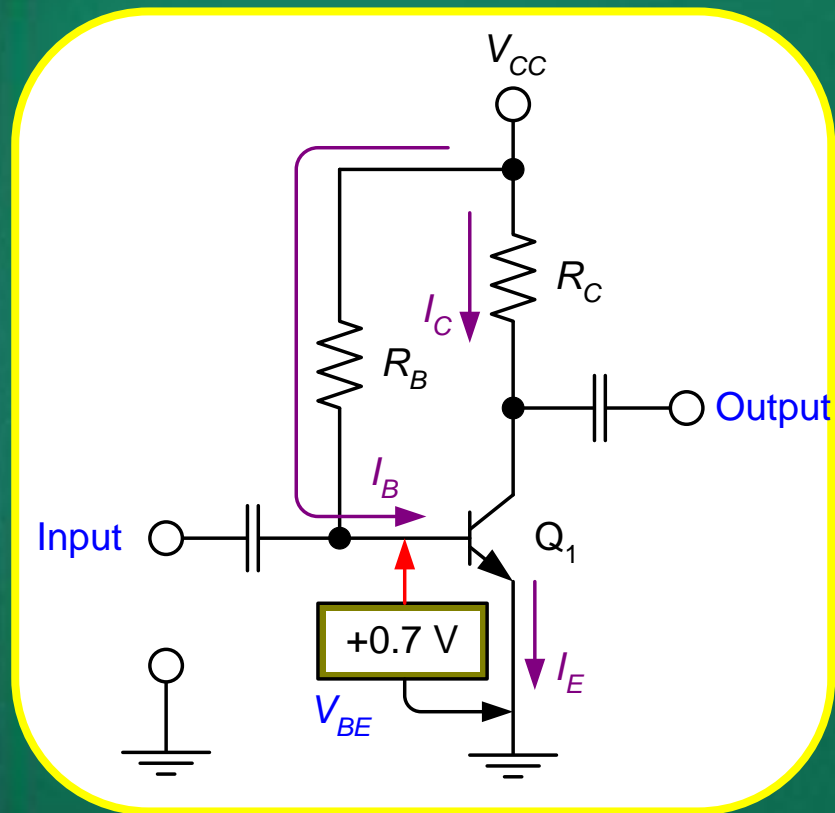

Load line equations:

$$I_{C(\text{sat})} \cong \frac{V_{CC}}{R_C}$$

$$V_{CE(\text{off})} = V_{CC}$$


Q-point equations:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = h_{FE} I_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

Voltage Divider Bias

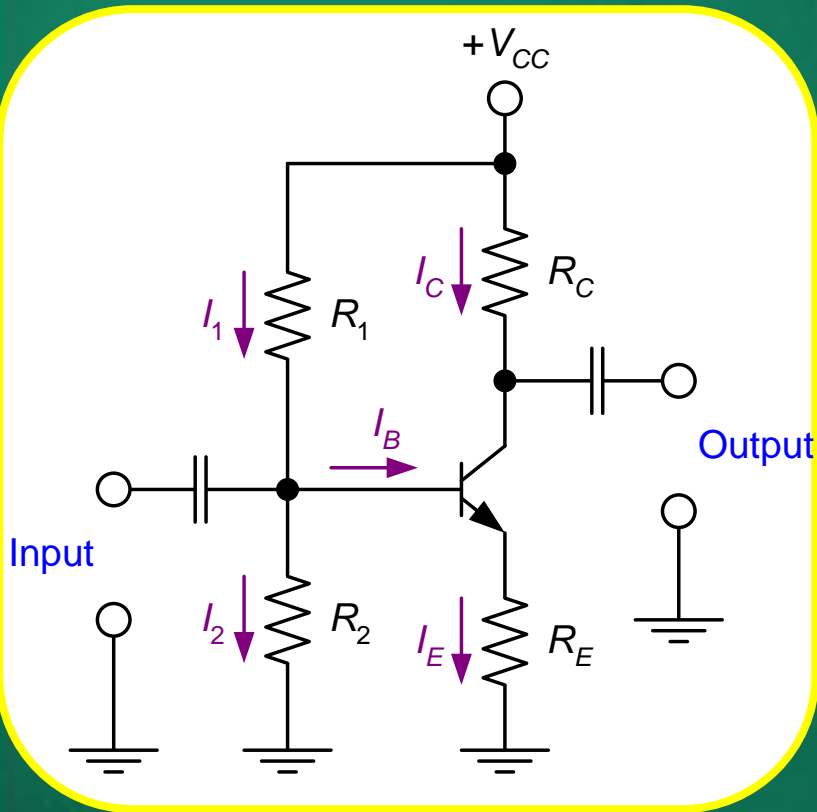


Voltage Divider Bias

Assume that $I_2 > 10I_B$.

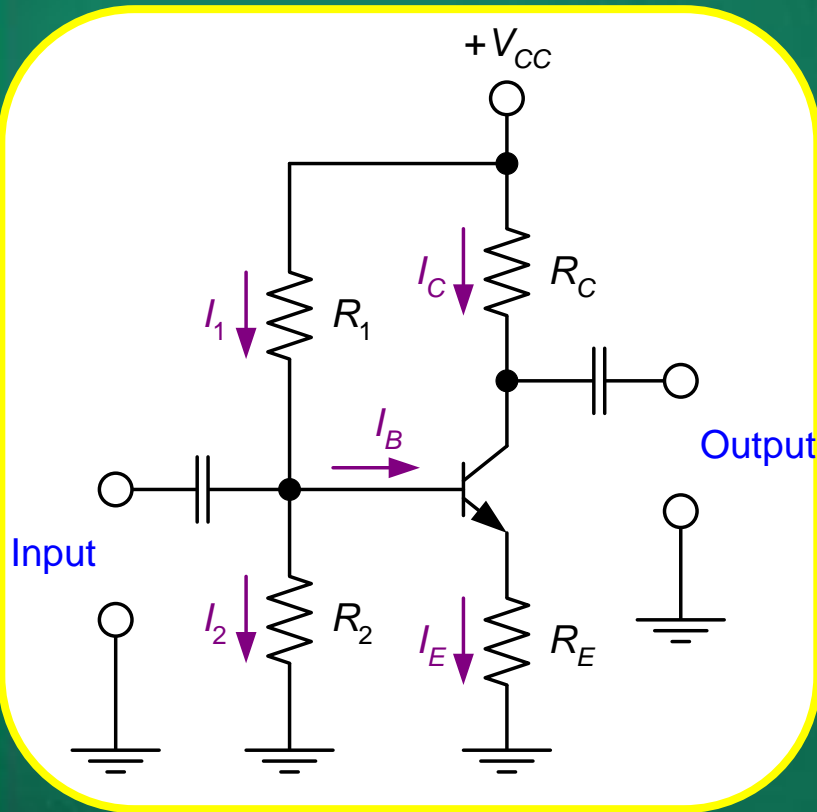

Voltage Divider Bias


Assume that $I_2 > 10I_B$.

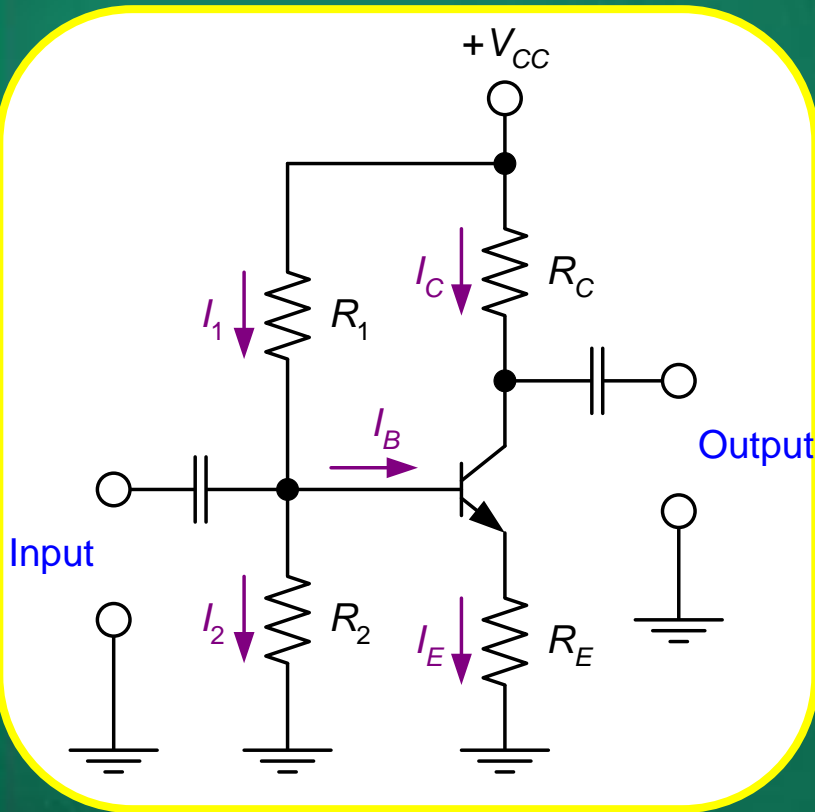

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

Voltage Divider Bias

Assume that $I_2 > 10I_B$.

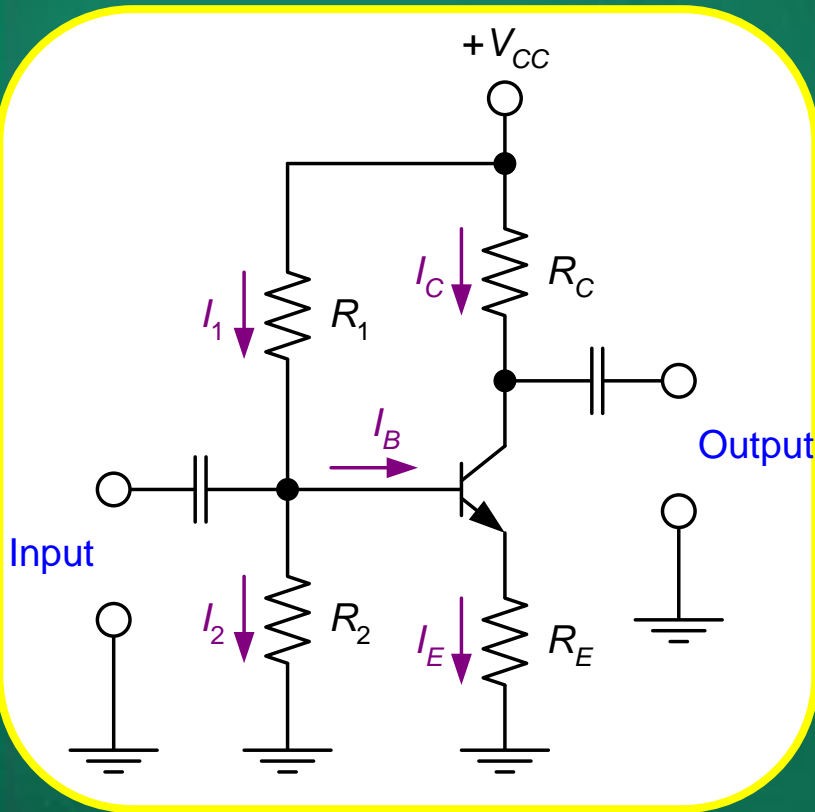


$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_E = V_B - 0.7V$$

Voltage Divider Bias

Assume that $I_2 > 10I_B$.

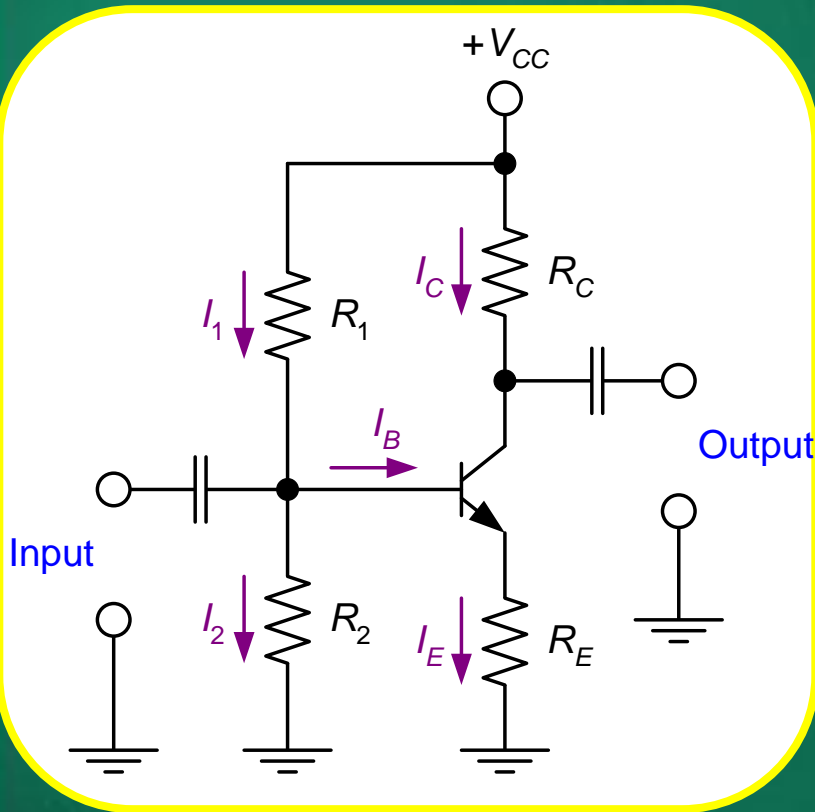


$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_E = V_B - 0.7V$$

$$I_E = \frac{V_E}{R_E}$$

Voltage Divider Bias

Assume that $I_2 > 10I_B$.

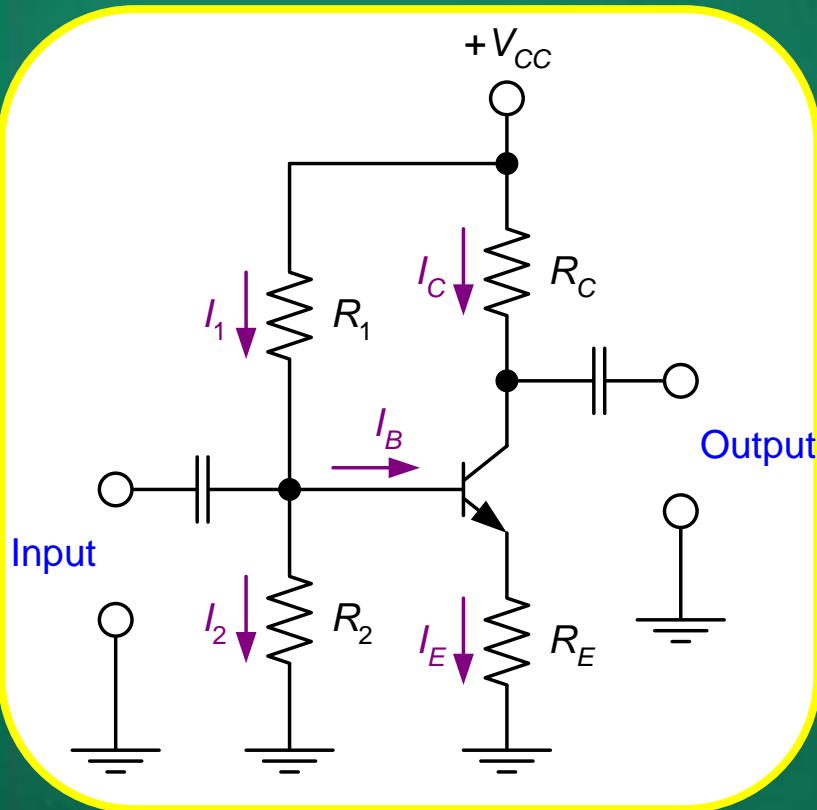

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$


$$V_E = V_B - 0.7V$$

$$I_E = \frac{V_E}{R_E}$$

Assume that $I_{CQ} \cong I_E$ (or $h_{FE} \gg 1$). Then

Voltage Divider Bias

Assume that $I_2 > 10I_B$.

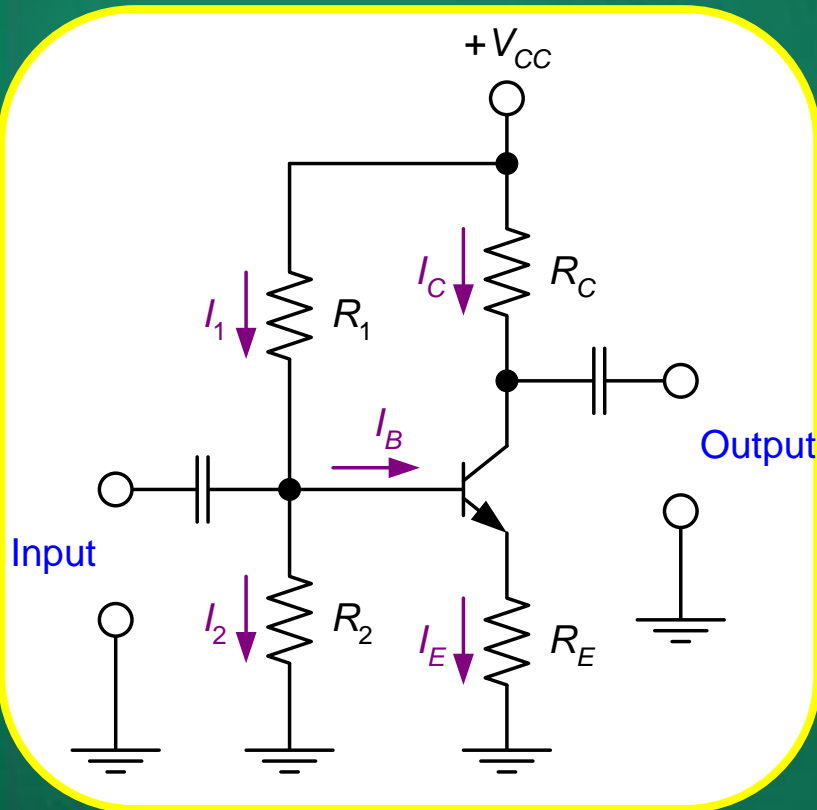

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_E = V_B - 0.7V$$


$$I_E = \frac{V_E}{R_E}$$

Assume that $I_{CQ} \cong I_E$ (or $h_{FE} \gg 1$). Then

$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E)$$

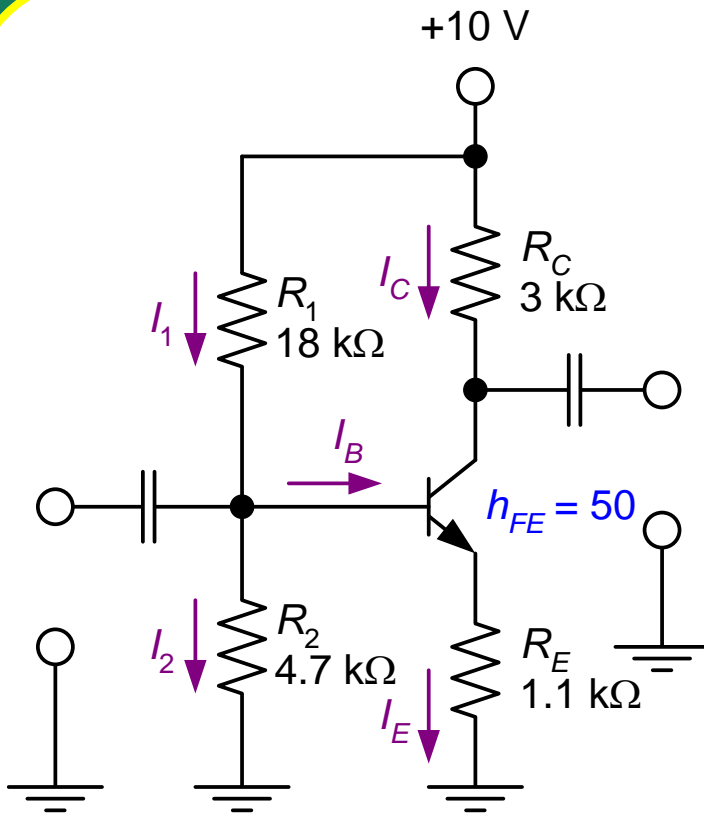
Example

Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.



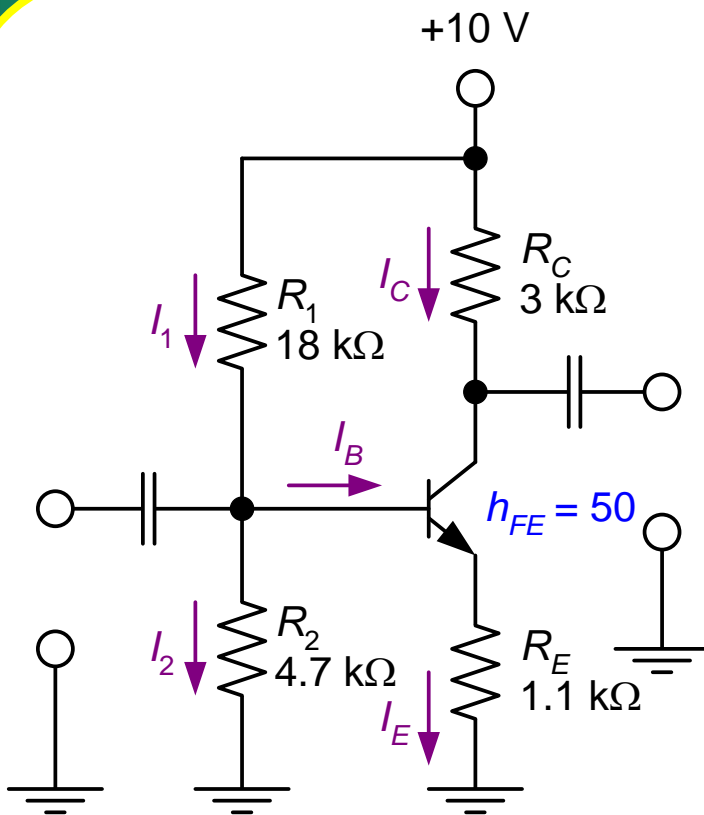Example


Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.



$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$
$$= (10\text{V}) \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} = 2.07\text{V}$$

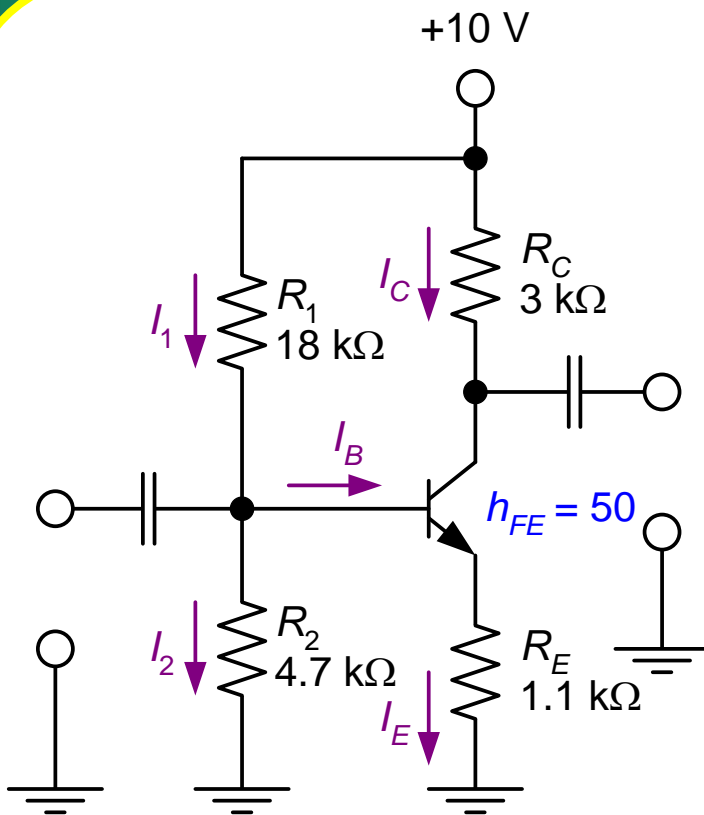Example

Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.




$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$
$$= (10\text{V}) \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} = 2.07\text{V}$$

$$V_E = V_B - 0.7\text{V}$$
$$= 2.07\text{V} - 0.7\text{V} = 1.37\text{V}$$

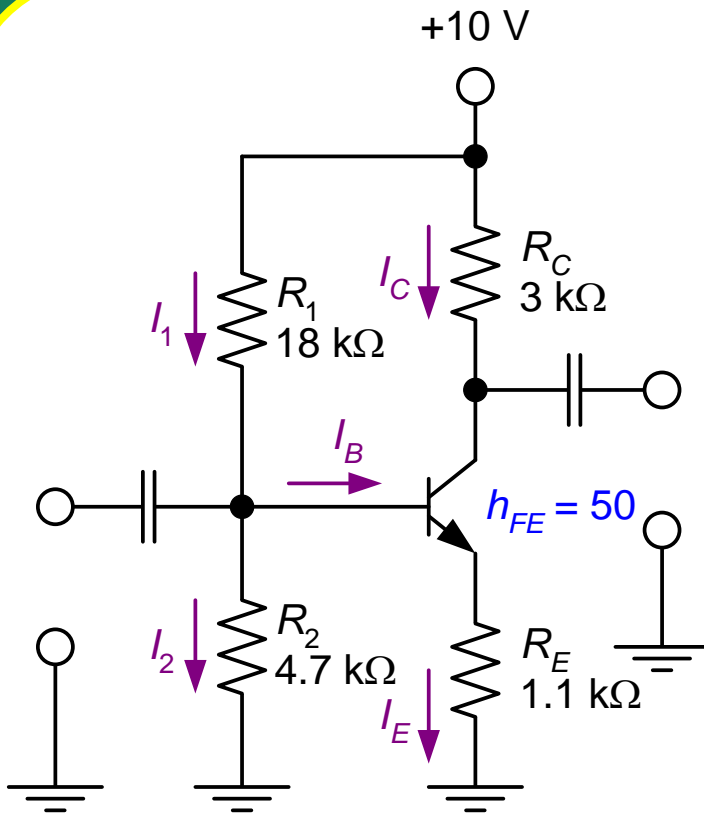Example

Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.




$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$
$$= (10\text{V}) \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} = 2.07\text{V}$$

$$V_E = V_B - 0.7\text{V}$$
$$= 2.07\text{V} - 0.7\text{V} = 1.37\text{V}$$

Because $I_{CQ} \approx I_E$ (or $h_{FE} \gg 1$),

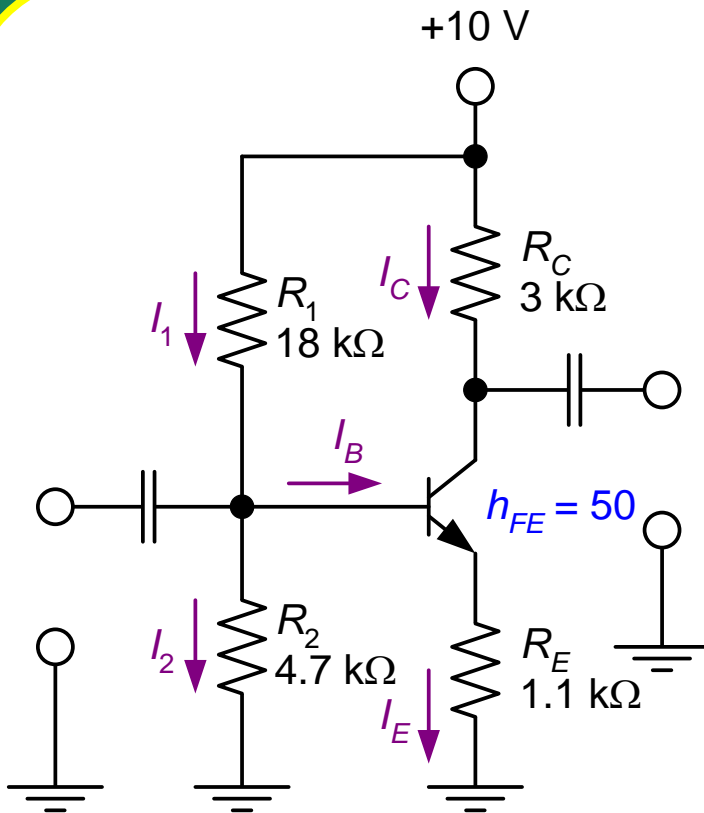Example

Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.



$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$
$$= (10\text{V}) \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} = 2.07\text{V}$$


$$V_E = V_B - 0.7\text{V}$$
$$= 2.07\text{V} - 0.7\text{V} = 1.37\text{V}$$

Because $I_{CQ} \cong I_E$ (or $h_{FE} \gg 1$),

$$I_{CQ} \cong \frac{V_E}{R_E} = \frac{1.37\text{V}}{1.1\text{k}\Omega} = 1.25\text{mA}$$

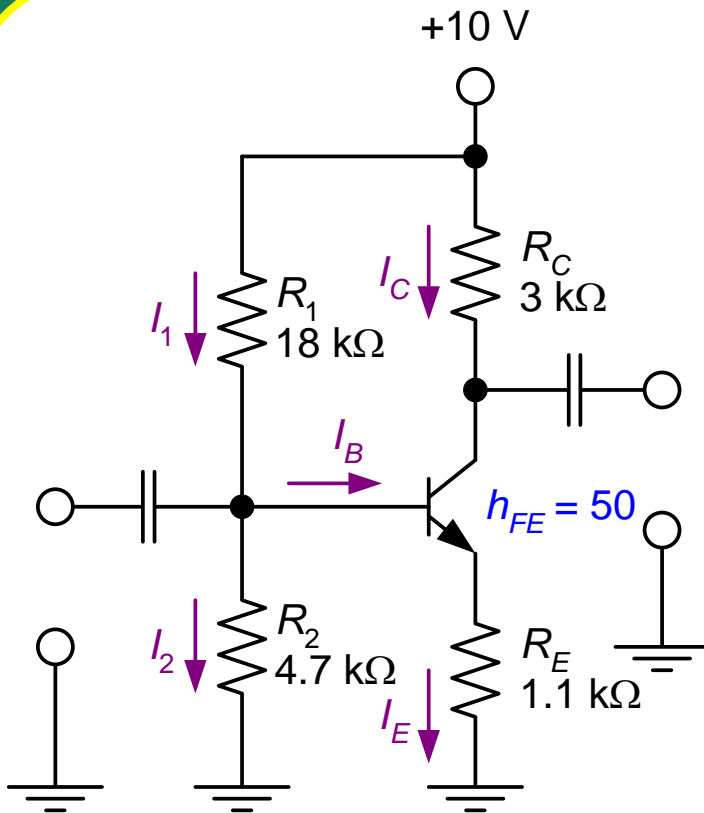Example

Determine the values of I_{CQ} and V_{CEQ} for the circuit shown below.



$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$
$$= (10\text{V}) \frac{4.7\text{k}\Omega}{22.7\text{k}\Omega} = 2.07\text{V}$$

$$V_E = V_B - 0.7\text{V}$$
$$= 2.07\text{V} - 0.7\text{V} = 1.37\text{V}$$


Because $I_{CQ} \cong I_E$ (or $h_{FE} \gg 1$),

$$I_{CQ} \cong \frac{V_E}{R_E} = \frac{1.37\text{V}}{1.1\text{k}\Omega} = 1.25\text{mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E)$$
$$= 10\text{V} - (1.25\text{mA})(4.1\text{k}\Omega) = 4.87\text{V}$$


Example

Verify that $I_2 > 10 I_B$.

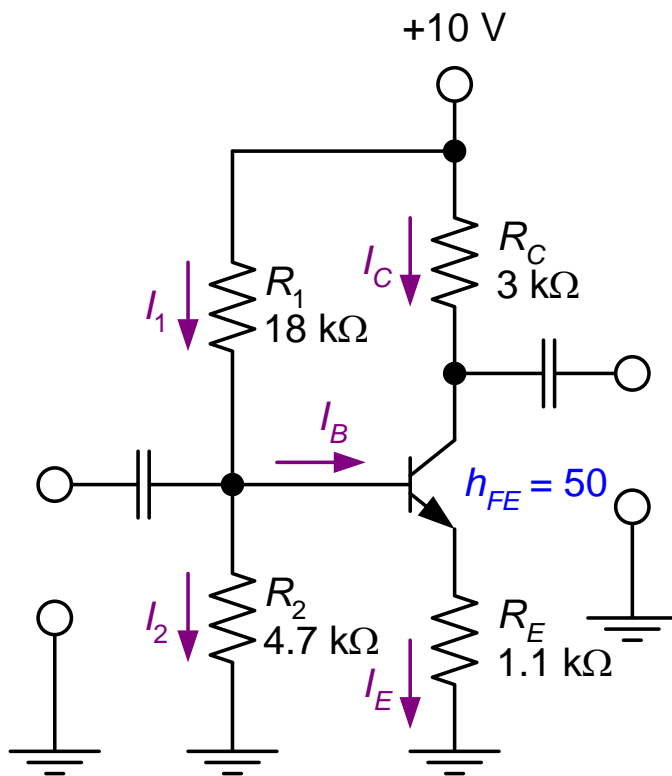

Example


Verify that $I_2 > 10 I_B$.

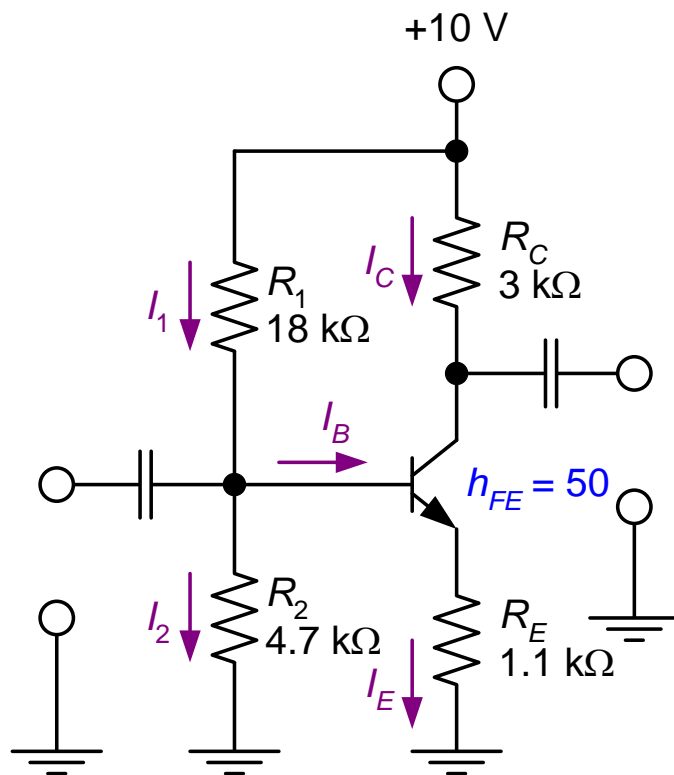

$$I_2 = \frac{V_B}{R_2} = \frac{2.07\text{V}}{4.7\text{k}\Omega} = 440.4\mu\text{A}$$

Example

Verify that $I_2 > 10 I_B$.

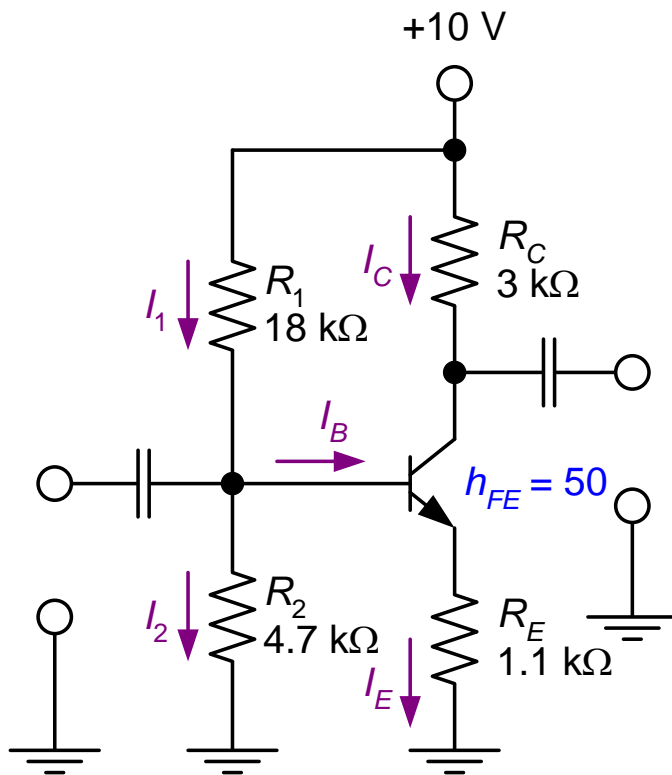


$$I_2 = \frac{V_B}{R_2} = \frac{2.07\text{V}}{4.7\text{k}\Omega} = 440.4\mu\text{A}$$

$$I_B = \frac{I_E}{h_{FE} + 1} = \frac{1.25\text{mA}}{50+1} = 24.51\mu\text{A}$$

Example

Verify that $I_2 > 10 I_B$.

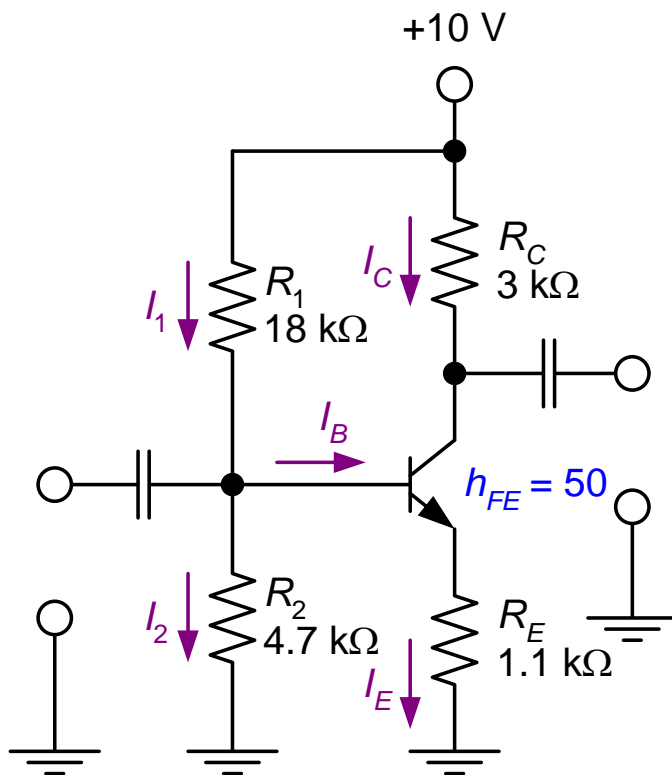

$$I_2 = \frac{V_B}{R_2} = \frac{2.07\text{V}}{4.7\text{k}\Omega} = 440.4\mu\text{A}$$

$$I_B = \frac{I_E}{h_{FE} + 1} = \frac{1.25\text{mA}}{50 + 1} = 24.51\mu\text{A}$$

$$\therefore I_2 > 10 I_B$$

Which value of h_{FE} to use?

Transistor specification sheet may list any combination of the following h_{FE} : max. h_{FE} , min. h_{FE} , or typ. h_{FE} . Use typical value if there is one. Otherwise, use

Which value of h_{FE} to use?

Transistor specification sheet may list any combination of the following h_{FE} : max. h_{FE} , min. h_{FE} , or typ. h_{FE} . Use typical value if there is one. Otherwise, use

$$h_{FE(\text{ave})} = \sqrt{h_{FE(\text{min})} \times h_{FE(\text{max})}}$$

Example

A voltage-divider bias circuit has the following values:

$R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.

Assuming the transistor has $h_{FE}(\text{max})=300$ and $h_{FE}(\text{min})=100$, determine the value of I_B for the circuit.

Example

A voltage-divider bias circuit has the following values:

$R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.

Assuming the transistor has $h_{FE}(\text{max})=300$ and $h_{FE}(\text{min})=100$, determine the value of I_B for the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = (10\text{V}) \frac{680\Omega}{2180\Omega} = 3.12\text{V}$$

Example

A voltage-divider bias circuit has the following values:
 $R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.
Assuming the transistor has $h_{FE}(\text{max})=300$ and $h_{FE}(\text{min})=100$,
determine the value of I_B for the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = (10\text{V}) \frac{680\Omega}{2180\Omega} = 3.12\text{V}$$

$$V_E = V_B - 0.7\text{V} = 3.12\text{V} - 0.7\text{V} = 2.42\text{V}$$

Example

A voltage-divider bias circuit has the following values:
 $R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.
Assuming the transistor has $h_{FE}(\text{max})=300$ and $h_{FE}(\text{min})=100$,
determine the value of I_B for the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = (10\text{V}) \frac{680\Omega}{2180\Omega} = 3.12\text{V}$$

$$V_E = V_B - 0.7\text{V} = 3.12\text{V} - 0.7\text{V} = 2.42\text{V}$$

$$I_{CQ} \cong I_E = \frac{V_E}{R_E} = \frac{2.42\text{V}}{240\Omega} = 10\text{mA}$$

Example

A voltage-divider bias circuit has the following values:
 $R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.
Assuming the transistor has $h_{FE(\text{max})}=300$ and $h_{FE(\text{min})}=100$,
determine the value of I_B for the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = (10\text{V}) \frac{680\Omega}{2180\Omega} = 3.12\text{V}$$

$$V_E = V_B - 0.7\text{V} = 3.12\text{V} - 0.7\text{V} = 2.42\text{V}$$

$$I_{CQ} \cong I_E = \frac{V_E}{R_E} = \frac{2.42\text{V}}{240\Omega} = 10\text{mA}$$

$$h_{FE(\text{ave})} = \sqrt{h_{FE(\text{min})} \times h_{FE(\text{max})}} = \sqrt{100 \times 300} = 173$$

Example

A voltage-divider bias circuit has the following values:
 $R_1=1.5\text{ k}\Omega$, $R_2=680\text{ }\Omega$, $R_C=260\text{ }\Omega$, $R_E=240\text{ }\Omega$ and $V_{CC}=10\text{ V}$.
Assuming the transistor has $h_{FE}(\text{max})=300$ and $h_{FE}(\text{min})=100$,
determine the value of I_B for the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = (10\text{V}) \frac{680\Omega}{2180\Omega} = 3.12\text{V}$$

$$V_E = V_B - 0.7\text{V} = 3.12\text{V} - 0.7\text{V} = 2.42\text{V}$$

$$I_{CQ} \cong I_E = \frac{V_E}{R_E} = \frac{2.42\text{V}}{240\Omega} = 10\text{mA}$$

$$h_{FE(\text{ave})} = \sqrt{h_{FE(\text{min})} \times h_{FE(\text{max})}} = \sqrt{100 \times 300} = 173$$

$$I_B = \frac{I_E}{h_{FE(\text{ave})} + 1} = \frac{10\text{mA}}{174} = 57.5\mu\text{A}$$

Stability of Voltage Divider Bias Circuit

The Q-point of voltage divider bias circuit is less dependent on h_{FE} than that of the base bias (fixed bias).

Stability of Voltage Divider Bias Circuit

The Q-point of voltage divider bias circuit is less dependent on h_{FE} than that of the base bias (fixed bias).

For example, if I_E is exactly 10 mA, the range of h_{FE} is 100 to 300. Then

Stability of Voltage Divider Bias Circuit

The Q-point of voltage divider bias circuit is less dependent on h_{FE} than that of the base bias (fixed bias).

For example, if I_E is exactly 10 mA, the range of h_{FE} is 100 to 300. Then

$$\text{At } h_{FE} = 100, I_B = \frac{I_E}{h_{FE} + 1} = \frac{10\text{mA}}{101} \cong 100\mu\text{A} \text{ and } I_{CQ} = I_E - I_B \cong 9.90\text{mA}$$

Stability of Voltage Divider Bias Circuit

The Q-point of voltage divider bias circuit is less dependent on h_{FE} than that of the base bias (fixed bias).


For example, if I_E is exactly 10 mA, the range of h_{FE} is 100 to 300. Then

$$\text{At } h_{FE} = 100, I_B = \frac{I_E}{h_{FE} + 1} = \frac{10\text{mA}}{101} \cong 100\mu\text{A} \text{ and } I_{CQ} = I_E - I_B \cong 9.90\text{mA}$$


$$\text{At } h_{FE} = 300, I_B = \frac{I_E}{h_{FE} + 1} = \frac{10\text{mA}}{301} \cong 33\mu\text{A} \text{ and } I_{CQ} = I_E - I_B \cong 9.97\text{mA}$$

Load Line for Voltage Divider Bias


Circuit values are from previous example

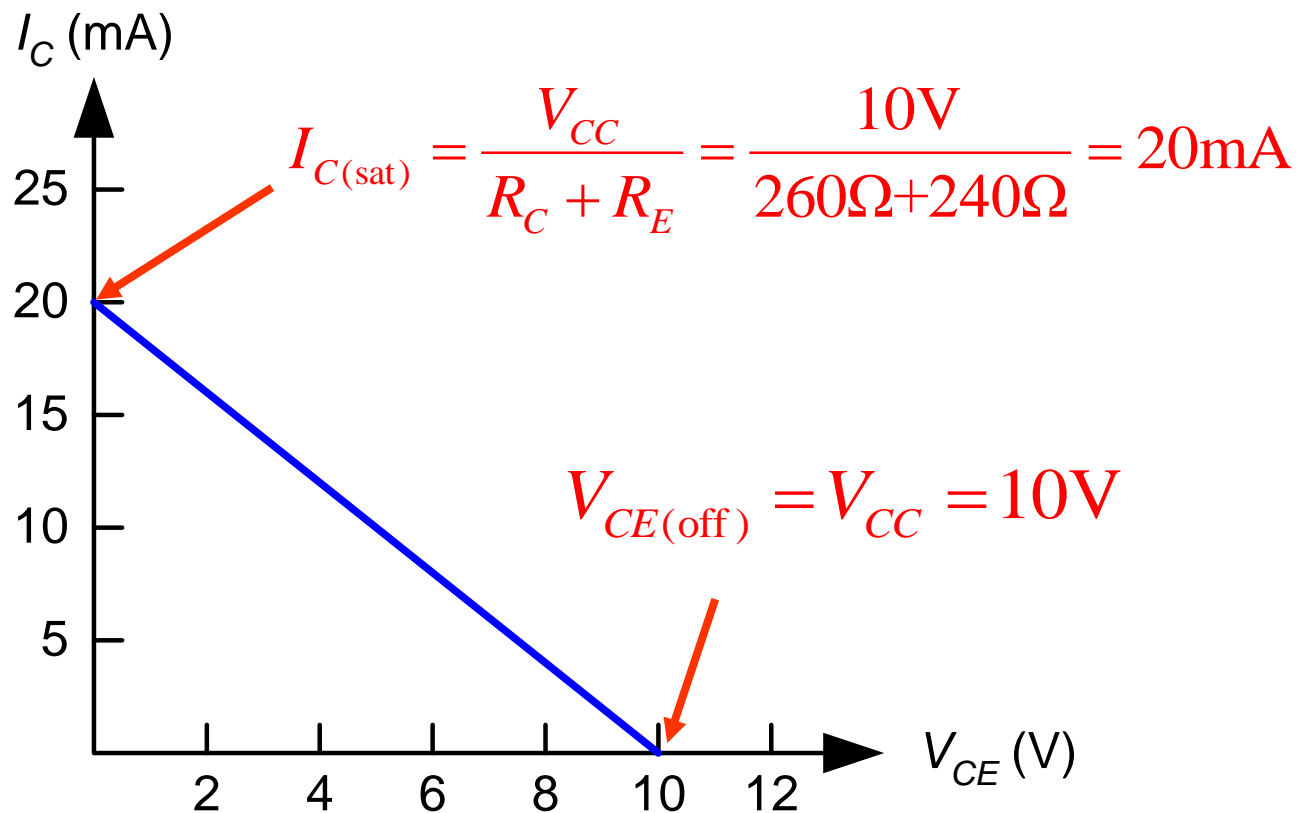

Base Input Resistance

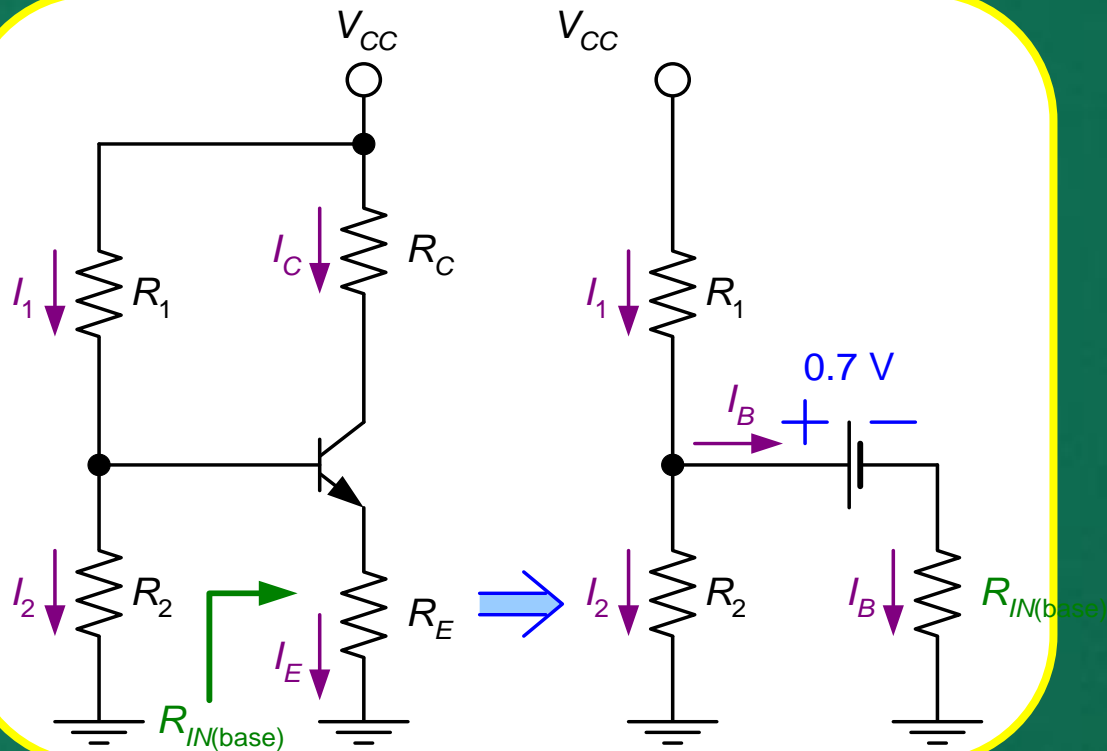


Base Input Resistance

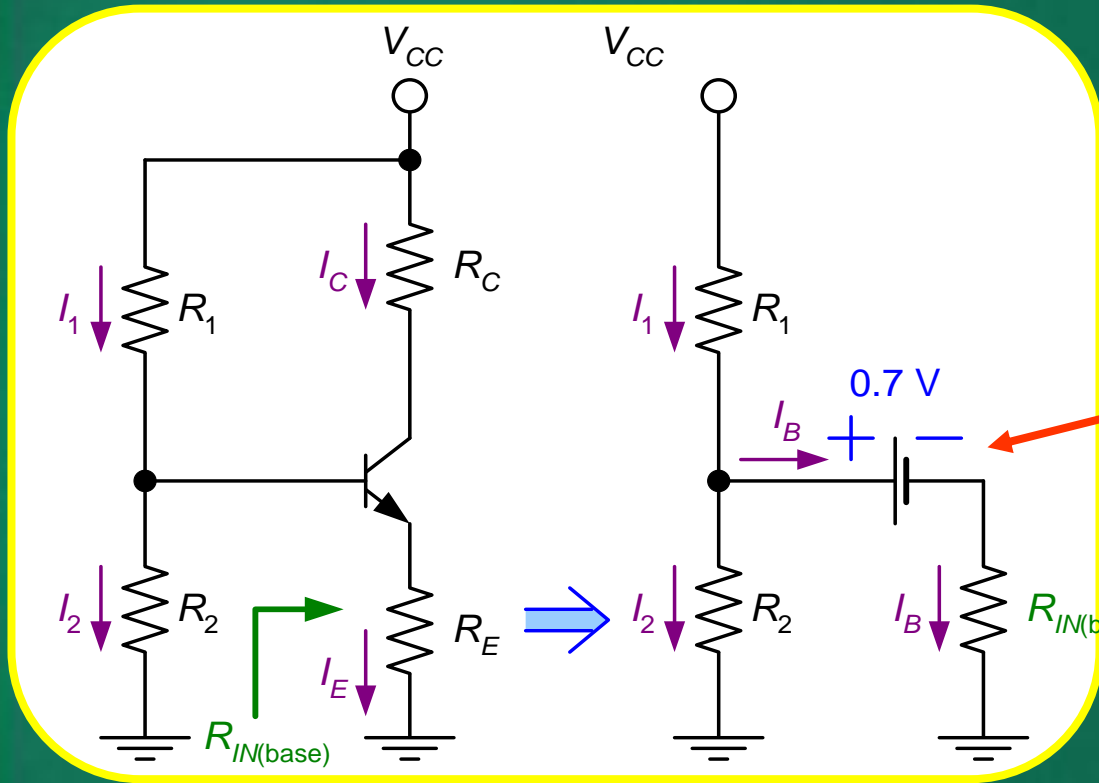

May be ignored.


Base Input Resistance

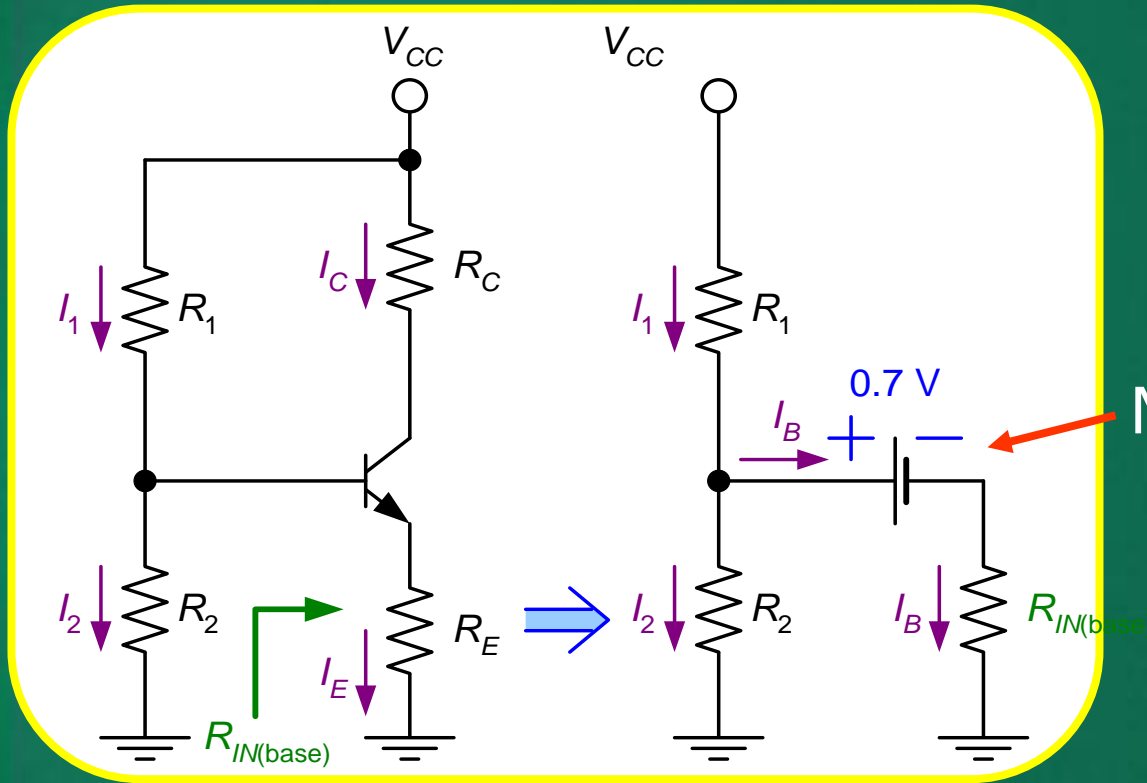

May be ignored.

$$V_E = I_E R_E = I_B (h_{FE} + 1) R_E$$

Base Input Resistance

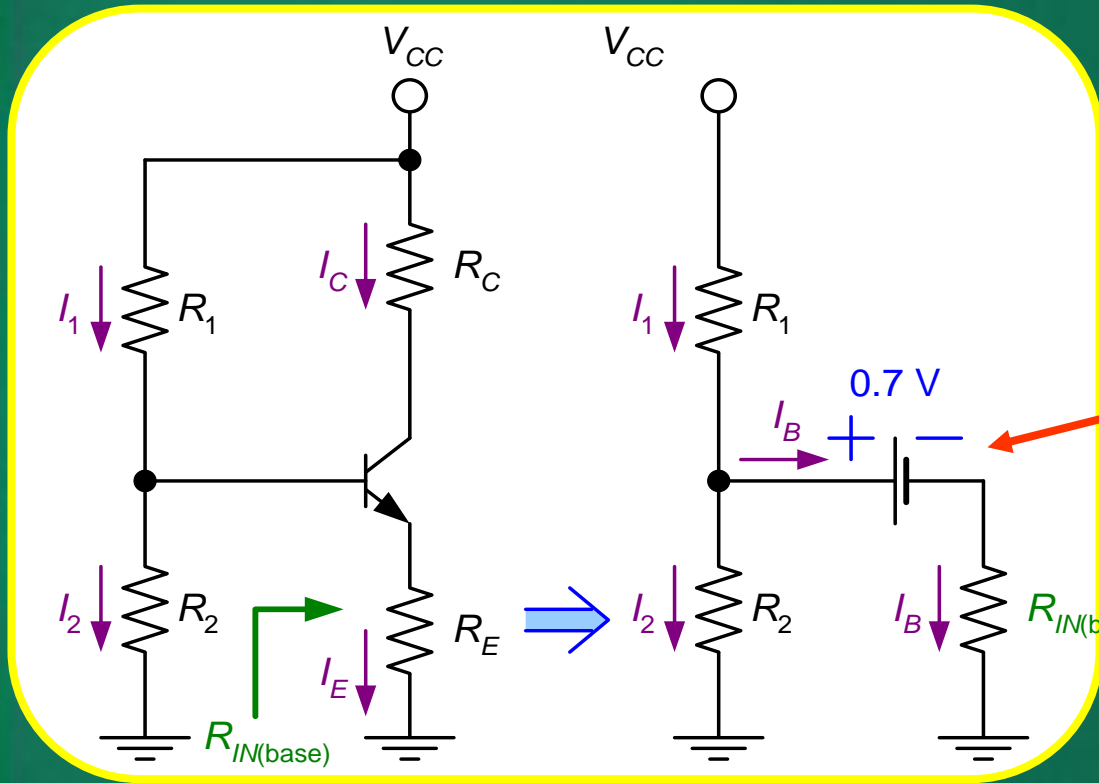


May be ignored.

$$V_E = I_E R_E = I_B (h_{FE} + 1) R_E$$


$$R_{IN(base)} = \frac{V_E}{I_B} = (h_{FE} + 1) R_E$$

$$\cong h_{FE} R_E$$

Base Input Resistance

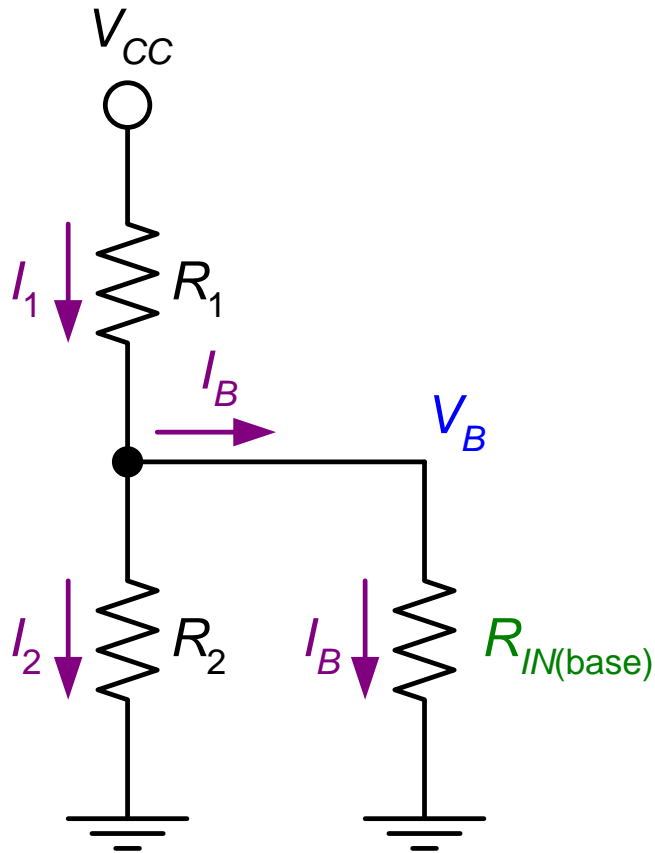


Base Input Resistance

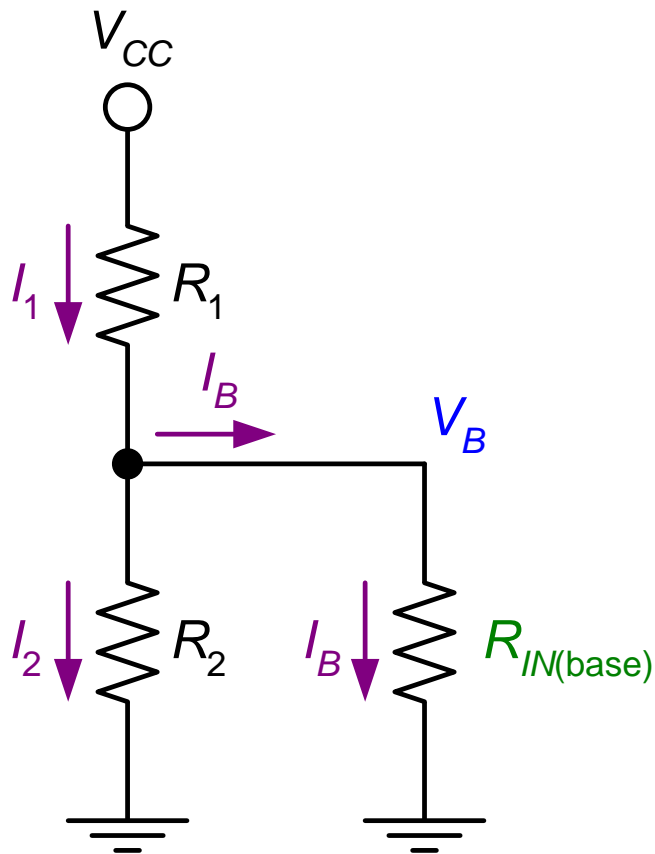

$$\begin{aligned} V_B &= \frac{R_2 // R_{IN(base)}}{R_1 + R_2 // R_{IN(base)}} V_{CC} \\ &= \frac{R_2 // (h_{FE} R_E)}{R_1 + R_2 // (h_{FE} R_E)} V_{CC} \\ &= \frac{R_{EQ}}{R_1 + R_{EQ}} V_{CC} \quad \left| \quad R_{EQ} = R_2 // (h_{FE} R_E) \right. \end{aligned}$$

Base Input Resistance

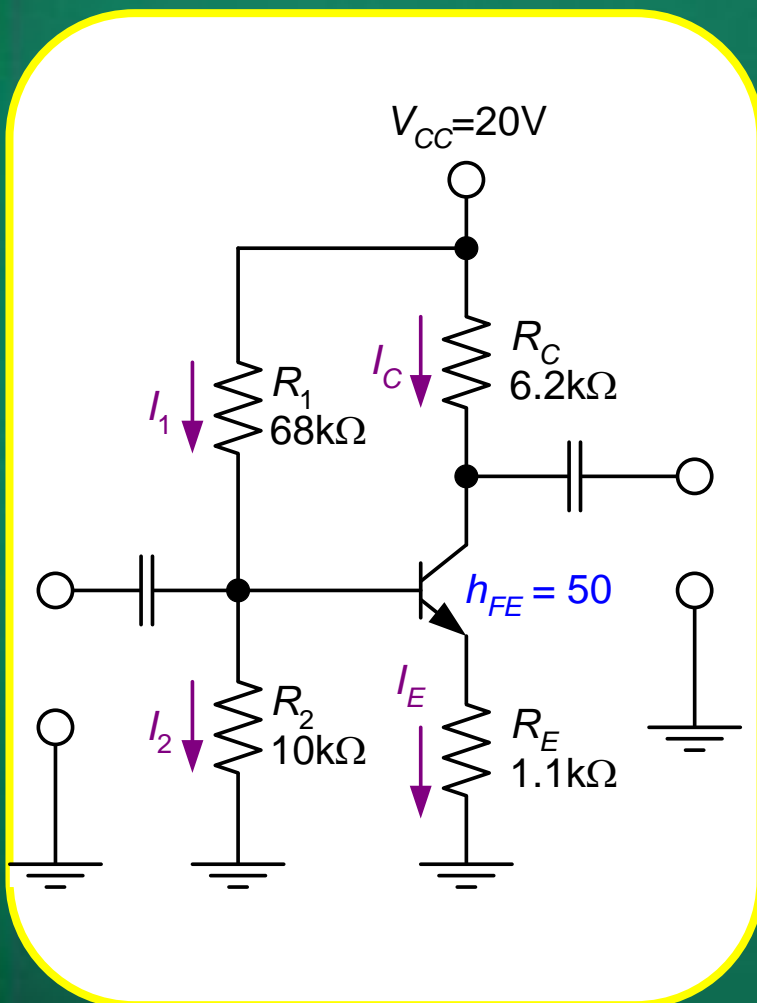

$$R_{EQ} = R_2 \parallel (h_{FE} R_E)$$

$$= 10\text{k}\Omega \parallel (50 \times 1.1\text{k}\Omega) = 8.46\text{k}\Omega$$

$$V_B \cong V_{CC} \frac{R_{EQ}}{R_1 + R_{EQ}}$$

$$= (20\text{V}) \frac{8.46\text{k}\Omega}{68\text{k}\Omega + 8.46\text{k}\Omega} = 2.21\text{V}$$


$$I_{CQ} \cong I_E = \frac{V_E}{R_E} = \frac{V_B - 0.7\text{V}}{R_E}$$

$$= \frac{2.21\text{V} - 0.7\text{V}}{1.1\text{k}\Omega} = 1.37\text{mA}$$


$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E)$$

$$= 20\text{V} - (1.37\text{mA})(7.3\text{k}\Omega) = 9.99\text{V}$$

Voltage Divider Bias Characteristics

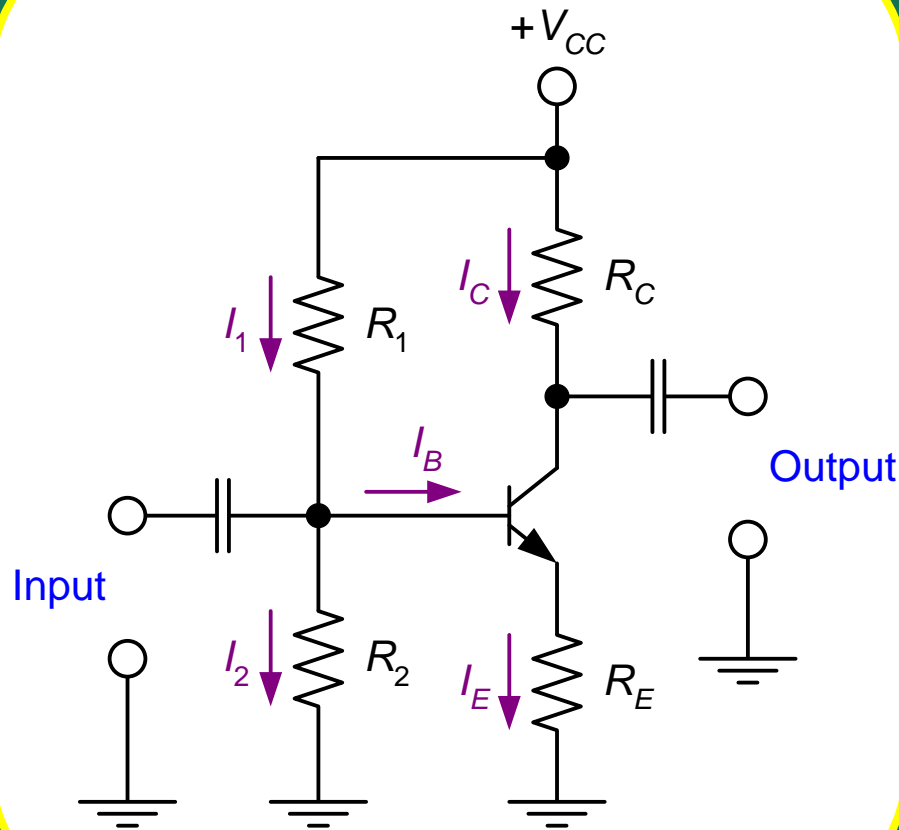


Voltage Divider Bias Characteristics

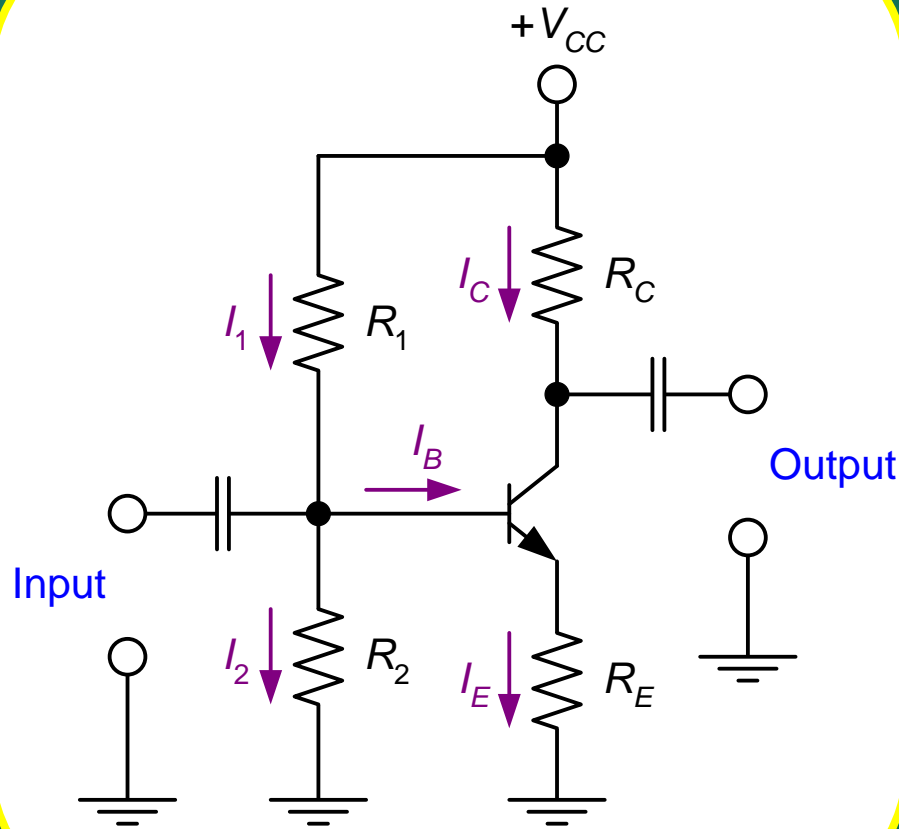

Circuit recognition: The voltage divider in the base circuit.

Voltage Divider Bias Characteristics

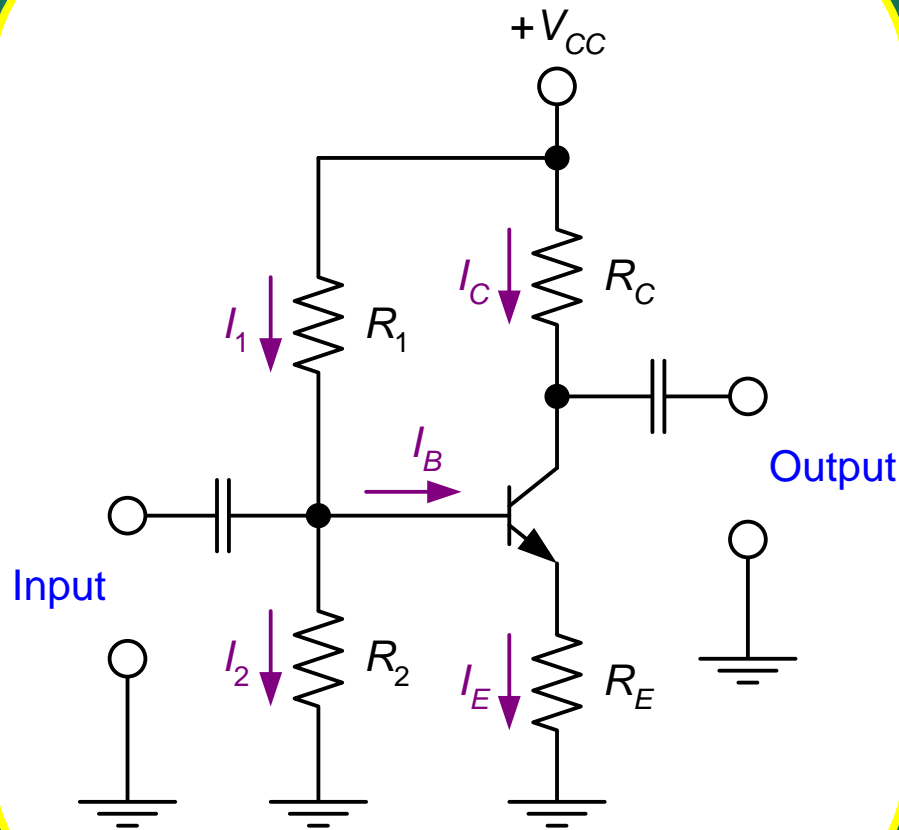

Circuit recognition: The voltage divider in the base circuit.


Advantages: The circuit Q-point values are stable against changes in h_{FE} .

Disadvantages: Requires more components than most other biasing circuits.


Applications: Used primarily to bias linear amplifier.

Voltage Divider Bias Characteristics

Load line equations:

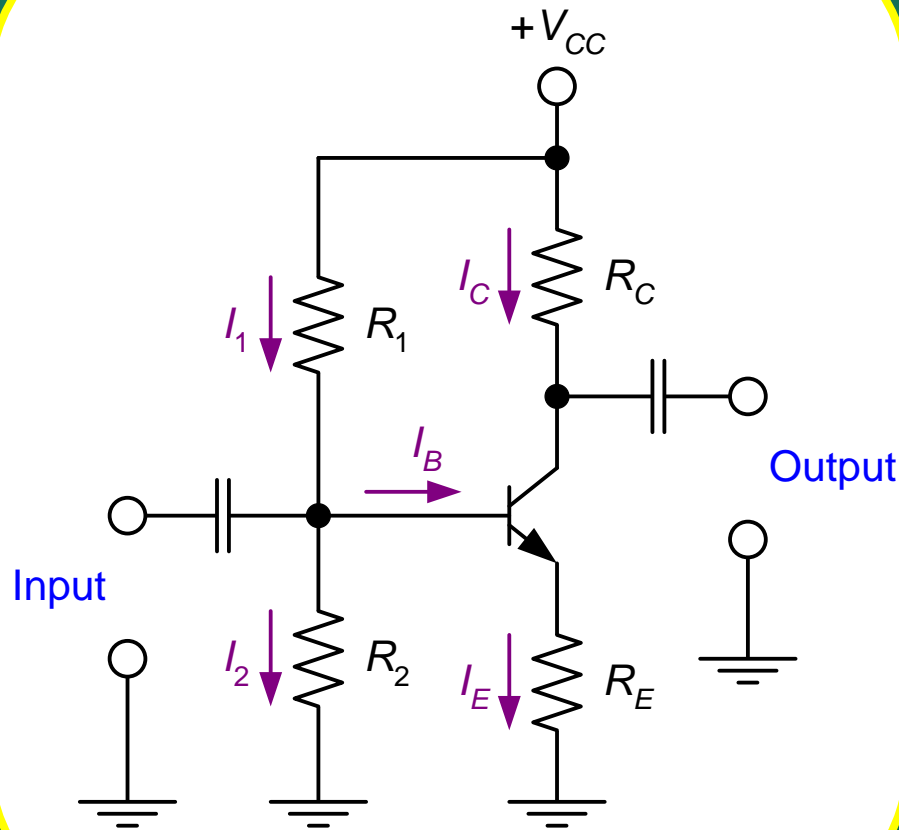

Voltage Divider Bias Characteristics

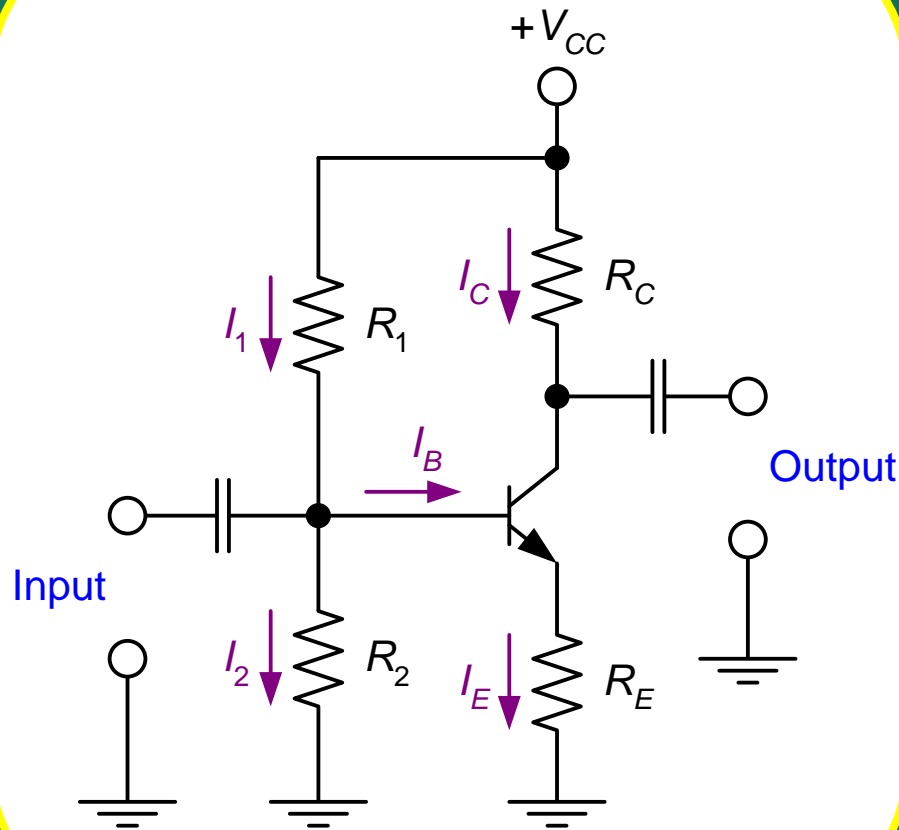


Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE(\text{off})} = V_{CC}$$

Voltage Divider Bias Characteristics

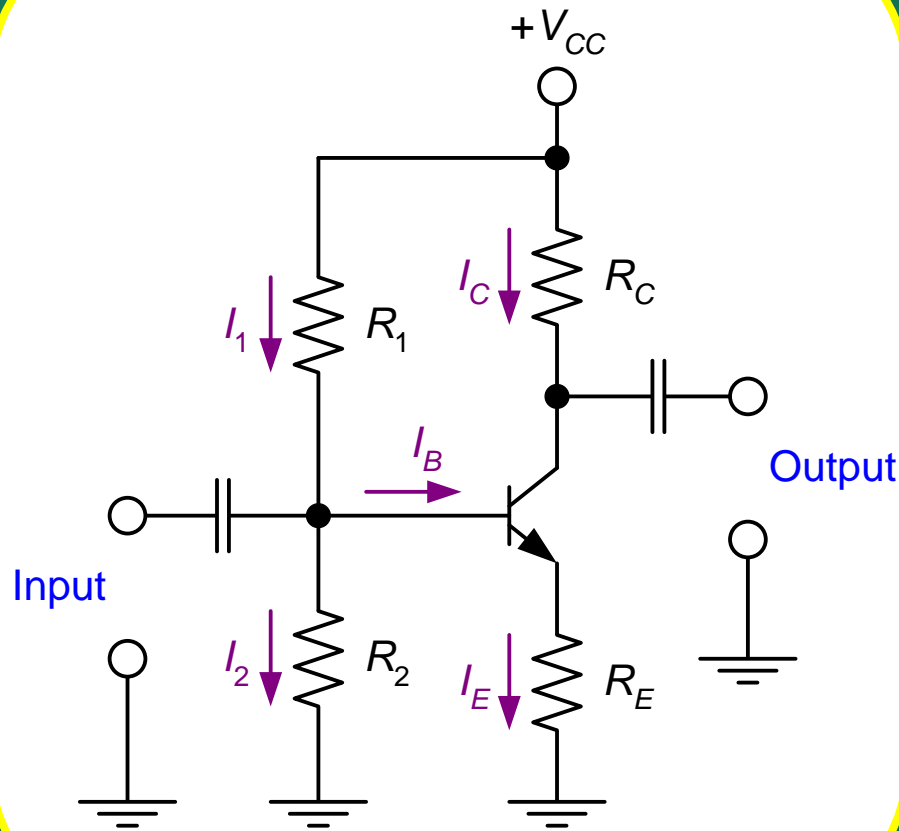


Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE(\text{off})} = V_{CC}$$

Q-point equations (assume that $h_{FE}R_E > 10R_2$):

Voltage Divider Bias Characteristics

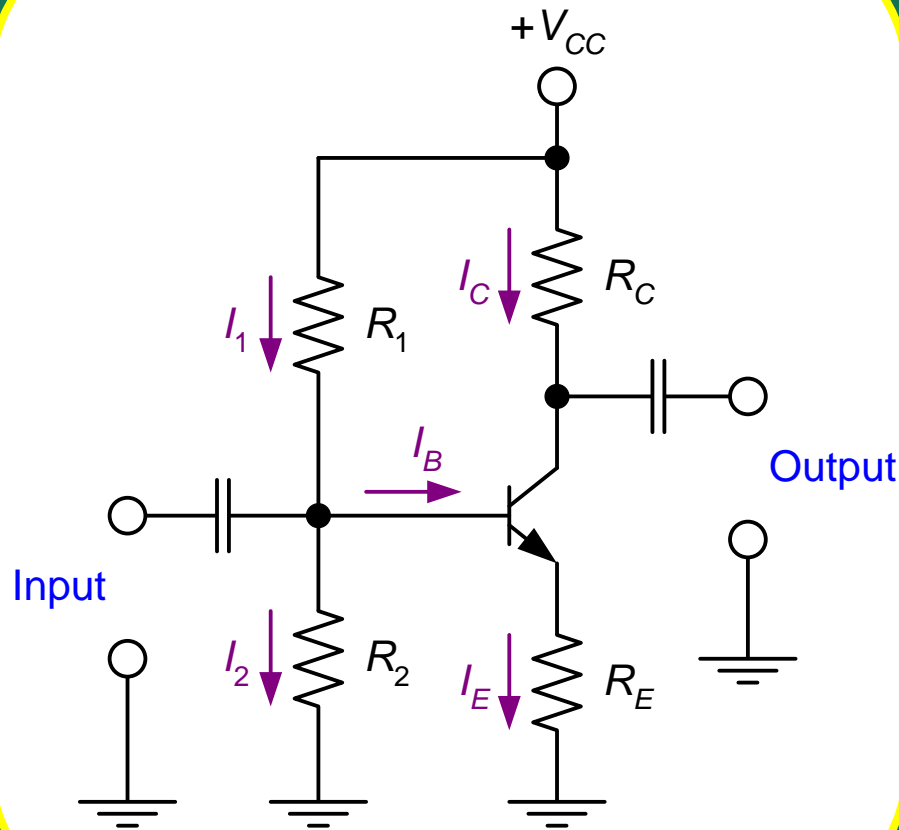

Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C + R_E}$$

$$V_{CE(\text{off})} = V_{CC}$$

Q-point equations (assume that $h_{FE}R_E > 10R_2$):

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_E = V_B - 0.7V$$

$$I_{CQ} \cong I_E = \frac{V_E}{R_E}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E)$$


Other Transistor Biasing Circuits

□ Emitter Bias Circuits


□ Feedback Bias Circuits

- Collector Feedback Bias**
- Emitter Feedback Bias**

Emitter Bias

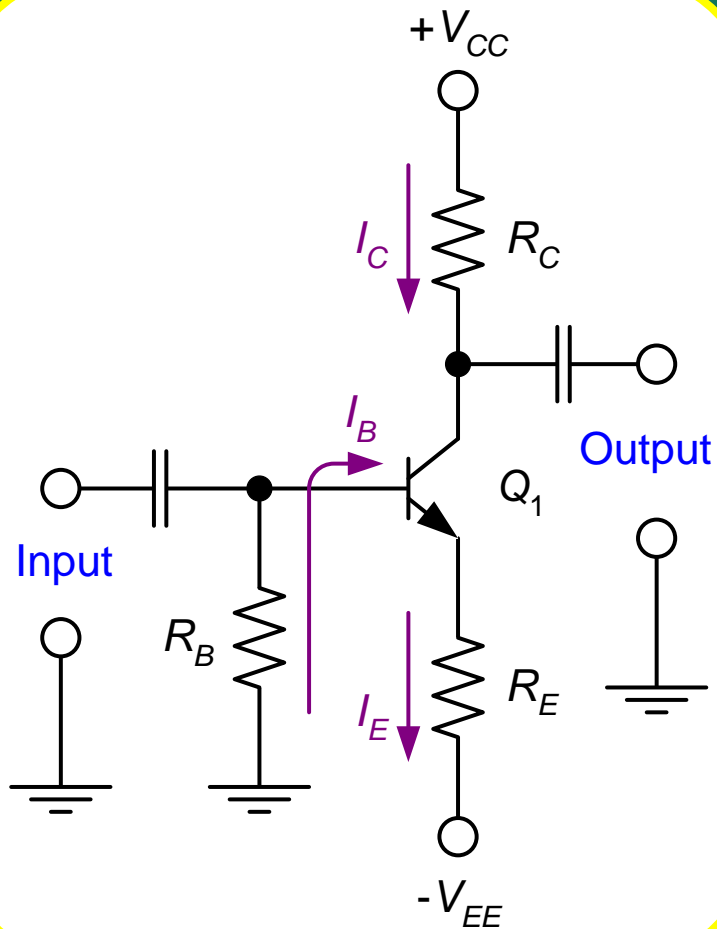


Emitter Bias

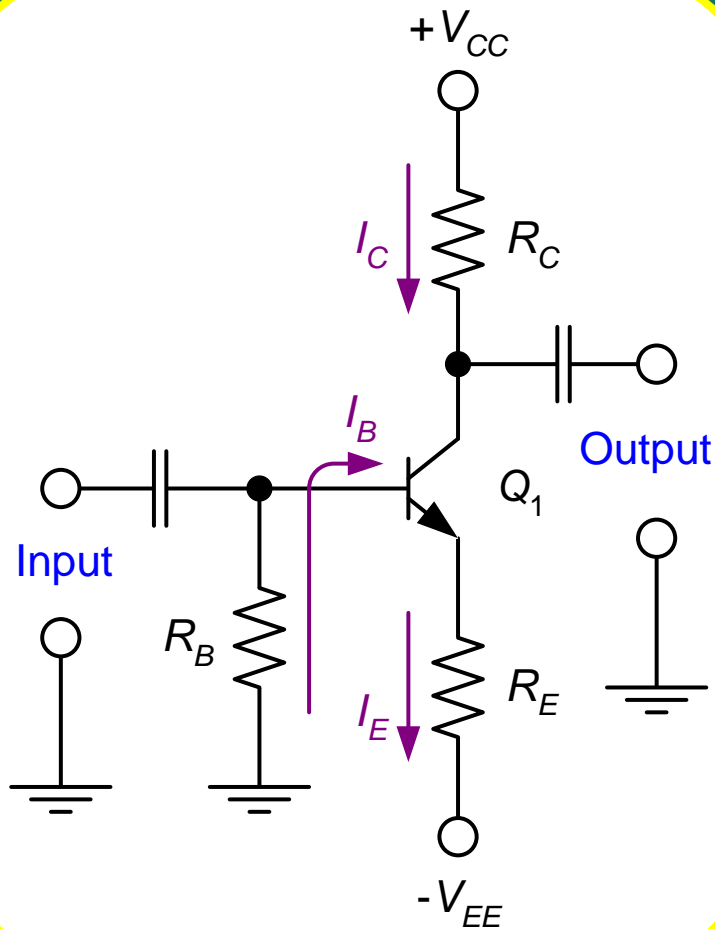

Assume that the transistor operation is in active region.


Emitter Bias

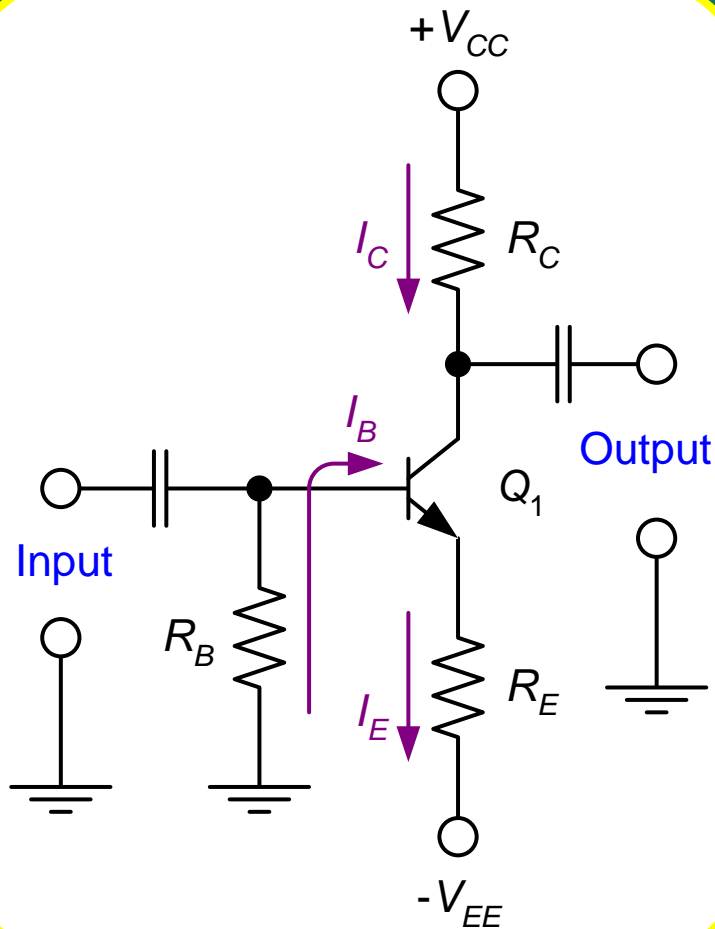

Assume that the transistor operation is in active region.

$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$

Emitter Bias

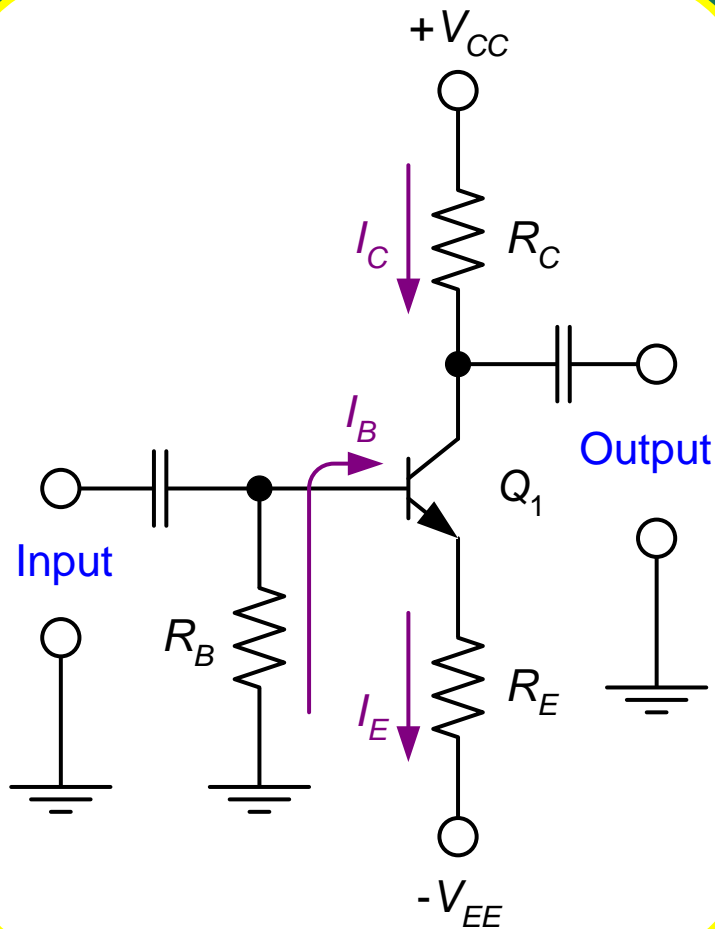


Assume that the transistor operation is in active region.

$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$

$$I_C = h_{FE} I_B$$

Emitter Bias

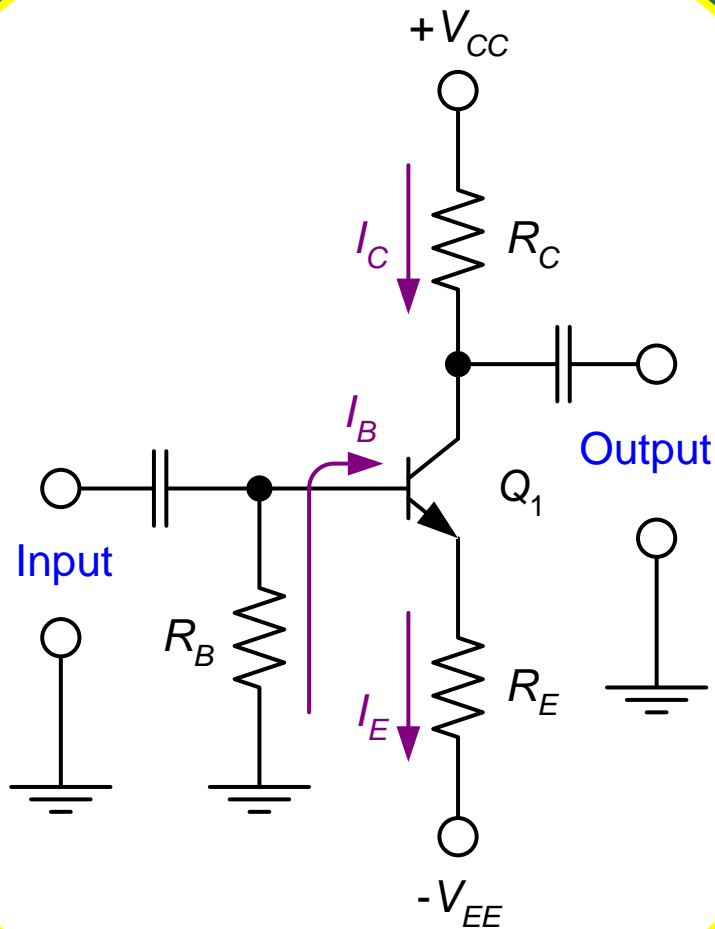


Assume that the transistor operation is in active region.

$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$

$$I_C = h_{FE} I_B$$

$$I_E = (h_{FE} + 1) I_B$$

Emitter Bias

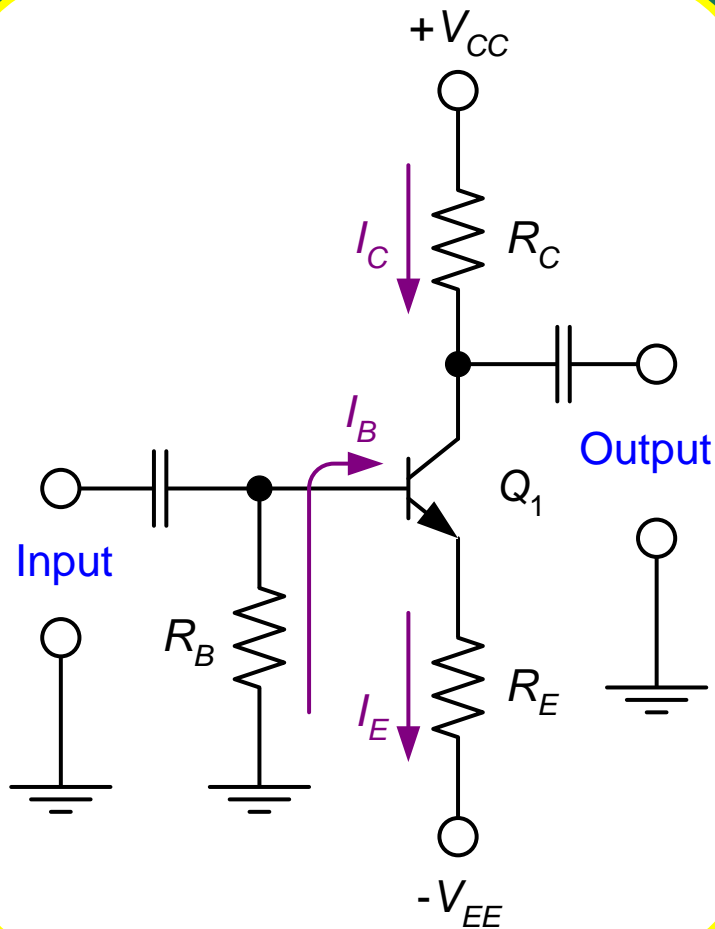

Assume that the transistor operation is in active region.


$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$

$$I_C = h_{FE} I_B$$

$$I_E = (h_{FE} + 1) I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE}$$

Emitter Bias

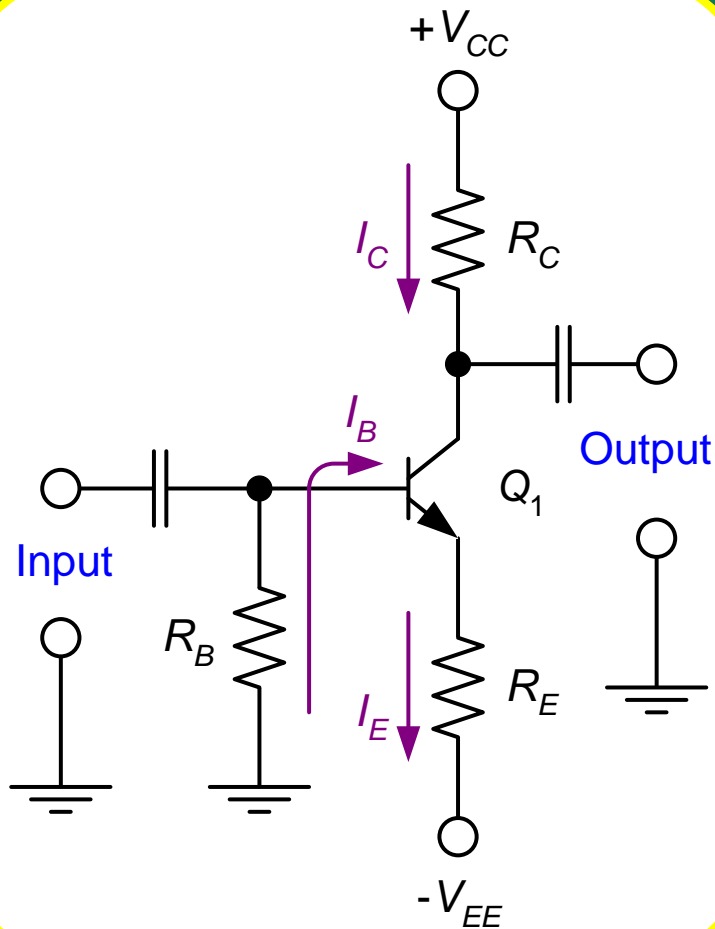

Assume that the transistor operation is in active region.

$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$


$$I_C = h_{FE} I_B$$

$$I_E = (h_{FE} + 1) I_B$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE}$$

Assume that $h_{FE} \gg 1$.

Emitter Bias

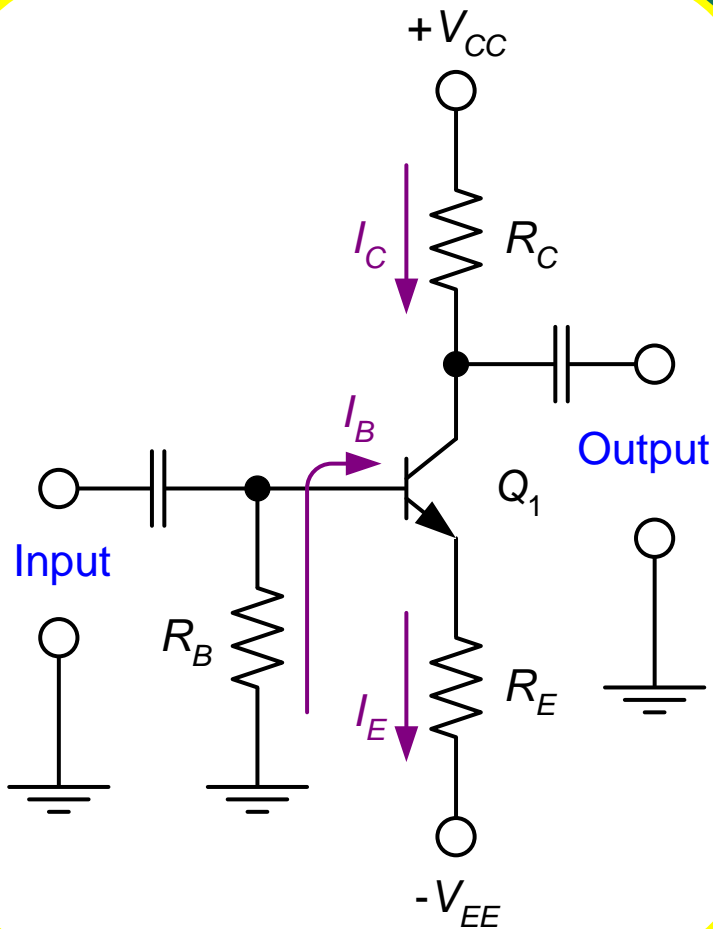

Assume that the transistor operation is in active region.

$$I_B = \frac{V_{EE} - 0.7V}{R_B + (h_{FE} + 1)R_E}$$

$$I_C = h_{FE} I_B$$

$$I_E = (h_{FE} + 1) I_B$$


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE}$$

Assume that $h_{FE} \gg 1$.

$$V_{CE} \cong V_{CC} - I_C (R_C + R_E) + V_{EE}$$


Emitter Bias

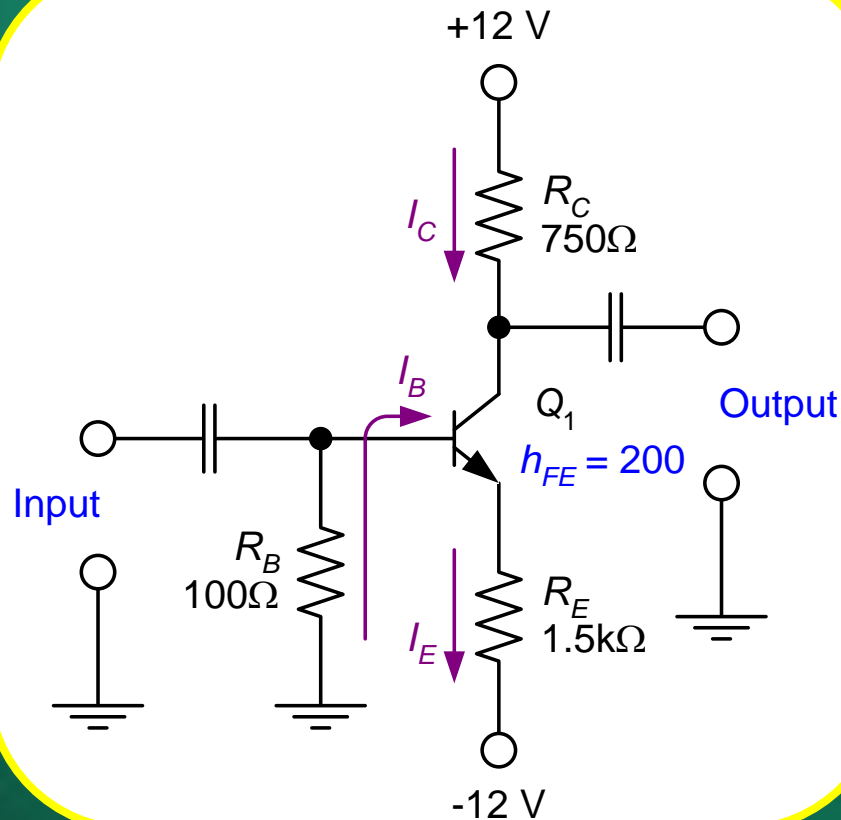Determine the values of I_{CQ} and V_{CEQ} for the amplifier circuit.



Emitter Bias

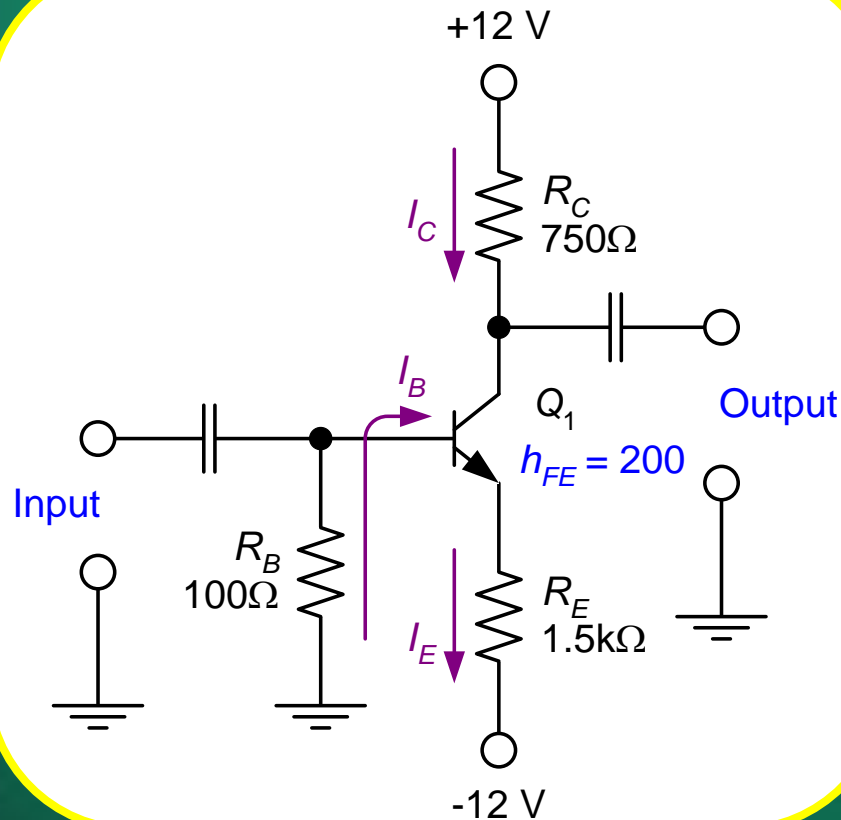
Determine the values of I_{CQ} and V_{CEQ} for the amplifier circuit.



$$I_B = \frac{12V - 0.7V}{R_B + (h_{FE} + 1)R_E}$$
$$= \frac{11.3V}{100\Omega + 201 \times 1.5k\Omega} = 37.47\mu A$$

Emitter Bias

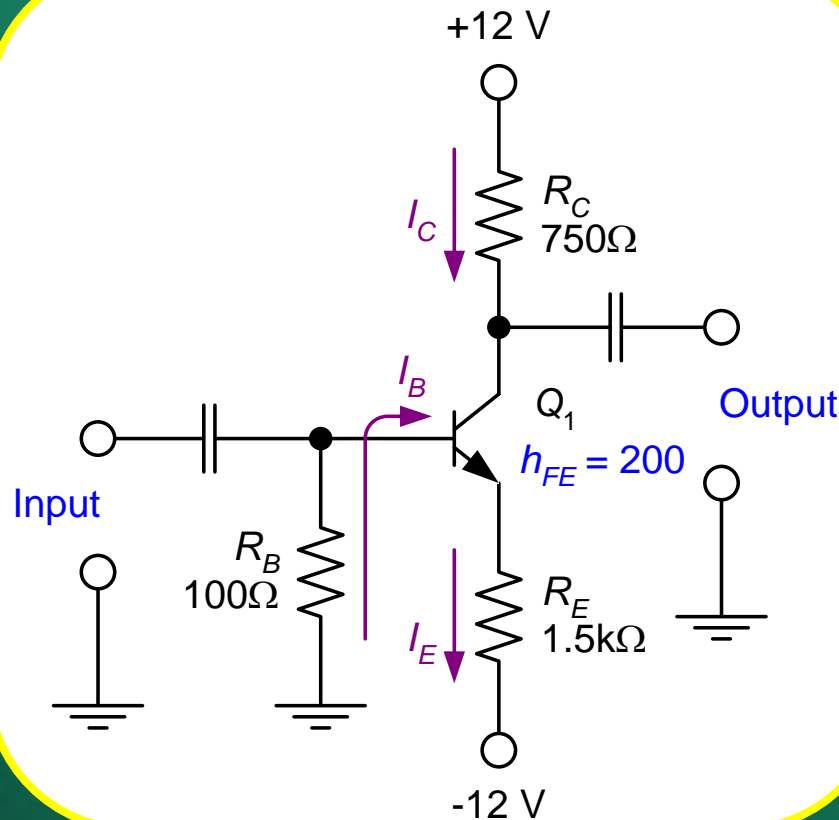Determine the values of I_{CQ} and V_{CEQ} for the amplifier circuit.




$$I_B = \frac{12V - 0.7V}{R_B + (h_{FE} + 1)R_E}$$
$$= \frac{11.3V}{100\Omega + 201 \times 1.5k\Omega} = 37.47\mu A$$

$$I_{CQ} = h_{FE} I_B = 200 \times 37.47\mu A$$
$$= 7.49mA$$

Emitter Bias

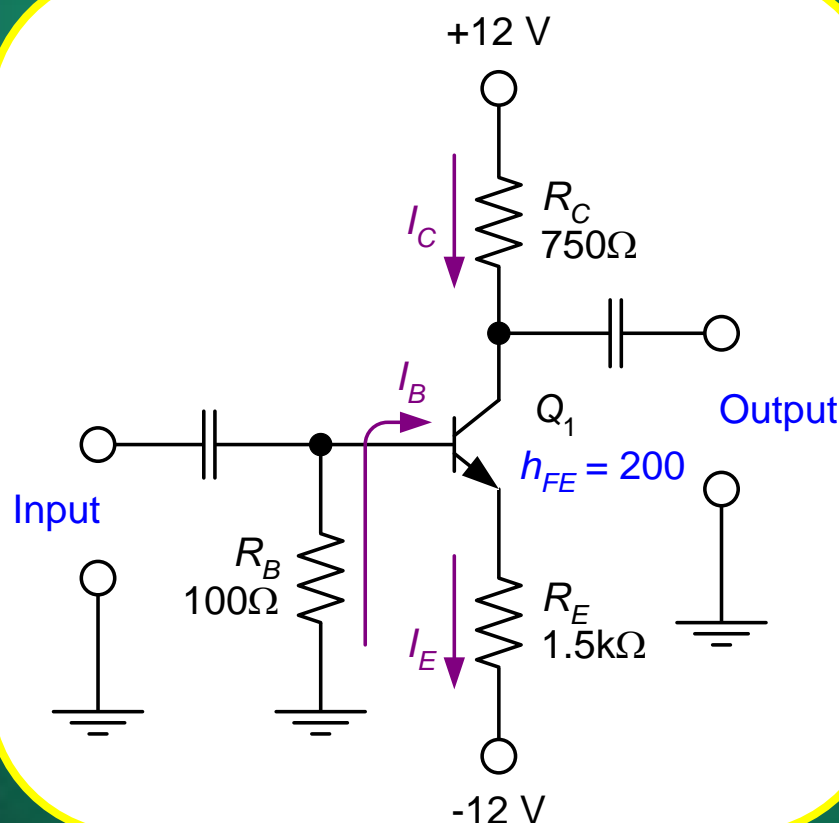Determine the values of I_{CQ} and V_{CEQ} for the amplifier circuit.




$$I_B = \frac{12V - 0.7V}{R_B + (h_{FE} + 1)R_E}$$
$$= \frac{11.3V}{100\Omega + 201 \times 1.5k\Omega} = 37.47\mu A$$


$$I_{CQ} = h_{FE} I_B = 200 \times 37.47\mu A$$
$$= 7.49mA$$

$$V_{CEQ} \cong V_{CC} - I_C (R_C + R_E) - (-V_{EE})$$
$$= 24V - 7.49mA (750\Omega + 1.5k\Omega)$$
$$= 7.14V$$

Load Line for Emitter Bias Circuit

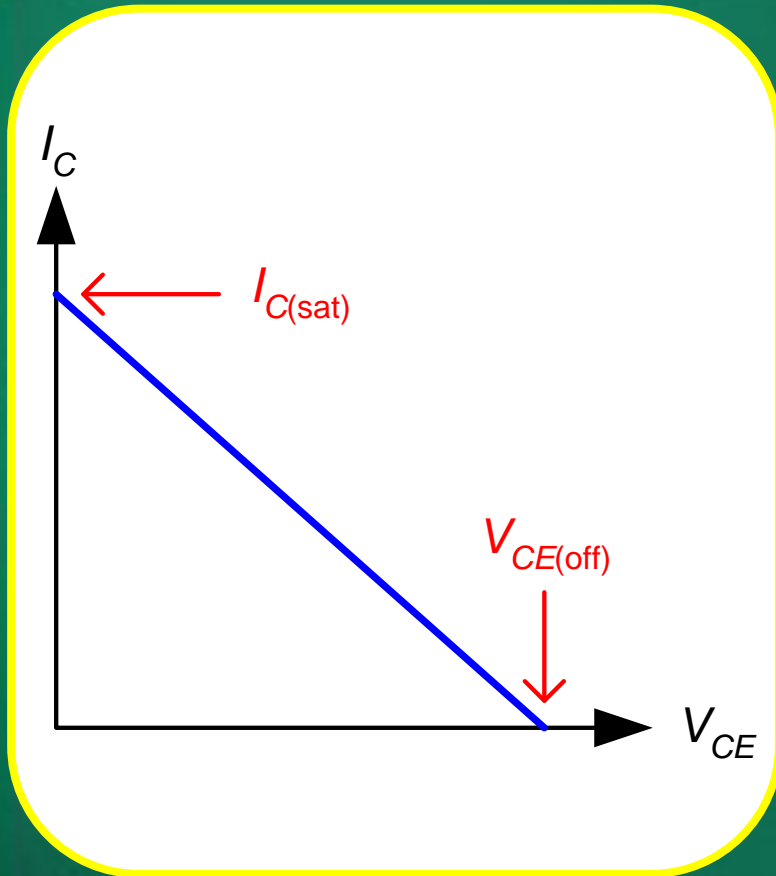


Load Line for Emitter Bias Circuit

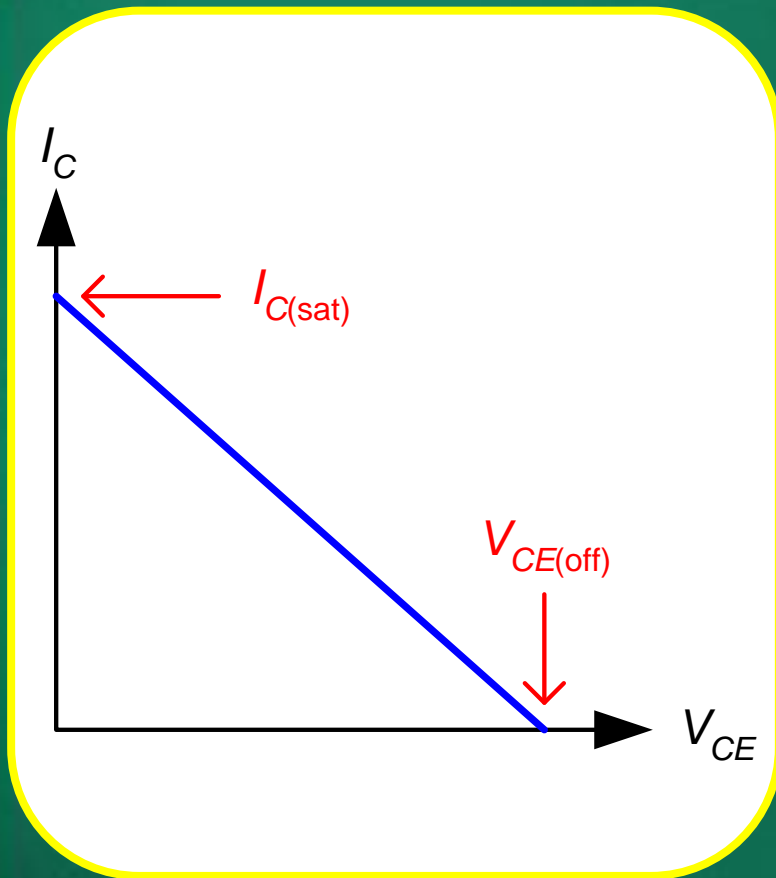

$$I_{C(sat)} = \frac{V_{CC} - (-V_{EE})}{R_C + R_E} = \frac{V_{CC} + V_{EE}}{R_C + R_E}$$


Load Line for Emitter Bias Circuit

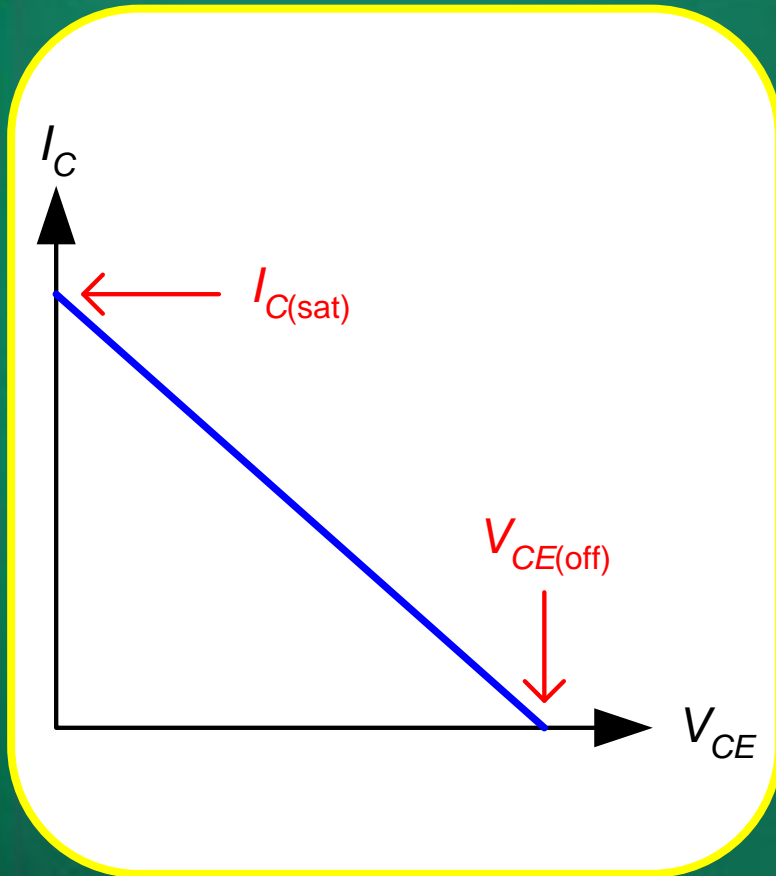


$$I_{C(sat)} = \frac{V_{CC} - (-V_{EE})}{R_C + R_E} = \frac{V_{CC} + V_{EE}}{R_C + R_E}$$

$$V_{CE(off)} = V_{CC} - (-V_{EE}) = V_{CC} + V_{EE}$$

Emitter Bias Characteristics

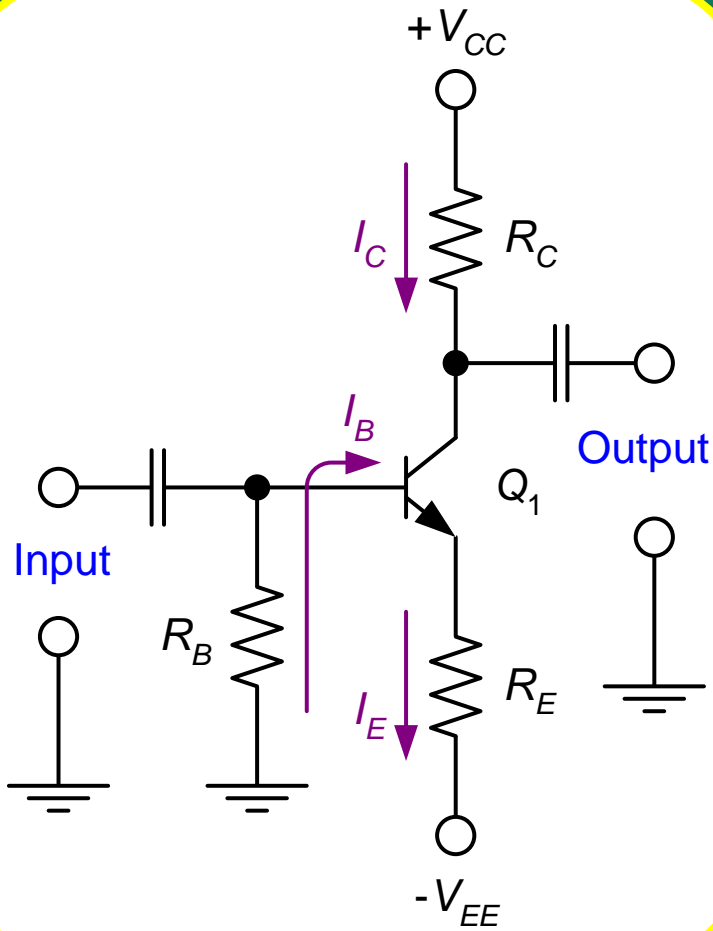


Emitter Bias Characteristics

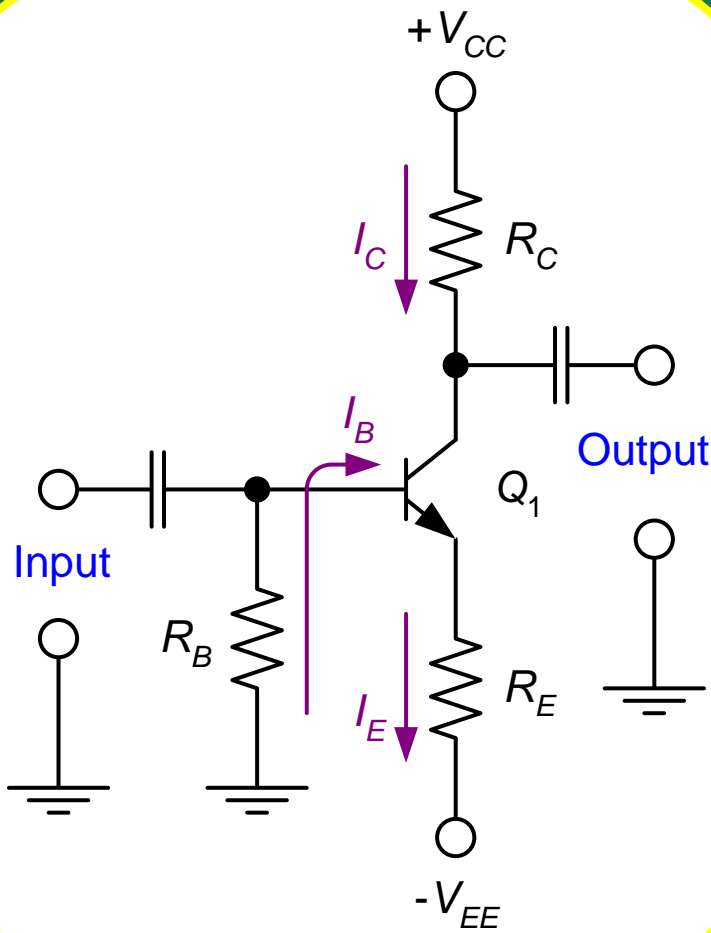

Circuit recognition: A split (dual-polarity) power supply and the base resistor is connected to ground.

Emitter Bias Characteristics

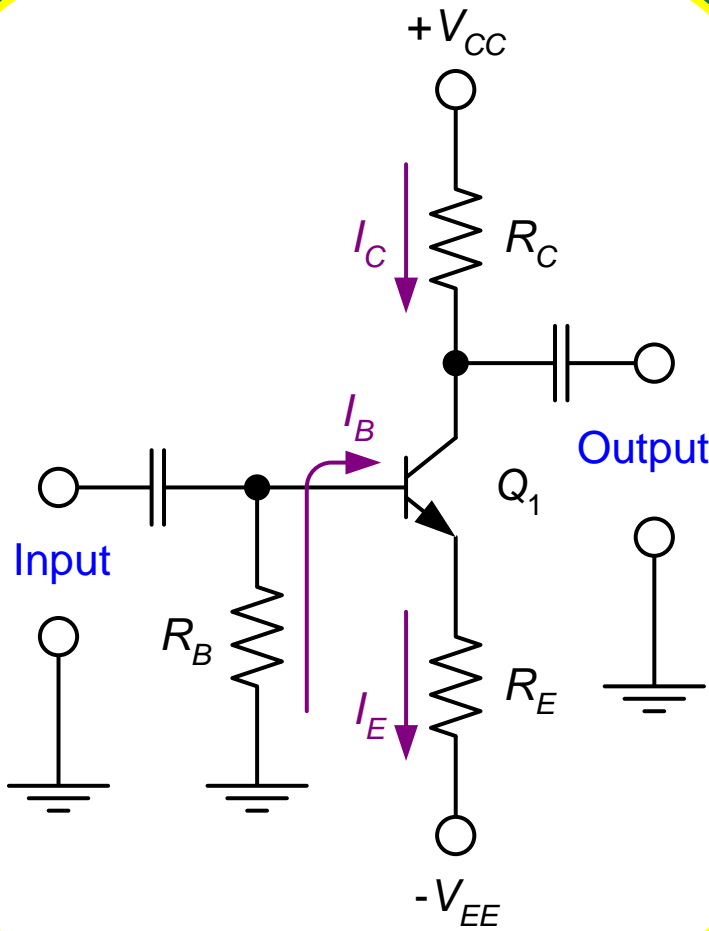


Circuit recognition: A split (dual-polarity) power supply and the base resistor is connected to ground.

Advantage: The circuit Q-point values are stable against changes in h_{FE} .

Disadvantage: Requires the use of dual-polarity power supply.


Applications: Used primarily to bias linear amplifiers.

Emitter Bias Characteristics

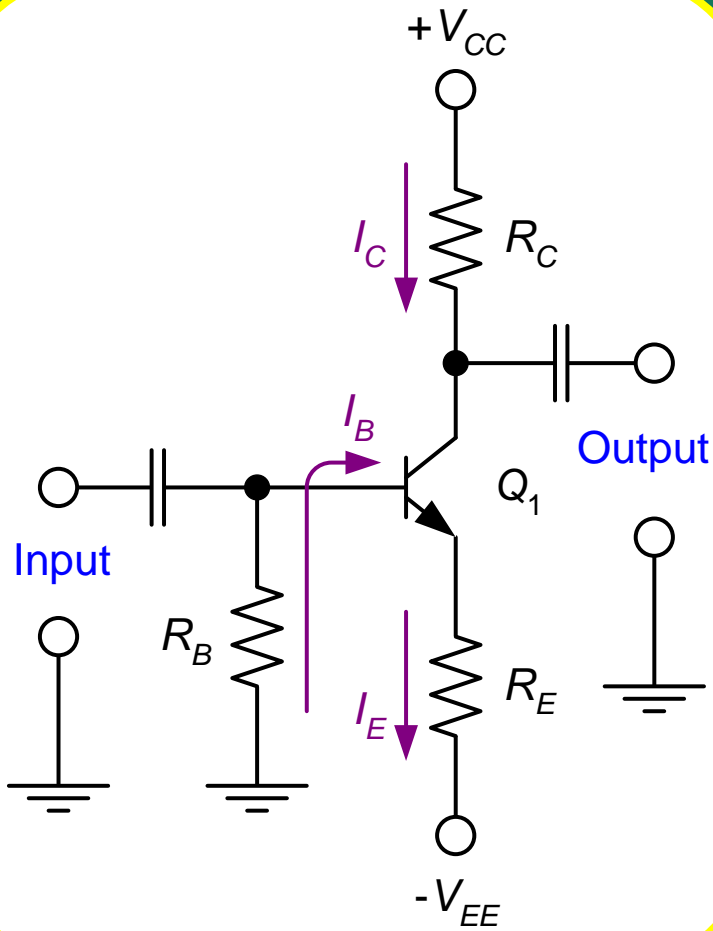

Load line equations:

Emitter Bias Characteristics

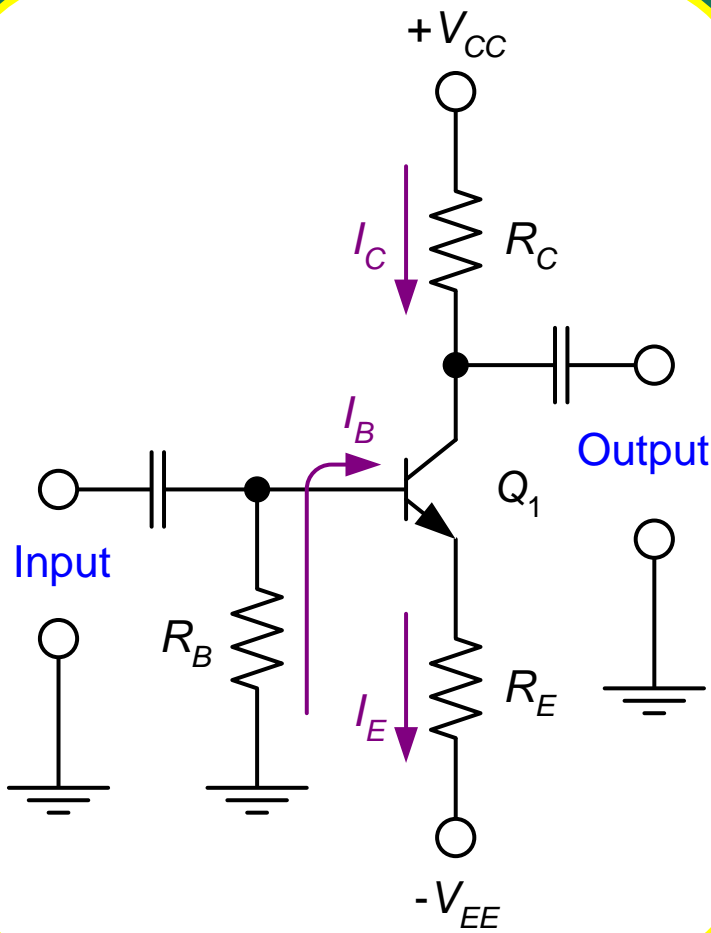


Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC} + V_{EE}}{R_C + R_E}$$

$$V_{CE(\text{off})} = V_{CC} + V_{EE}$$

Emitter Bias Characteristics

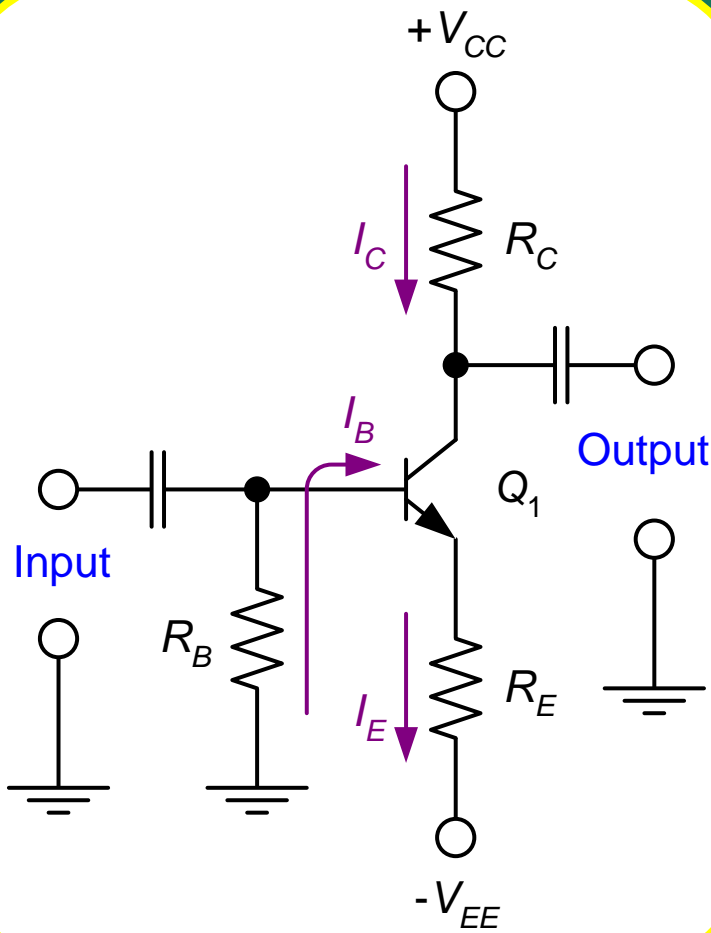


Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC} + V_{EE}}{R_C + R_E}$$

$$V_{CE(\text{off})} = V_{CC} + V_{EE}$$

Q-point equations:

Emitter Bias Characteristics

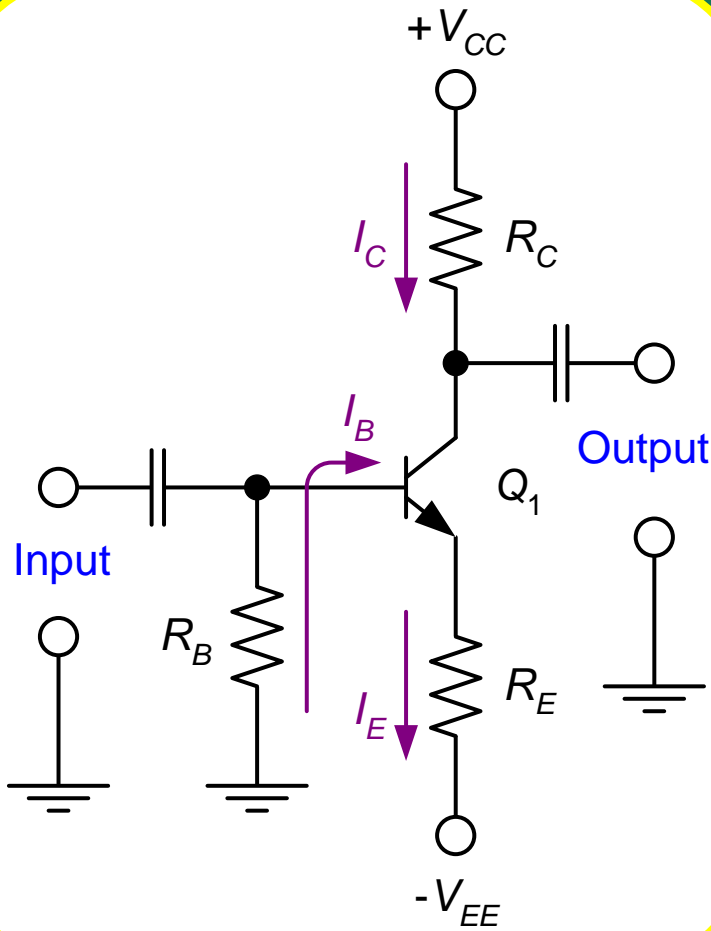

Load line equations:

$$I_{C(\text{sat})} = \frac{V_{CC} + V_{EE}}{R_C + R_E}$$


$$V_{CE(\text{off})} = V_{CC} + V_{EE}$$

Q-point equations:


$$I_{CQ} = (h_{FE}) \frac{-V_{BE} + V_{EE}}{R_B + (h_{FE} + 1)R_E}$$

$$V_{CEQ} \cong V_{CC} - I_{CQ}(R_C + R_E) + V_{EE}$$

Collector Feedback Bias

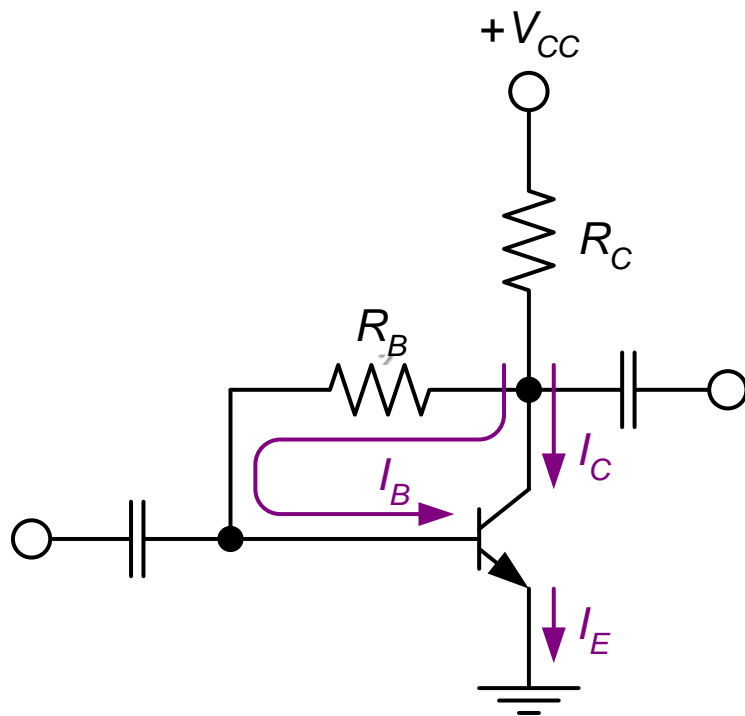


Collector Feedback Bias

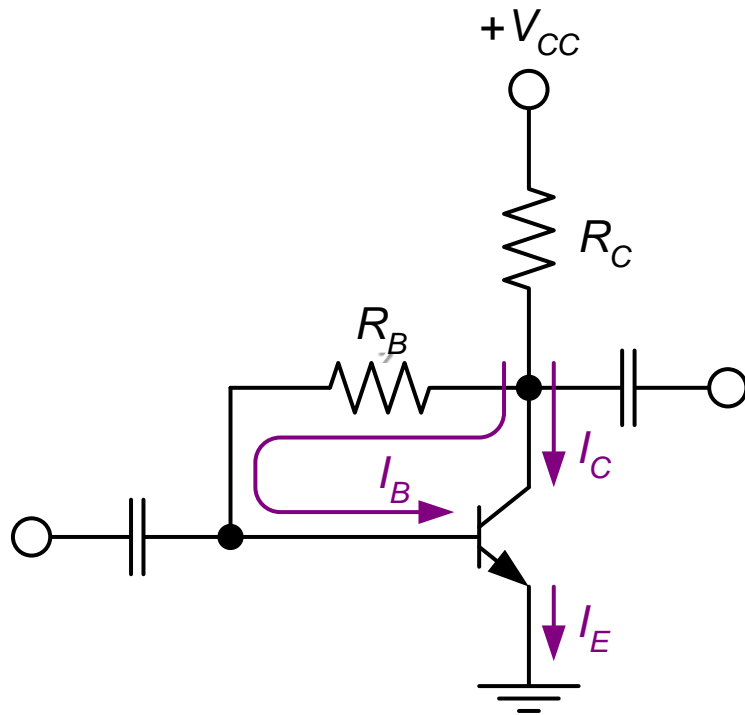

$$V_{CC} = (I_C + I_B)R_C + I_BR_B + V_{BE}$$


Collector Feedback Bias

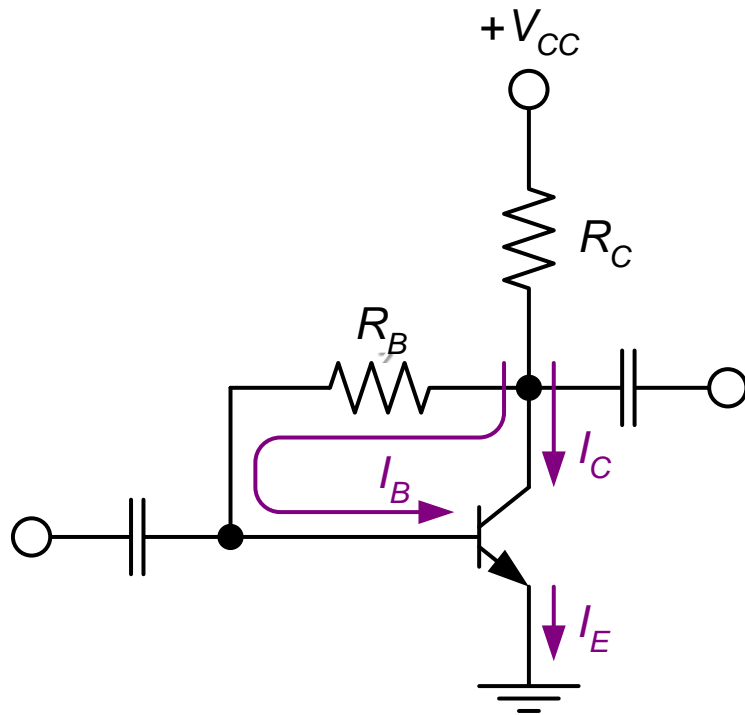

$$V_{CC} = (I_C + I_B)R_C + I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$

Collector Feedback Bias

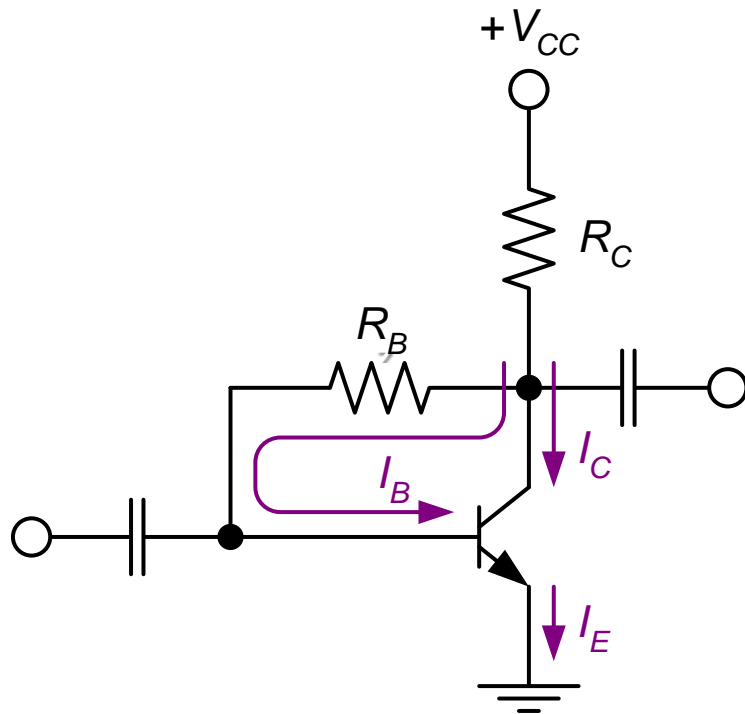


$$V_{CC} = (I_C + I_B)R_C + I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$

$$I_{CQ} = h_{FE} I_B$$

Collector Feedback Bias

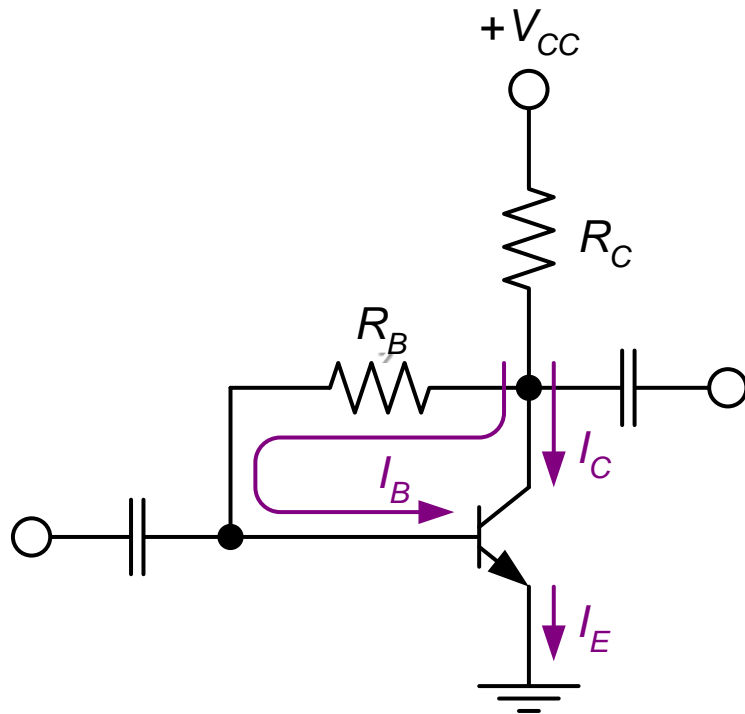

$$V_{CC} = (I_C + I_B)R_C + I_B R_B + V_{BE}$$


$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$

$$I_{CQ} = h_{FE} I_B$$

$$V_{CEQ} = V_{CC} - (h_{FE} + 1)I_B R_C$$
$$\cong V_{CC} - I_{CQ} R_C$$

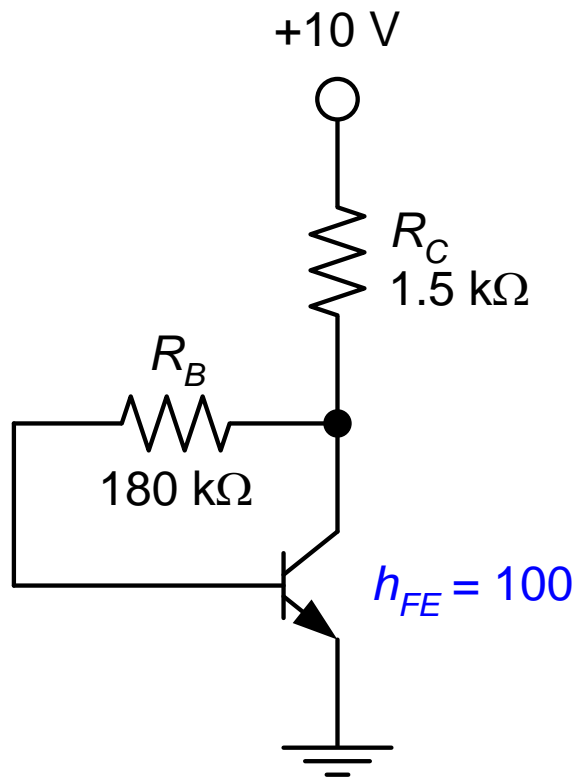
Example

Determine the values of I_{CQ} and V_{CEQ} for the amplifier shown



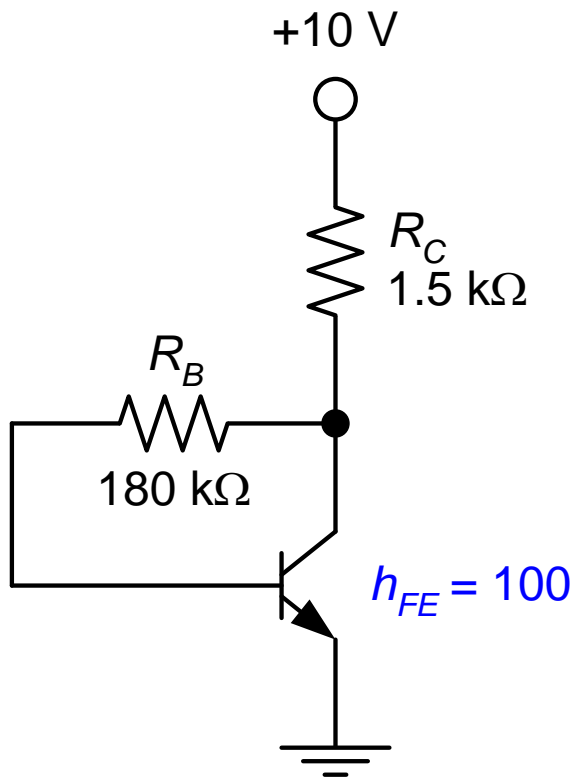Example


Determine the values of I_{CQ} and V_{CEQ} for the amplifier shown



$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_C}$$
$$= \frac{10\text{V} - 0.7\text{V}}{180\text{k}\Omega + 101 \times 1.5\text{k}\Omega} = 28.05\mu\text{A}$$

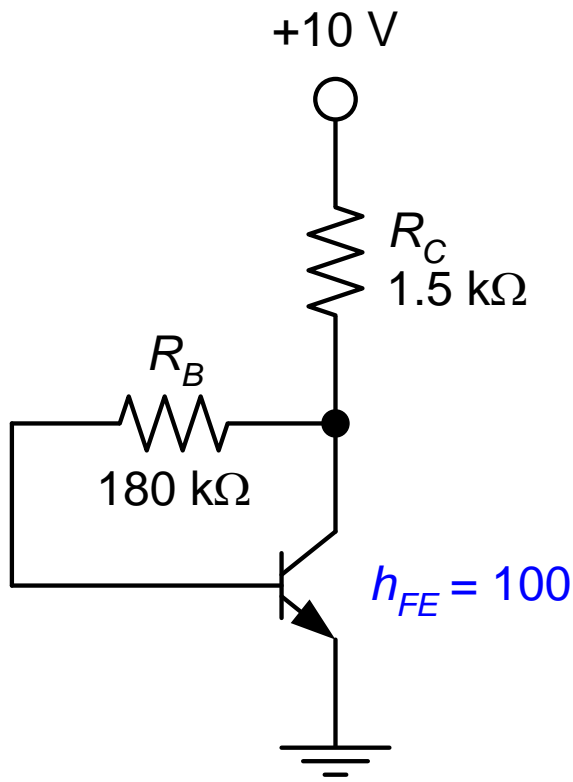Example

Determine the values of I_{CQ} and V_{CEQ} for the amplifier shown




$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1) R_C}$$
$$= \frac{10\text{V} - 0.7\text{V}}{180\text{k}\Omega + 101 \times 1.5\text{k}\Omega} = 28.05\mu\text{A}$$

$$I_{CQ} = h_{FE} I_B = 100 \times 28.05\mu\text{A}$$
$$= 2.805\text{mA}$$

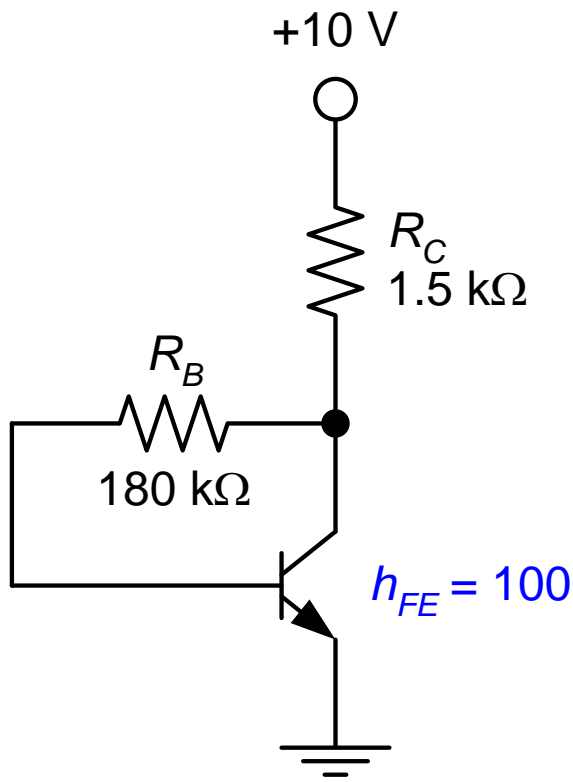Example

Determine the values of I_{CQ} and V_{CEQ} for the amplifier shown




$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_C}$$
$$= \frac{10\text{V} - 0.7\text{V}}{180\text{k}\Omega + 101 \times 1.5\text{k}\Omega} = 28.05\mu\text{A}$$


$$I_{CQ} = h_{FE} I_B = 100 \times 28.05\mu\text{A}$$
$$= 2.805\text{mA}$$

$$V_{CEQ} = V_{CC} - (h_{FE} + 1)I_B R_C$$
$$= 10\text{V} - 101 \times 28.05\mu\text{A} \times 1.5\text{k}\Omega$$
$$= 5.75\text{V}$$

Circuit Stability

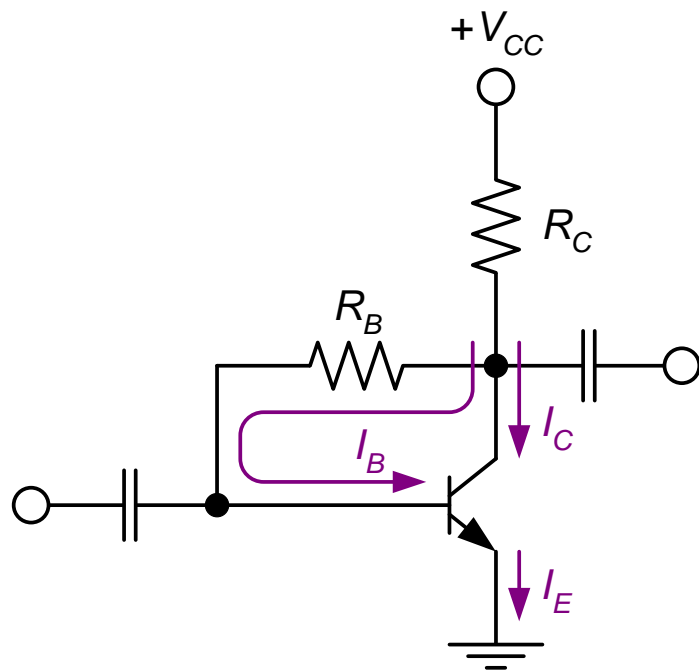

Circuit Stability

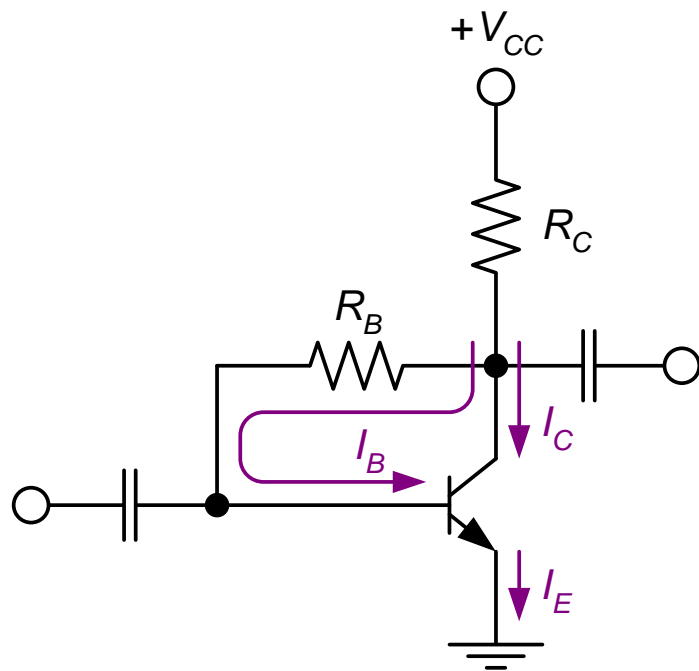

h_{FE} increases



I_C increases (if I_B is the same)



V_{CE} decreases




I_B decreases




I_C does not increase that much.

Good Stability. Less dependent on h_{FE} and temperature.

Collector Feedback Characteristics

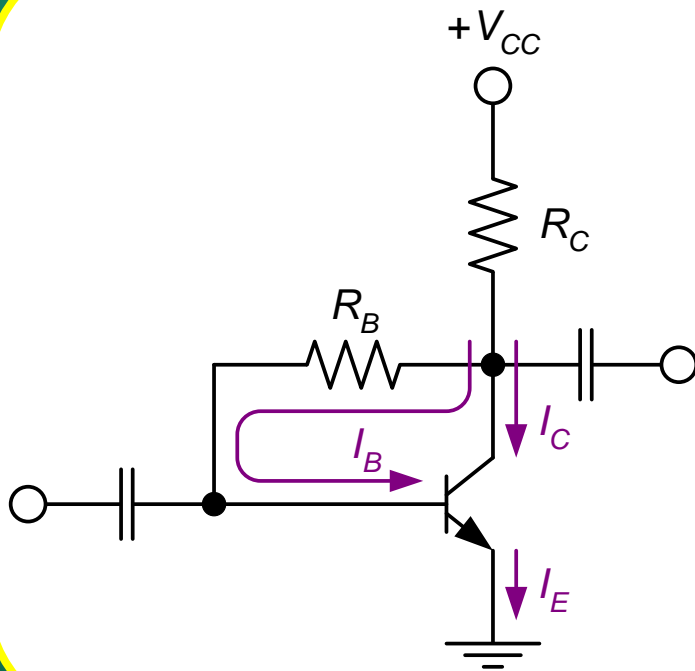


Collector Feedback Characteristics

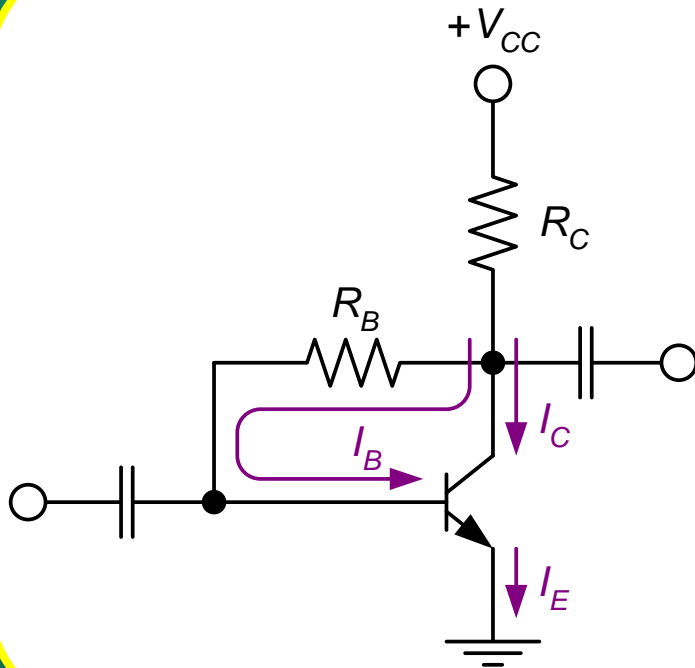

Circuit recognition: The base resistor is connected between the base and the collector terminals of the transistor.

Collector Feedback Characteristics

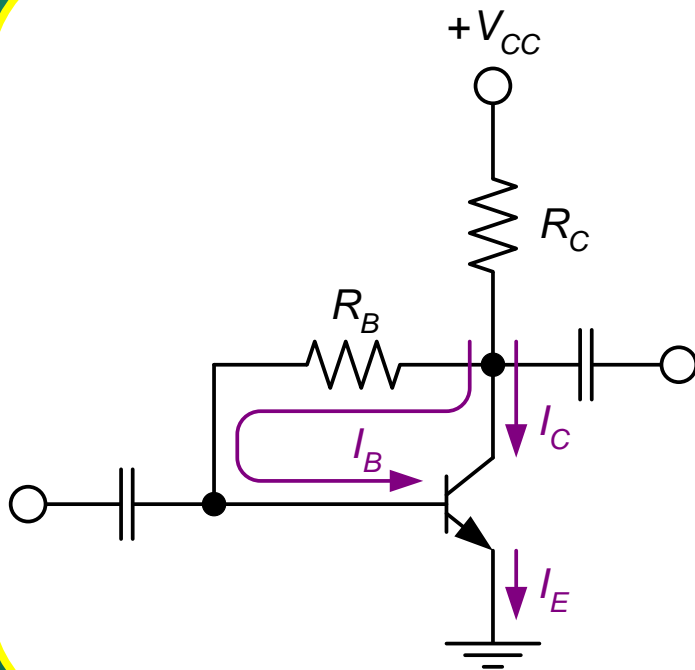


Circuit recognition: The base resistor is connected between the base and the collector terminals of the transistor.

Advantage: A simple circuit with relatively stable Q-point.

Disadvantage: Relatively poor ac characteristics.


Applications: Used primarily to bias linear amplifiers.

Collector Feedback Characteristics

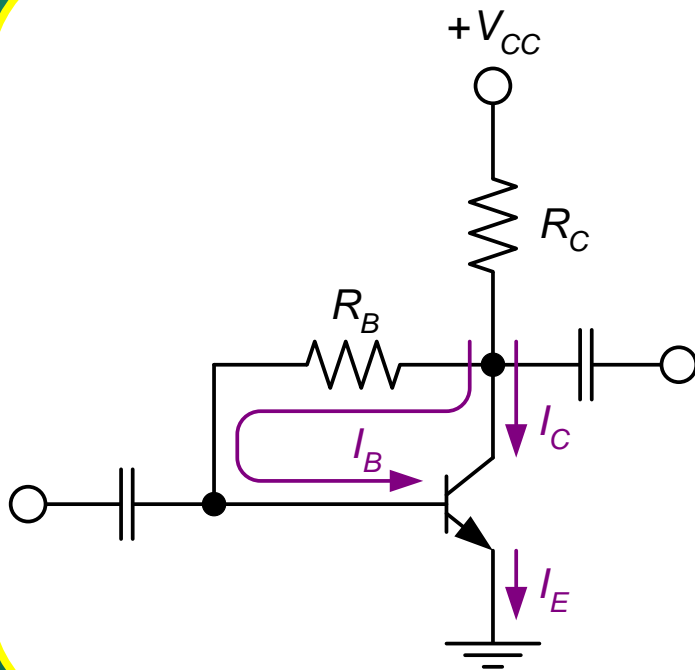

Q-point relationships:


Collector Feedback Characteristics

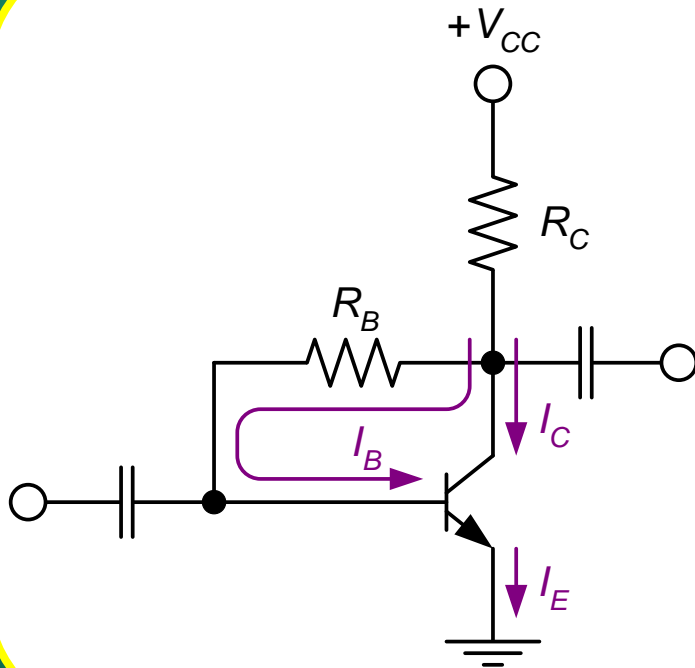

Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$

Collector Feedback Characteristics

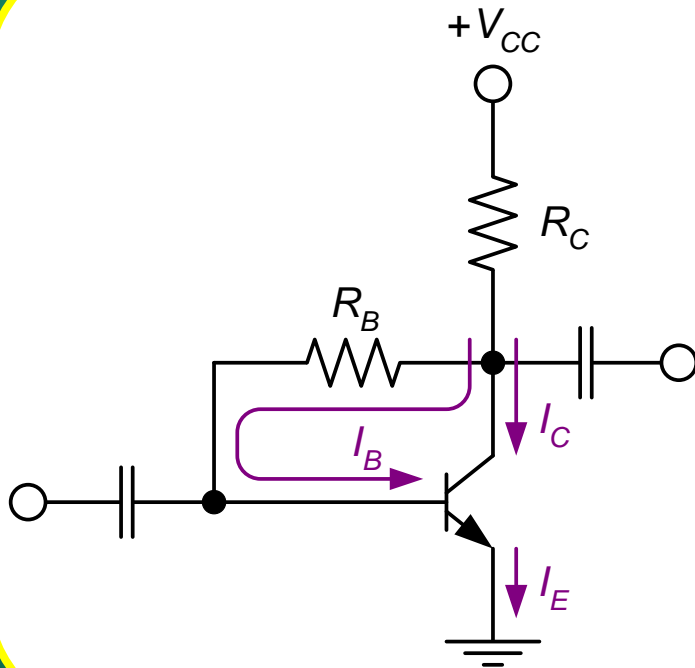


Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$

$$I_{CQ} = h_{FE} I_B$$

Collector Feedback Characteristics

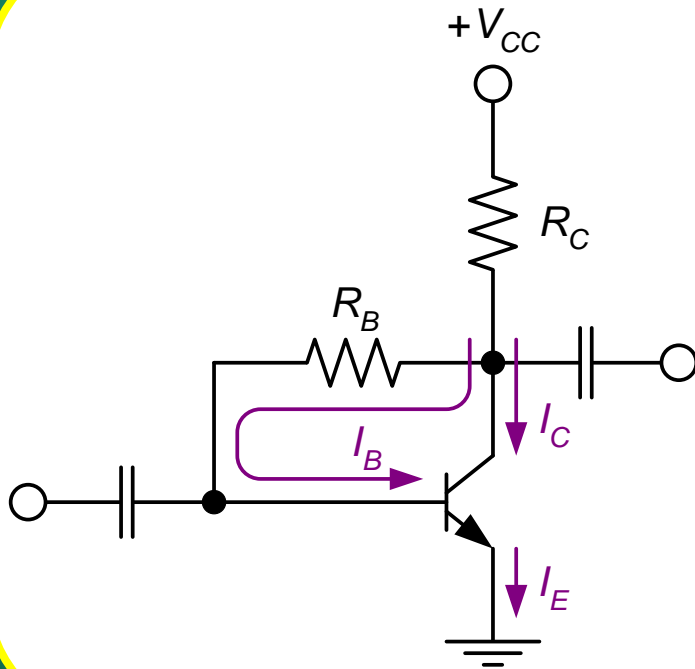


Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{(h_{FE} + 1)R_C + R_B}$$


$$I_{CQ} = h_{FE} I_B$$

$$V_{CEQ} \cong V_{CC} - I_{CQ} R_C$$

Emitter Feedback Bias

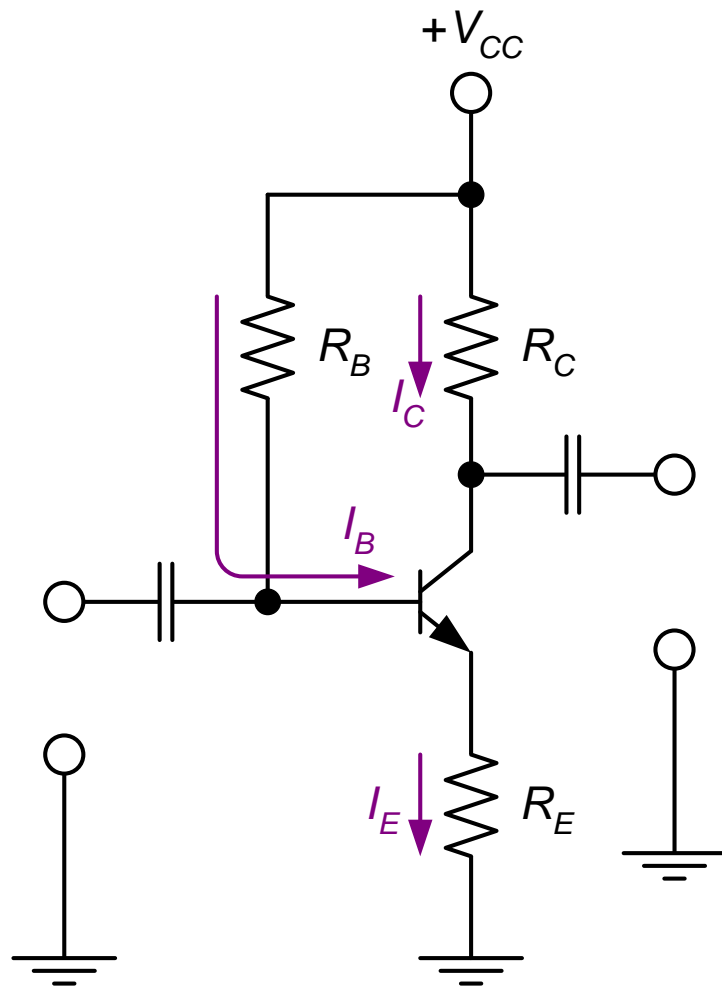


Emitter Feedback Bias

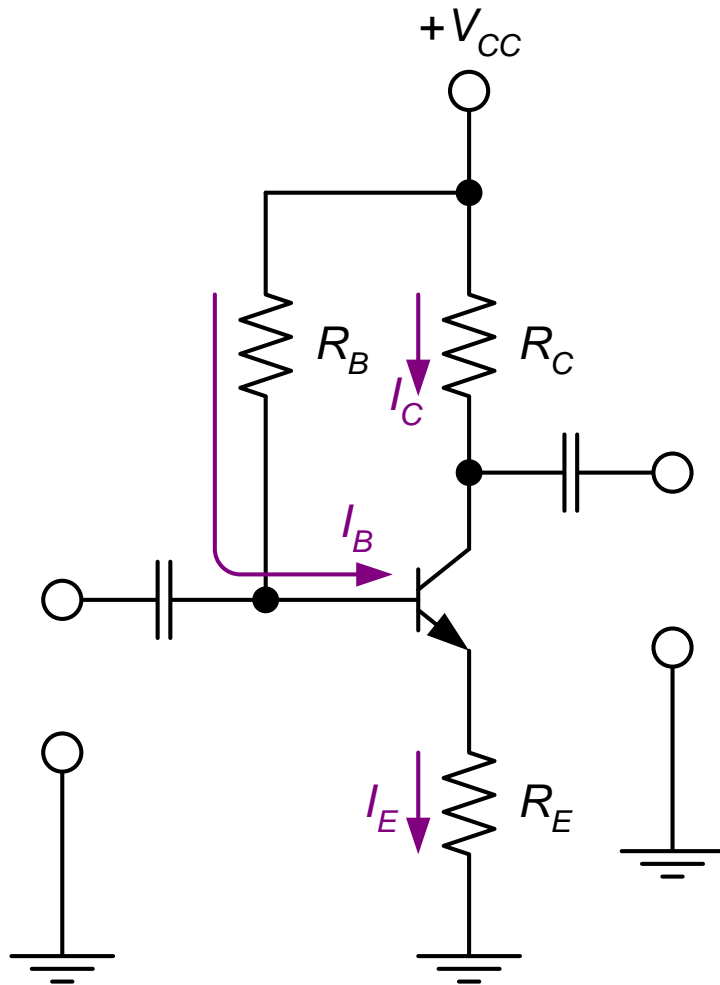

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$


Emitter Feedback Bias

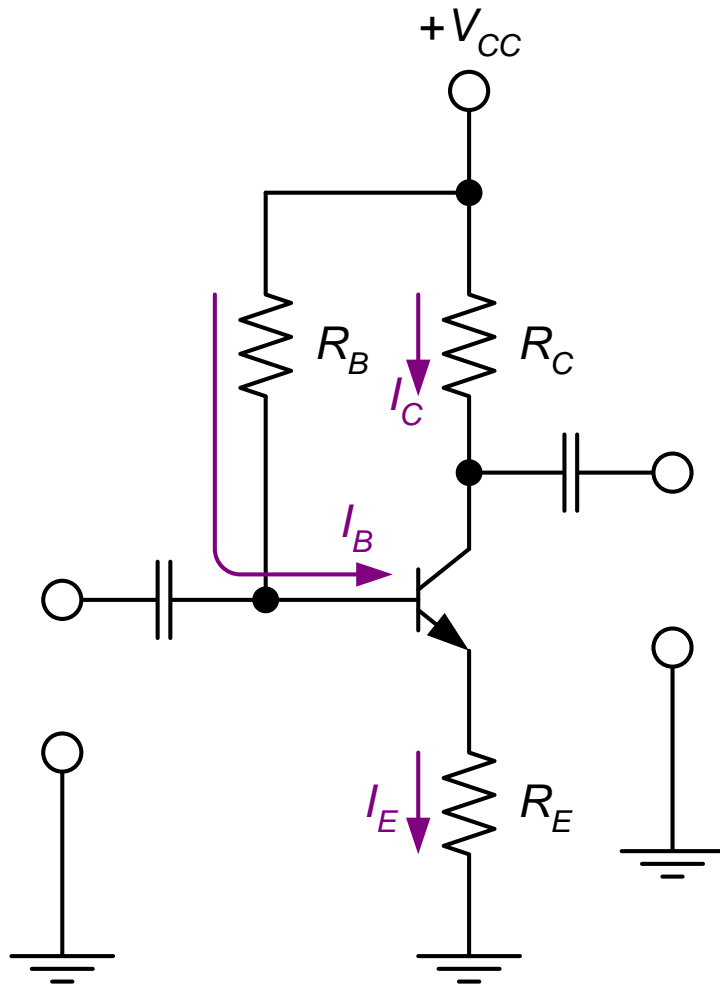

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

$$I_{CQ} = h_{FE} I_B$$

Emitter Feedback Bias

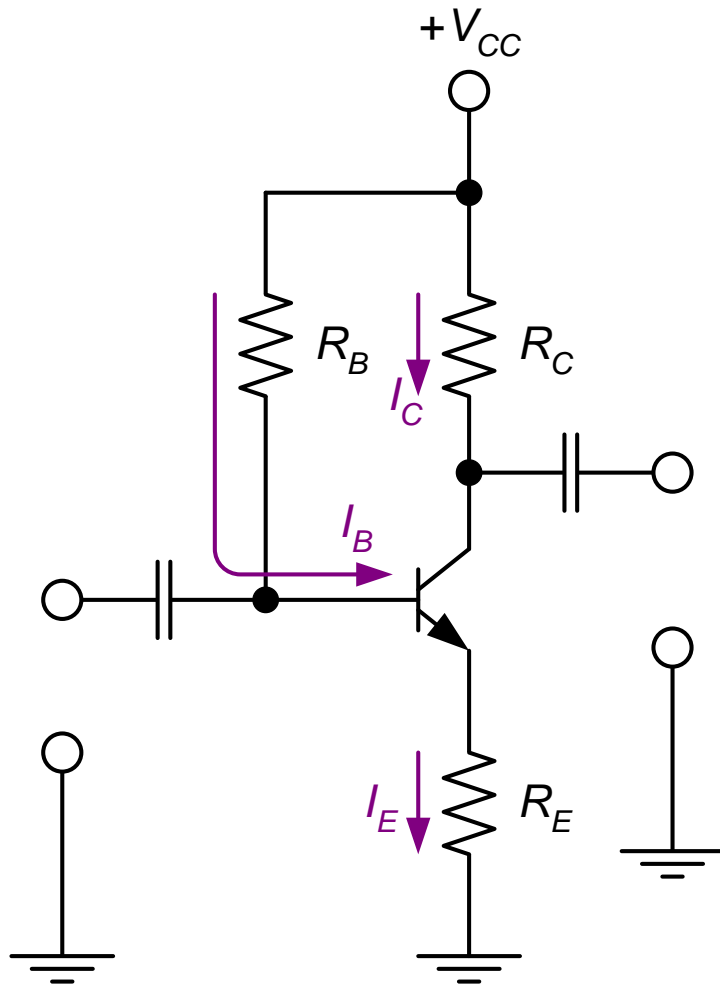


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

$$I_{CQ} = h_{FE} I_B$$

$$I_E = (h_{FE} + 1) I_B$$

Emitter Feedback Bias

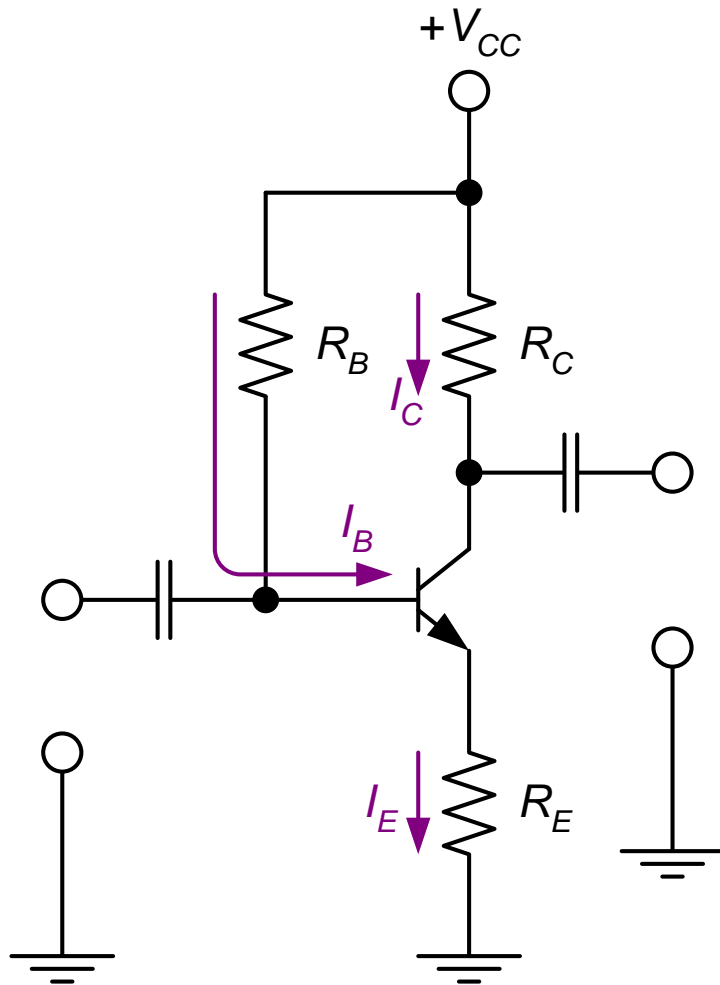


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

$$I_{CQ} = h_{FE} I_B$$


$$I_E = (h_{FE} + 1) I_B$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C - I_E R_E \\ &\cong V_{CC} - I_{CQ} (R_C + R_E) \end{aligned}$$

Example

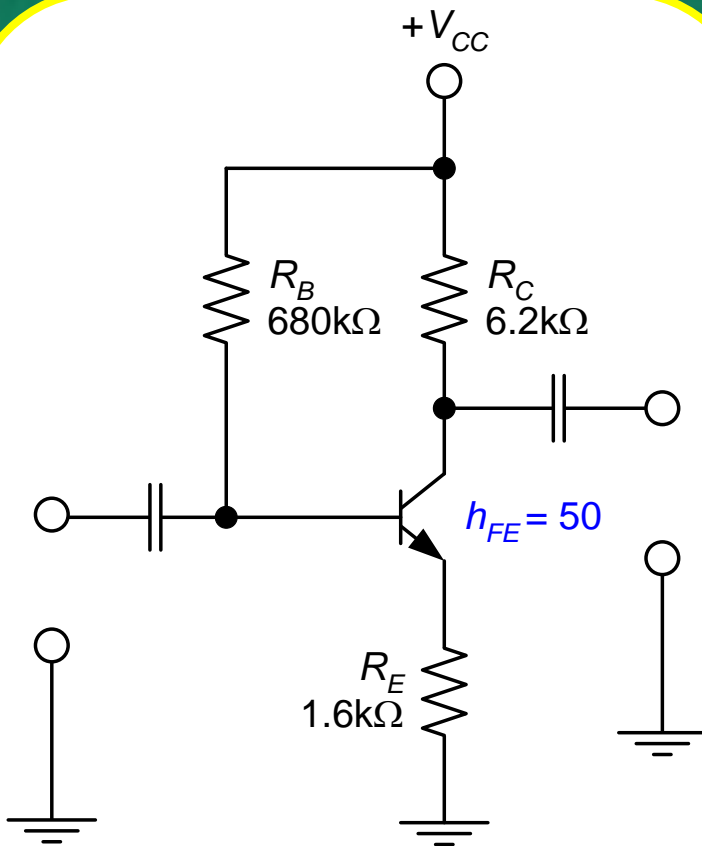


Example

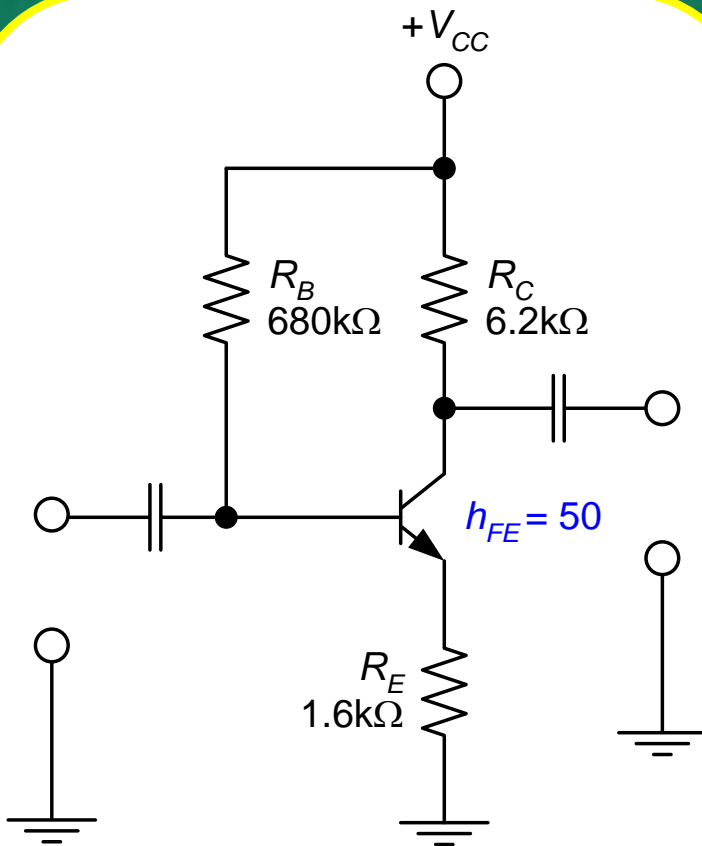

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E} = \frac{16\text{V} - 0.7\text{V}}{680\text{k}\Omega + 51 \times 1.6\text{k}\Omega} = 20.09\mu\text{A}$$


Example

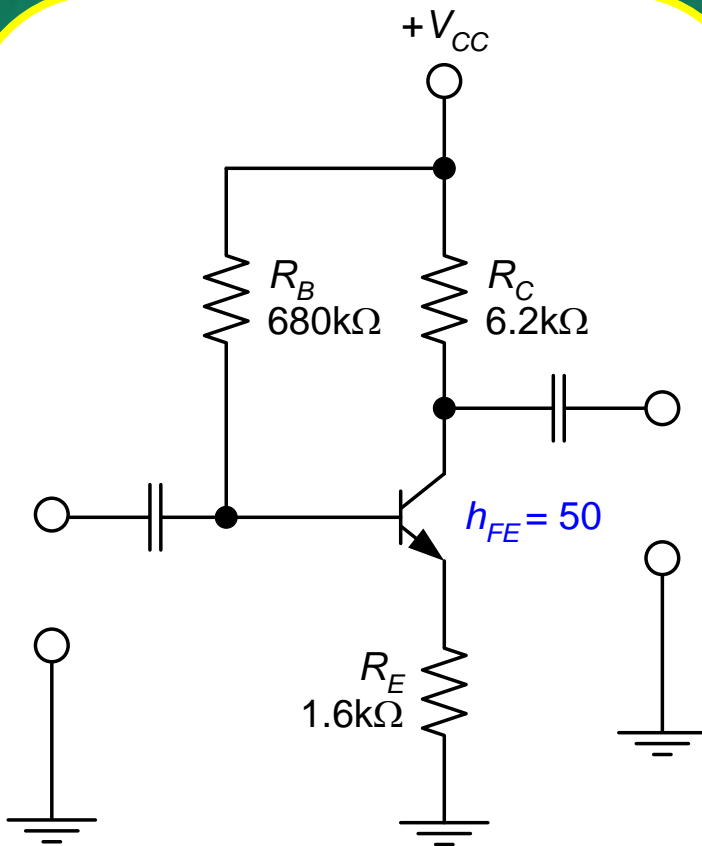

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E} = \frac{16\text{V} - 0.7\text{V}}{680\text{k}\Omega + 51 \times 1.6\text{k}\Omega} = 20.09\mu\text{A}$$

$$I_{CQ} = h_{FE} I_B = 50 \times 20.09\mu\text{A} = 1\text{mA}$$

Example

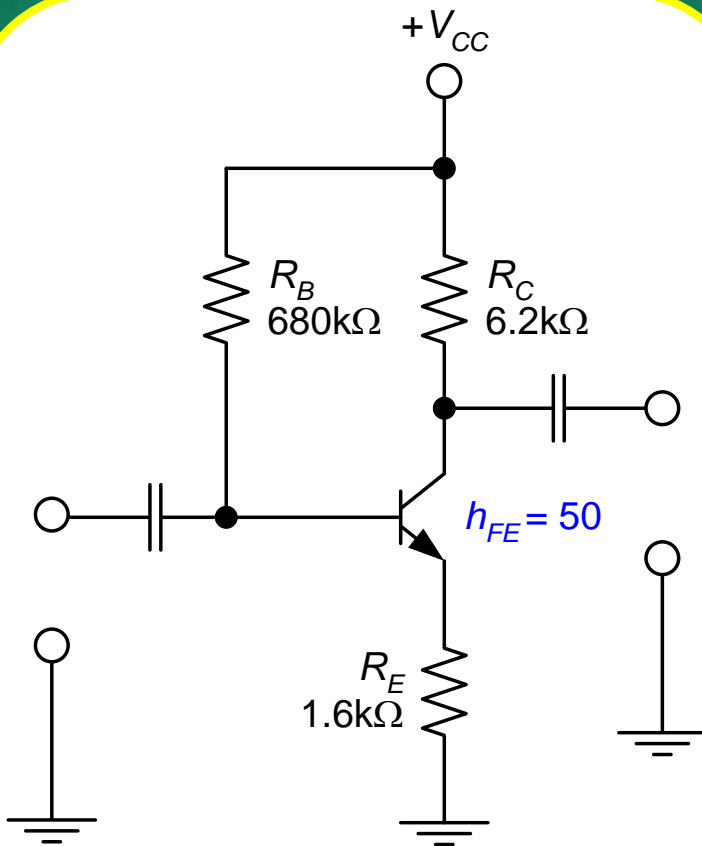


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E} = \frac{16\text{V} - 0.7\text{V}}{680\text{k}\Omega + 51 \times 1.6\text{k}\Omega} = 20.09\mu\text{A}$$


$$I_{CQ} = h_{FE} I_B = 50 \times 20.09\mu\text{A} = 1\text{mA}$$

$$V_{CEQ} \cong V_{CC} - I_{CQ} (R_C + R_E) = 16\text{V} - (1\text{mA})(7.8\text{k}\Omega) = 8.2\text{V}$$

Circuit Stability

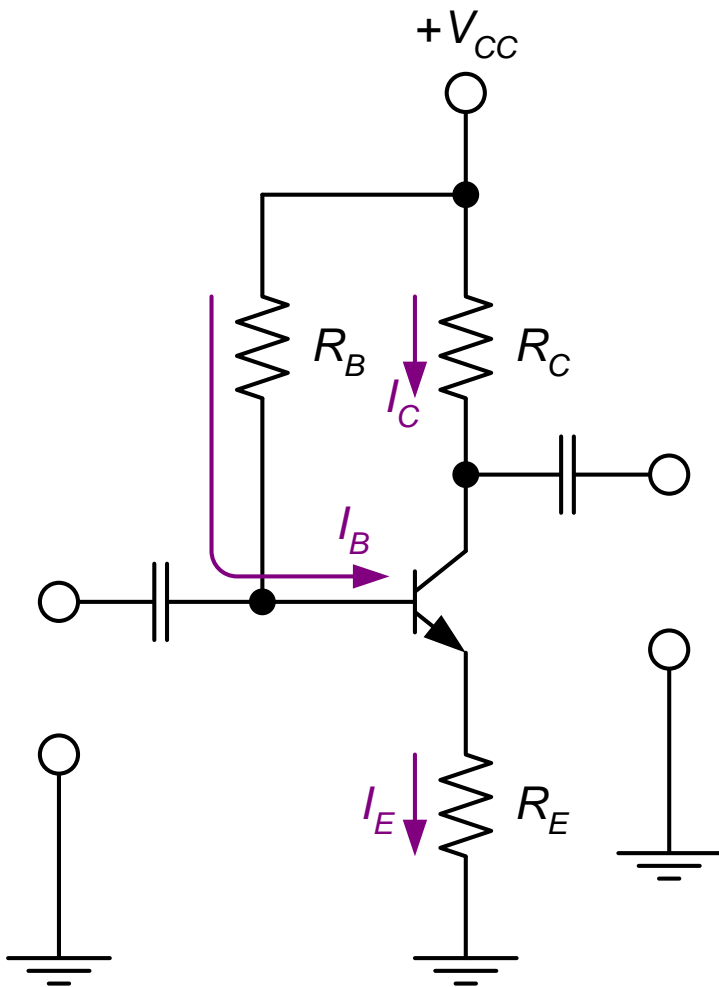

Circuit Stability

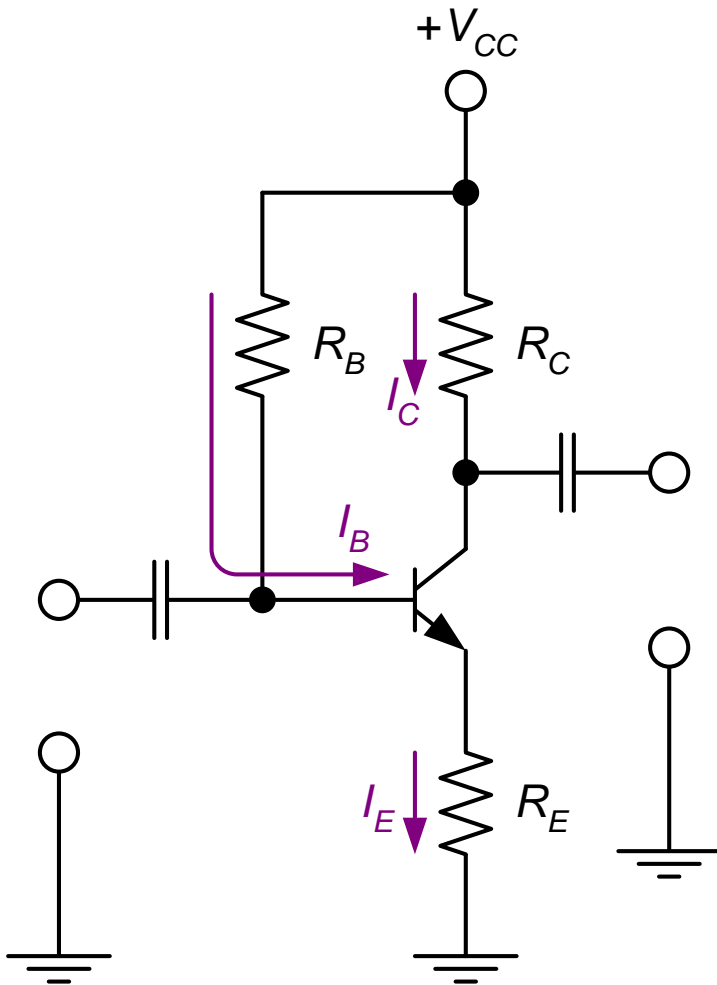

h_{FE} increases



I_C increases (if I_B is the same)



V_E increases




I_B decreases




I_C does not increase that much.

I_C is less dependent on h_{FE} and temperature.

Emitter Feedback Characteristics

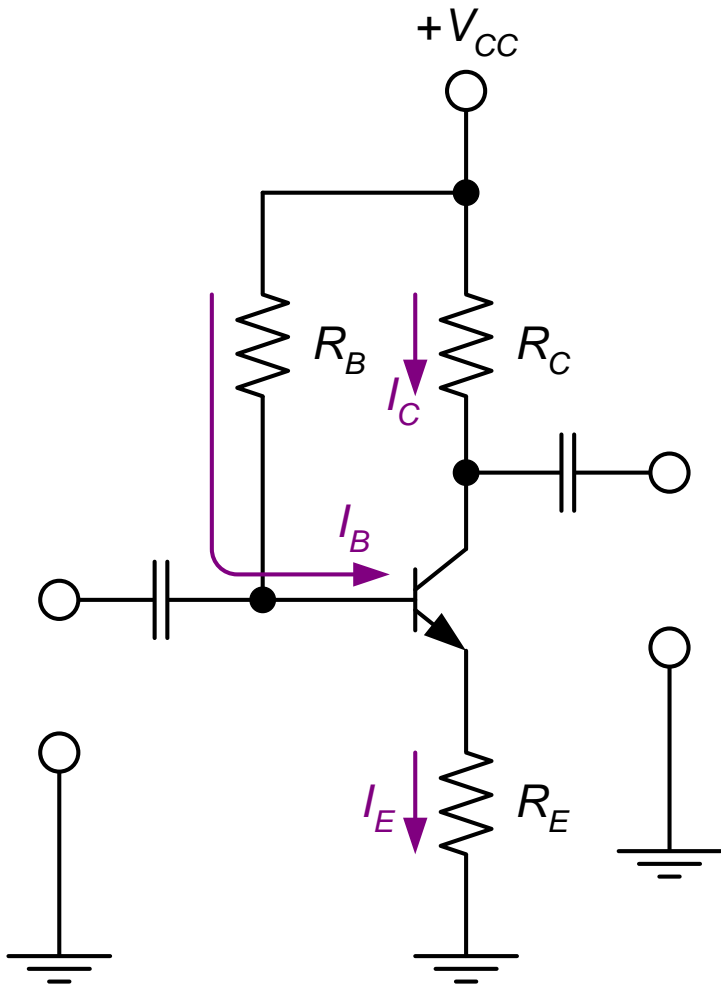


Emitter Feedback Characteristics

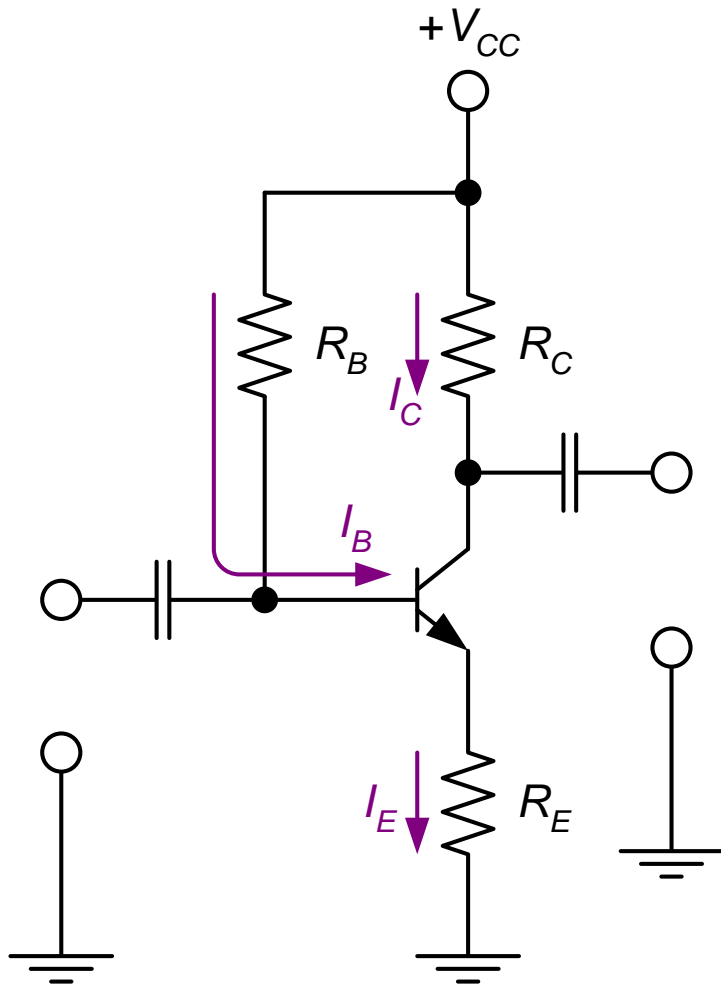

Circuit recognition: Similar to voltage divider bias with R_2 missing (or base bias with R_E added).

Emitter Feedback Characteristics

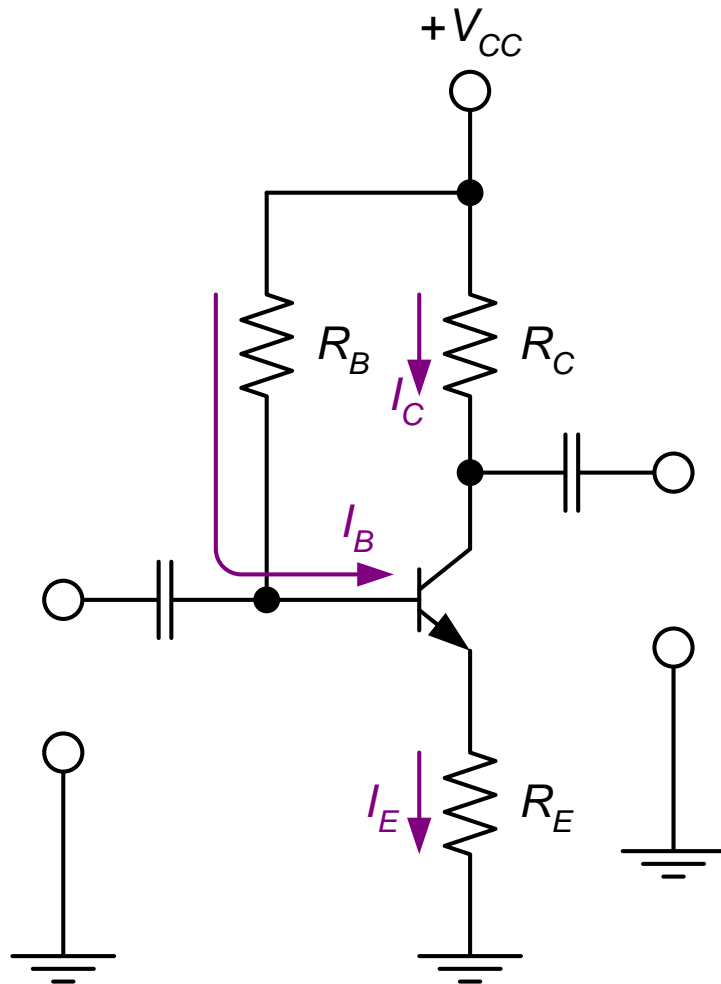


Circuit recognition: Similar to voltage divider bias with R_2 missing (or base bias with R_E added).

Advantage: A simple circuit with relatively stable Q-point.

Disadvantage: Requires more components than collector-feedback bias.


Applications: Used primarily to bias linear amplifiers.

Emitter Feedback Characteristics

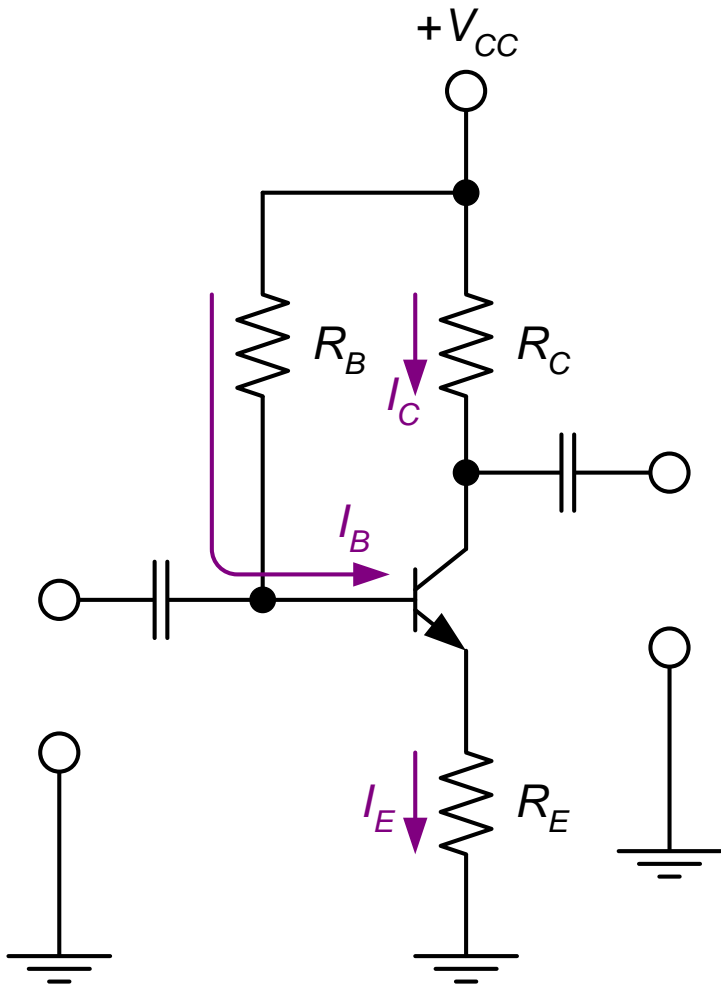

Q-point relationships:


Emitter Feedback Characteristics

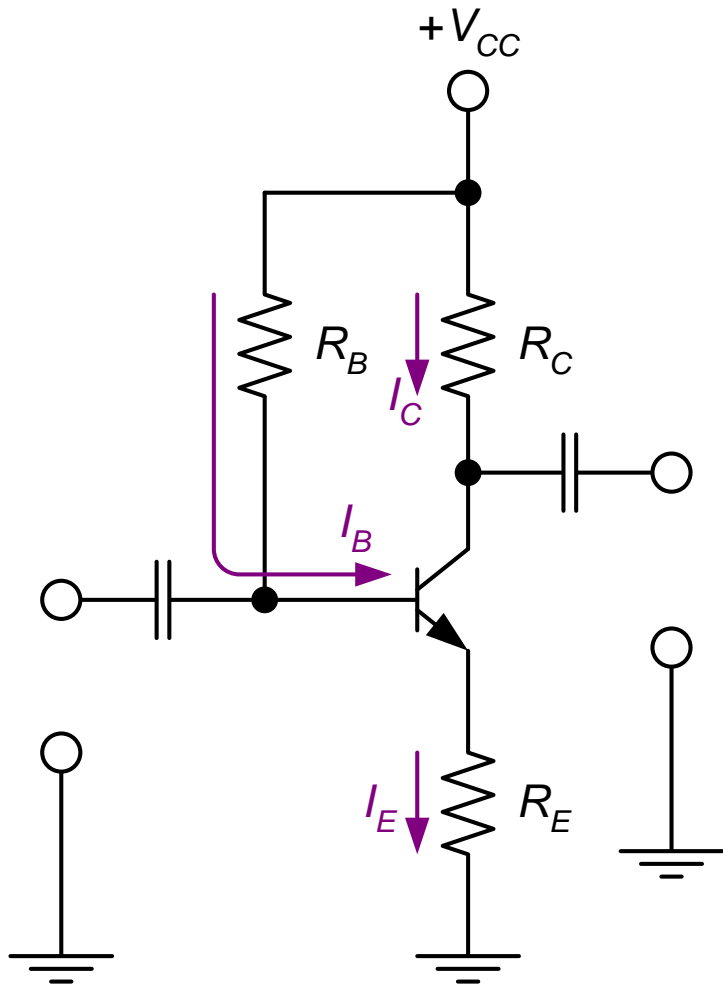

Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

Emitter Feedback Characteristics

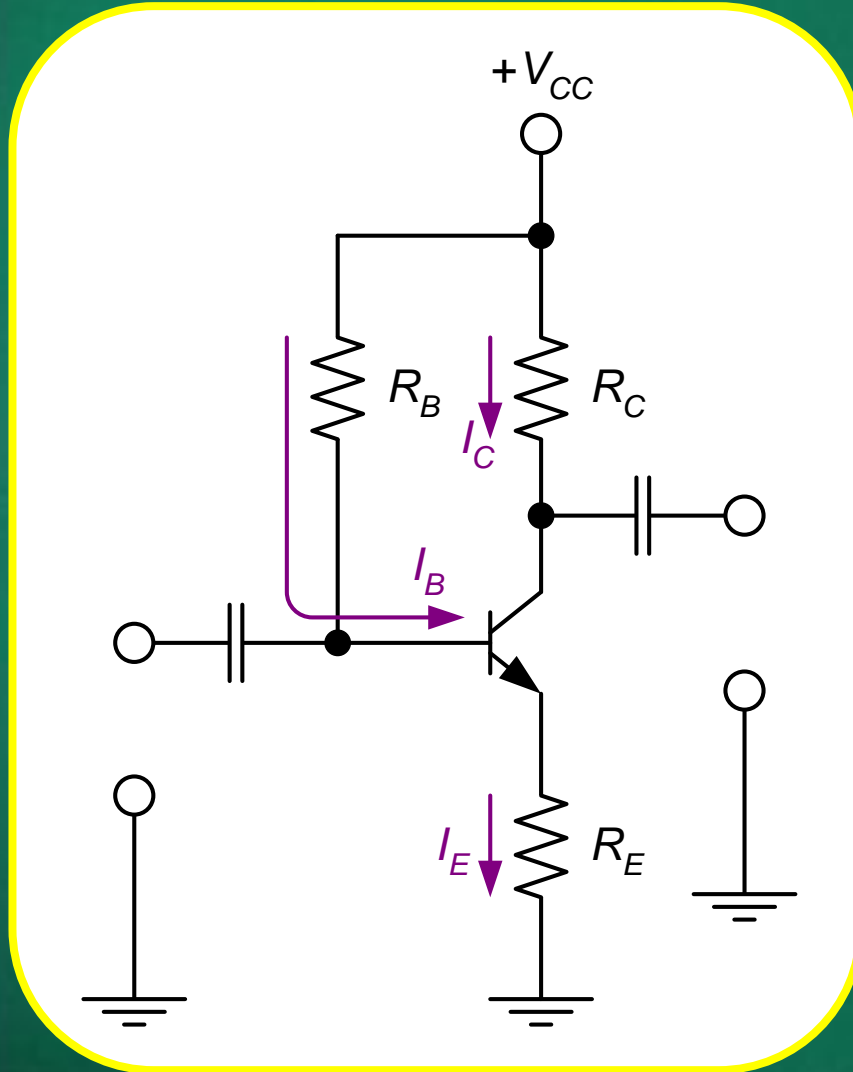


Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

$$I_{CQ} = h_{FE} I_B$$

Emitter Feedback Characteristics

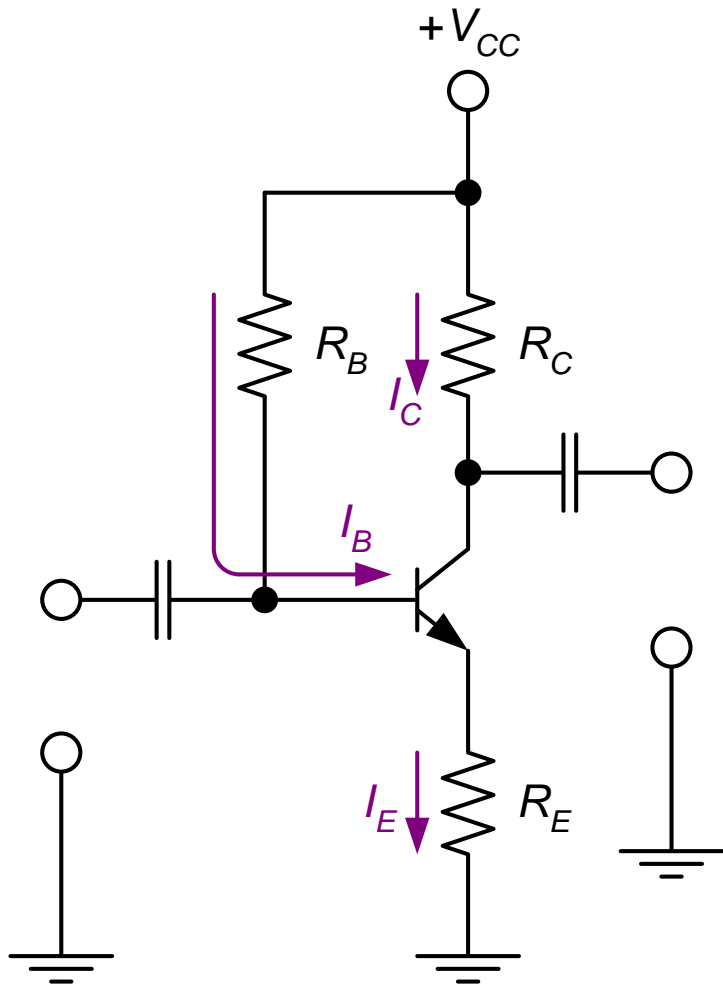

Q-point relationships:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (h_{FE} + 1)R_E}$$

$$I_{CQ} = h_{FE} I_B$$

$$V_{CEQ} \cong V_{CC} - I_{CQ} (R_C + R_E)$$