

Basic Electronic Circuits (IEC-103)

Lecture-09

DC Power Supplies

Power Supply

- ☐ **All electronic circuits need a power source to work.**
- ☐ **For electronic circuits made up of transistors and / or ICs, this power source must be a DC voltage of a specific value.**
- ☐ **A battery is a common DC voltage source for some types of electronic equipment especially portables like cell phones and iPods.**
- ☐ **Most non-portable equipment uses power supplies that operate from the AC power line but produce one or more DC outputs.**

Power Supplies

Bench Power Supply



Power Supplies

Bench Power Supply



Switch Mode Power Supply



Power Supplies


Bench Power Supply



Switch Mode Power Supply



Laptop Charger

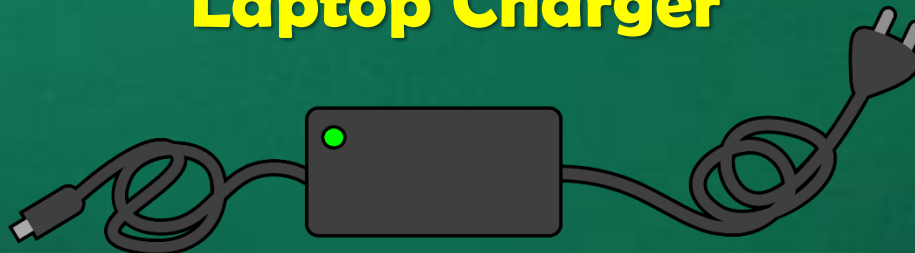

Power Supply System



Power Supply System



- ❑ The power supply system has output which is used to power an electronic circuit.


Power Supply System




- ❑ The power supply system has output which is used to power an electronic circuit.
- ❑ The input is 230 V 50 Hz mains supply.

Power Supply Characteristics

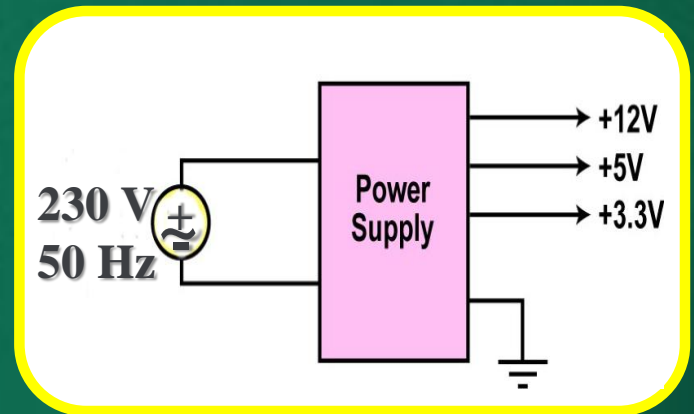- ❑ **The input is the 230 V 50 Hz AC power line.**
- ❑ **The power supply converts the AC into DC and provides one or more DC output voltages.**
- ❑ **Common voltages are 48, 24, 15, 12, 9, 5, 3.3, 2.5, 1.8, 1.5, 1.2 and 1 V.**
- ❑ **A good example of a modern power supply is the one inside a PC that furnishes 12, 5, 3.3 and 1.2 V.**




Power Supply Characteristics

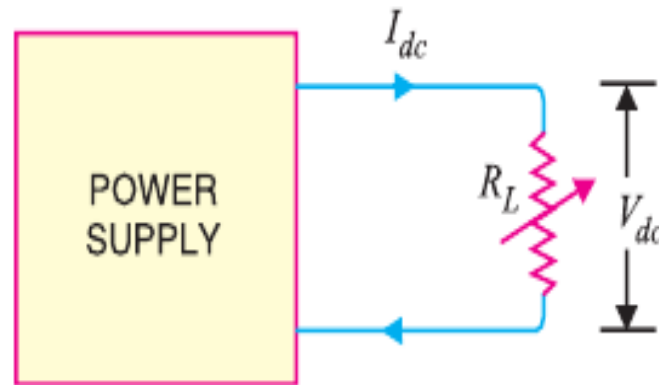

Note: In spite of variations in the load or variations in the input voltage, the output voltage should be maintained constant.

Power Supply Characteristics

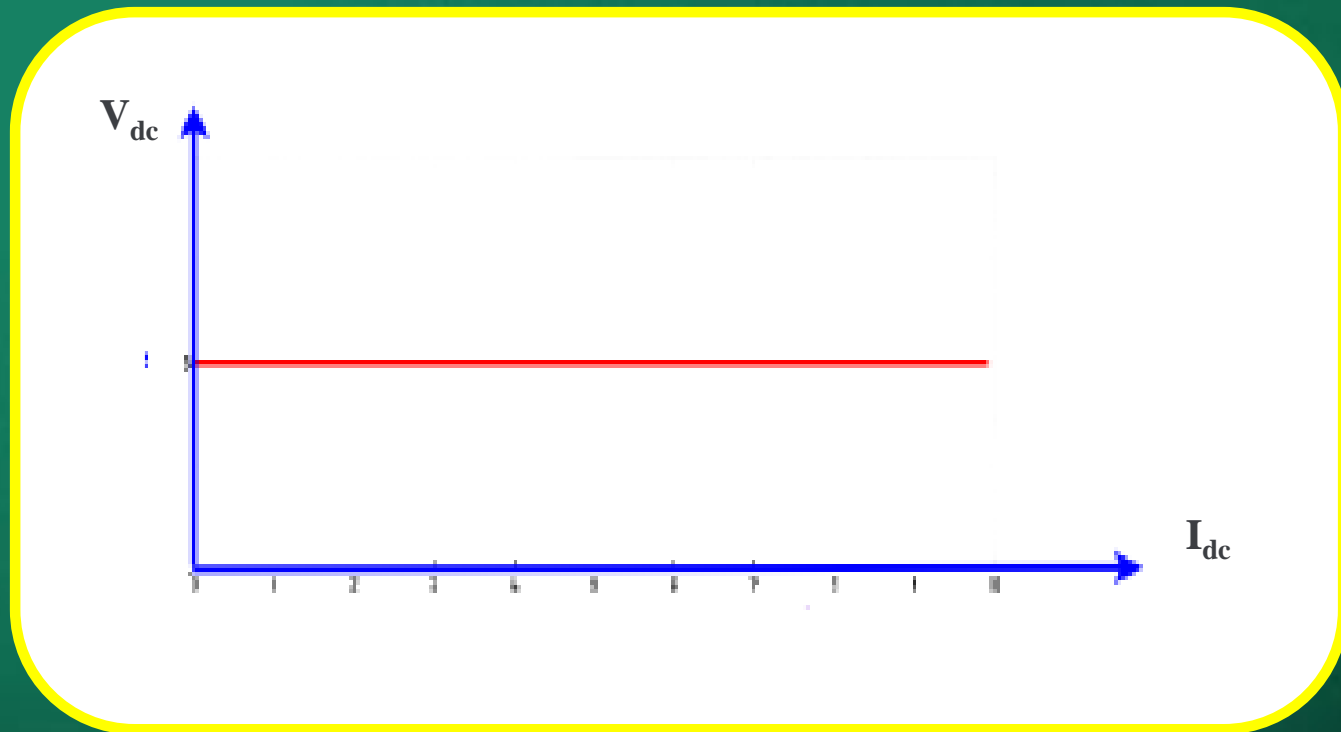VI characteristics of an ideal regulated power supply




Different Stages of a Power Supply




AC Mains


Different Stages of a Power Supply

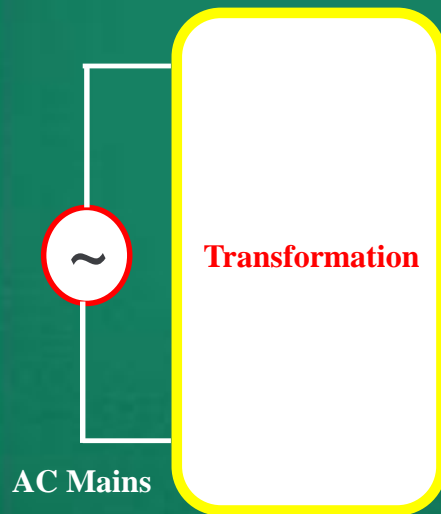


Different Stages of a Power Supply

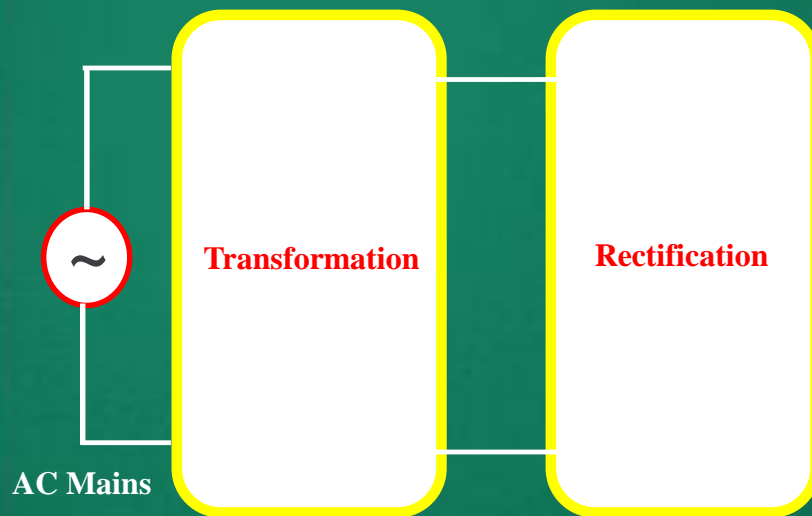


Different Stages of a Power Supply

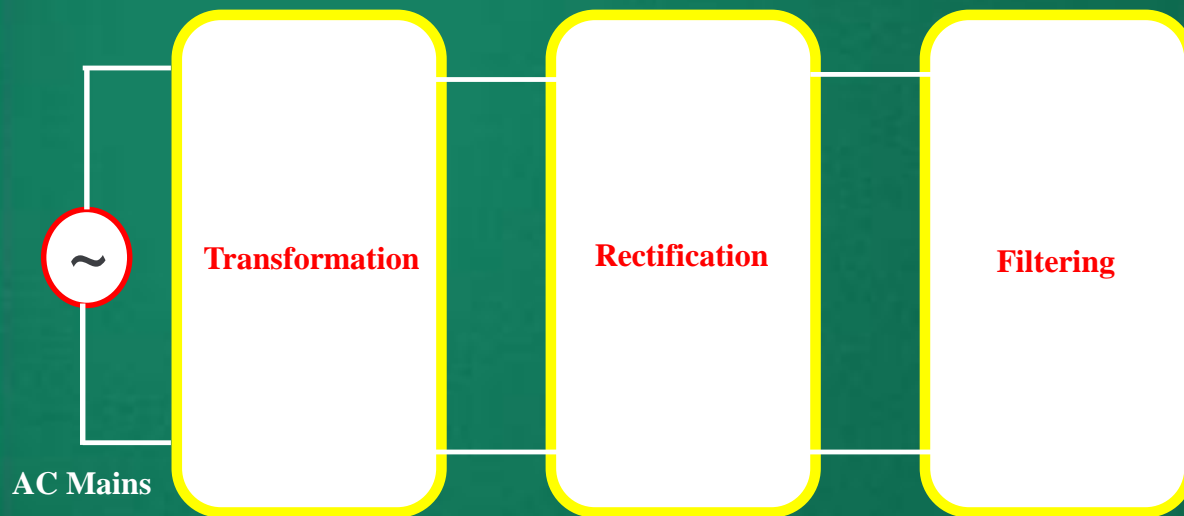

Different Stages of a Power Supply

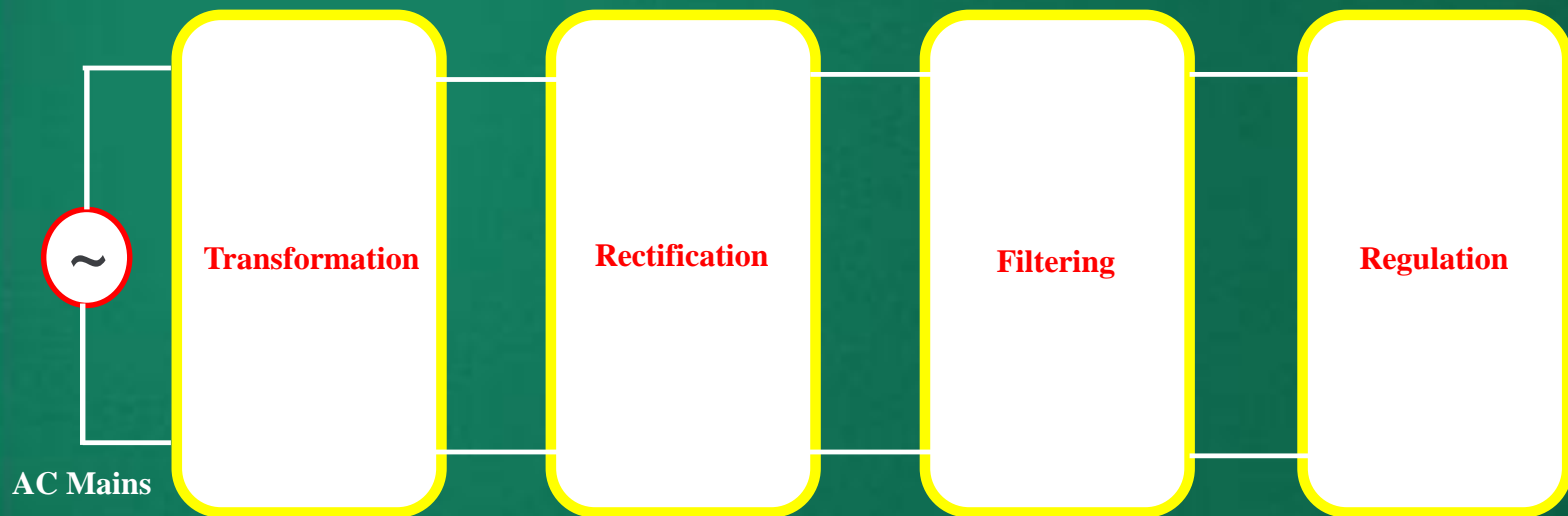

Different Stages of a Power Supply

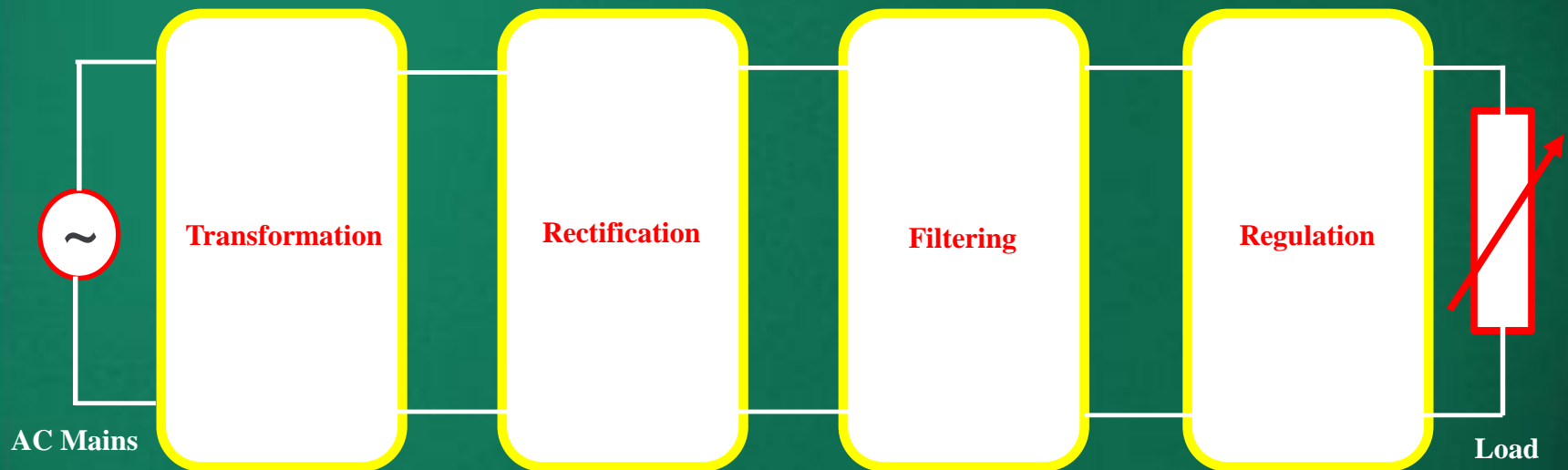

Realization of each Stage

Realization of each Stage

□ Voltage Transformation

Realization of each Stage

☐ Voltage Transformation

☐ Step down Transformer

Realization of each Stage

☐ Voltage Transformation

☐ Step down Transformer

☐ Rectification

Realization of each Stage

☐ Voltage Transformation

- ☐ Step down Transformer

☐ Rectification

- ☐ Half Wave Rectifier
- ☐ Full Wave Rectifier (Centre Tap)
- ☐ Full Wave Bridge Rectifier

Realization of each Stage

☐ Voltage Transformation

- ☐ Step down Transformer

☐ Rectification

- ☐ Half Wave Rectifier
- ☐ Full Wave Rectifier (Centre Tap)
- ☐ Full Wave Bridge Rectifier

☐ Filtering

Realization of each Stage

☐ Voltage Transformation

- ☐ Step down Transformer

☐ Rectification

- ☐ Half Wave Rectifier
- ☐ Full Wave Rectifier (Centre Tap)
- ☐ Full Wave Bridge Rectifier

☐ Filtering

- ☐ Capacitor Filter

Realization of each Stage

☐ Voltage Transformation

- ☐ Step down Transformer

☐ Rectification

- ☐ Half Wave Rectifier
- ☐ Full Wave Rectifier (Centre Tap)
- ☐ Full Wave Bridge Rectifier

☐ Filtering

- ☐ Capacitor Filter

☐ Regulation

Realization of each Stage

☐ Voltage Transformation

- ☐ Step down Transformer

☐ Rectification

- ☐ Half Wave Rectifier
- ☐ Full Wave Rectifier (Centre Tap)
- ☐ Full Wave Bridge Rectifier


☐ Filtering

- ☐ Capacitor Filter


☐ Regulation

- ☐ Zener Regulator

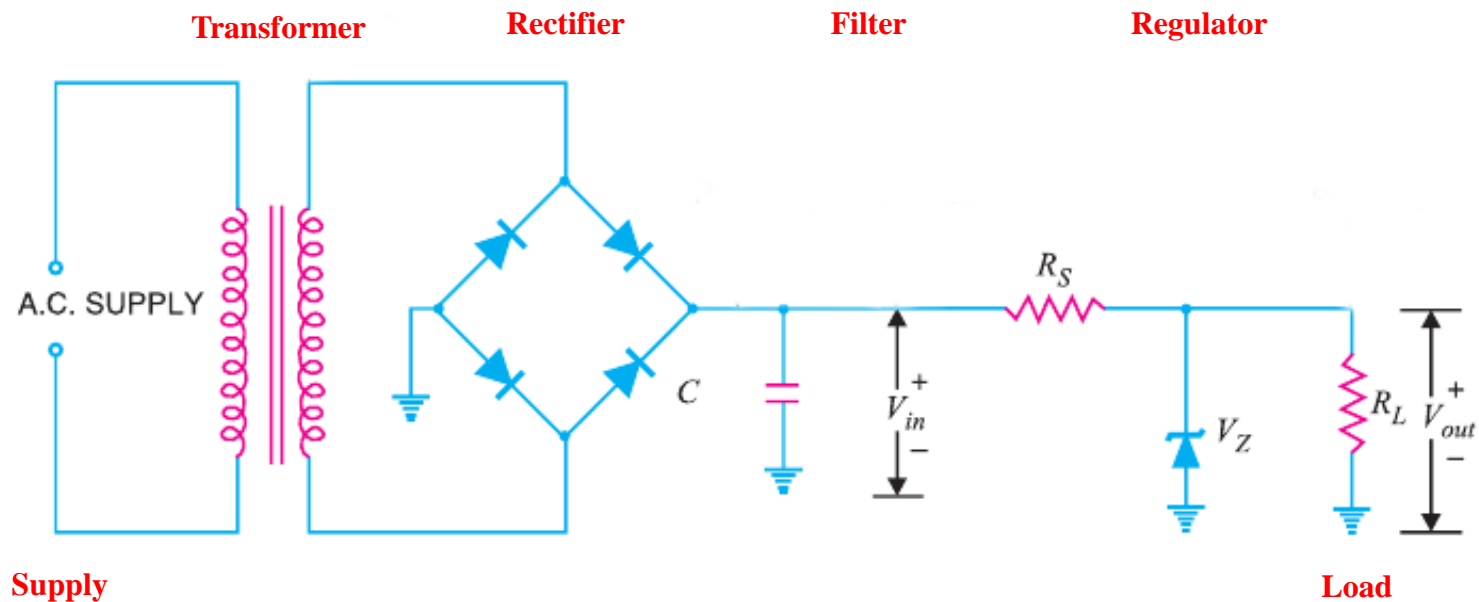
Circuit Diagram of a Simple Regulated Power Supply



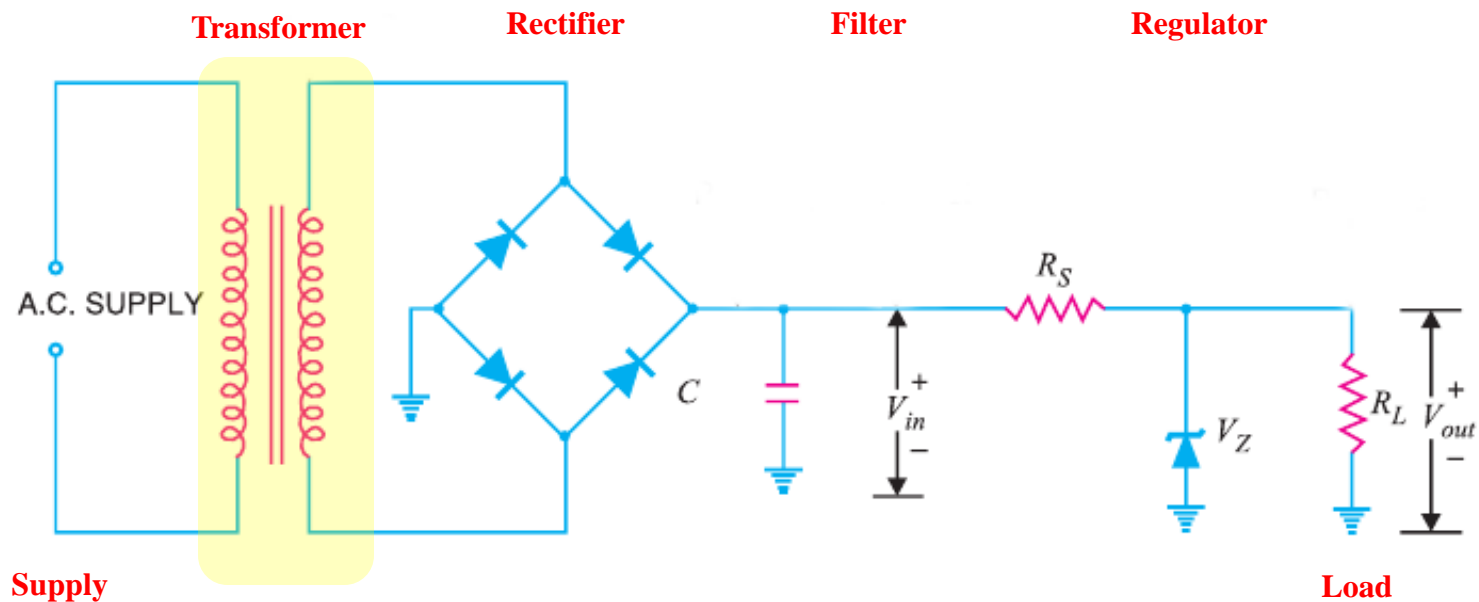
Circuit Diagram of a Simple Regulated Power Supply



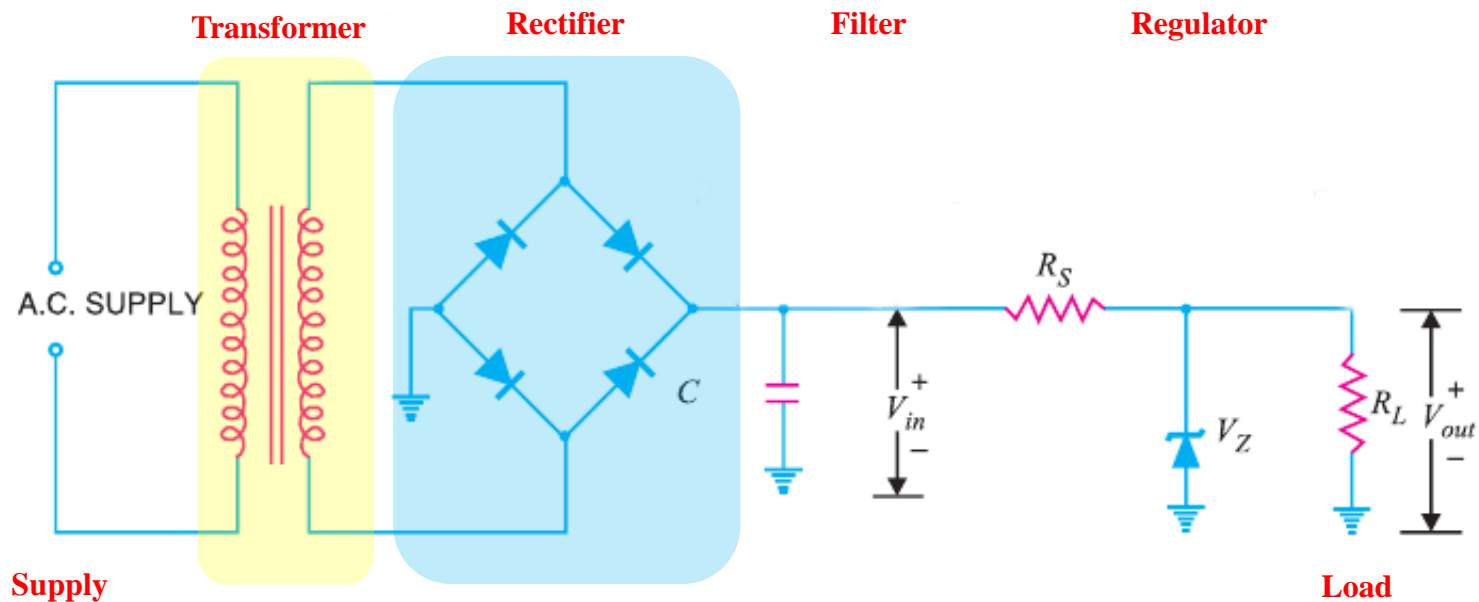
Circuit Diagram of a Simple Regulated Power Supply



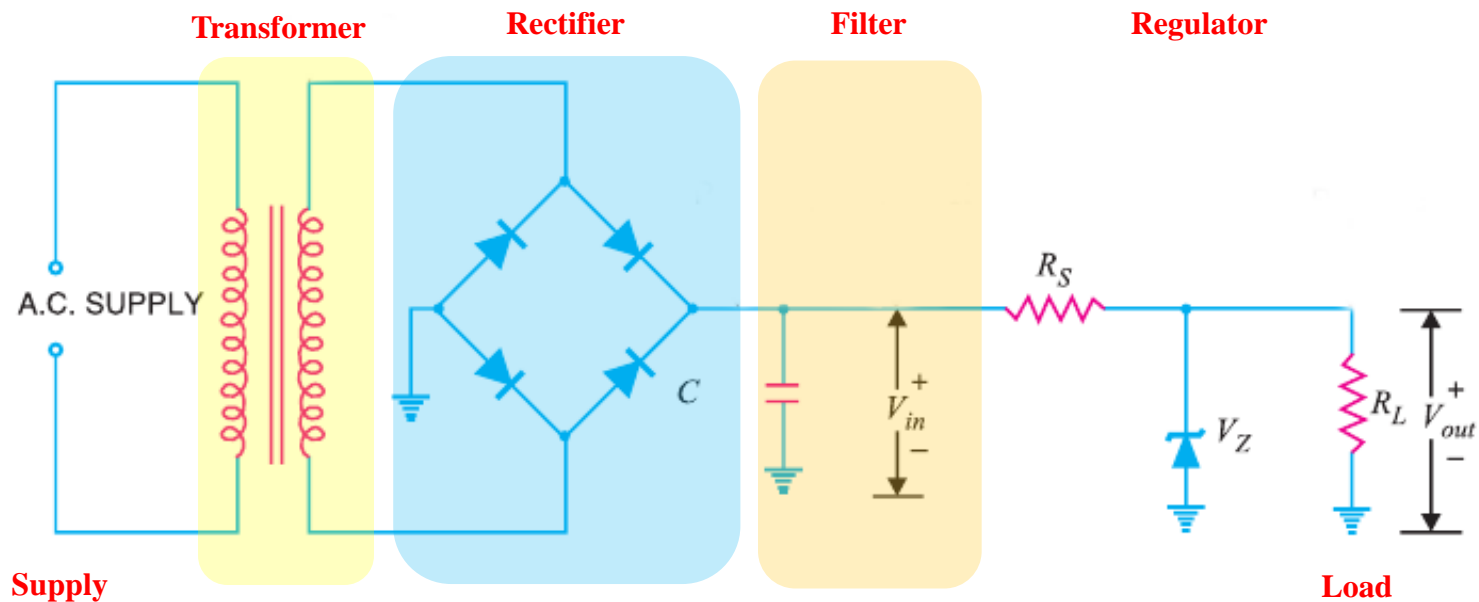
Circuit Diagram of a Simple Regulated Power Supply



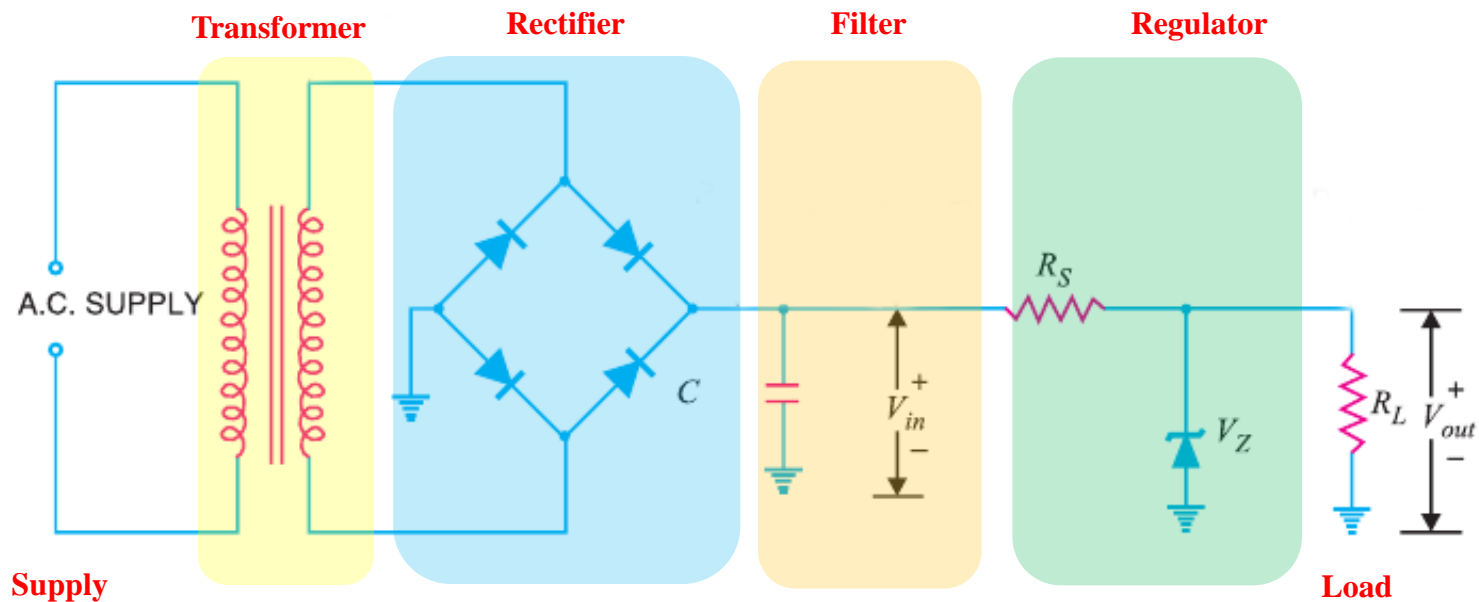
Circuit Diagram of a Simple Regulated Power Supply




Output Waveform after each Stage

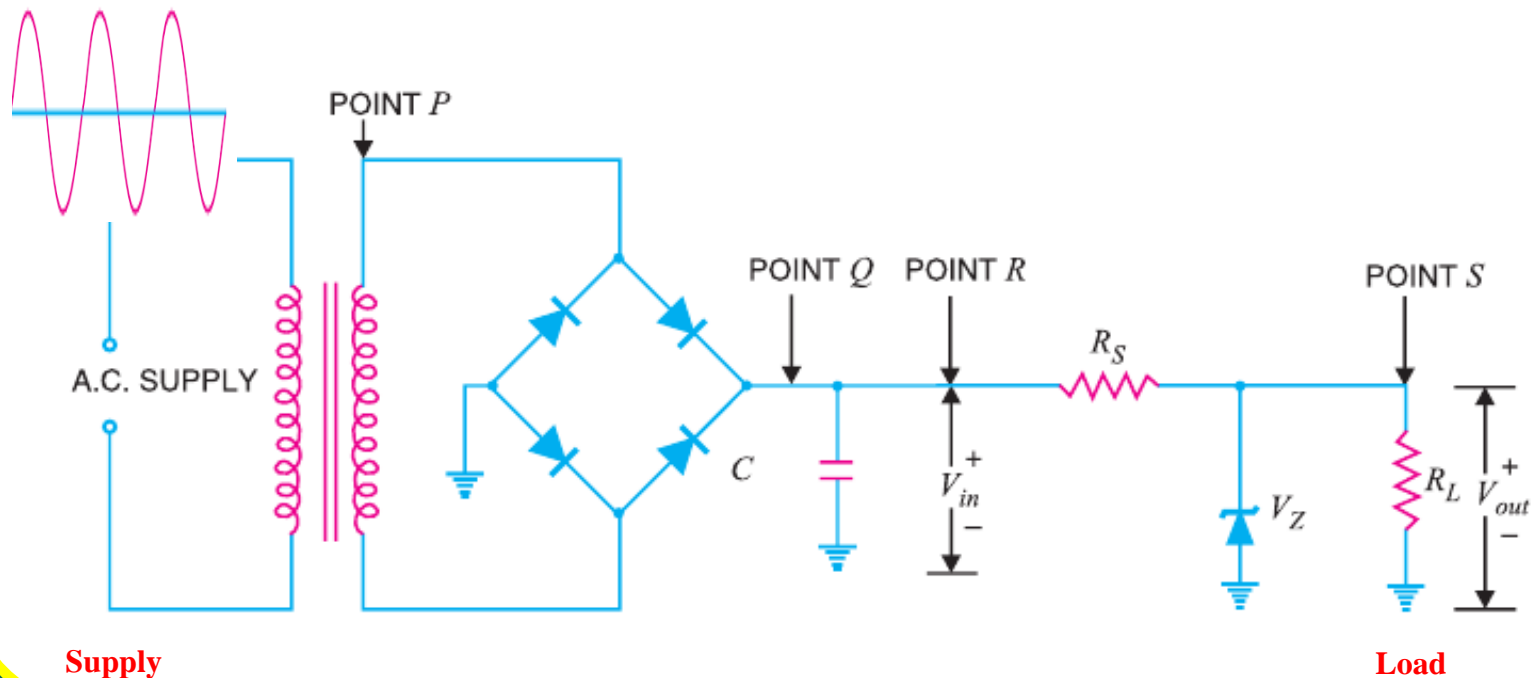


Output Waveform after each Stage

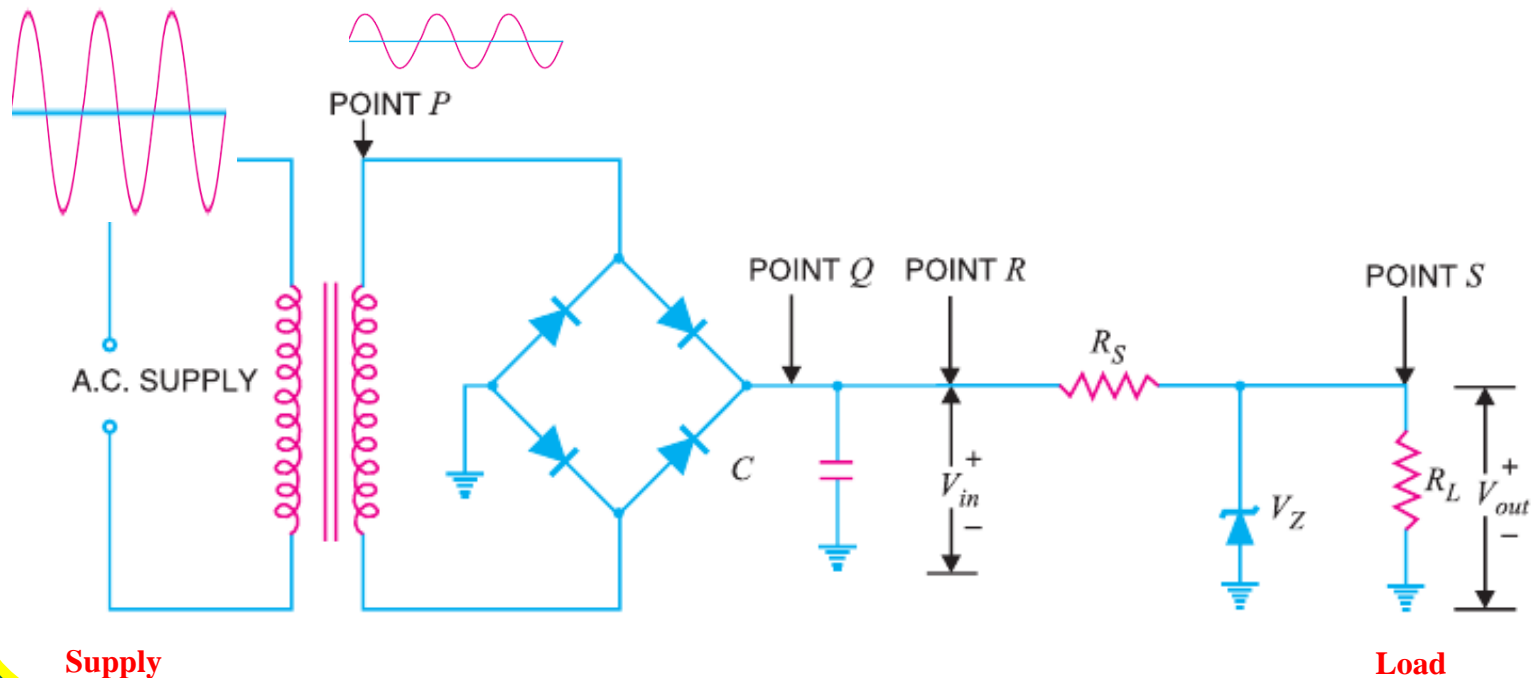


Output Waveform after each Stage

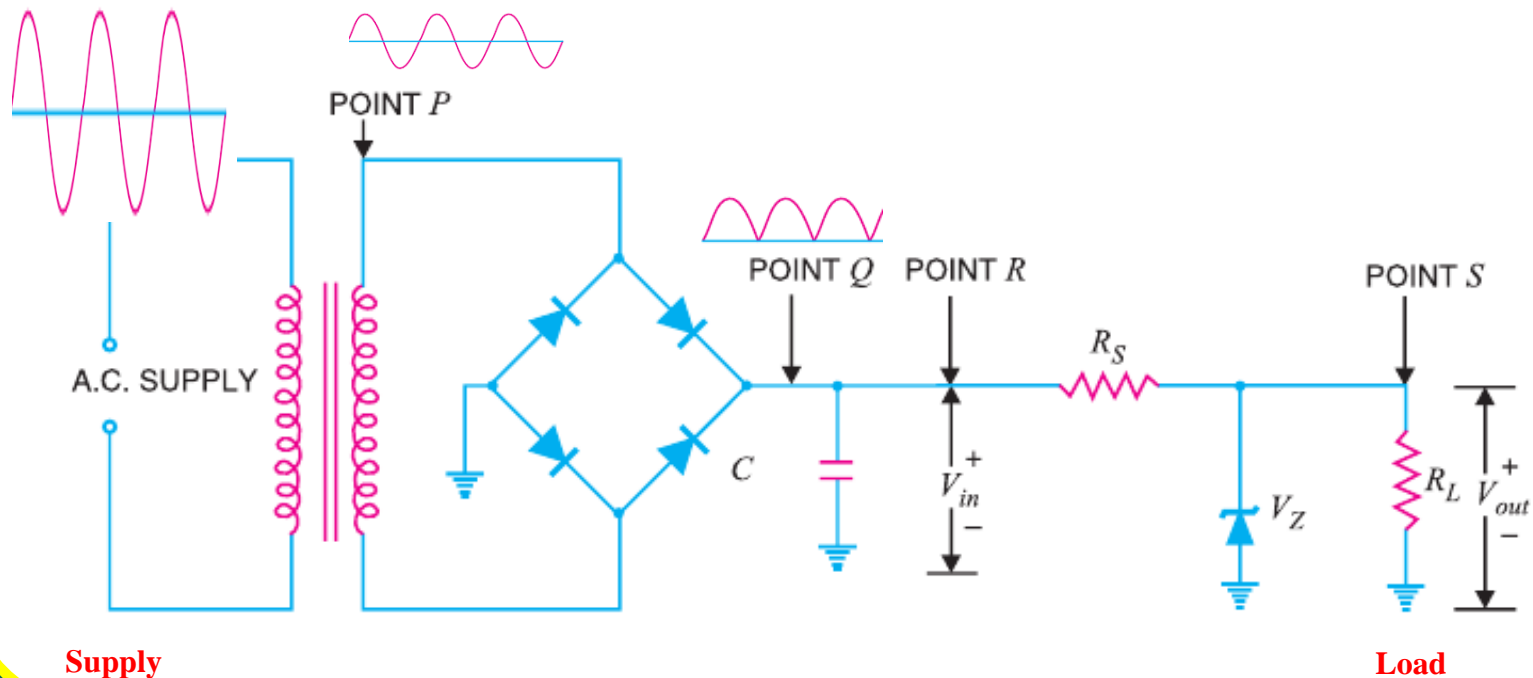

Output Waveform after each Stage

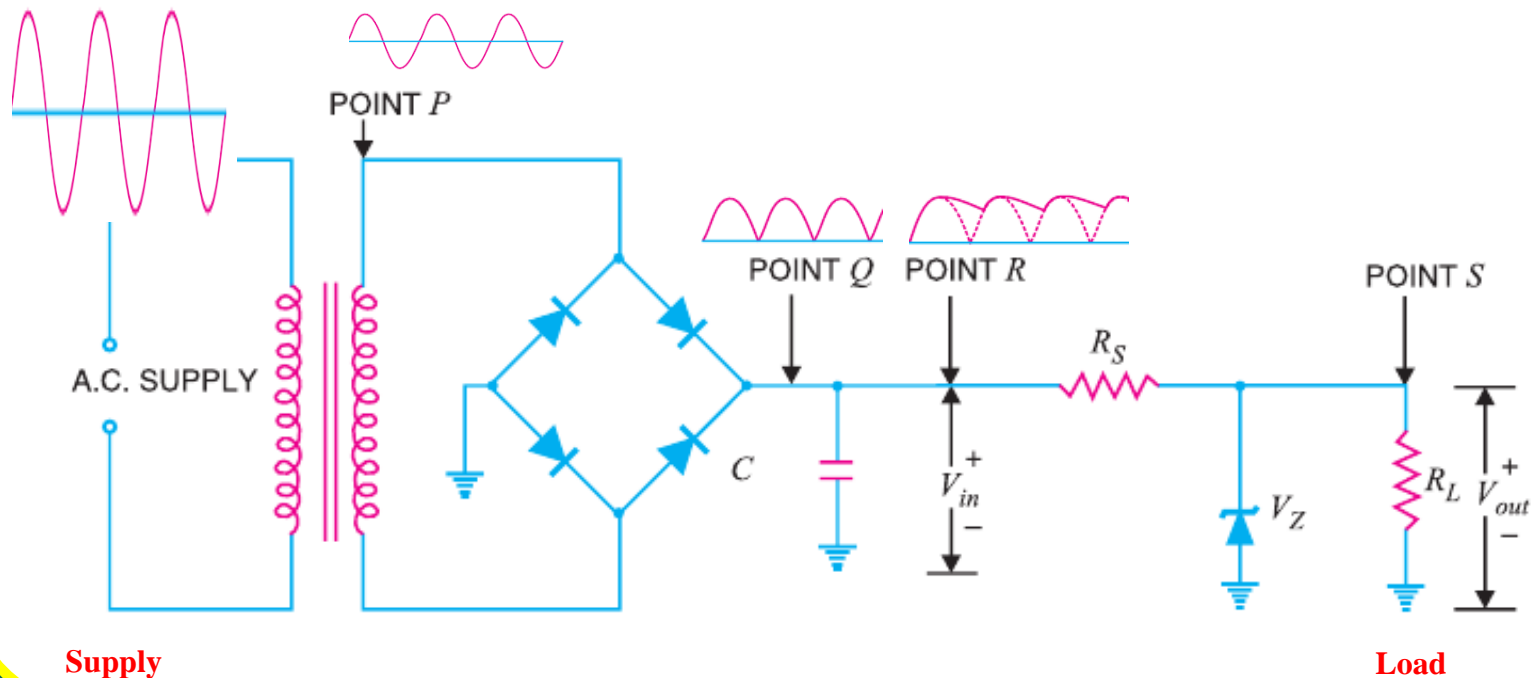

Output Waveform after each Stage

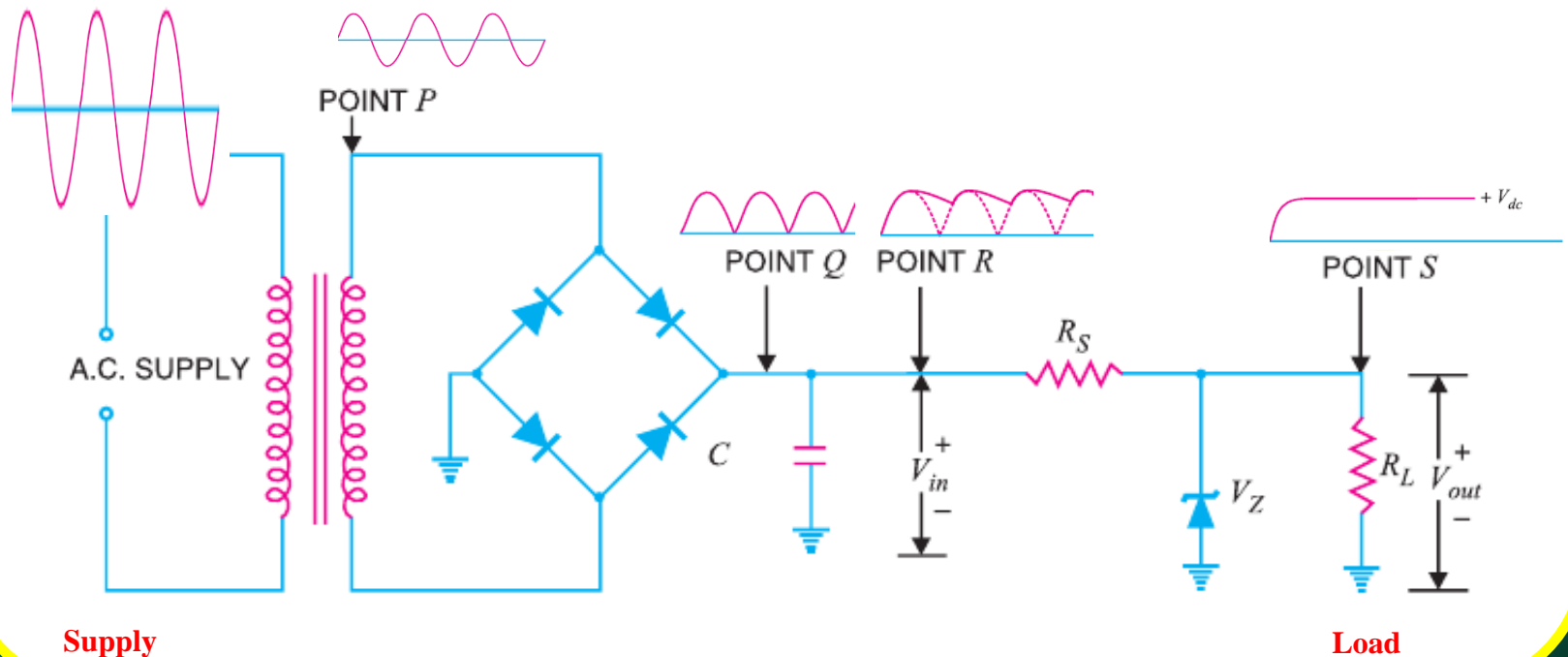

Quality of a Power Supply

Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

Quality of a Power Supply

❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

- ❑ **Load Regulation:** Is the capability to maintain a constant voltage (or current) level on the output channel of a power supply despite changes in the load.

Quality of a Power Supply

- ❑ **Ripple Factor:** The ratio of rms value of AC to DC component of a signal.

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}}$$

- ❑ **Load Regulation:** Is the capability to maintain a constant voltage (or current) level on the output channel of a power supply despite changes in the load.

$$\% LR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

Transformers

Transformers

- **Transformer is an AC device which can step up or step down AC voltages.**

Transformers

- ❑ Transformer is an AC device which can step up or step down AC voltages.
- ❑ Secondly transformer isolates the rectifier circuit from power line and thus reduces the risk of electric shock.

Transformers

- ❑ Transformer is an AC device which can step up or step down AC voltages.
- ❑ Secondly transformer isolates the rectifier circuit from power line and thus reduces the risk of electric shock.




Without Centre Tap




With Centre Tap

Transformer

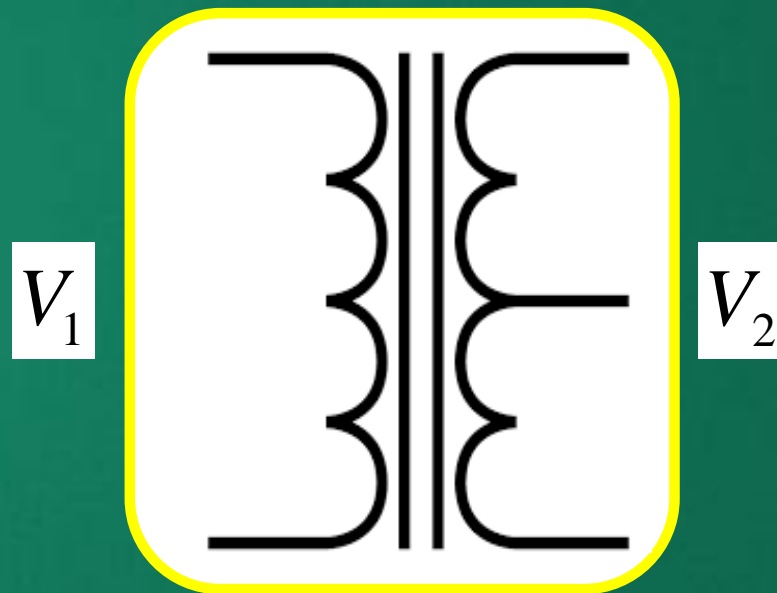

Transformer

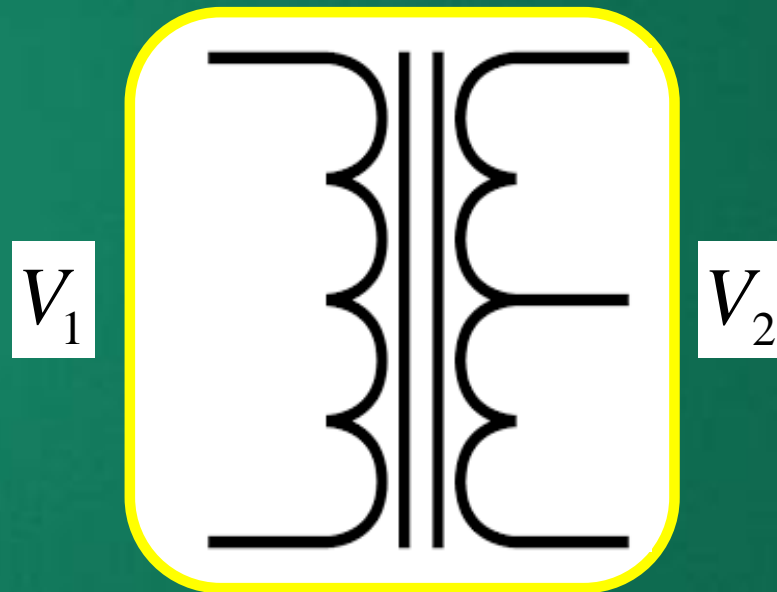

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

Rectifiers

Rectifiers

- The rectifier converts the AC sinusoidal signal into a pulsating DC wave.

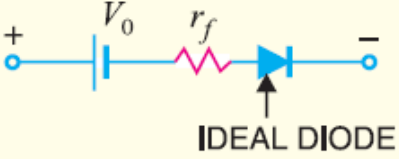
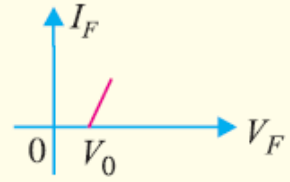
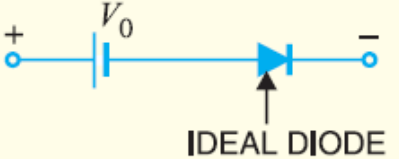
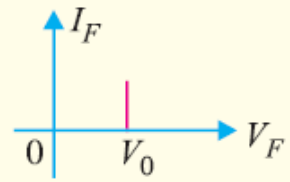

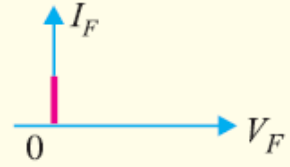
Rectifiers

- ❑ The rectifier converts the AC sinusoidal signal into a pulsating DC wave.
- ❑ There are several forms of rectifiers use but all of them use diodes.


Rectifiers

- ❑ The rectifier converts the AC sinusoidal signal into a pulsating DC wave.
- ❑ There are several forms of rectifiers use but all of them use diodes.
- ❑ Can be classified into two types
 - Half wave rectifiers
 - Full wave rectifiers


Diode Equivalent Circuits

S.No.	Type	Model	Characteristic
1.	Approximate model		
2.	Simplified model		
3.	Ideal Model		


Half Wave Rectifier

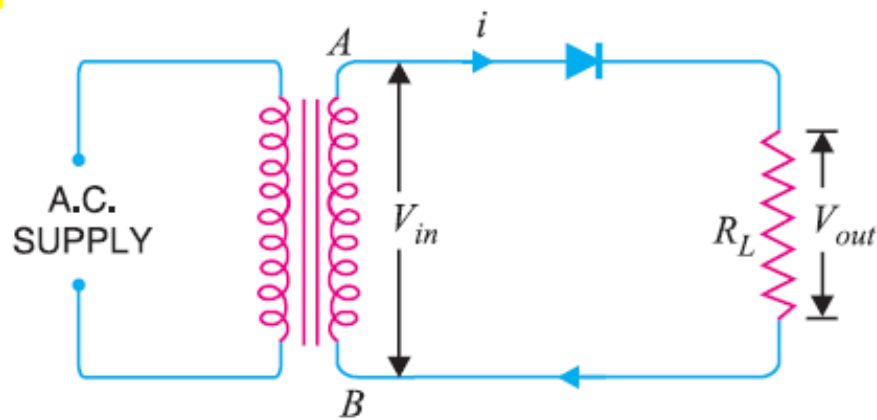




Half Wave Rectifier

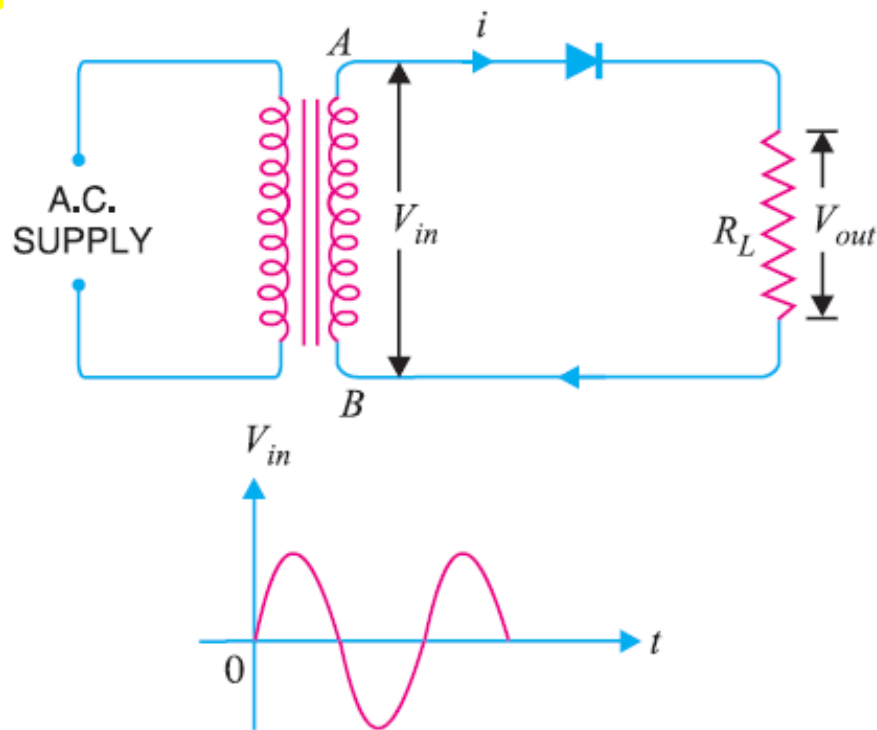

Half Wave Rectifier

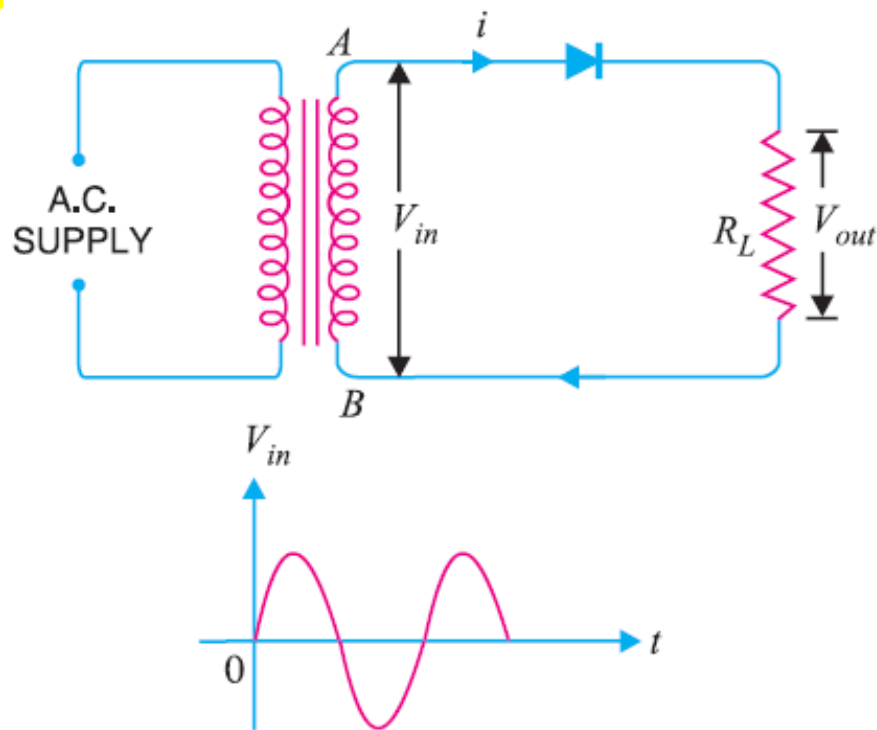

Half Wave Rectifier

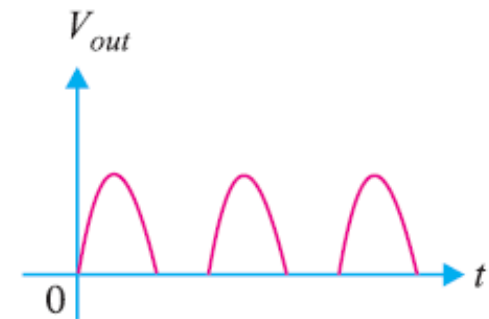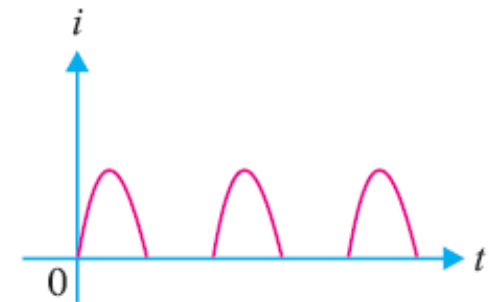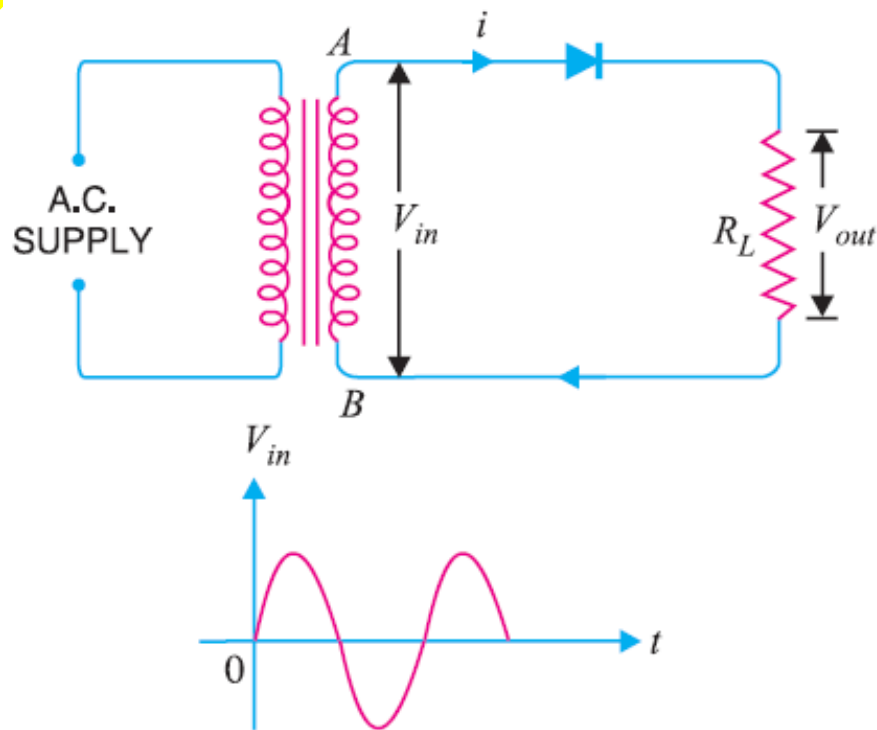

Half Wave Rectifier

Half Wave Rectifier

□ Ripple Factor

Half Wave Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

Half Wave Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

□ The ripple content is high, so an elaborate filter is required to produce steady current.

Half Wave Rectifier

□ Ripple Factor


$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2} \sqrt{\pi^2 - 4} = 1.21$$

- The ripple content is high, so an elaborate filter is required to produce steady current.
- It delivers power only half the time, therefore output is low.

Full Wave Rectifiers

□ Full Wave Rectifiers



- Centre-Tap Full Wave Rectifier

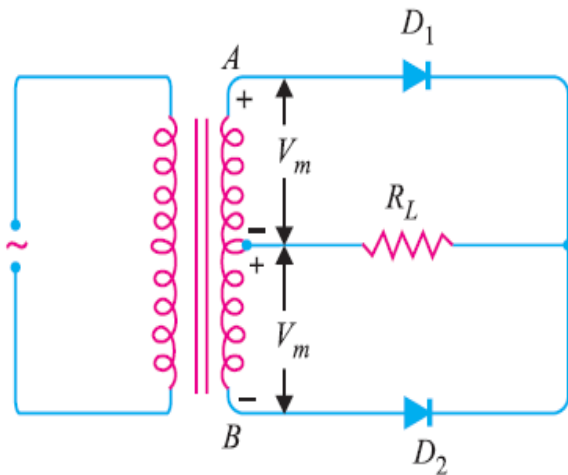


Full Wave Rectifiers

□ Full Wave Rectifiers

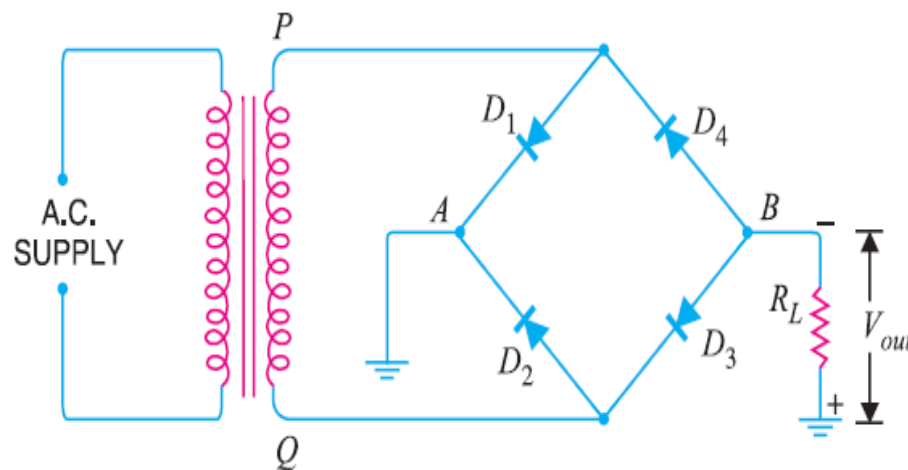
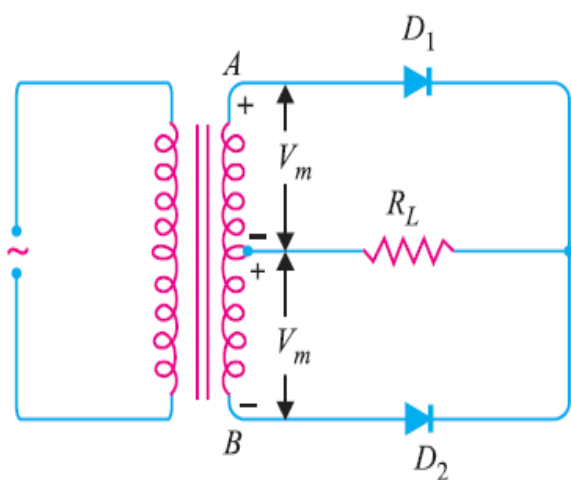
- Centre-Tap Full Wave Rectifier
- Full Wave Bridge Rectifier



Centre-Tap Full Wave Rectifier

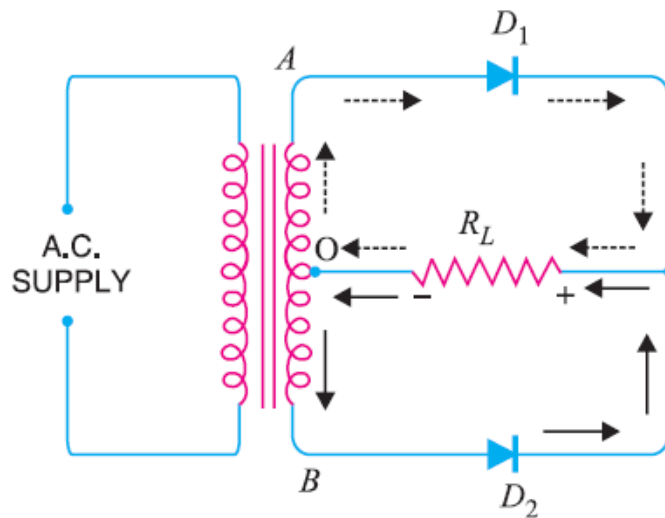

Centre-Tap Full Wave Rectifier

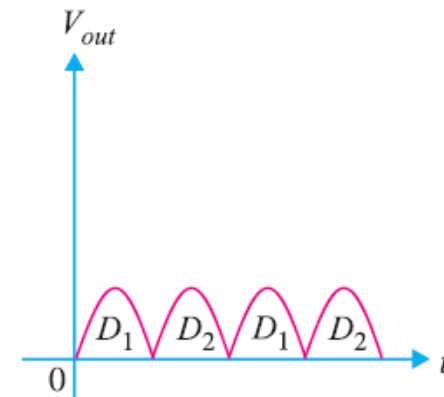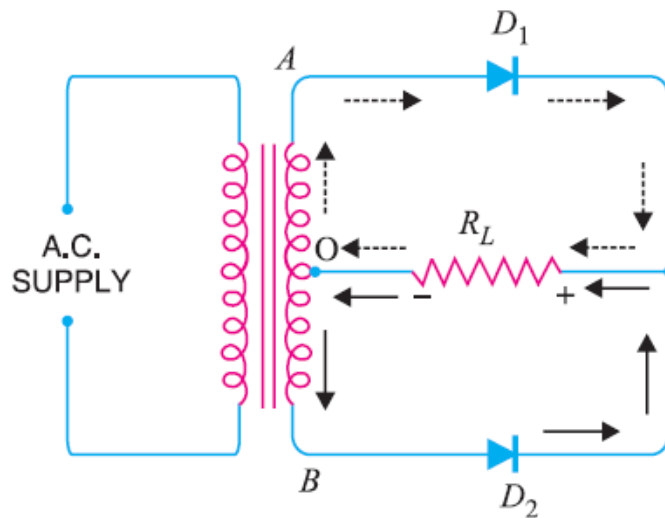

Centre-Tap Full Wave Rectifier

Centre-Tap Full Wave Rectifier

□ **Ripple Factor**

Centre-Tap Full Wave Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

Centre-Tap Full Wave Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Transformer with centre-tap is needed.

Centre-Tap Full Wave Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Transformer with centre-tap is needed.

□ The diodes must have high PIV ($2V_m$).

Centre-Tap Full Wave Rectifier

❑ Ripple Factor


$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

❑ Transformer with centre-tap is needed.

❑ The diodes must have high PIV ($2V_m$).

❑ The DC output is small because each diode utilizes only one half of the transformer's secondary voltage

Full Wave Bridge Rectifier

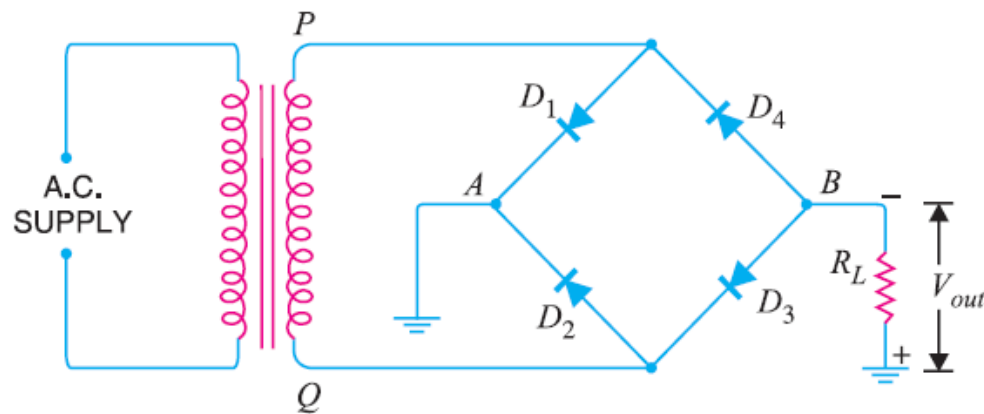

Full Wave Bridge Rectifier

Full Wave Bridge Rectifier

□ Ripple Factor

Full Wave Bridge Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

Full Wave Bridge Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Need for centre tapped transformer is eliminated

Full Wave Bridge Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

□ Need for centre tapped transformer is eliminated

□ The output is twice that of centre tap circuit for same secondary voltage.

Full Wave Bridge Rectifier

□ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

- Need for centre tapped transformer is eliminated
- The output is twice that of centre tap circuit for same secondary voltage.
- The PIV is half that of centre tap circuit (for same DC output).

Full Wave Bridge Rectifier

❑ Ripple Factor

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{\sqrt{\pi^2 - 8}}{2\sqrt{2}} = 0.48$$

- ❑ Need for centre tapped transformer is eliminated
- ❑ The output is twice that of centre tap circuit for same secondary voltage.
- ❑ The PIV is half that of centre tap circuit (for same DC output).
- ❑ It requires 4 diodes.

Filters

Filters

- ❑ The rectifier produces a pulsating DC with high ripple content.

Filters



- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to remove pulsations and create almost a smooth DC output across the load.

Filters


- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to remove pulsations and create almost a smooth DC output across the load.
- ❑ The most common filter is a large capacitor

Filters

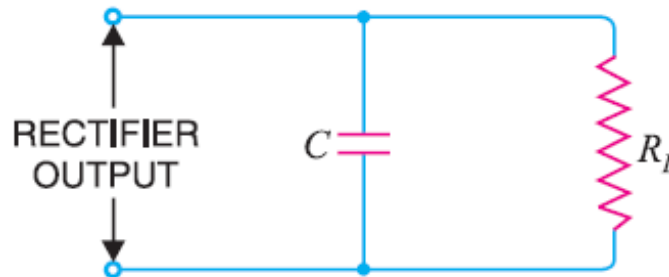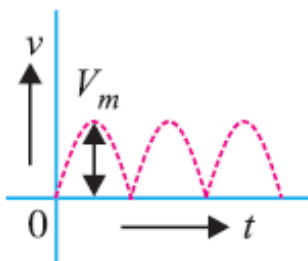
- ❑ The rectifier produces a pulsating DC with high ripple content.
- ❑ There filter is used to remove pulsations and create almost a smooth DC output across the load.
- ❑ The most common filter is a large capacitor



Capacitor Filter

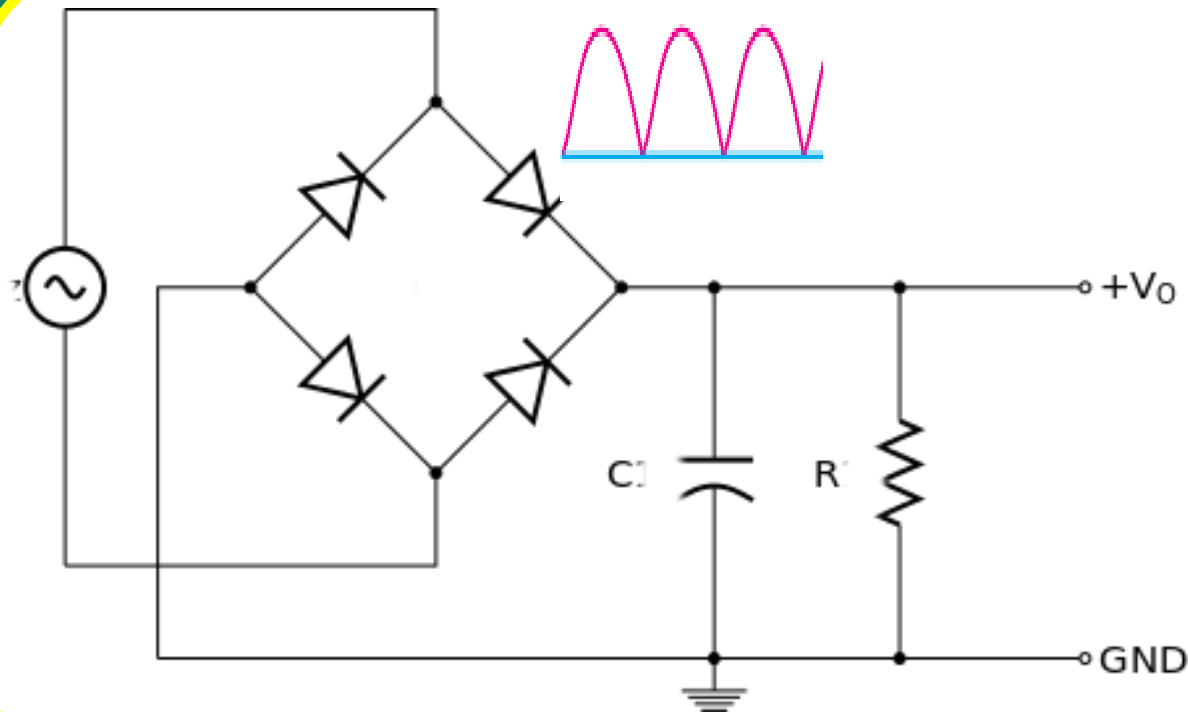

Capacitor Filter

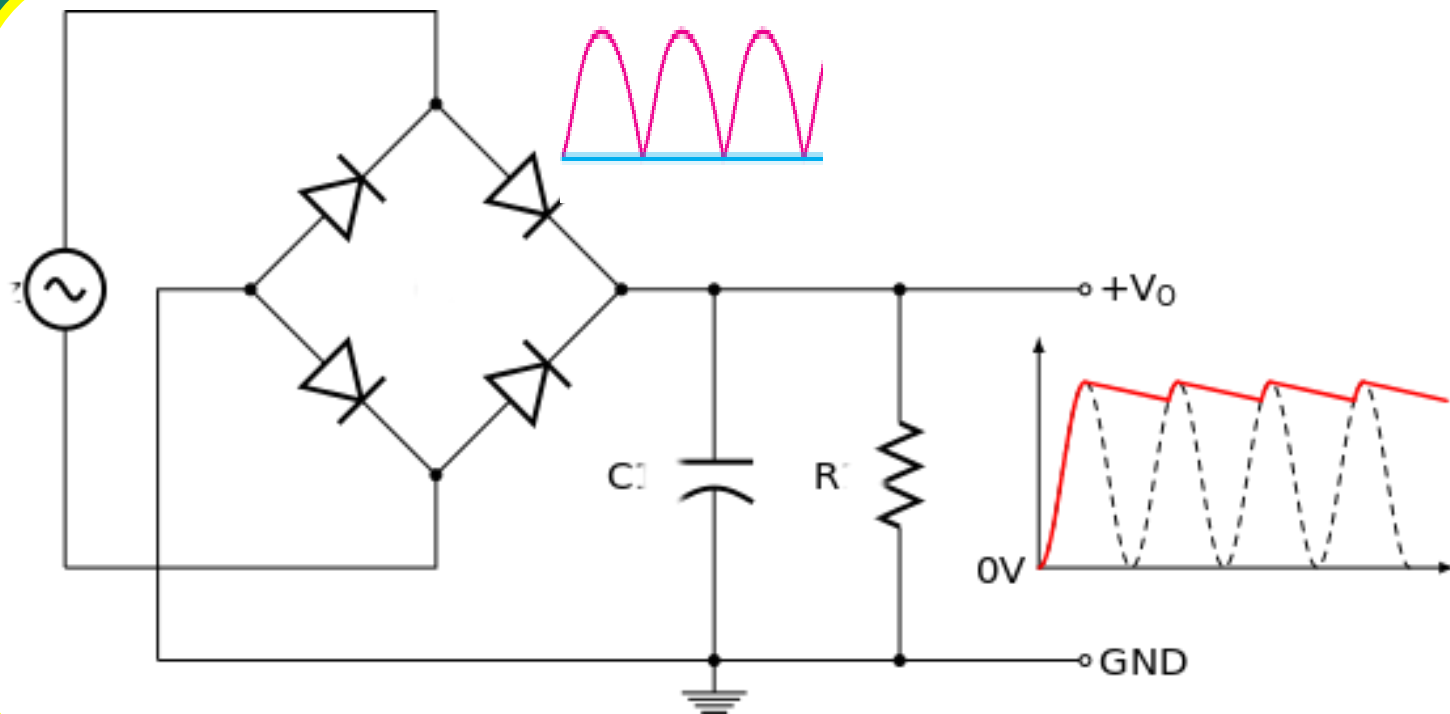

Capacitor Filter

□ Ripple Factor (Full Wave Rectifier)

Capacitor Filter

□ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3}fRC}$$

Capacitor Filter

□ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3}fRC}$$

□ Larger the value of capacitor, lesser will be the ripple.

Capacitor Filter

❑ Ripple Factor (Full Wave Rectifier)

$$\gamma = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \frac{1}{2\sqrt{3}fRC}$$

❑ Larger the value of capacitor, lesser will be the ripple.

❑ If the load is connected across the filter, the power supply is termed as unregulated power supply.