

Basic Electronic Circuits (IEC-103)

Lecture-19

Multistage Amplifiers

Multistage Amplifiers

- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance

Multistage Amplifiers


- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance
- ❑ **Solution** – transistor amplifier circuits can be connected in series or cascaded amplifiers

Multistage Amplifiers

- ❑ Many applications cannot be handled with single-transistor amplifiers in order to meet the specification of a given amplification factor, input resistance and output resistance
- ❑ **Solution** – transistor amplifier circuits can be connected in series or cascaded amplifiers
- ❑ This can be done either to increase the overall small-signal voltage gain or provide an overall voltage gain greater than 1 with a very low output resistance


Multistage Amp Configuration

Cascade/RC coupling

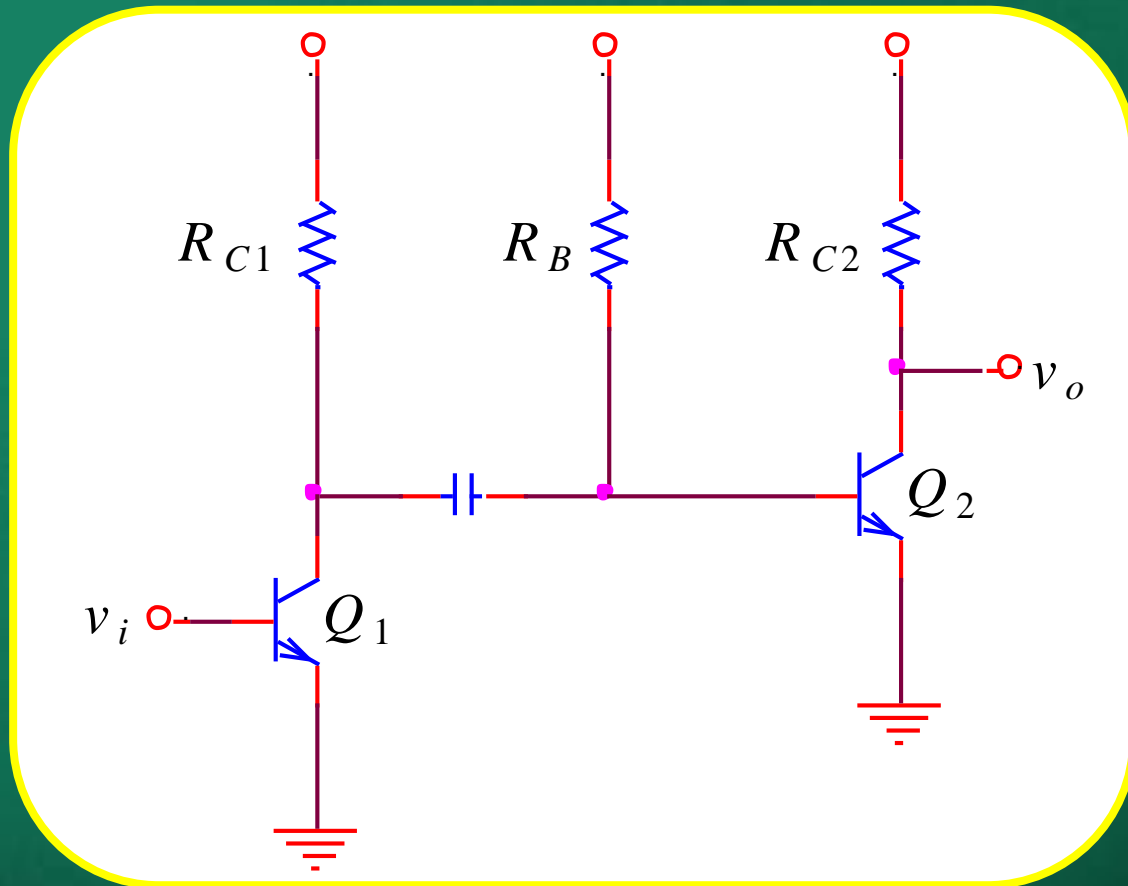


Multistage Amp Configuration

Cascode

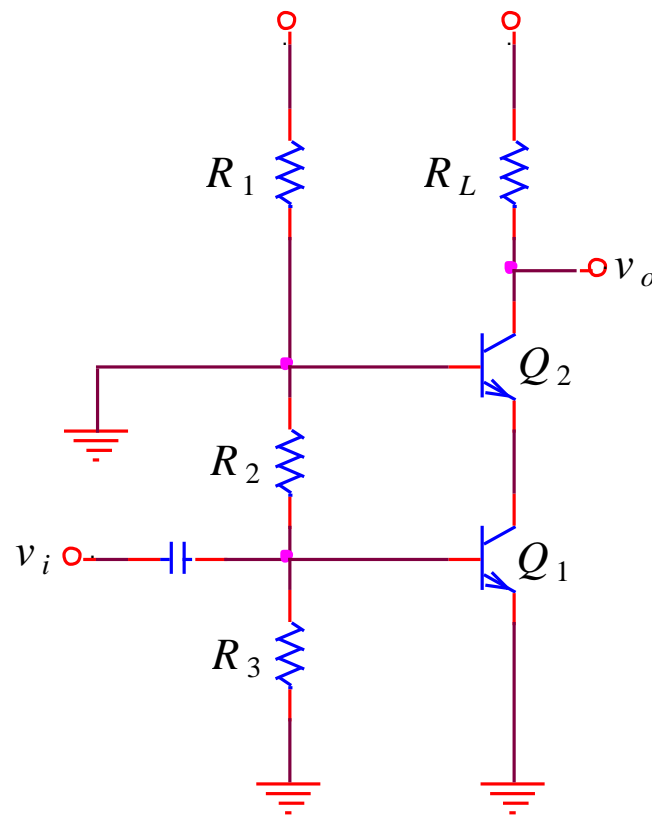


Multistage Amp Configuration

Darlington/Direct coupling

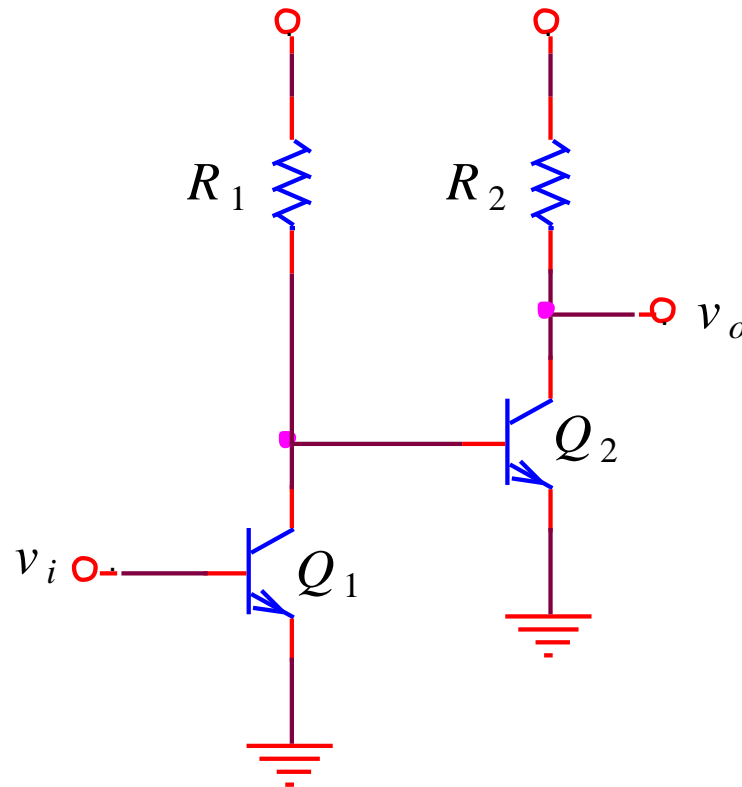

Multistage Amp Configuration

Transformer coupling

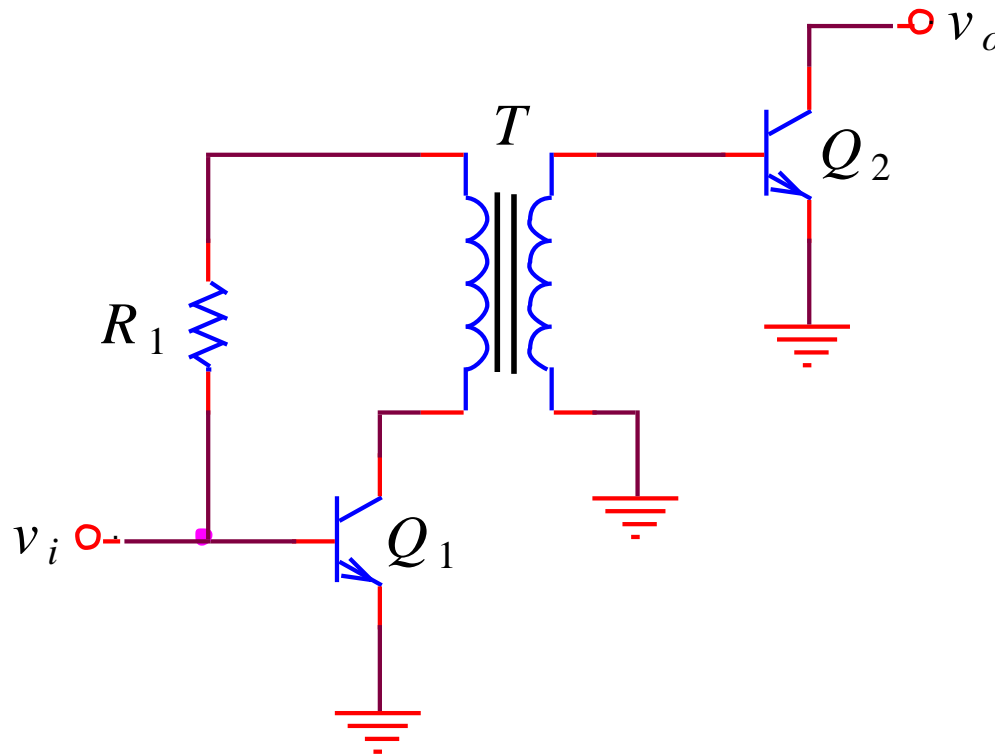

Cascade Connection

Cascade Connection

- ❑ **The most widely used configuration.**

Cascade Connection

- ❑ **The most widely used configuration.**
- ❑ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**

Cascade Connection


- ☐ **The most widely used configuration.**
- ☐ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**
- ☐ **The signal developed across the collector resistor of each stage is coupled into the base of the next stage.**

Cascade Connection

- ☐ **The most widely used configuration.**
- ☐ **Coupling a signal from one stage to the another stage and block dc voltage from one stage to the another stage.**
- ☐ **The signal developed across the collector resistor of each stage is coupled into the base of the next stage.**
- ☐ **The overall gain = product of the individual gain.**

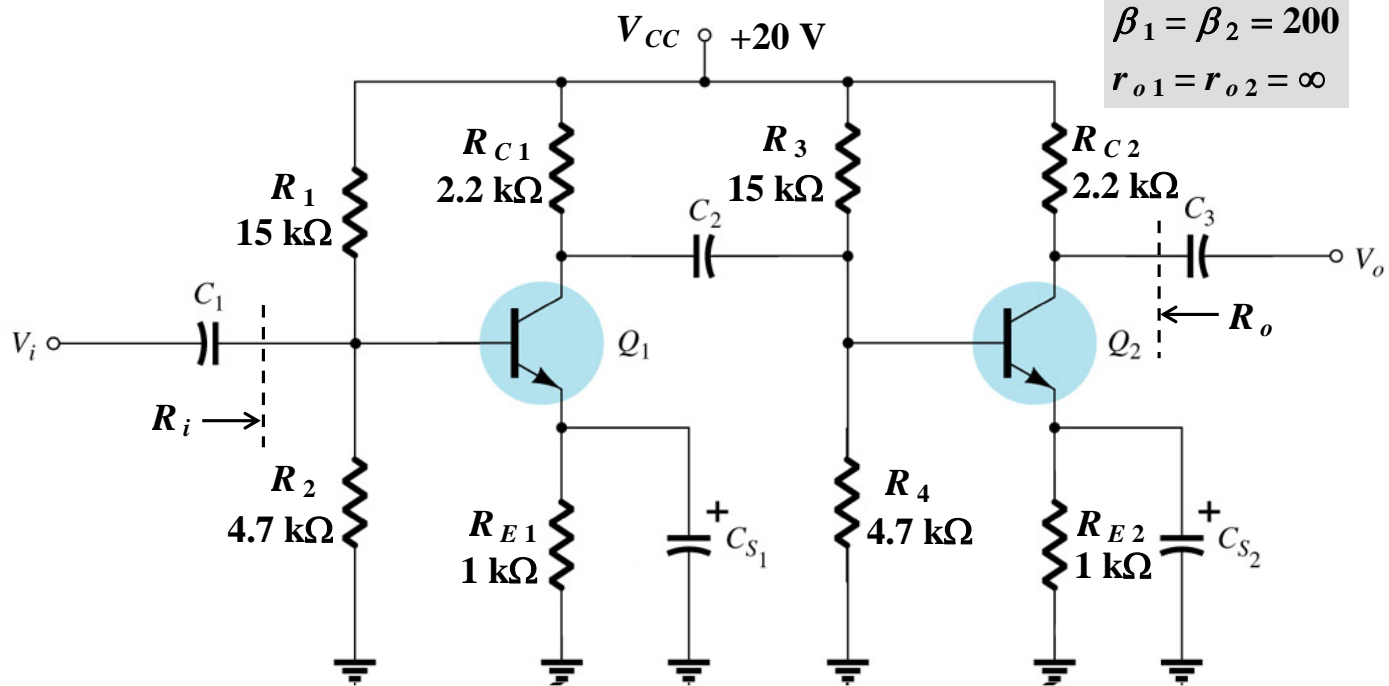
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



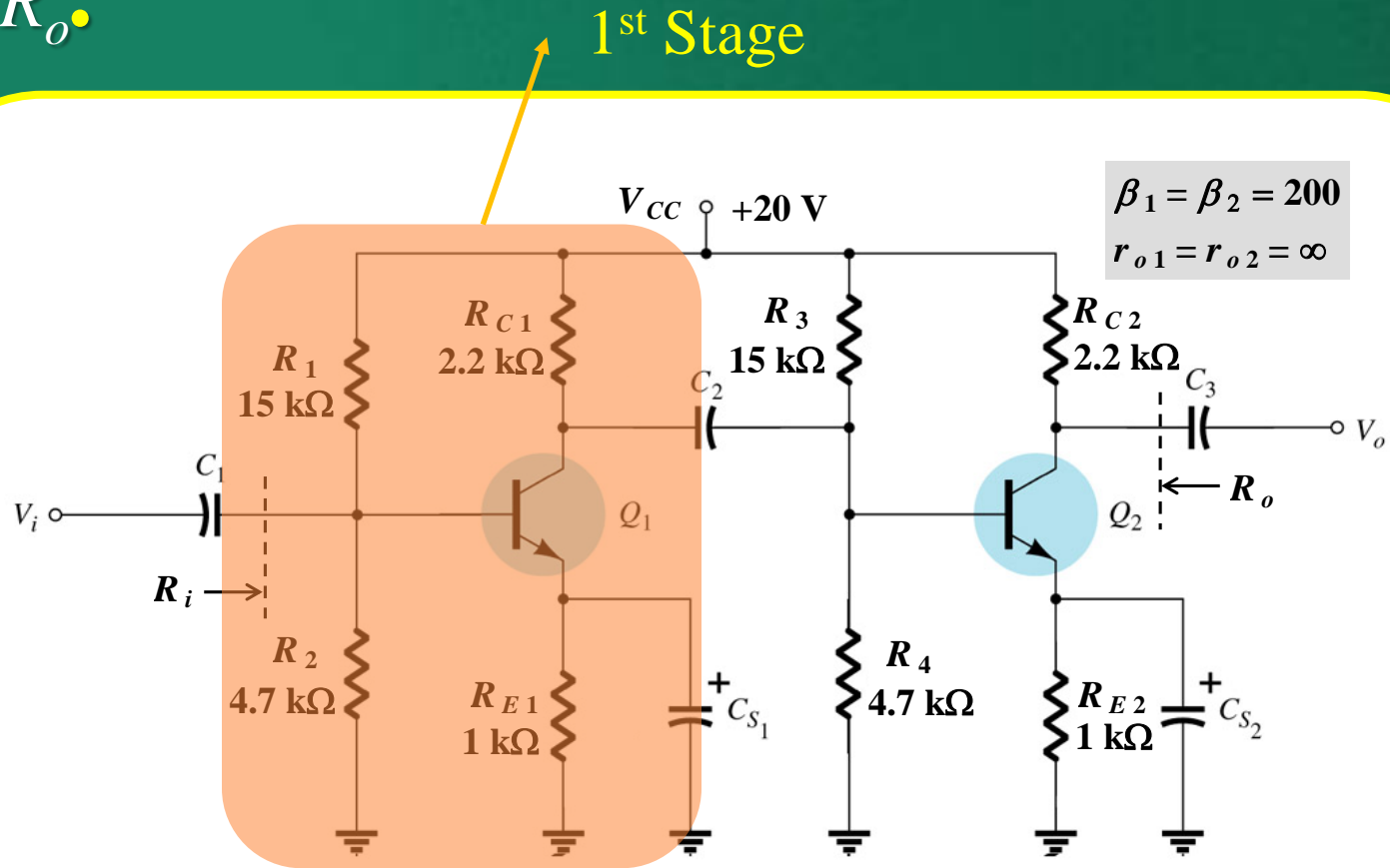
Example

Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



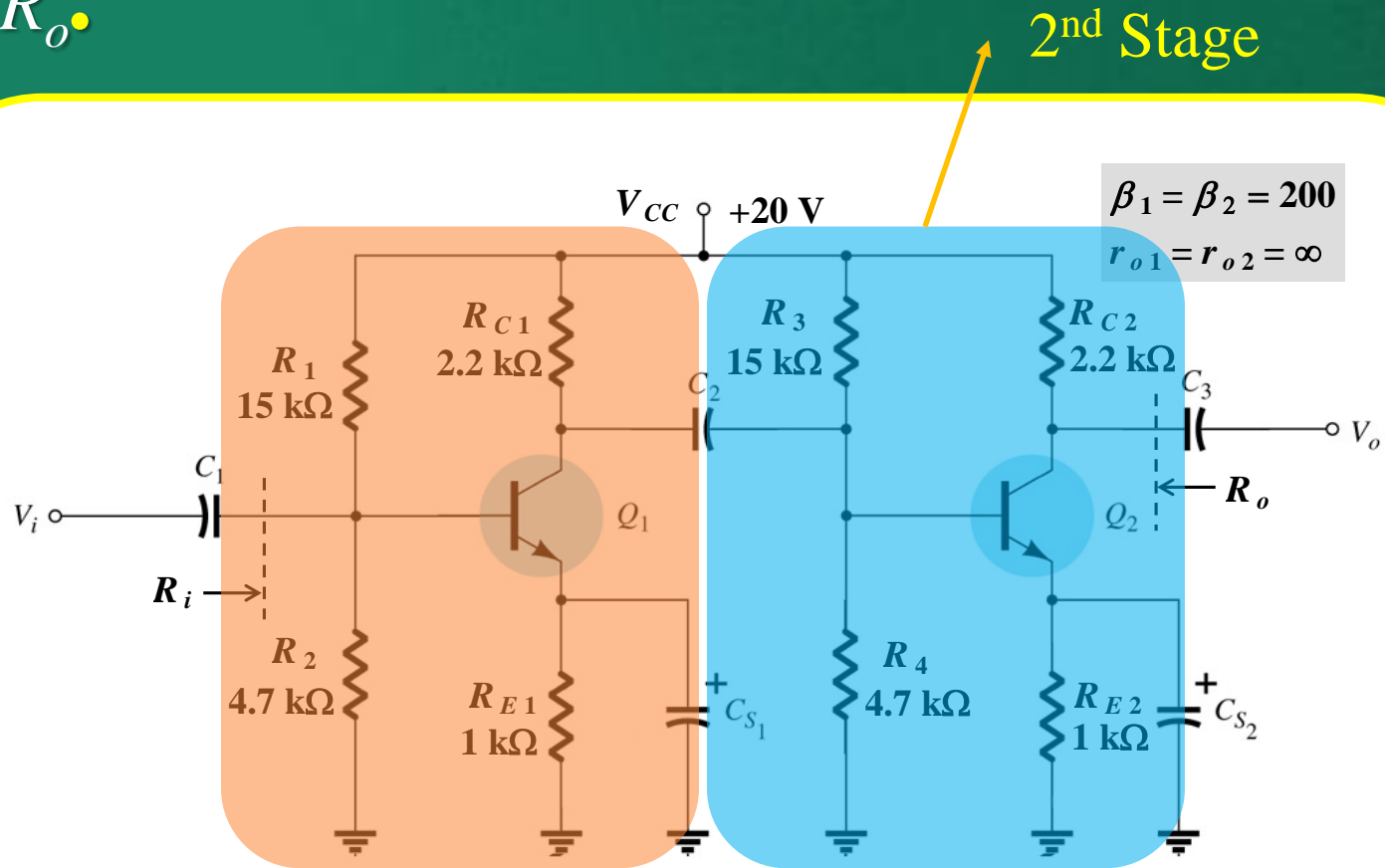Example


Draw the AC equivalent circuit and calculate A_v , R_i , and R_o .



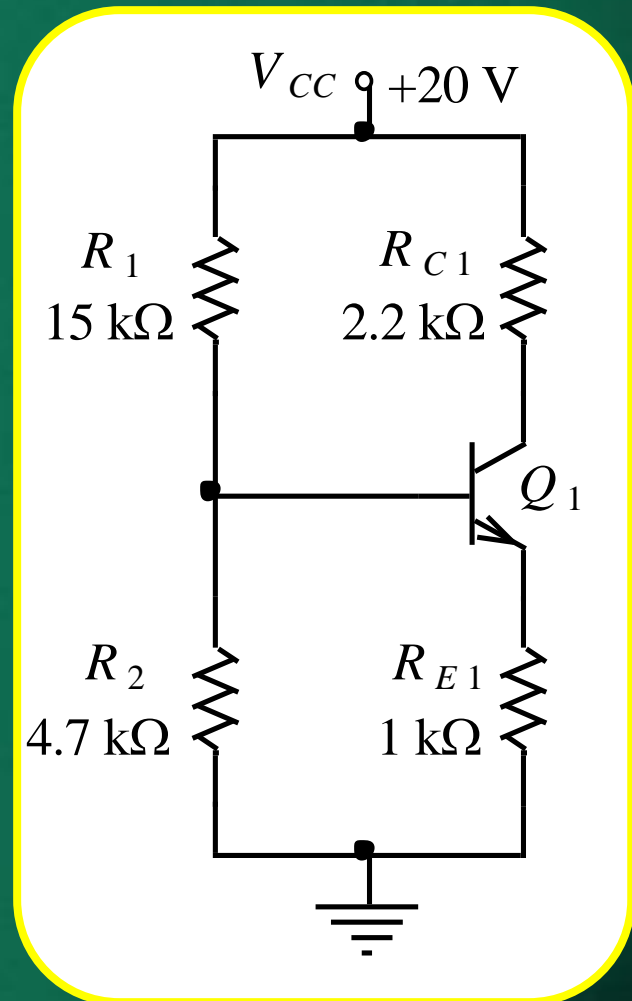Example (continued)


DC analysis

The circuit under DC condition (stage 1 and 2 are identical)



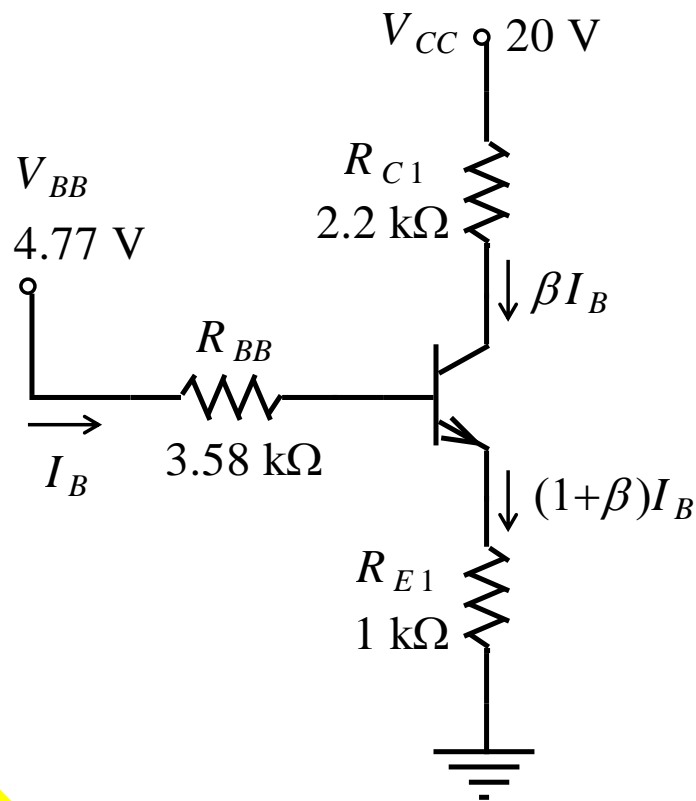Example (continued)

Applying Thévenin's theorem, the circuit becomes



$$I_{BQ1} = I_{BQ2} = 19.89\text{ }\mu\text{A}$$

$$I_{CQ1} = I_{CQ2} = 3.979\text{ mA}$$


$$r_{\pi1} = r_{\pi2} = 1.307\text{ k}\Omega$$

$$g_{m1} = g_{m2} = 0.153\text{ A/V}$$

Example (continued)

AC analysis


The small-signal equivalent circuit

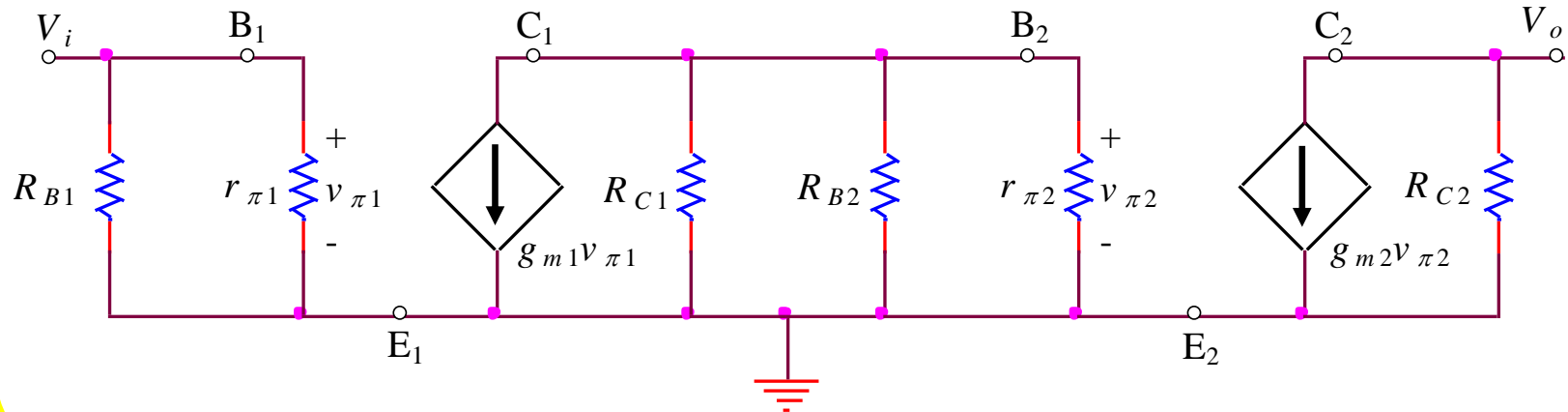

Example (continued)

AC analysis

The small-signal equivalent circuit

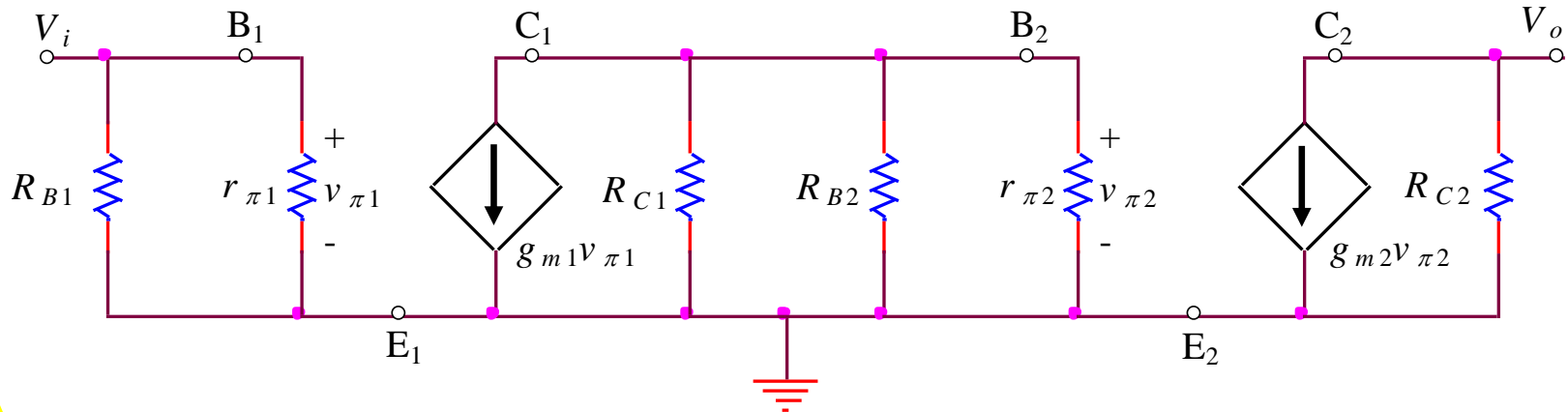

$$R_{B1} = R_1 // R_2$$

$$R_{B2} = R_3 // R_4$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

Example (continued)

$$V_o = -g_{m2}v_{\pi2}R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi2}} = -g_{m2}R_{C2}$$

$$v_{\pi2} = -g_{m1}v_{\pi1}(R_{C1} // R_{B2} // r_{\pi2})$$

Example (continued)

$$V_o = -g_{m2} v_{\pi 2} R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi 2}} = -g_{m2} R_{C2}$$

$$v_{\pi 2} = -g_{m1} v_{\pi 1} (R_{C1} // R_{B2} // r_{\pi 2})$$

$$= -g_{m1} V_i (R_{C1} // R_{B2} // r_{\pi 2})$$

$$[v_{\pi 1} = V_i]$$

Example (continued)

$$V_o = -g_{m2} v_{\pi 2} R_{C2}$$

$$A_2 = \frac{V_o}{v_{\pi 2}} = -g_{m2} R_{C2}$$

$$v_{\pi 2} = -g_{m1} v_{\pi 1} (R_{C1} // R_{B2} // r_{\pi 2})$$

$$= -g_{m1} V_i (R_{C1} // R_{B2} // r_{\pi 2})$$

$$[v_{\pi 1} = V_i]$$

$$A_1 = \frac{v_{\pi 2}}{V_i} = -g_{m2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Example (continued)

The small-signal voltage gain

$$A = A_1 A_2 = g_{m1} g_{m2} R_{C2} (R_{C1} // R_{B2} // r_{\pi 2})$$

Substituting values

$$R_{B1} = R_{B2} = R_3 // R_4 = 15 // 4.7 = 3.579 \text{ k}\Omega$$

$$R_{C1} // R_{B2} // r_{\pi 2} = 2.2 // 3.579 // 1.307 = 667 \text{ }\Omega$$

$$A = 0.153 \times 0.153 \times 2200 \times 667 = 34350 \text{ V/V}$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

Example (continued)

The input resistance

$$R_{in} = R_{B1} // r_{\pi 1} = 3.579 // 1.307 = 0.957 \text{ k}\Omega$$

The output resistance

$$R_o = R_{C2} = 2.2 \text{ k}\Omega$$

Cascode Connection

Cascode Connection

- ❑ A cascode connection has one transistor on top of (in series with) another

Cascode Connection

- ❑ A cascode connection has one transistor on top of (in series with) another
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)


Cascode Connection

- ❑ A cascode connection has one transistor on top of (in series with) another
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)
- ❑ The o/p signal current of Q_1 is the i/p signal of Q_2 .

Cascode Connection


- ❑ A cascode connection has one transistor on top of (in series with) another
- ❑ The i/p applied to a C-E amplifier (Q_1) whose output is used to drive a C-B amplifier. (Q_2)
- ❑ The o/p signal current of Q_1 is the i/p signal of Q_2 .
- ❑ The advantage: provides a high i/p impedance. The C-B stage providing good high frequency operation

Cascode Amplifier

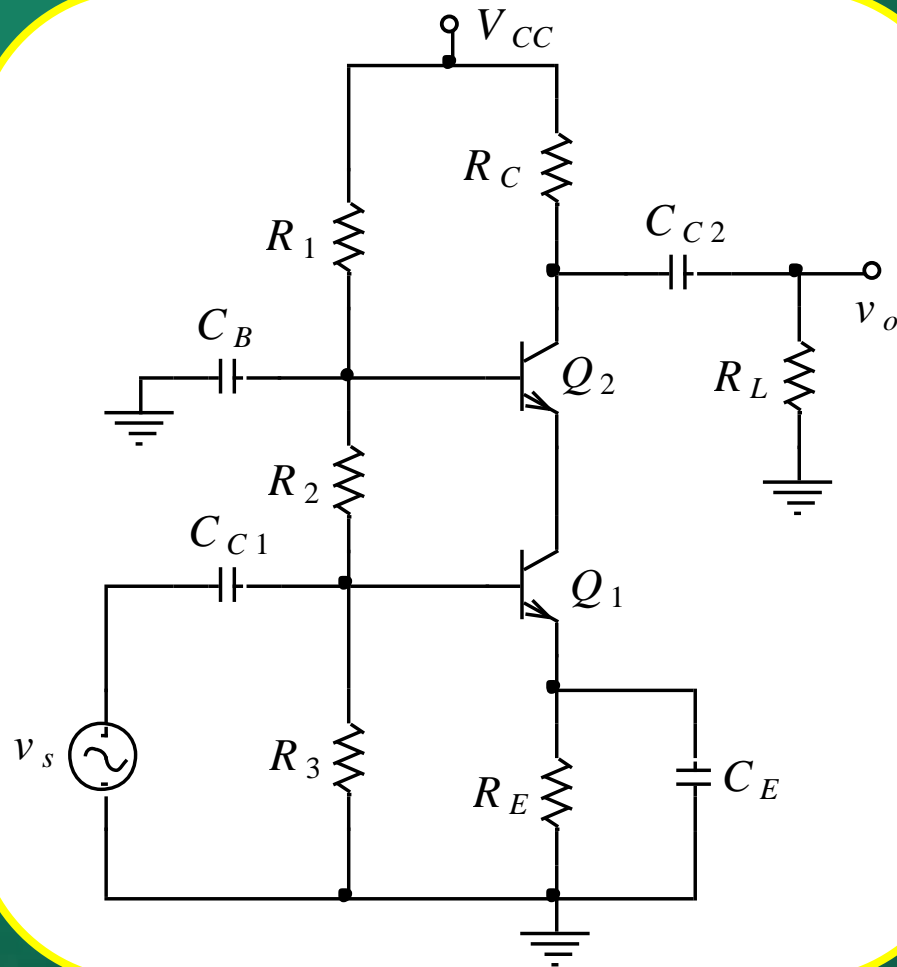

Cascode Amplifier

DC analysis

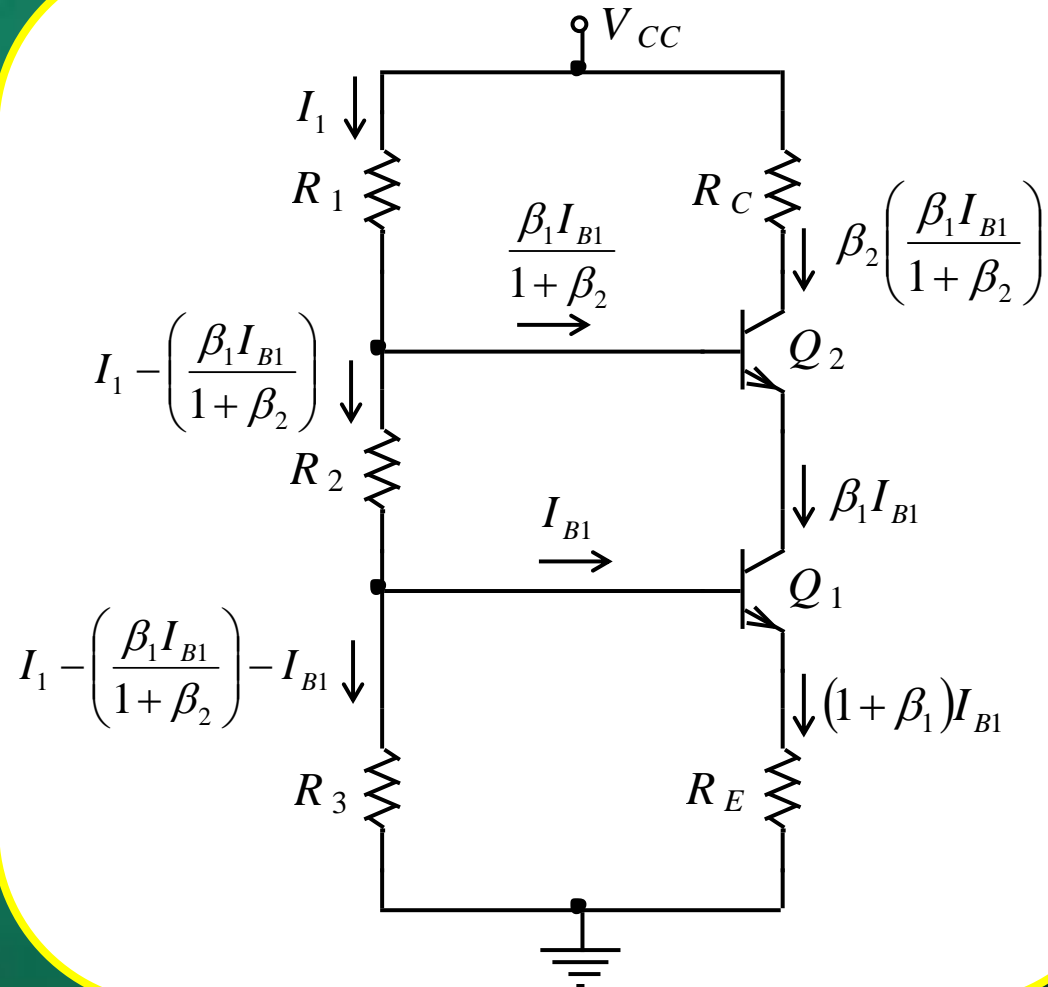

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ for both BJT's

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ **for both BJT's**

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ **for both BJT's**

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$

$$R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = 0.7 + R_E (\beta_1 + 1) I_{B1}$$

Cascode Amplifier

Assuming $V_{BE} = 0.7 \text{ V}$ for both BJT's

$$R_1 I_1 + R_2 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} \right) + R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = V_{CC}$$


$$R_3 \left(I_1 - \frac{\beta_1 I_{B1}}{\beta_2 + 1} - I_{B1} \right) = 0.7 + R_E (\beta_1 + 1) I_{B1}$$

The above equations may solved for the two unknown currents namely I_1 and I_{B1} .

Cascode Amplifier

AC analysis

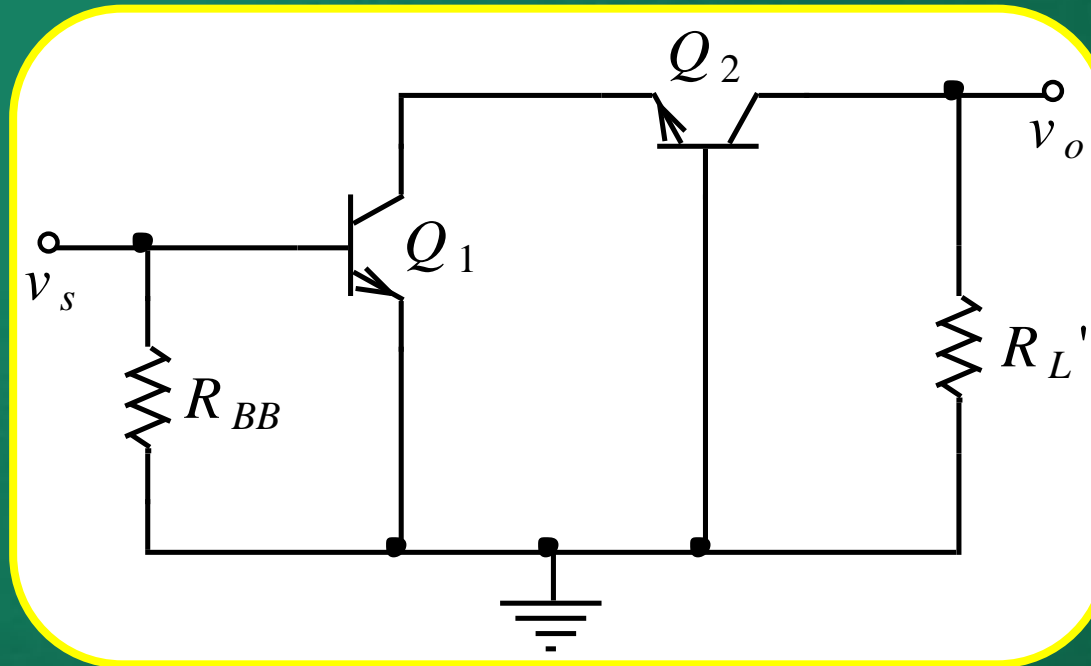
The equivalent circuit under AC condition



Cascode Amplifier

AC analysis

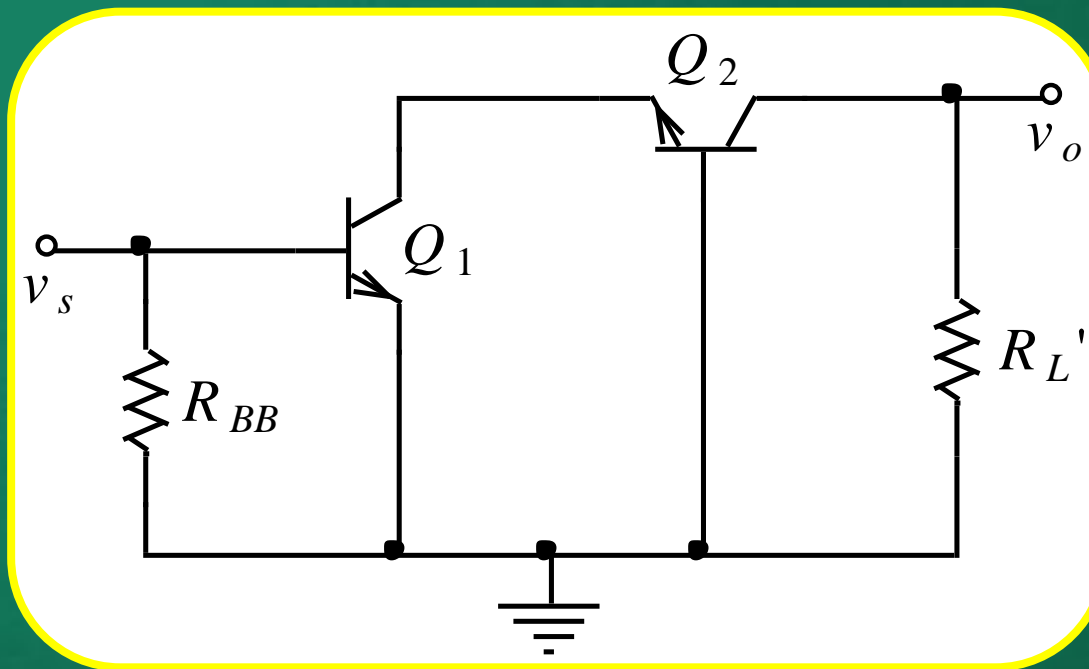The equivalent circuit under AC condition




$$R_{BB} = R_2 // R_3$$

$$R_L' = R_C // R_L$$


Cascode Amplifier

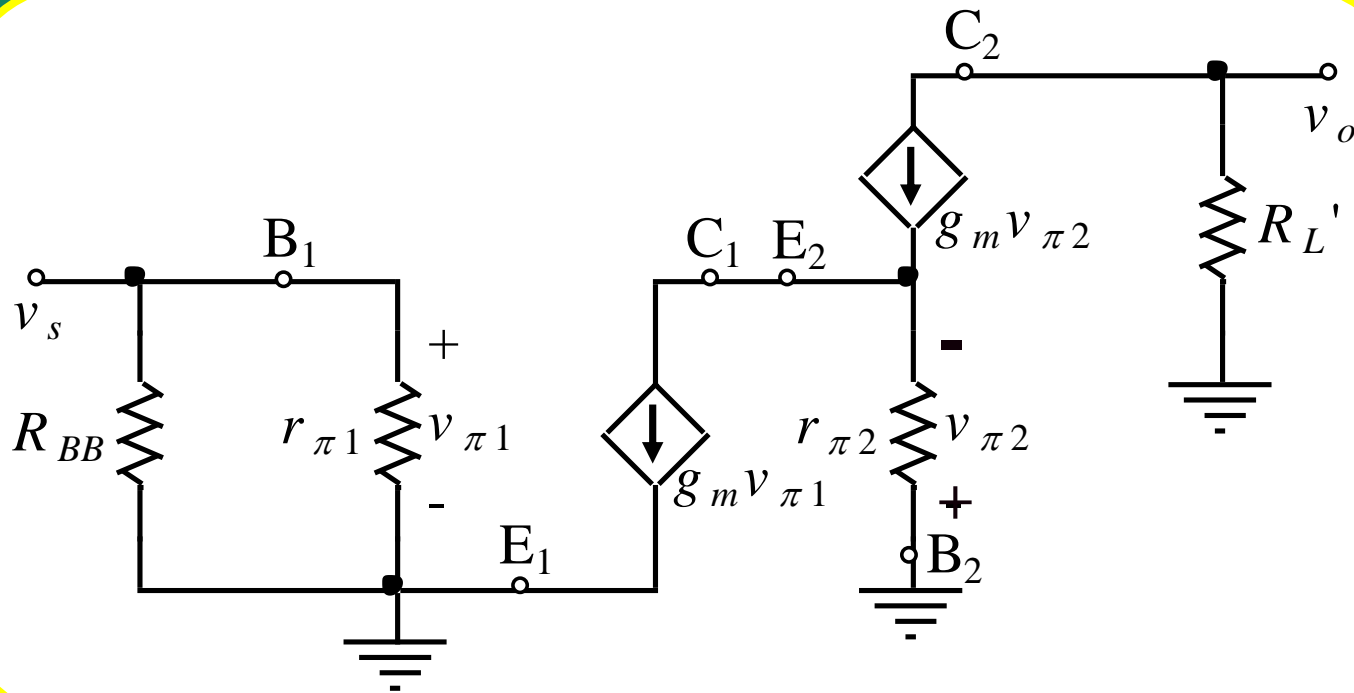The ac equivalent circuit using hybrid- π model



Cascode Amplifier

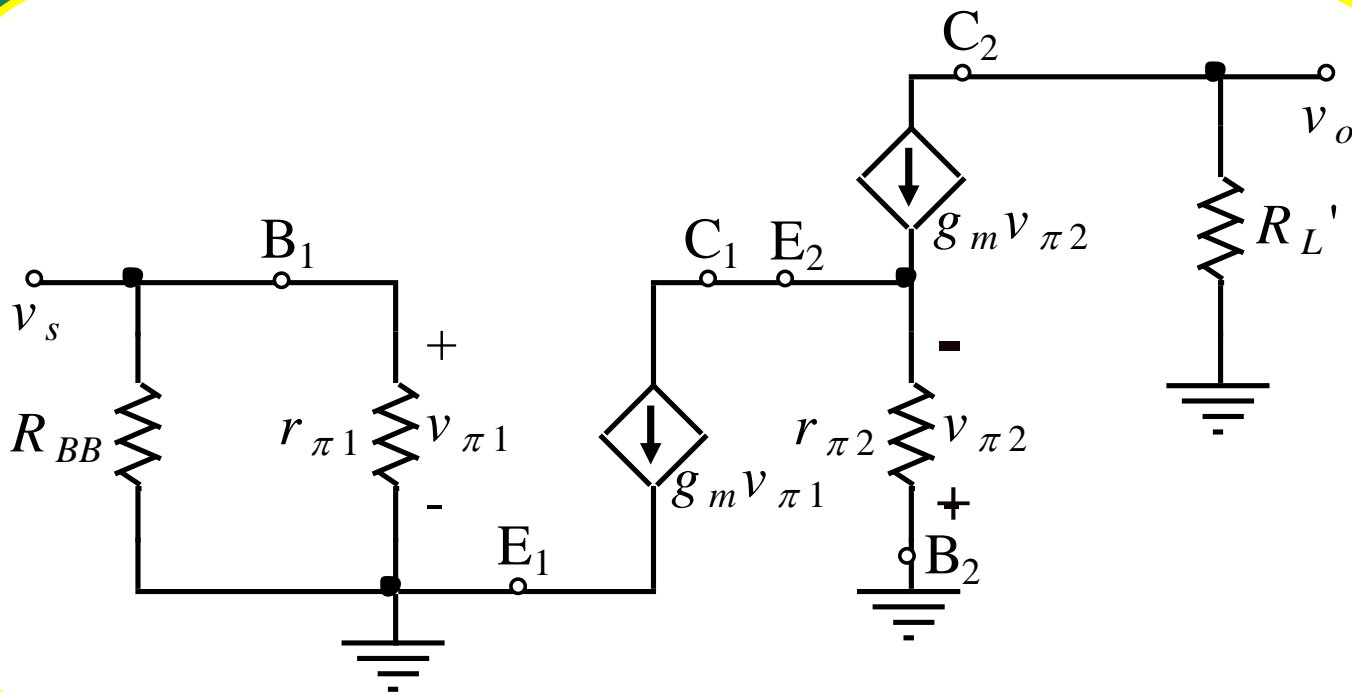The ac equivalent circuit using hybrid- π model



$$R_{BB} = R_2 // R_3$$

$$R_L' = R_C // R_L$$

Cascode Amplifier

$$v_o = -g_{m2}v_{\pi2}R_L' \quad (1)$$

Cascode Amplifier

$$v_o = -g_{m2}v_{\pi2}R_L' \quad (1)$$

At node E_2

$$g_{m1}v_{\pi1} = \frac{v_{\pi2}}{r_{\pi2}} + g_{m2}v_{\pi2}$$

Or

$$v_{\pi2} = \frac{g_{m1}r_{\pi2}v_{\pi1}}{1 + g_{m2}r_{\pi2}}$$

Cascode Amplifier

$$v_o = -g_{m2} v_{\pi 2} R_L' \quad (1)$$

At node E_2

$$g_{m1} v_{\pi 1} = \frac{v_{\pi 2}}{r_{\pi 2}} + g_{m2} v_{\pi 2}$$

Or

$$v_{\pi 2} = \frac{g_{m1} r_{\pi 2} v_{\pi 1}}{1 + g_{m2} r_{\pi 2}}$$

Substituting in (1);

$$v_o = -\left(\frac{g_{m1} g_{m2} r_{\pi 2}}{1 + g_{m2} r_{\pi 2}} \right) R_L' v_{\pi 1} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L' v_s$$

Cascode Amplifier

The small-signal voltage gain

$$A_v = \frac{v_o}{v_s} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L'$$

Cascode Amplifier

The small-signal voltage gain

$$A_v = \frac{v_o}{v_s} = -g_{m1} \left(\frac{\beta_2}{1 + \beta_2} \right) R_L'$$

When $\beta_2 \gg 1$


$$A_v \cong -g_{m1} R_L'$$

Darlington Connection

Darlington pair

Internal connection;

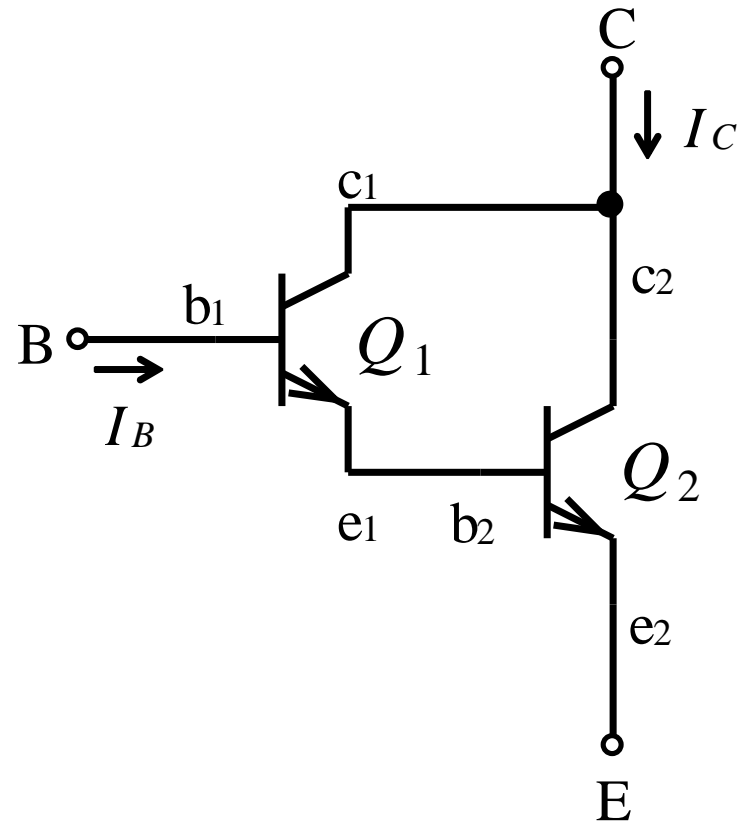
- **Collectors of Q_1 and Q_2**
- **Emitter of Q_1 and base of Q_2**



Provides high current gain : $I_C \cong \beta^2 I_B$


Darlington Connection

Currents in darlington pair

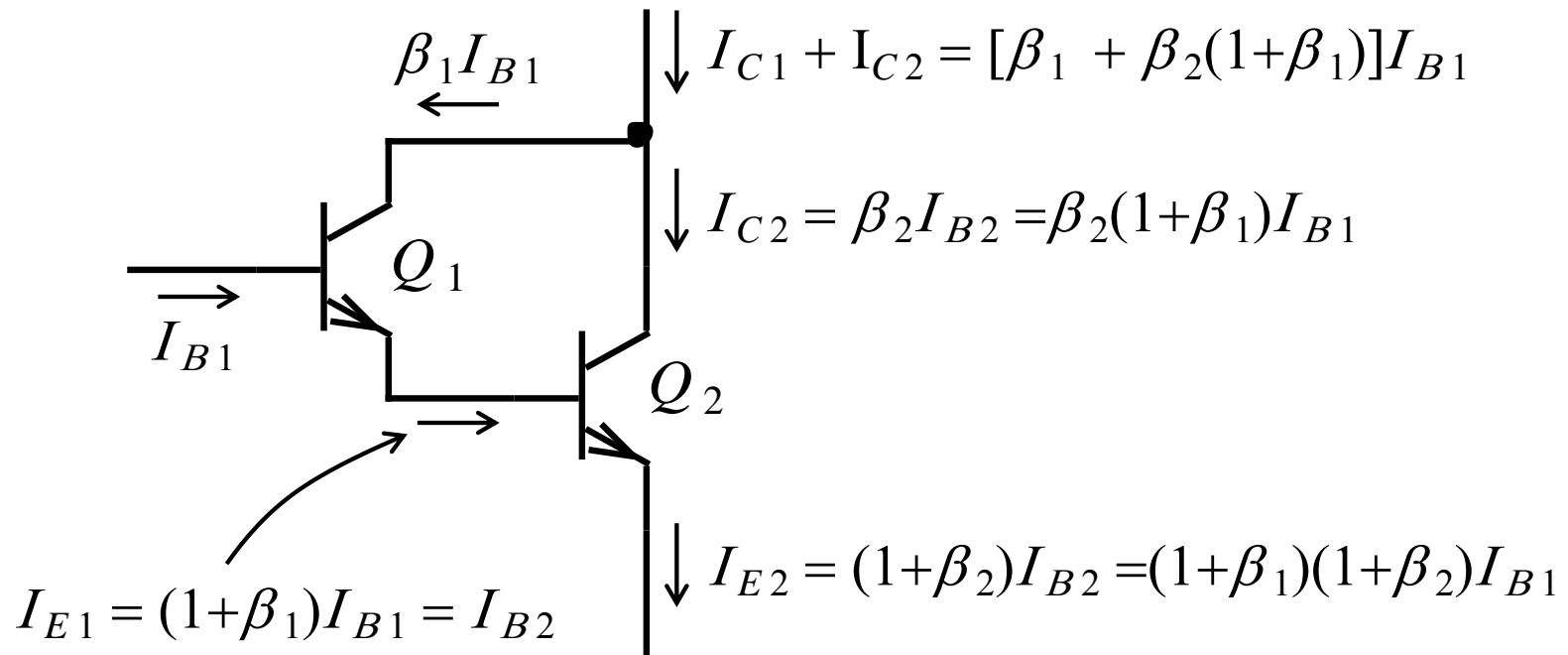


Darlington Connection

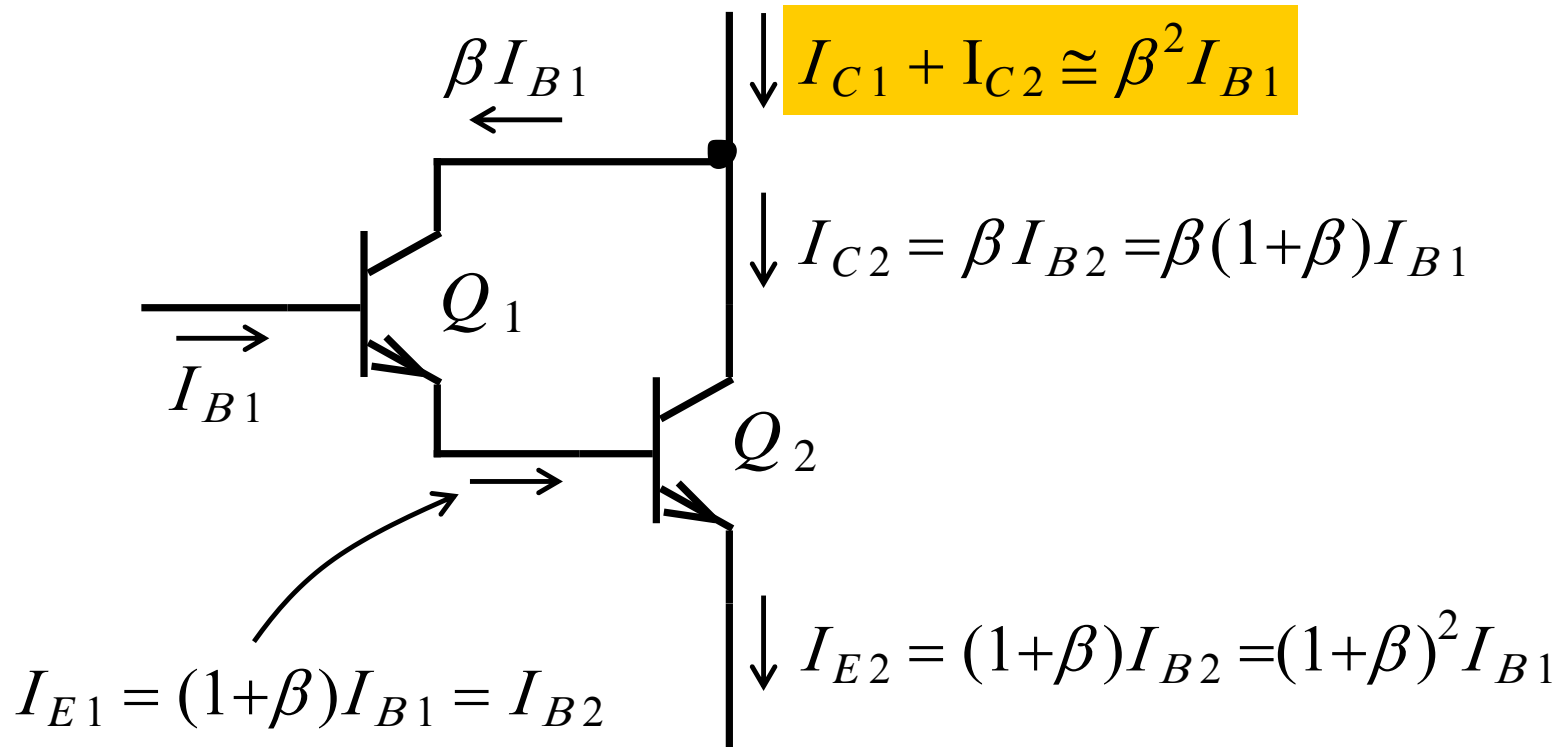If $\beta_1 = \beta_2 = \beta$ and assuming β is large




Darlington Connection

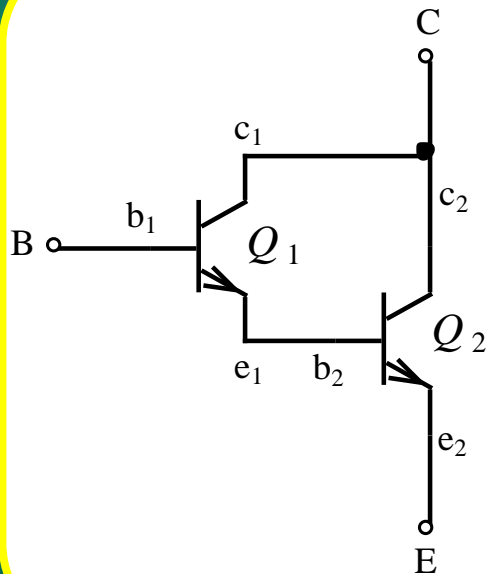Hybrid- π model (assuming $r_{o1} = r_{o2} = \infty$)




\equiv

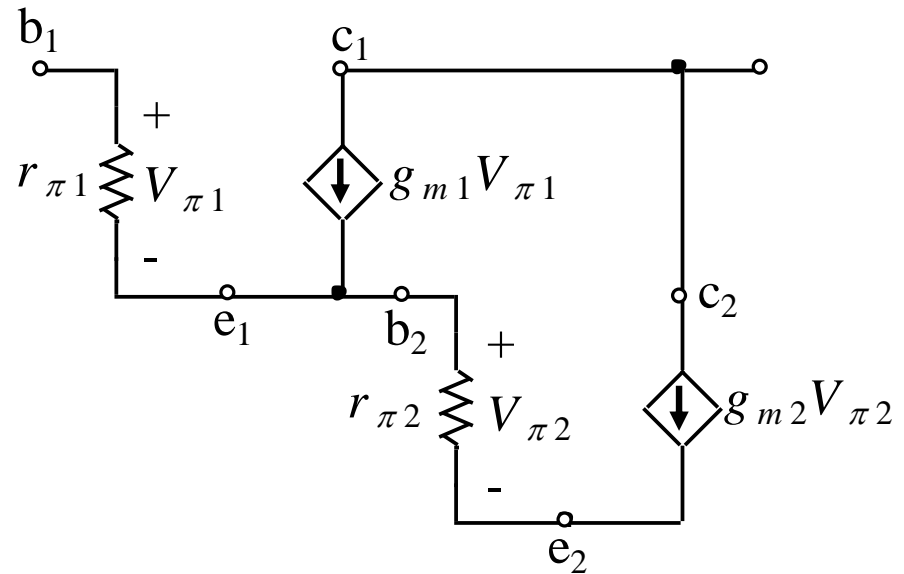

Darlington Connection


Darlington configuration provides

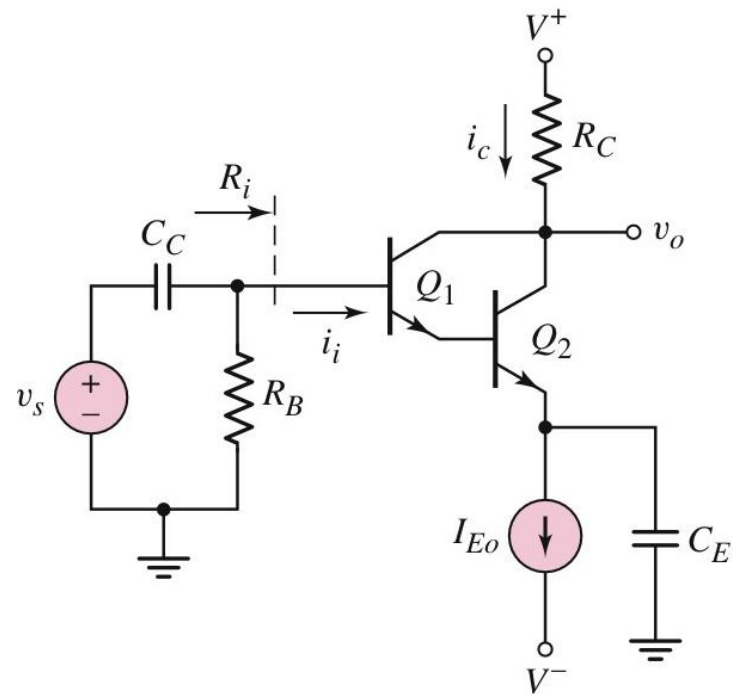- Increased current
- High input resistance




Darlington Connection

Small-signal equivalent circuit

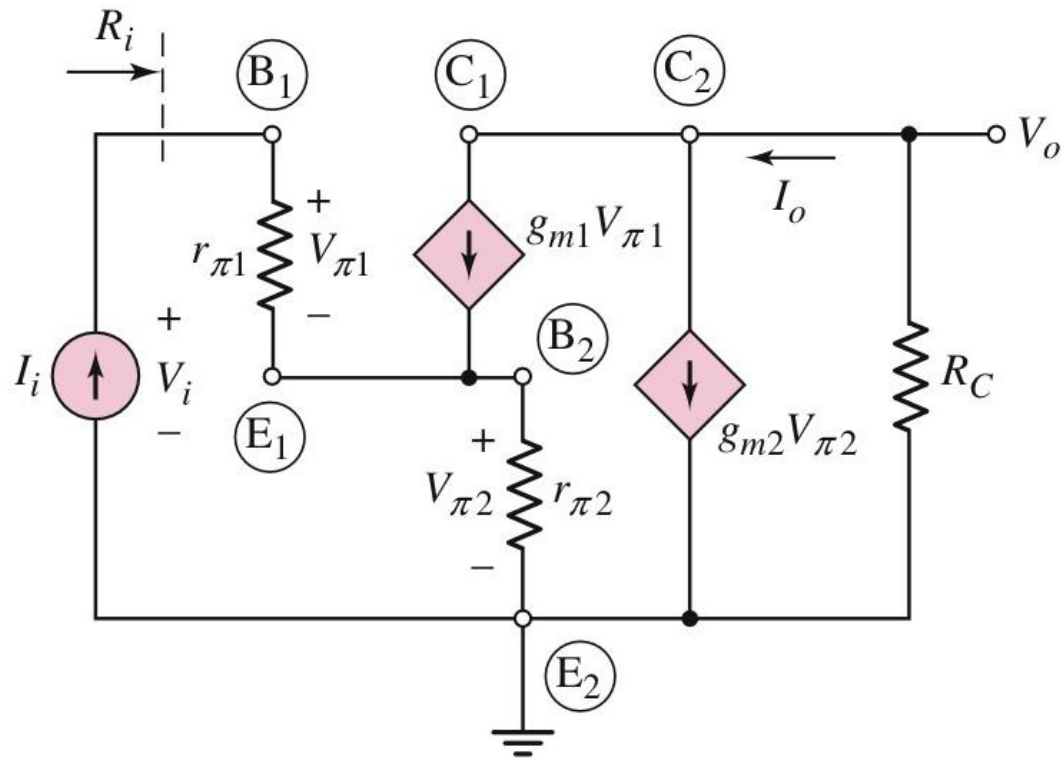


Darlington Connection

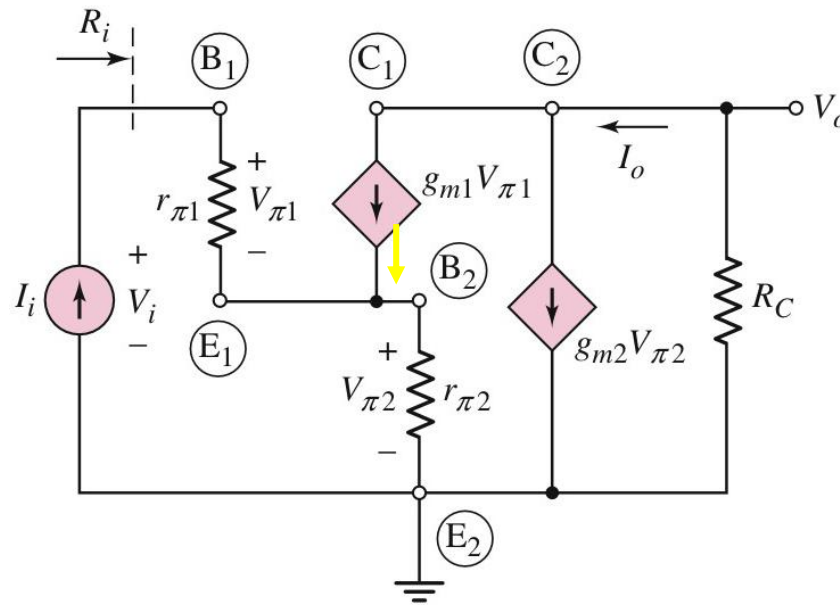

Darlington Connection

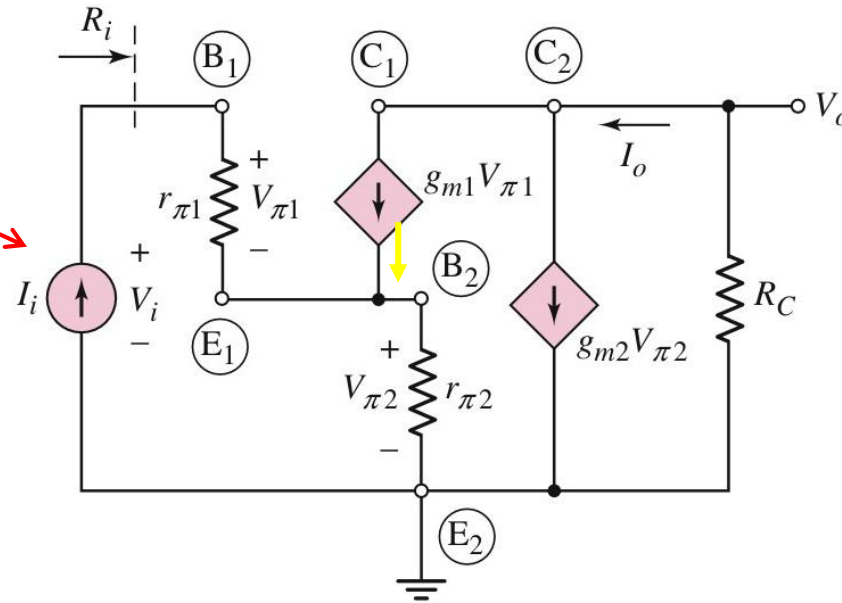
Input voltage source is transformed into current source



Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

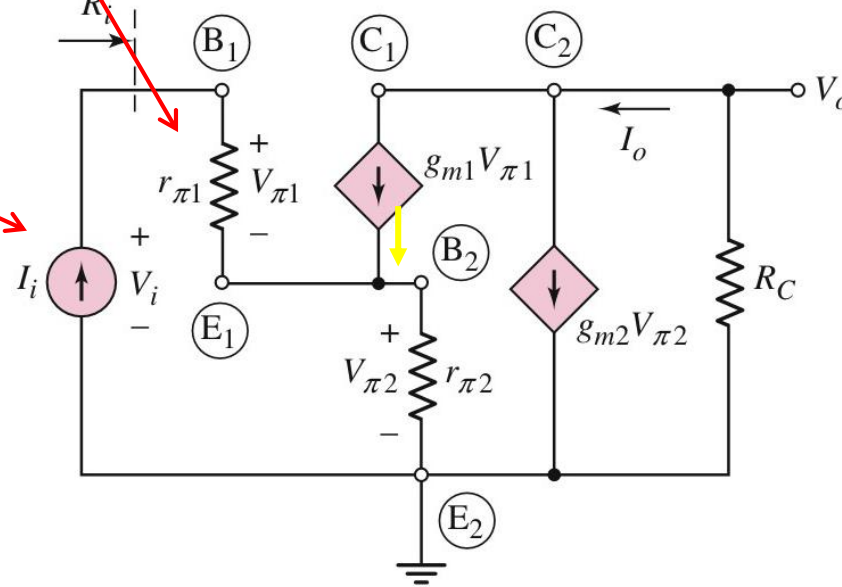Input voltage source is transformed into current source




Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

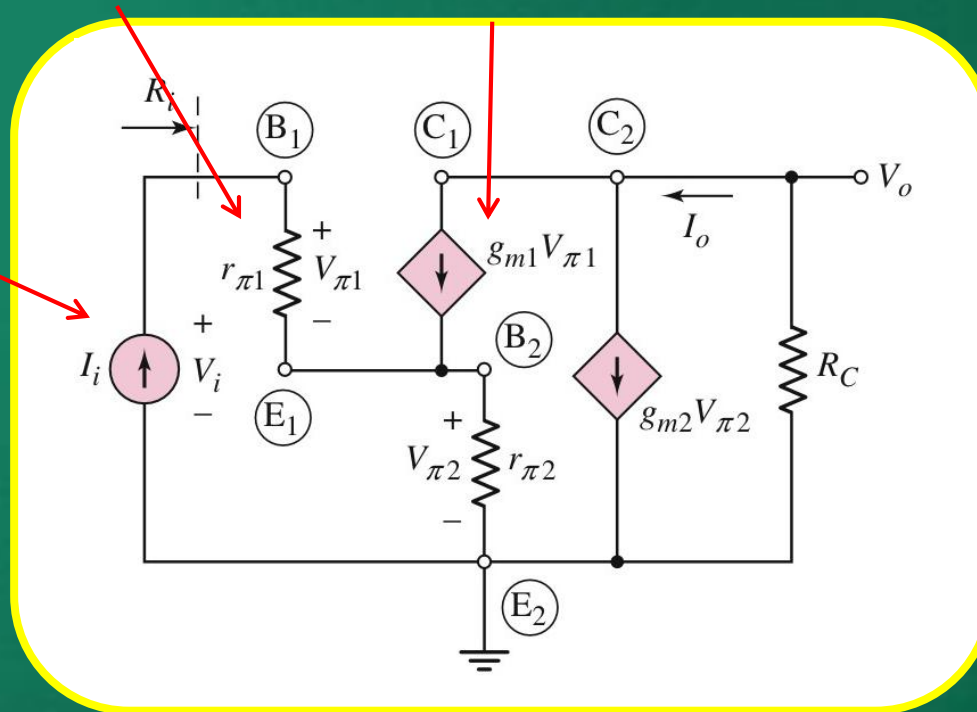Input voltage source is transformed into current source




Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

Input voltage source is transformed into current source

$$V_i = V_{\pi 1} + V_{\pi 2}$$

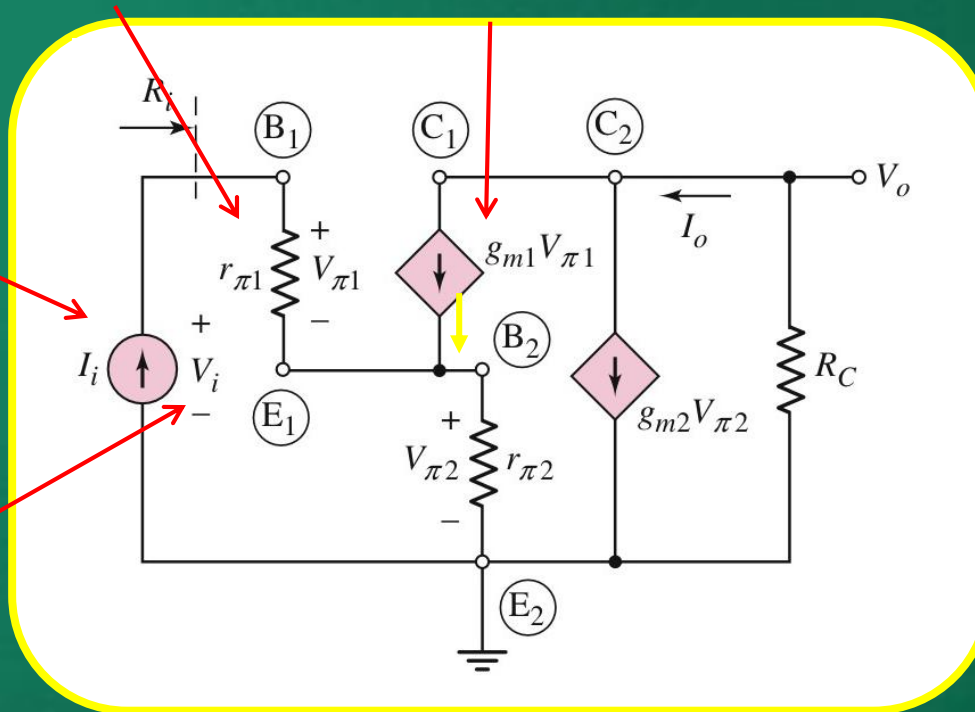


Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

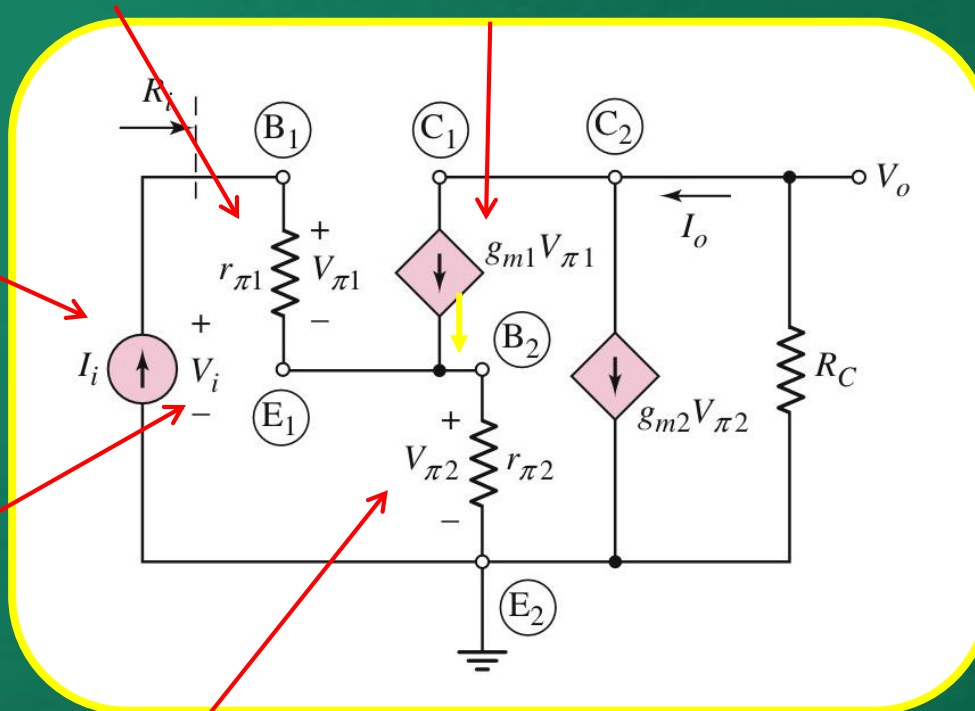Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$


$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

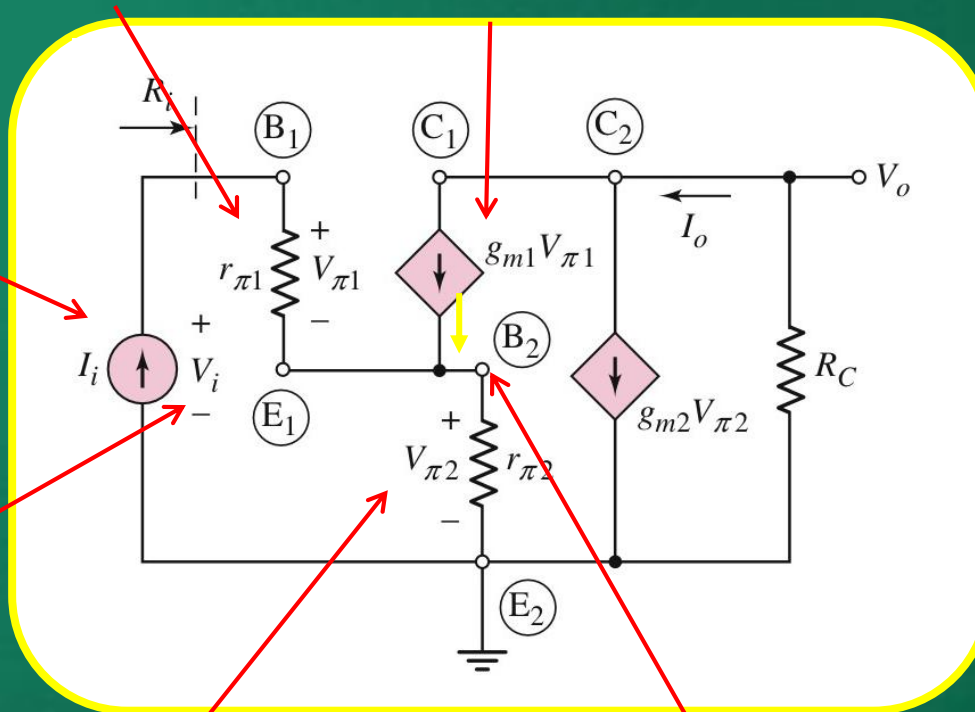Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$


$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

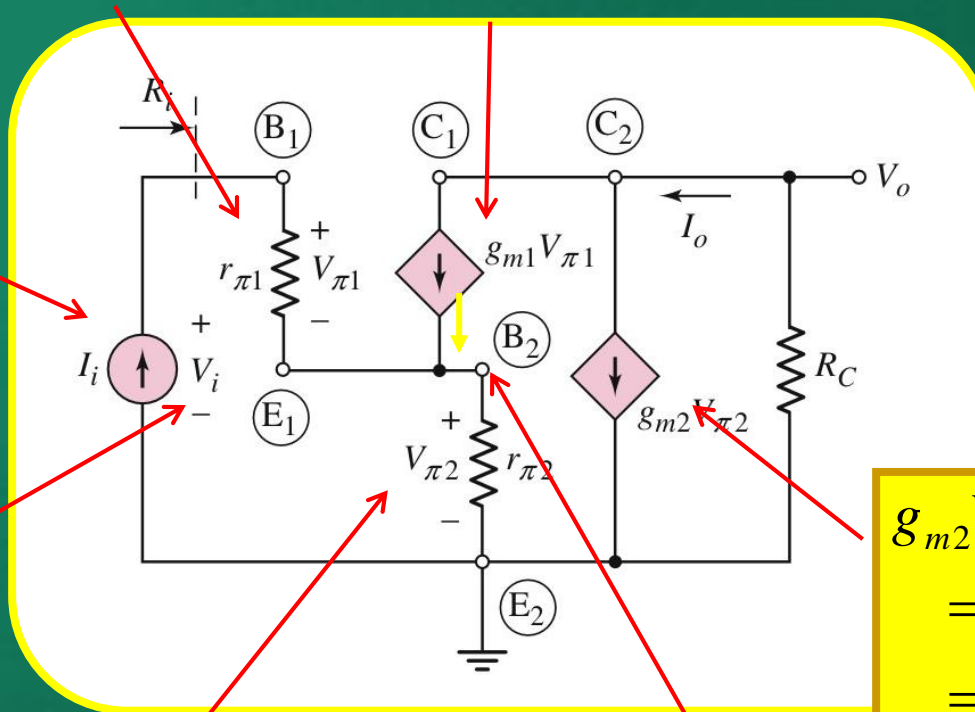Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$\begin{aligned} g_{m2} V_{\pi 2} &= g_{m2} (1 + \beta_1) I_i r_{\pi 2} \\ &= \beta_2 (1 + \beta_1) I_i \end{aligned}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$


Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$\begin{aligned} I_o &= g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} \\ &= \beta_1 I_i + \beta_2 (1 + \beta_1) I_i \end{aligned}$$

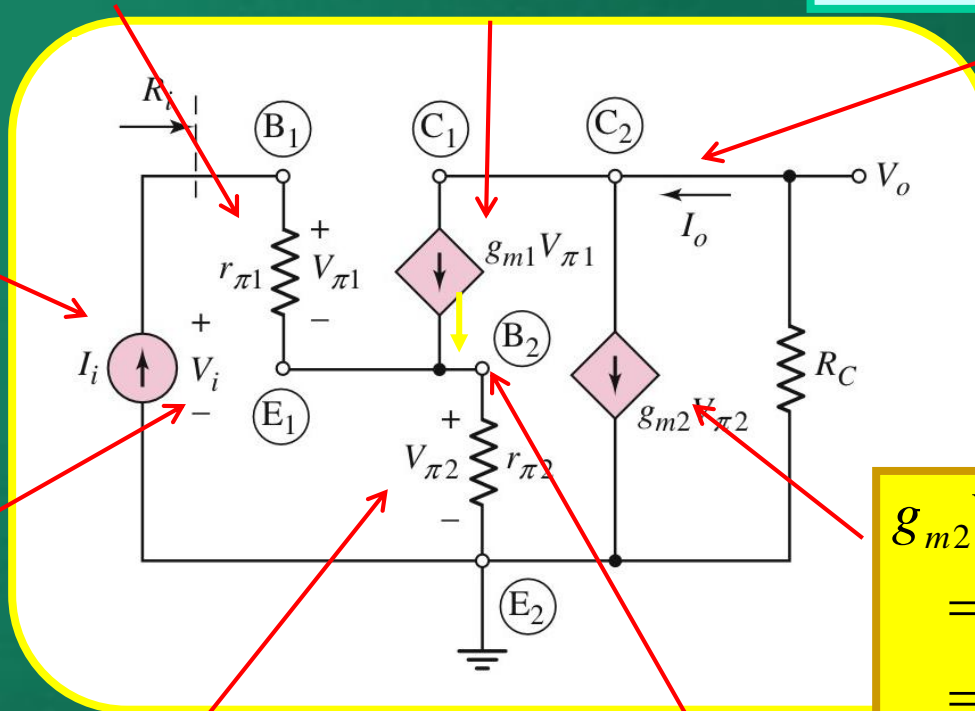Input voltage source is transformed into current source



$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$\begin{aligned} g_{m2} V_{\pi 2} &= g_{m2} (1 + \beta_1) I_i r_{\pi 2} \\ &= \beta_2 (1 + \beta_1) I_i \end{aligned}$$

$$V_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

Darlington Connection

$$V_{\pi 1} = I_i r_{\pi 1}$$



$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$

$$I_{b2} = I_i + \beta_1 I_i = (1 + \beta_1) I_i$$



$$V_{\pi 2} = I_{b2} r_{\pi 2} = (1 + \beta_1) I_i r_{\pi 2}$$

$$g_{m2} V_{\pi 2} = g_{m2} (1 + \beta_1) I_i r_{\pi 2} = \beta_2 (1 + \beta_1) I_i$$

$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

The current gain is

$$A_i = \frac{I_o}{I_i} = \beta_1 + \beta_2 (1 + \beta_1) \cong \beta_1 \beta_2$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

The input resistance is

$$R_i = \frac{V_i}{I_i} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

Darlington Connection

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + (1 + \beta_1) I_i r_{\pi 2}$$

The input resistance is

$$R_i = \frac{V_i}{I_i} = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

Approximate expression for the input resistance of the darlington configuration above is

$$R_i \cong 2\beta_1 r_{\pi 2}$$

since

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}}$$

&

$$I_{CQ1} \cong \frac{I_{CQ2}}{\beta_2}$$