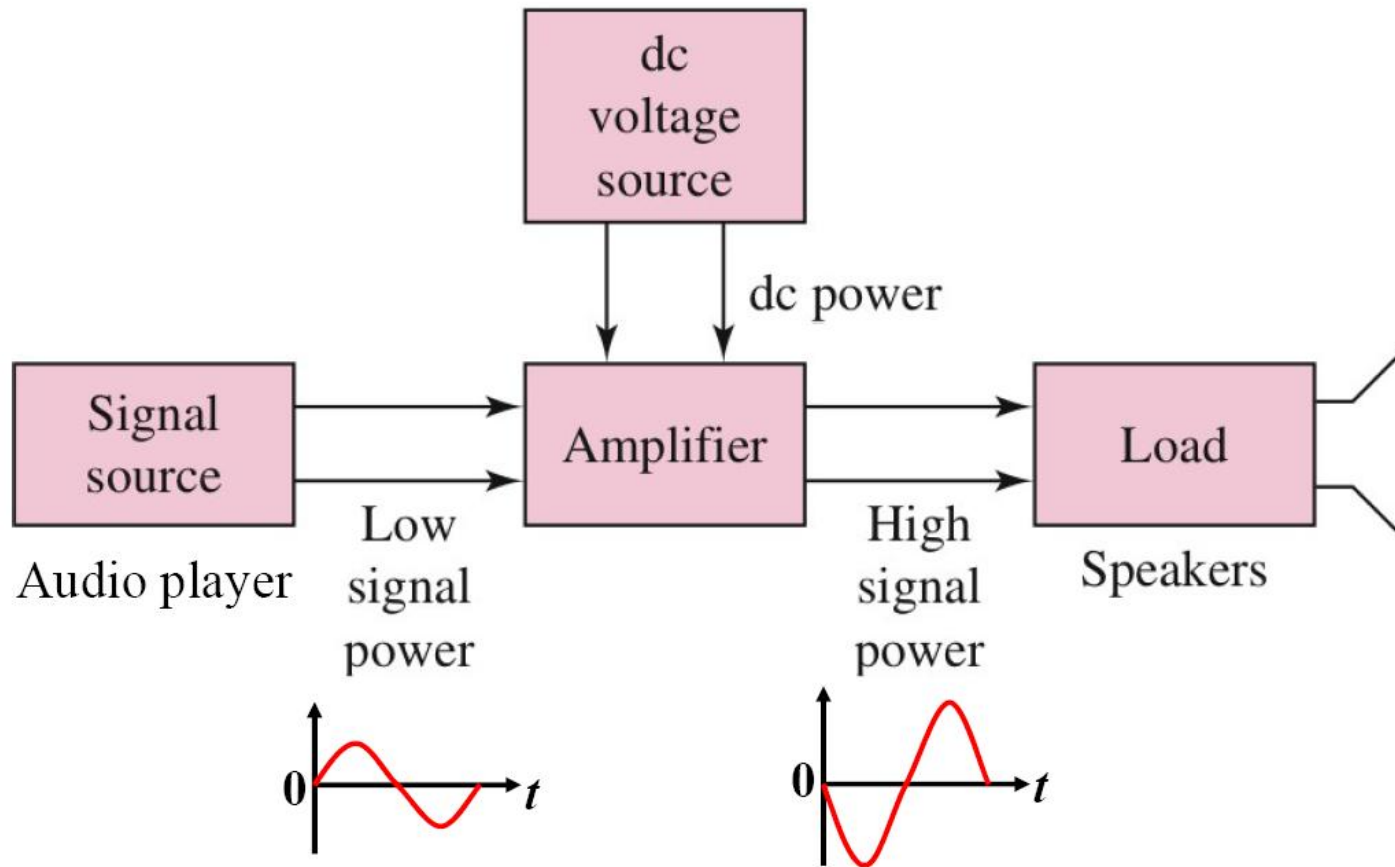


Basic Electronic Circuits (IEC-103)

Lecture-17

Small Signal Analysis



Linear Analog Amplifier



BJT Circuit Analysis

- ❑ **DC Analysis:** To fix DC operating point (Q point). Also called biasing of transistor.
- ❑ **Small Signal Analysis:** Analyze BJT circuits for signals being amplified. Small signal model is used for analysis.
- ❑ **The transistor is biased such a way to operate it in active region if used in amplifier circuit.**


Large Signal DC Analysis (Active Region)

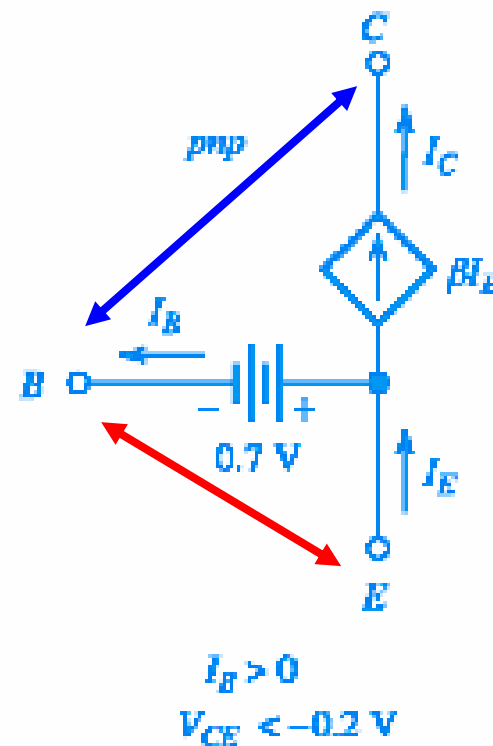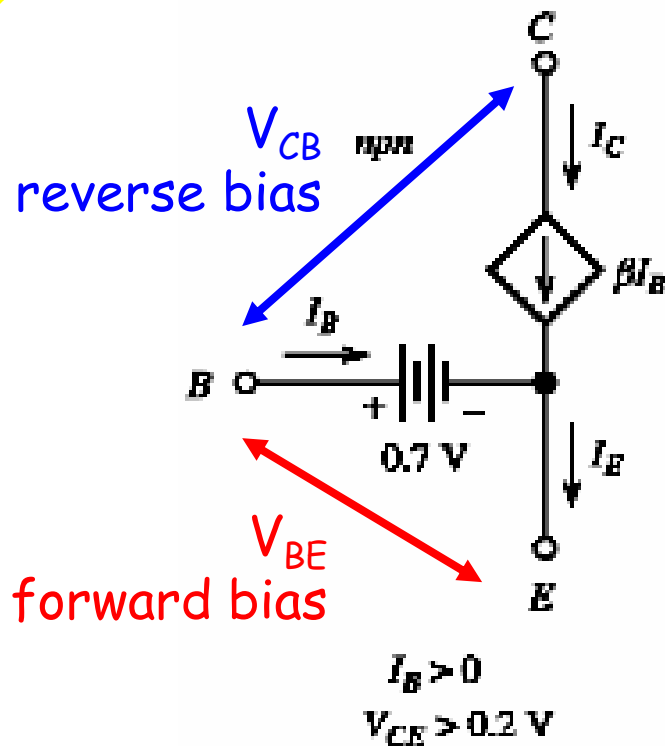

Notation in Transistor Analysis


S. No	Variable	Instantaneous AC	DC	Total
1	Emitter Current	i_e	I_E	i_E
2	Collector Current	i_c	I_C	i_C
3	Base Current	i_b	I_B	i_B
4	Collector-emitter Voltage	v_{ce}	V_{CE}	v_{CE}
5	Emitter-base Voltage	v_{eb}	V_{EB}	v_{EB}

Basic Characteristics of an Amplifier

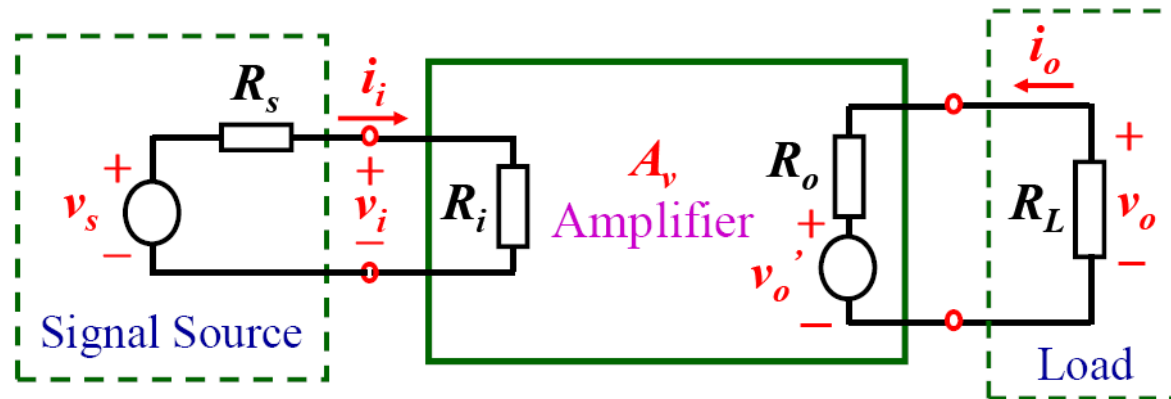


- **Amplifier Gain:** $A_v = \frac{v_o}{v_s}$
- **Input Resistance:** $R_i = \frac{v_i}{i_i}$
- **Output Resistance:** $R_o = \frac{v_o}{i_o} \bigg|_{v_s=0 \text{ (a short circuit), } R_L = \infty \text{ (an open circuit)}}$


Basic Common Emitter Amplifier

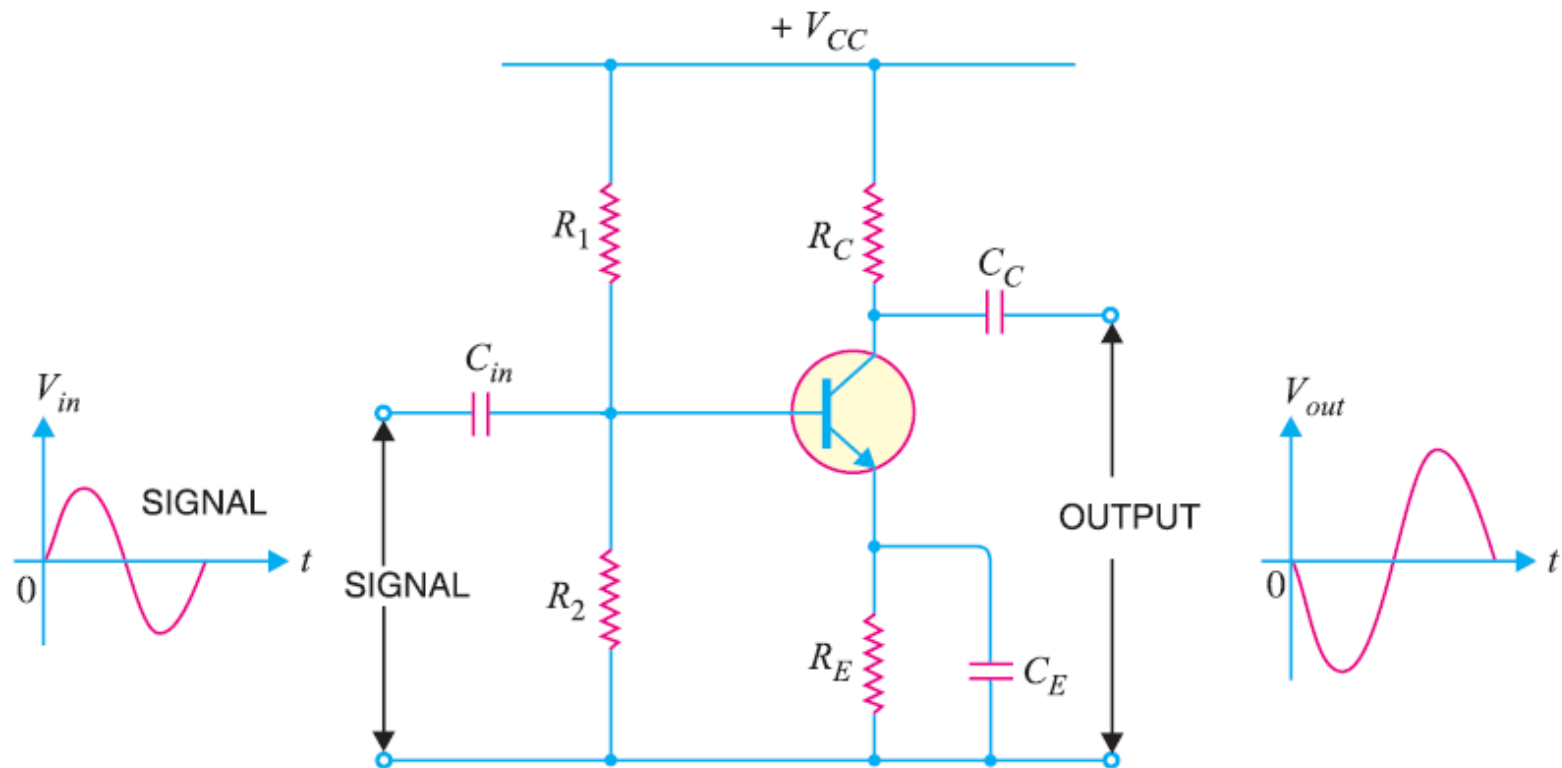



Graphical Analysis of BJT Amplifier

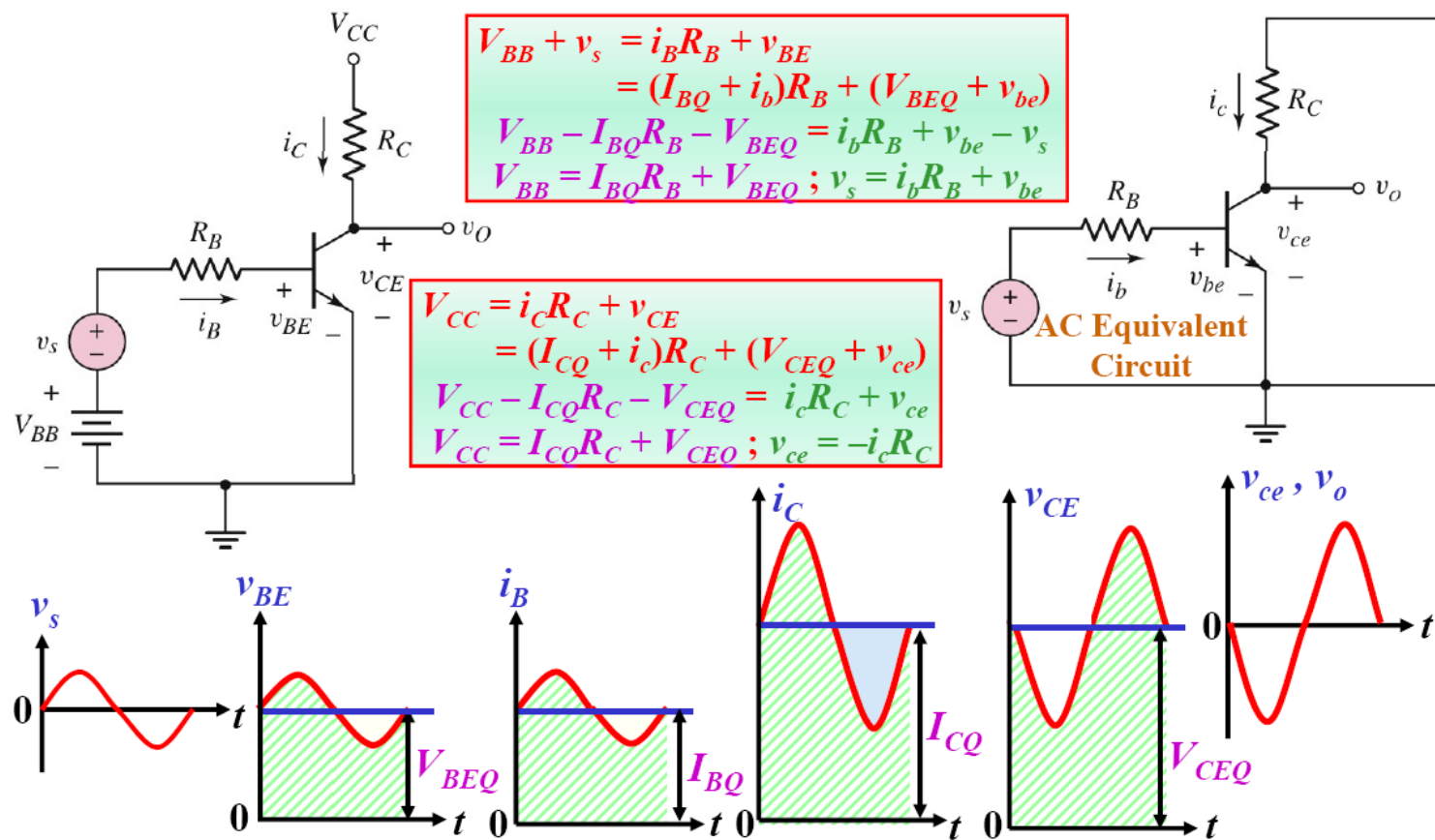

Graphical Analysis of BJT Amplifier

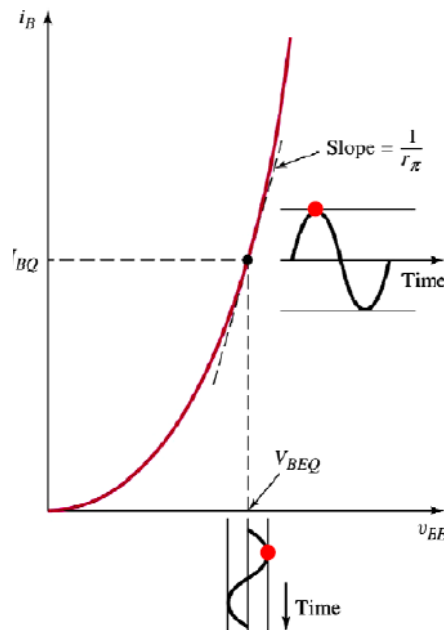


$$V_{BB} + v_s = i_B R_B + v_{BE}$$

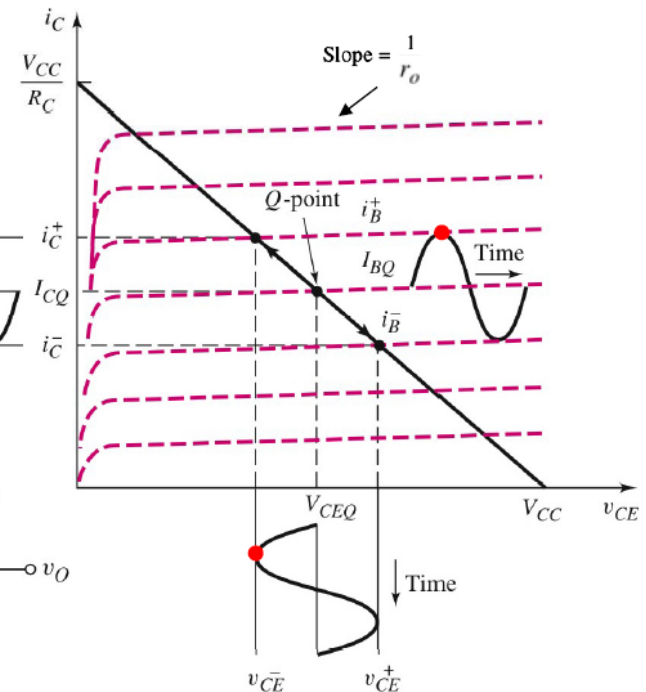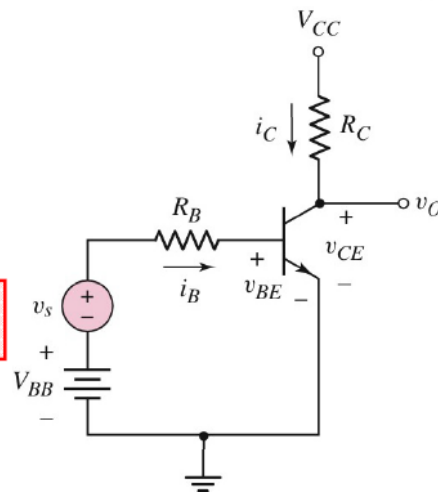

$$V_{CC} = i_C R_C + v_{CE}$$

Analysis of BJT Amplifiers


Function of each component:

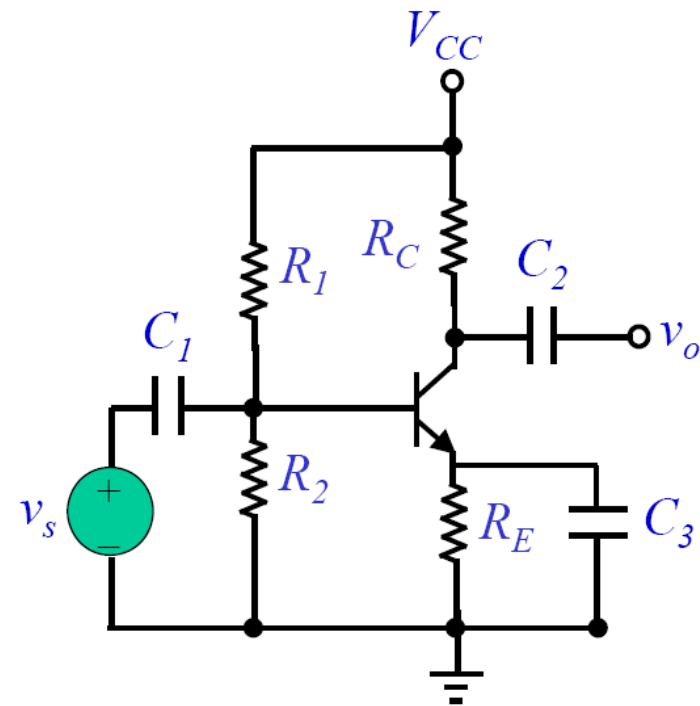

Analysis of BJT Amplifiers

Function of each component:


- Capacitors: Acting as an **open circuit** for a **dc** operation but a **short circuit** for an **ac** operation
(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_C| = (2 \pi f C)^{-1} = 8 \Omega$, which is usually smaller than $R_{TH} = R_1 // R_2$)

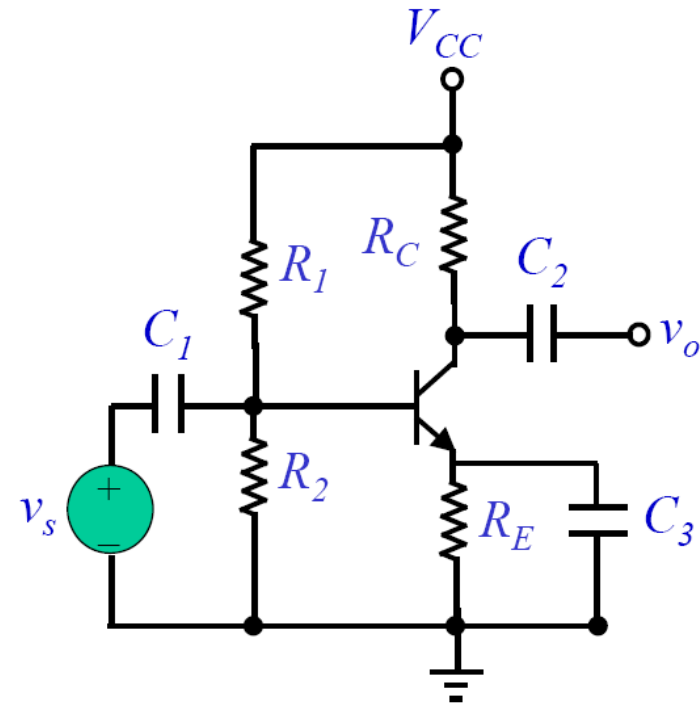

Analysis of BJT Amplifiers

Function of each component:


- Capacitors: Acting as an **open circuit** for a **dc** operation but a **short circuit** for an **ac** operation
(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_C| = (2 \pi f C)^{-1} = 8 \Omega$, which is usually smaller than $R_{TH} = R_1 // R_2$)
- R_1 , R_2 , R_C & R_E : Setting dc biasing **Q-point**

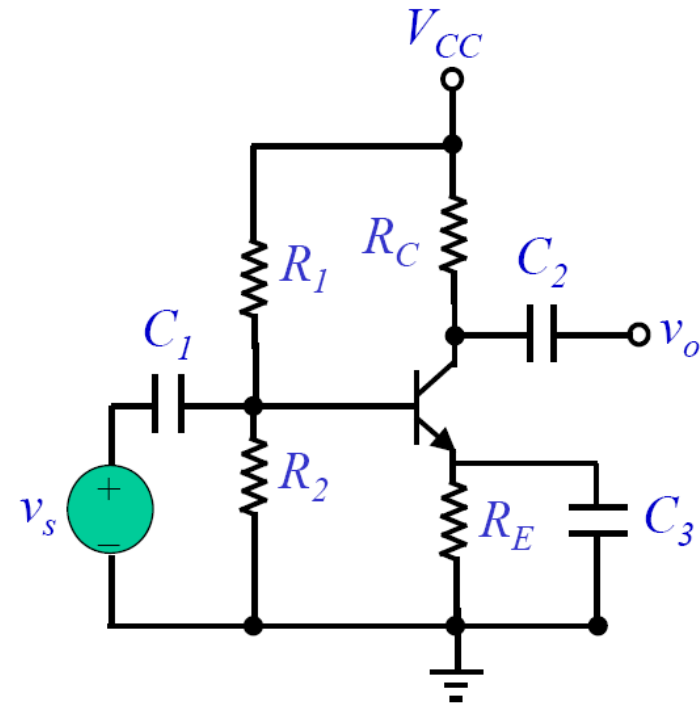


Analysis of BJT Amplifiers

Function of each component:


- Capacitors: Acting as an **open circuit** for a **dc** operation but a **short circuit** for an **ac** operation
(If $f = 10 \text{ kHz}$ & $C = 10 \mu\text{F}$, then $|Z_C| = (2 \pi f C)^{-1} = 8 \Omega$, which is usually smaller than $R_{TH} = R_1 // R_2$)
- R_1 , R_2 , R_C & R_E : Setting dc biasing **Q-point**
- R_C : Converting i_c variation into v_{ce} (or v_o) variation (**signal conversion**)

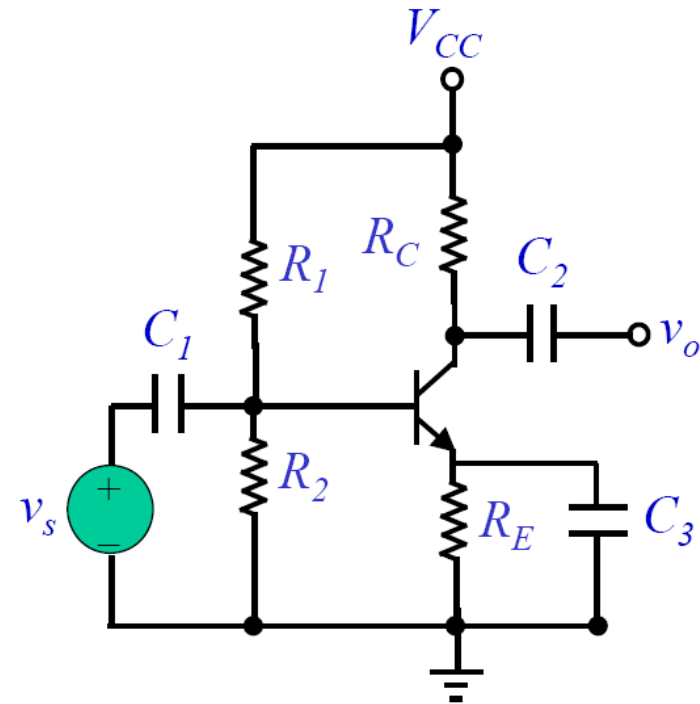

DC Analysis and Equivalent Circuits


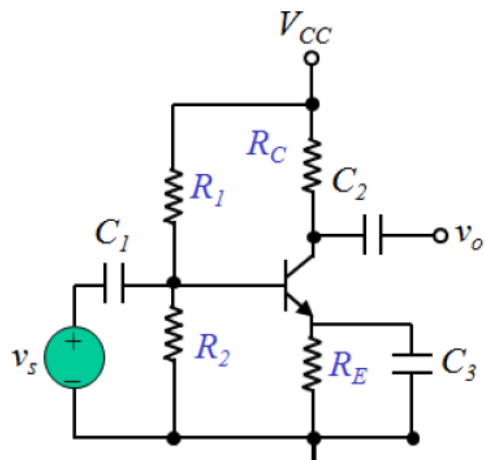


DC Analysis and Equivalent Circuits

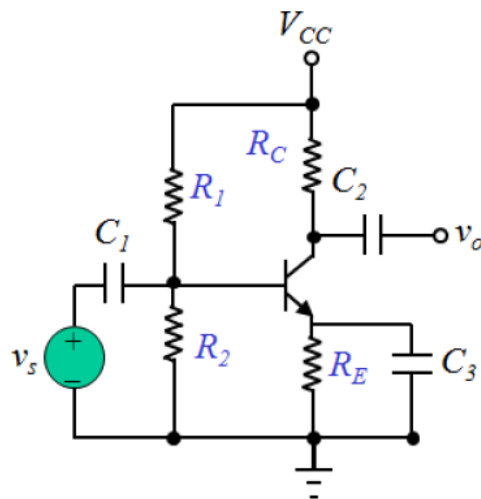


- ❑ To determine the dc biasing Q-point
 - Reduce all signal sources to **zero**
 - **Open** all capacitors
 - Draw & analyze the dc equivalent circuit

DC Analysis and Equivalent Circuits

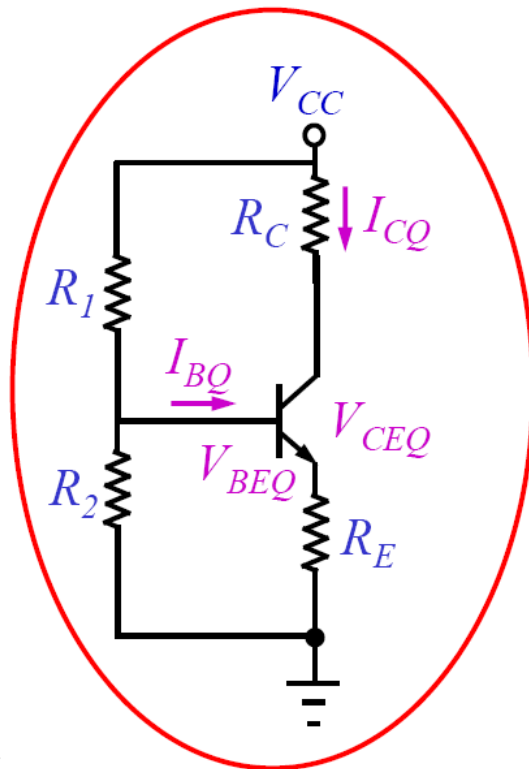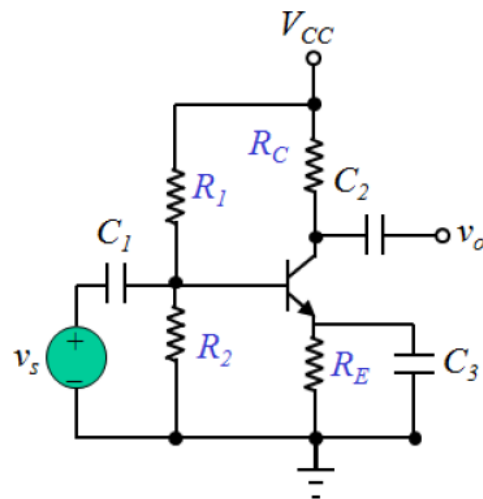


- ❑ To determine the dc biasing Q-point
 - Reduce all signal sources to **zero**
 - **Open** all capacitors
 - Draw & analyze the dc equivalent circuit

AC Analysis and Equivalent Circuits

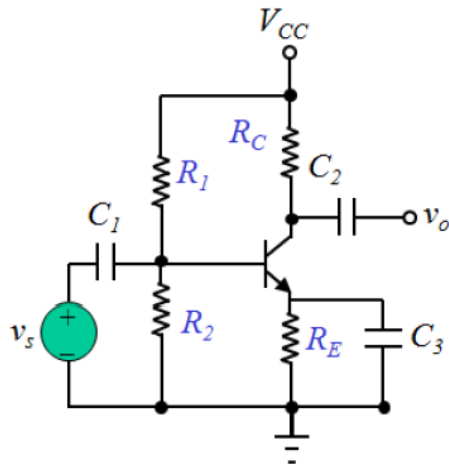


AC Analysis and Equivalent Circuits

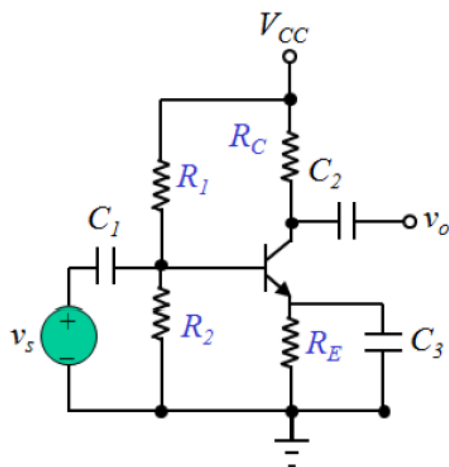


- ❑ To determine the ac characteristics (e.g., small-signal voltage gain, input & output impedances, frequency response, etc.)
 - Reduce all dc voltage sources to **zero**
 - **Short** all capacitors
 - Draw & analyze the ac equivalent circuit

AC Analysis and Equivalent Circuits

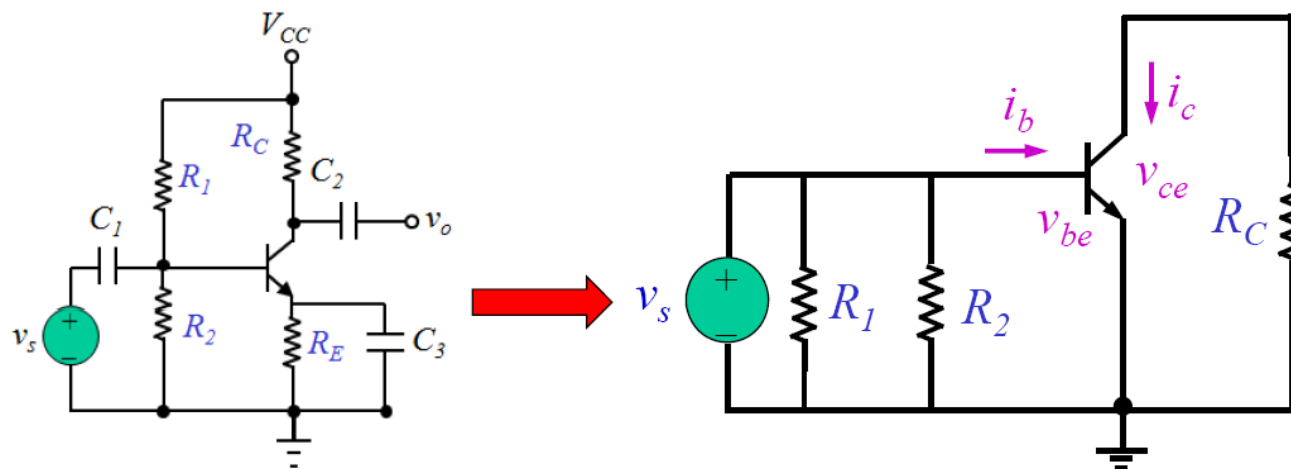


- ❑ To determine the ac characteristics (e.g., small-signal voltage gain, input & output impedances, frequency response, etc.)
 - Reduce all dc voltage sources to **zero**
 - **Short** all capacitors
 - Draw & analyze the ac equivalent circuit

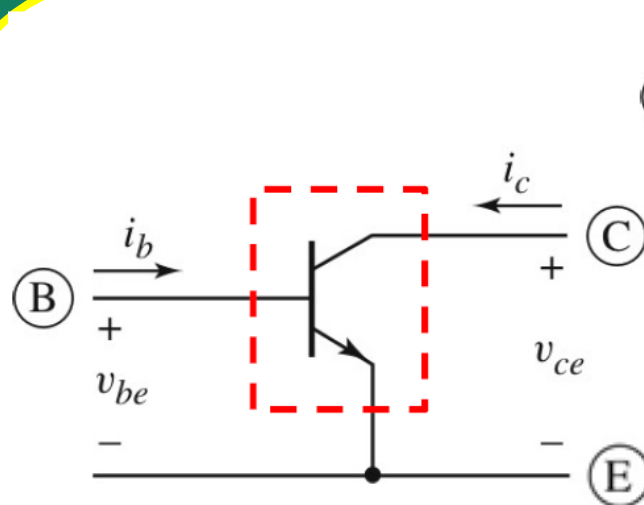Small Signal Hybrid- π Equivalent Circuit




BJT as a small-signal,
two-port network

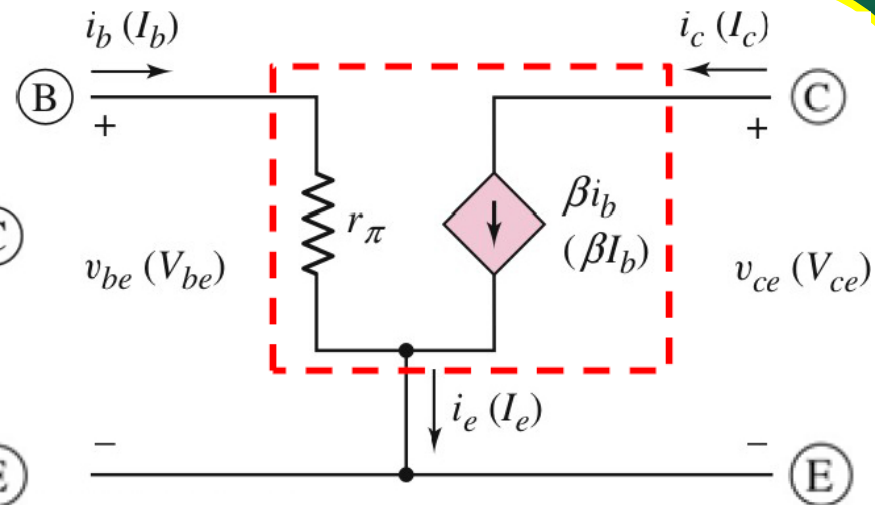

Small-signal hybrid- π
equivalent circuit

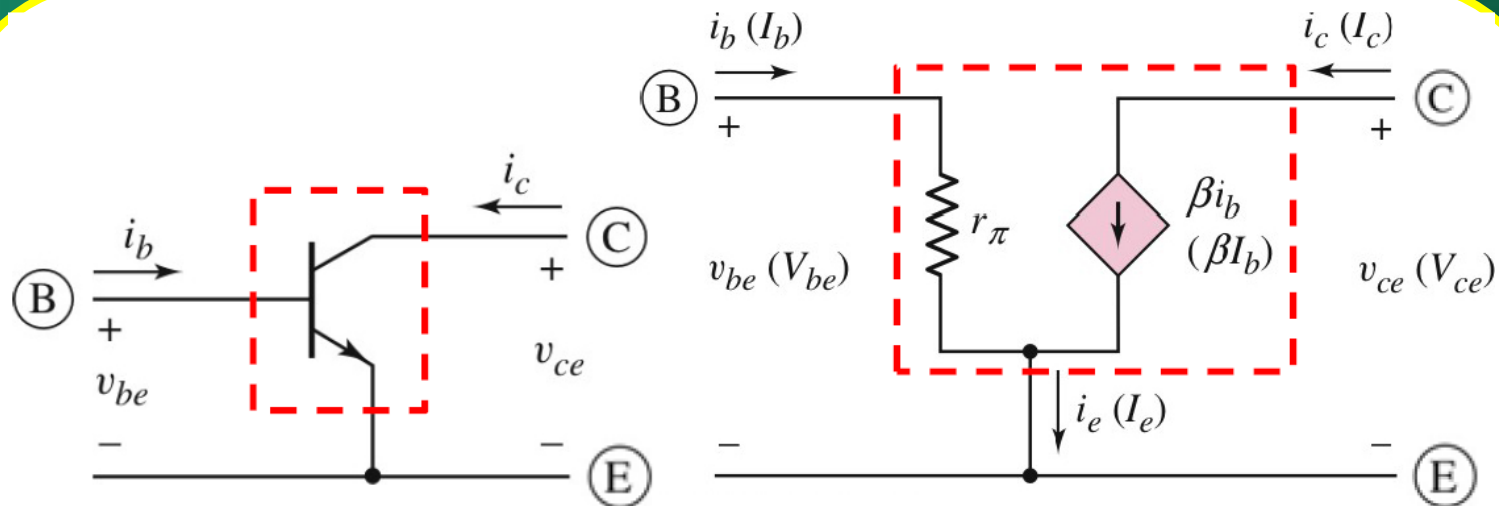Small Signal Hybrid- π Equivalent Circuit




**BJT as a small-signal,
two-port network**


**Small-signal hybrid- π
equivalent circuit**

- $\beta = i_c / i_b = I_c / I_b = \text{common-emitter current gain}$
- $r_\pi = v_{be} / i_b = V_{be} / I_b = V_T / I_{BQ} = \beta V_T / I_{CQ} = \text{small-signal resistance, where } V_T = kT / e = \text{thermal voltage}$

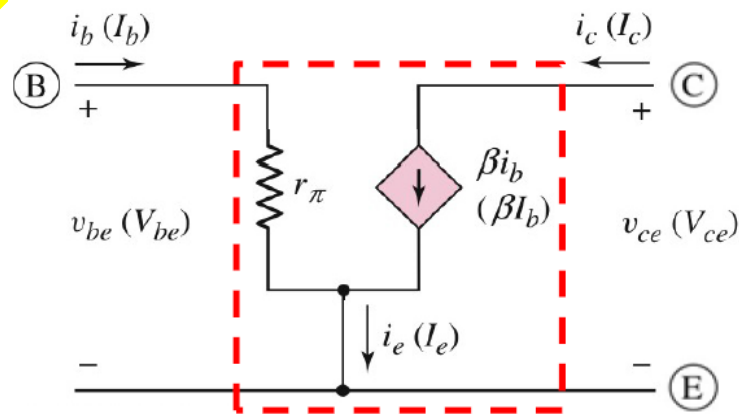Small Signal Hybrid- π Equivalent Circuit




With current gain
parameter

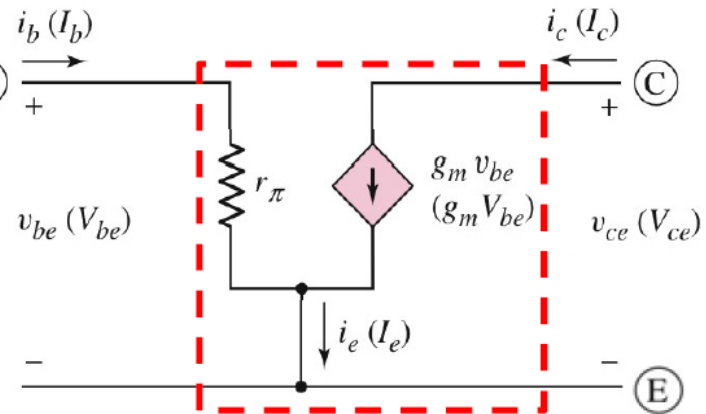


With transconductance
parameter

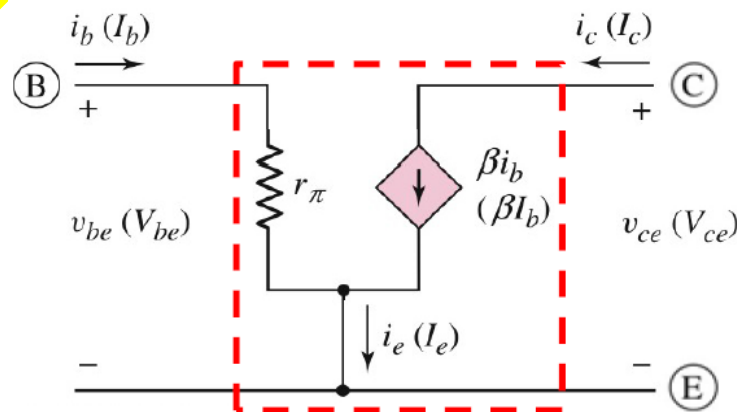Small Signal Hybrid- π Equivalent Circuit




With current gain parameter

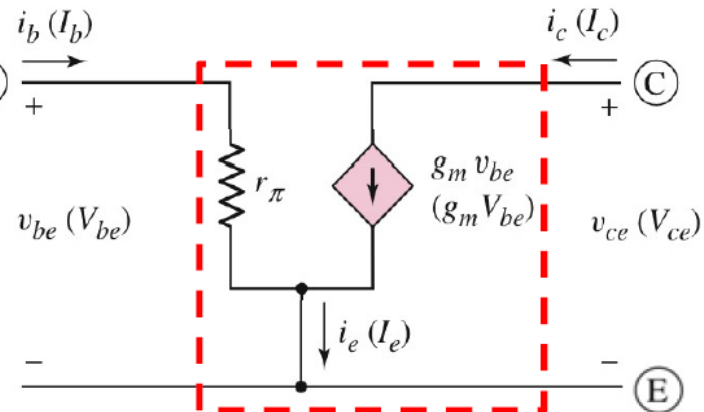


With transconductance parameter

- $g_m = \beta / r_\pi = I_{CQ} / V_T = \text{transconductance}$
- i_c is assumed to be independent of v_{ce} , which is not the case in practice & the assumption will be released later to include the “Early Effect”.


Small Signal Voltage Gain

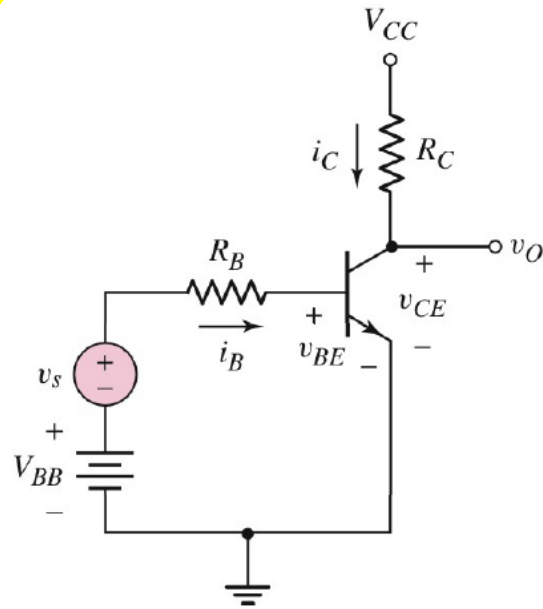

Small Signal Voltage Gain

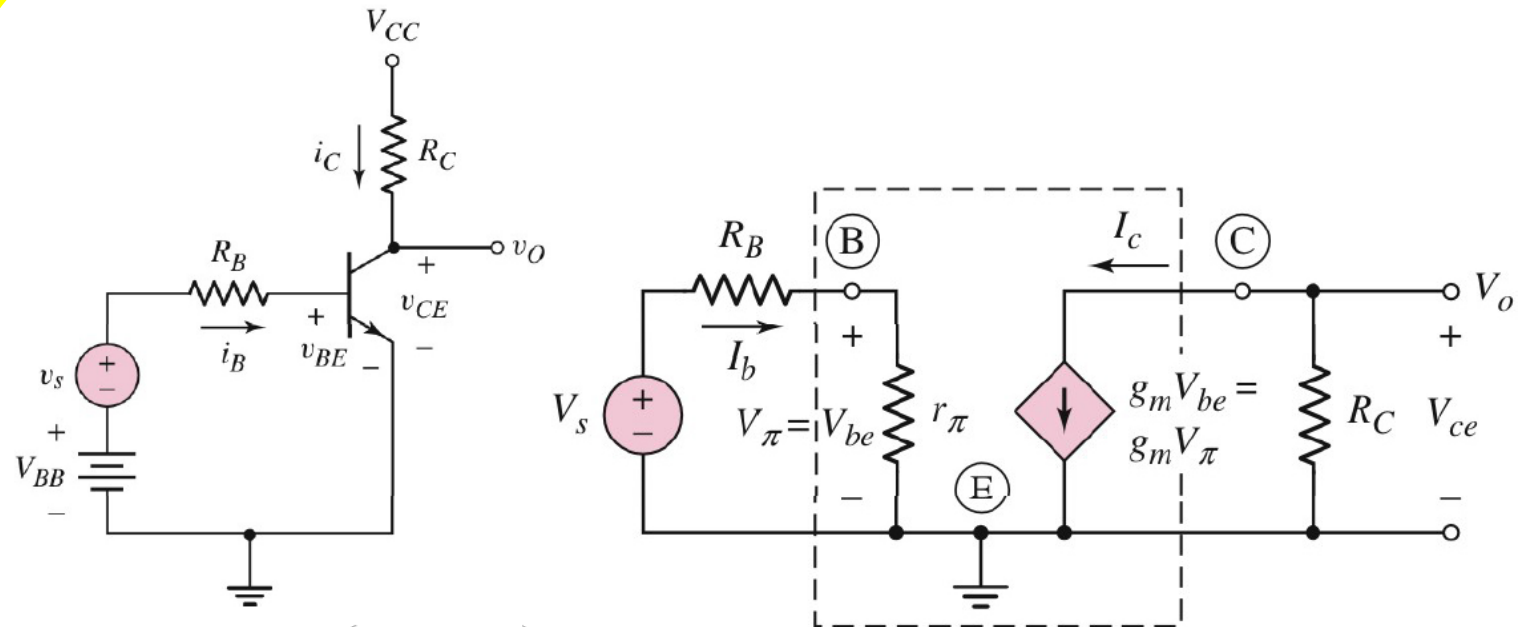



Small Signal Voltage Gain

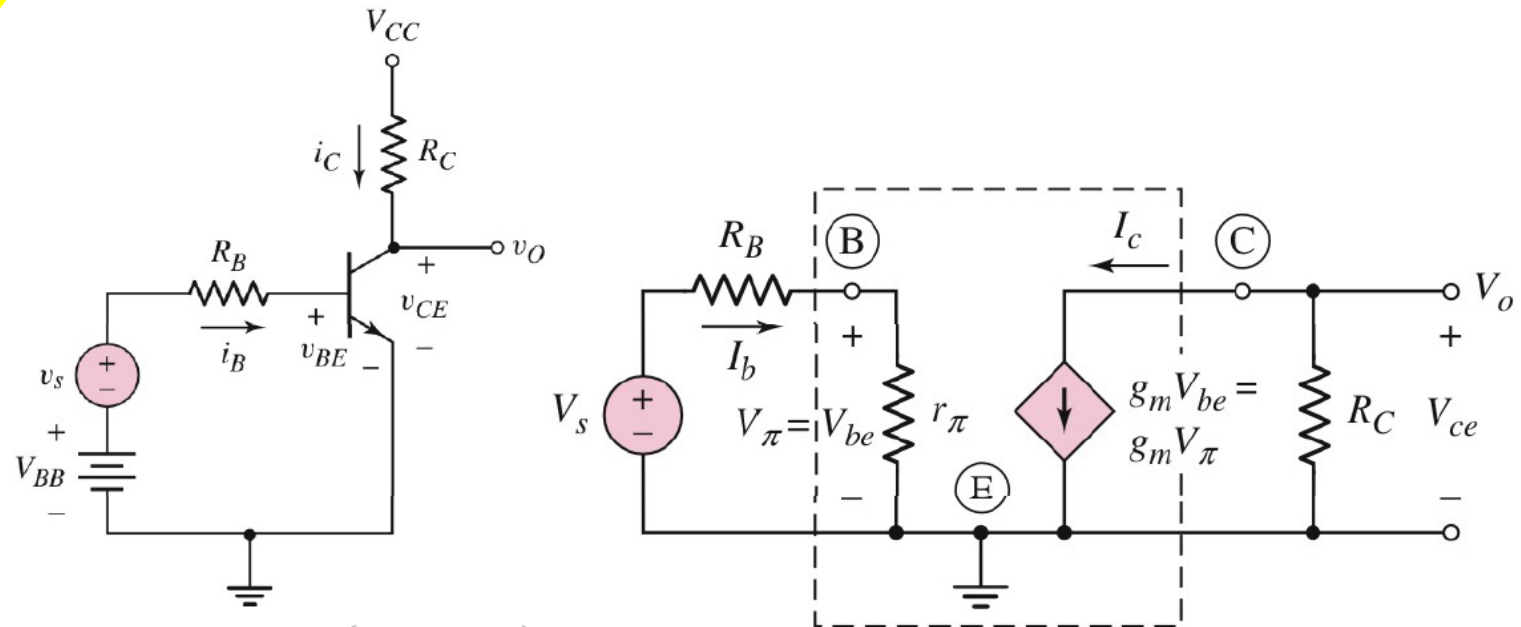

$$V_{\pi} = V_{be} = V_s \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_{\pi}) R_C = -(g_m V_{be}) R_C$$

Small Signal Voltage Gain

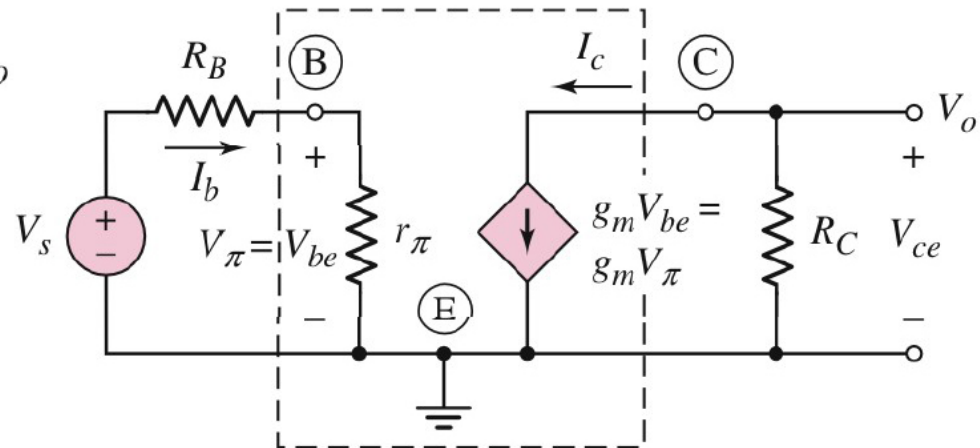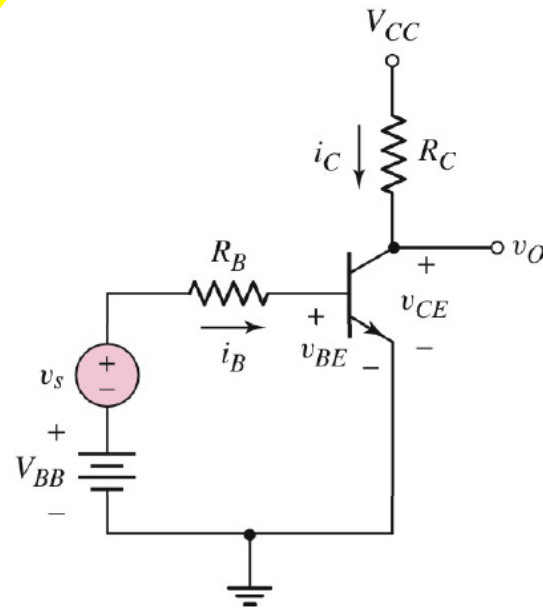

$$V_\pi = V_{be} = V_s \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$V_o = V_{ce} = -(g_m V_\pi) R_C = -(g_m V_{be}) R_C$$

Small-signal voltage gain:

$$A_v = \frac{V_o}{V_s} = -(g_m R_C) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$